

Sinteza električnih filtara

Dr Miroslav Lutovac

Overview

- Analog filter specification
- Analog filter design steps
- Analog filter classification
- Sensitivity
- Optimum cascading sequence
- Examples
- MATLAB `cheb1ord`, `cheb1ap`


What are analog filters?

- **Analog filters** are frequency-selective circuits that are used to amplify or attenuate a single sinusoidal signal component or a portion of the signal frequency spectrum
- **Passband** is a range of frequencies in which the sinusoidal signals are amplified or passed without considerable attenuation
- **Stopband** is a frequency range in which the sinusoidal signals are significantly attenuated
- **Specification** is the required minimum and maximum of attenuation or amplification, along with corresponding edge frequencies of passbands and stopbands

What is analog filter design?

- ***Analog filter design*** is a process in which we construct an electrical circuit that meets the given specification
- Design starts with the specification and it consists of four basic steps:
 1. ***approximation***
 2. ***realization***
 3. ***study of imperfections***
 4. ***implementation***
- There is an infinite number of circuits that meet the specification; therefore, the filter design is by no means unique

Classic filter design

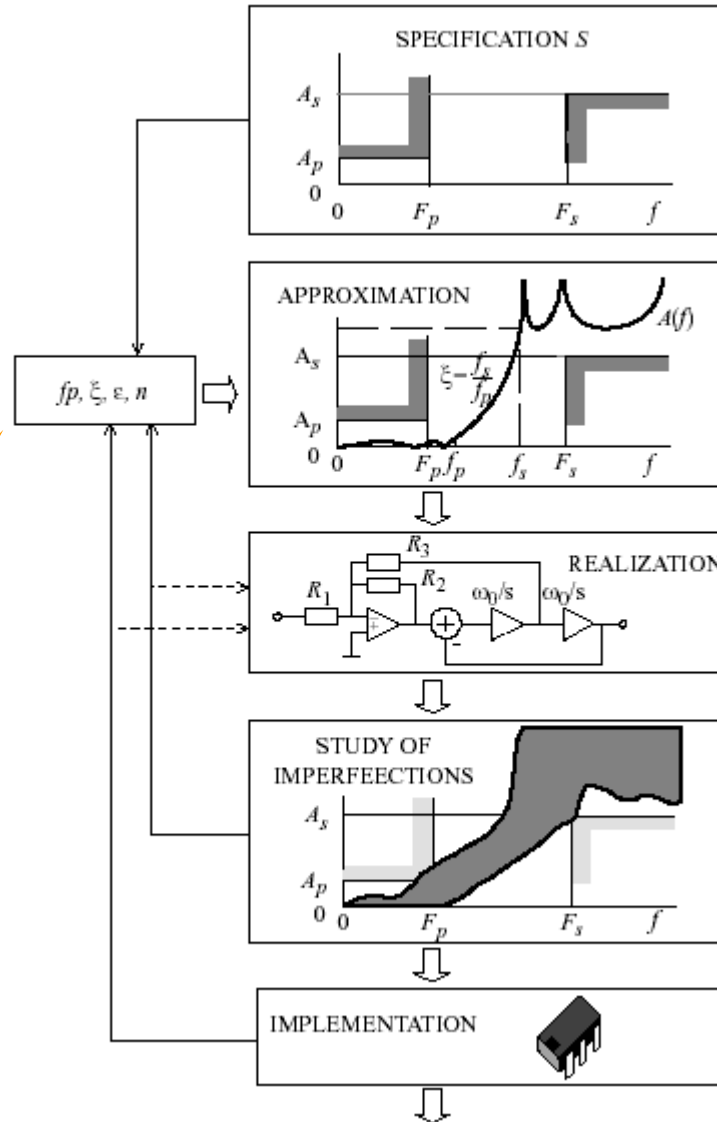

If requirements are not met, realization step (new circuit) or the approximation step must be redone

Specification example

- Assume we want to design an analog lowpass filter that passes signals over the range $0 \leq f \leq F_p$ and attenuates signals for $f \geq F_s > F_p$
- Range $0 \leq f \leq F_p$ is passband, and $f \geq F_s$ is stopband;
 F_p is **passband edge frequency** and
 F_s is **stopband edge frequency**
- We require that attenuation
in passband must not exceed A_p dB
in stopband should be no less than A_s dB
- A_p is maximum **passband attenuation**
 A_s is minimum **stopband attenuation**
- Four quantities that specify lowpass filter
 $S = \{F_p, F_s, A_p, A_s\}$ is the **lowpass specification**

Approximation step

- **Approximation step:** we construct filter transfer function $H(s)$, which is a rational function in the complex frequency s
- **Attenuation approximation function**, simply **attenuation**, $A(f) = -20 \log_{10}|H(j2\pi f)|$, must satisfy the specification S

$$\begin{aligned} 0 \leq A(f) \leq A_p, & \quad 0 \leq f \leq F_p \\ A_s \leq A(f), & \quad F_s \leq f \end{aligned}$$

Realization step

- ***Realization step*** is the process of converting the transfer function into a circuit (sometimes called the realization)
- Designers are interested in realizations which are economical, simple, cheap, with small noise and distortion, and with high dynamic range and which are not seriously affected by small changes in the element values (tolerances, temperature and humidity variations, aging drift)
- Numerical values of the elements are calculated from the transfer function

Study of imperfections

- In practice, the filter is implemented with nonideal elements
- Designer must accomplish the ***study of imperfections*** which includes ***tolerance analysis*** and ***study of parasitics***
- If specification can be met only with high-precision expensive components, then the designer has to choose another transfer function and reevaluate realization or approximation steps

Implementation step

- In the ***implementation step*** a device called the product prototype, also called the ***implementation***, is constructed and tested
- Cost of the mass production depends on the type of components, packaging, methods of manufacturing, testing, and tuning
- The best implementation is a device with no need for tuning
- If the requirements are not met, then the realization step (new circuit) or the approximation step must be redone

Analog filter classification (1)

- **Lowpass filter** passes signals over the range $0 \leq f \leq F_p$ but attenuates signals for $f \geq F_s > F_p$
- **Highpass filter** passes signals for $f \geq F_p$ but attenuates signals over the range $0 \leq f \leq F_s < F_p$
- **Bandpass filter** passes signals for $F_{p1} \leq f \leq F_{p2}$ but attenuates signals for $0 \leq f \leq F_{s1} < F_{p1}$ and $f \geq F_{s2} > F_{p2}$
- **Bandreject** or **bandstop filter** passes signals for $0 \leq f \leq F_{p1} < F_{s1}$ and $f \geq F_{p2} > F_{s2}$ but attenuates signals over the range $F_{s1} \leq f \leq F_{s2}$

Analog filter classification (2)

- **Allpass filter** or **phase equalizer** passes signals without attenuation and shapes the phase response
- **Lowpass-notch filter** rejects signals at frequencies $f \approx f_z$ but passes signals at high frequencies ($f \gg f_z$) with some attenuation
- **Highpass-notch filter** rejects sinusoidal signals at frequencies $f \approx f_z$ but passes signals at low frequencies ($f \ll f_z$) with some attenuation
- **Amplitude equalizer** or **bump filter** slightly amplifies or attenuates signals over a range of frequencies

Decomposition of transfer functions

- To reduce the sensitivity of a transfer function with respect to deviations of the element values and to simplify the tuning process of the filter, it is preferable to realize the filter by a **cascade** of the **first-order** and **second-order** filter sections
- Cascade approach consists of realizing each of the sections by an appropriate circuit and connecting these circuits in cascade
- Overall transfer function is expressed as a product of first-order and second-order functions

Optimum cascading sequence

- After a transfer function is decomposed into first-order and second-order functions designer has to choose the ***optimal cascading sequence***
- For the maximal dynamic range, the optimal sequence of the second-order filter sections is the sequence in which the preceding section has lower Q-factor than the following section
- If the input signal contains an undesired signal with very large amplitude, this signal has to be filtered out by the very first section, which should have a transfer function zero at the frequency of the undesired signal

Production yield

- Before the filter is manufactured, the effects of manufacturing **tolerances** and component **imperfections** have to be analyzed
- Designer should predict variations of the filter performances and the production yield
- **Yield** is the ratio of (a) the number of manufactured filters satisfying the specification to (b) the total number of manufactured filters
- High yield is desirable for **profitability**

Sensitivity

- The simplest way to predict the yield is to use the concept of **sensitivity** assuming that the component changes are small

- Single-parameter **relative sensitivity** of a function

$$S_{x_i}^F = \frac{x_i}{F} \frac{\partial F}{\partial x_i}$$

- **Expected relative variation** in function

$$\frac{\Delta F}{F} = \sum_{i=1}^n S_{x_i}^F \frac{\Delta x_i}{x_i}$$

- Example: If a sensitivity is 1, then a 1% change in the variable (component value) will cause a 1% change in the function; when a sensitivity is zero, then any change in variable will not affect the function

Upper limit of the relative variation

- **Worst-case method** gives the absolute relative variation assuming that all changes are at their extreme

$$\left. \frac{\Delta F}{F} \right|_{\text{worst case}} = \sum_{i=1}^n \left| S_{x_i}^F \frac{\Delta x_i}{x_i} \right|$$

- **Schoeffler criterion** method is closer to the variation obtained by statistical computations

$$\left. \frac{\Delta F}{F} \right|_{\text{Schoeffler}} = \sqrt{\sum_{i=1}^n \left| S_{x_i}^F \frac{\Delta x_i}{x_i} \right|^2}$$

- **Monte Carlo method** relies on extensive simulation of the filter realization (circuit) with randomly chosen element values

Osetljivost amplitudske funkcije

$$H(s) = \frac{1}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

The squared magnitude response is

$$M^2(\omega) = \frac{1}{(-\omega^2 + \omega_p^2)^2 + \left(\frac{\omega_p}{Q_p}\right)^2 \omega^2}$$

Amplitudska funkcija - pol

The sensitivity of the magnitude response to the pole magnitude is


$$S_{\omega_p}^{M(\omega)}(\omega) = -\frac{2\left(1 - \frac{\omega^2}{\omega_p^2}\right) + \frac{\omega^2}{\omega_p^2 Q_p^2}}{\left(1 - \frac{\omega^2}{\omega_p^2}\right)^2 + \frac{\omega^2}{\omega_p^2 Q_p^2}}$$

The extremes of $S_{\omega_p}^{M(\omega)}(\omega)$ are

$$S_{\omega_p}^{M(\omega)}(\omega)\Big|_{\min} \approx -Q_p \quad \text{for} \quad \frac{\omega}{\omega_p} \approx 1 - \frac{1}{2Q_p} \quad \text{and} \quad Q_p \gg 1$$

$$S_{\omega_p}^{M(\omega)}(\omega)\Big|_{\max} \approx Q_p \quad \text{for} \quad \frac{\omega}{\omega_p} \approx 1 + \frac{1}{2Q_p} \quad \text{and} \quad Q_p \gg 1$$

Amplitudska funkcija - pol

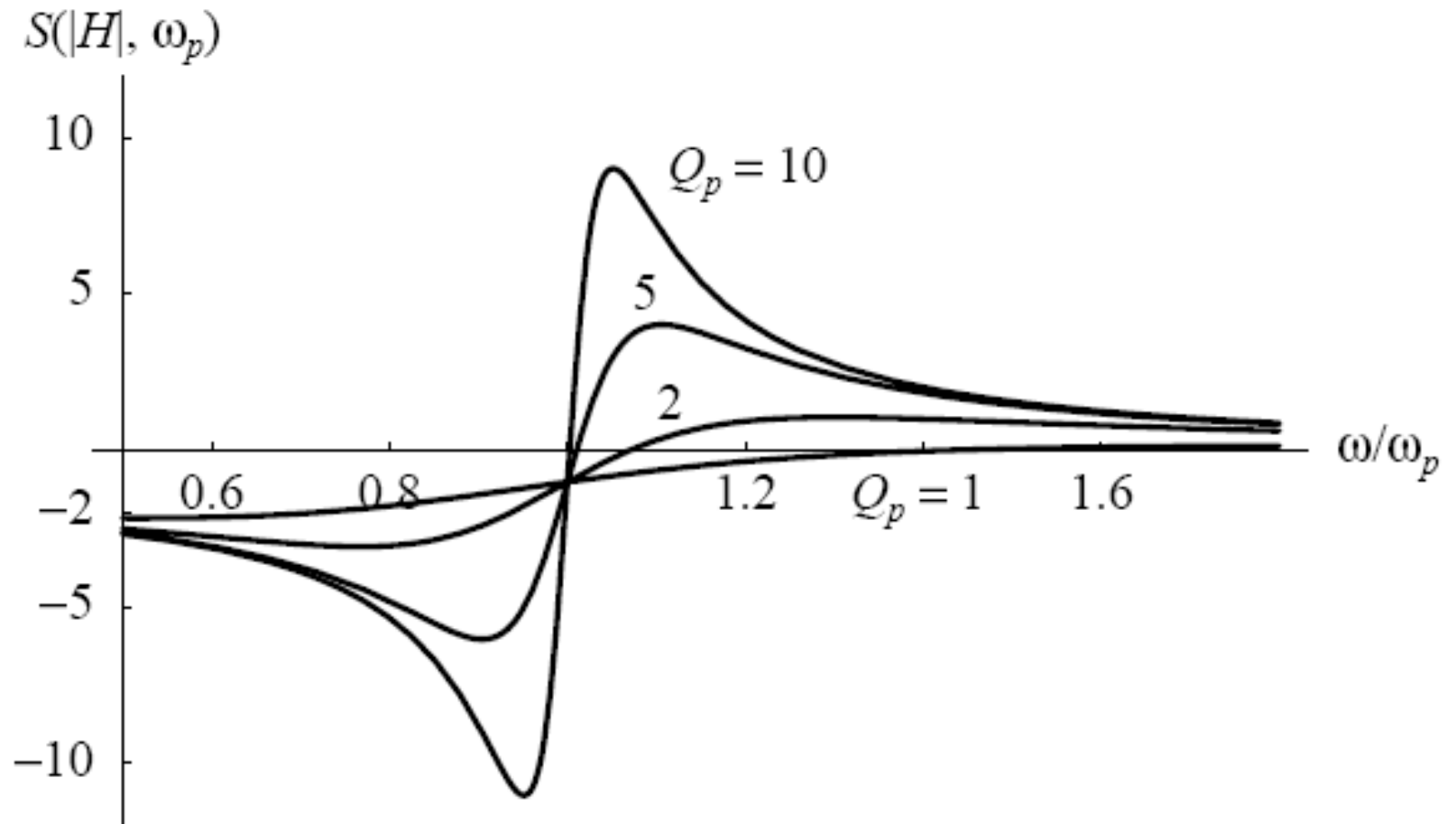

Amplitudska funkcija – Q-factor


the sensitivity to the pole Q-factor is

$$S_{Q_p}^{M(\omega)}(\omega) = \frac{\frac{\omega^2}{\omega_p^2 Q_p^2}}{\left(1 - \frac{\omega^2}{\omega_p^2}\right)^2 + \frac{\omega^2}{\omega_p^2 Q_p^2}}$$

$$S_{Q_p}^{M(\omega)}(\omega) \Big|_{\max} = 1$$

$$\left| S_{\omega_p}^{M(\omega)}(\omega) \right|_{\max} \approx Q_p \left| S_{Q_p}^{M(\omega)}(\omega) \right|_{\max}$$

Amplitudska funkcija – Q-factor

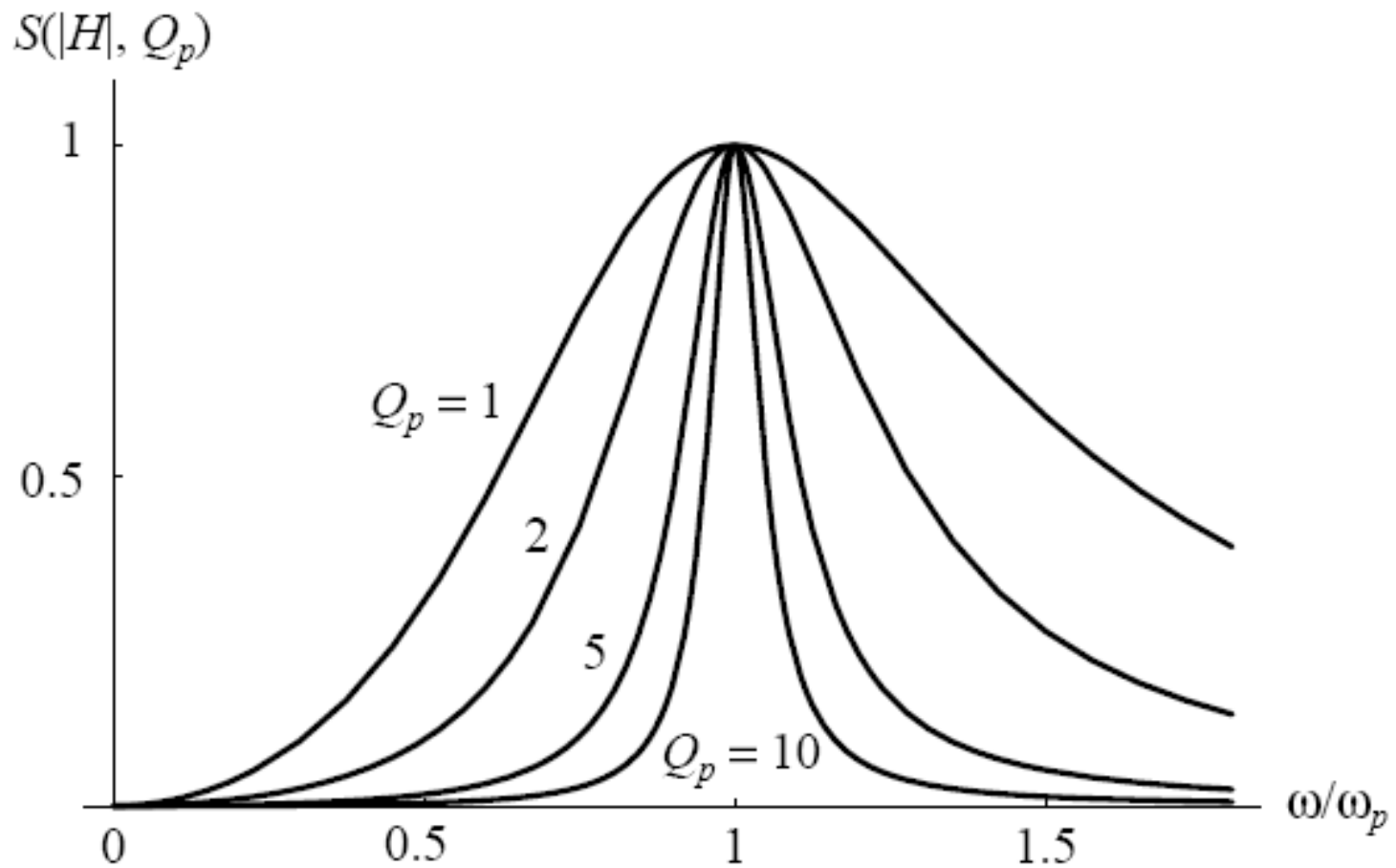

Najgori slučaj

$$S_{\omega_p}^{M(\omega)}(\omega) \Big|_{\max} \approx Q_p$$

$$S_{Q_p}^{M(\omega)}(\omega) \Big|_{\max} = 1$$

Zavisi od
komponenti

$$\frac{\Delta M(\omega)}{M(\omega)} \Big|_{\text{worst case}} = \sum_i \left| S_{\omega_p}^{M(\omega)} S_{x_i}^{\omega_p} \frac{\Delta x_i}{x_i} \right| + \sum_i \left| S_{Q_p}^{M(\omega)} S_{x_i}^{Q_p} \frac{\Delta x_i}{x_i} \right|$$

Zavisi od
funkcije
prenosa

Zavisi od
izbora
električnog
kola

Zavisi od
funkcije
prenosa

Zavisi od
izbora
električnog
kola

Osetljivost slabljenja


$$\Delta G(\omega) \approx S_{x_i}^{G(\omega)} \frac{\Delta x_i}{x_i} = \frac{20}{\ln 10} S_{x_i}^{M(\omega)} \frac{\Delta x_i}{x_i} \approx 8.686 S_{x_i}^{M(\omega)} \frac{\Delta x_i}{x_i}$$

Osetljivost na nule prenosa

$$H(s) = \frac{s^2 + \omega_z^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

$$S_{\omega_z}^{M(\omega)}(\omega) = \frac{2}{1 - \frac{\omega^2}{\omega_p^2} \frac{\omega_p^2}{\omega_z^2}}$$

$S(|H|, \omega_z)$

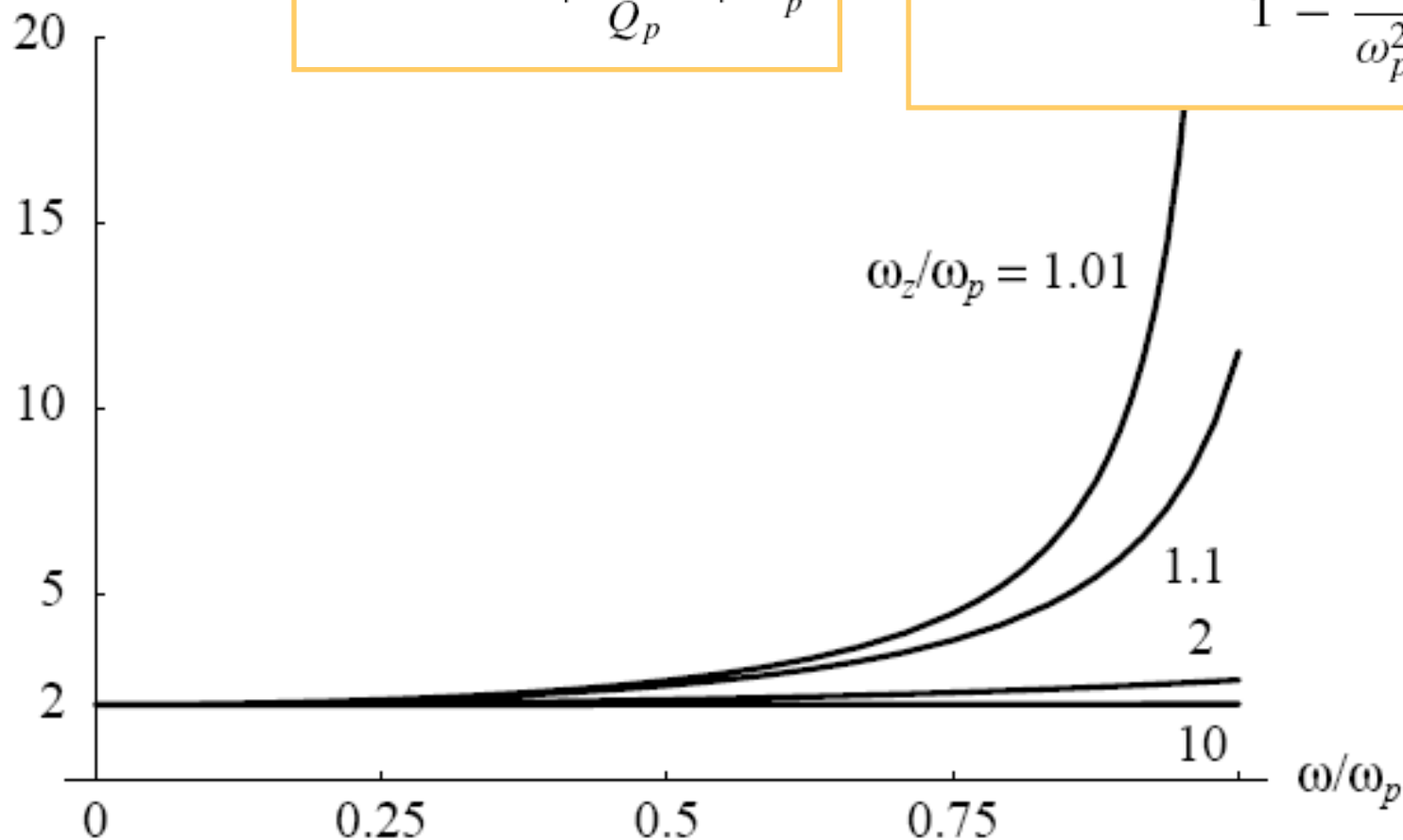

Sumarna osetljivost

$$S_x^F = \sum_{i=1}^n S_{x_i}^F$$

$$\sum_{i=1}^{n_R} S_{R_i}^{Q_P} = \sum_{k=1}^{n_C} S_{C_k}^{Q_P} = 0$$

$$\sum_{i=1}^{n_R} S_{R_i}^{\omega_P} = \sum_{k=1}^{n_C} S_{C_k}^{\omega_P} = -1$$

Osetljivost je 0!

$$\frac{\Delta M(\omega)}{M(\omega)} = S_{\omega_p}^{M(\omega)} \frac{\Delta x}{x} \left(\sum_{i=1}^{n_R} S_{R_i}^{\omega_p} - \sum_{k=1}^{n_C} S_{C_k}^{\omega_p} \right)$$

$$\frac{\Delta R}{R} = -\frac{\Delta C}{C} = \frac{\Delta x}{x}$$

Temperaturni
koeficijent je isti
a suprotnog znaka

$$\frac{\Delta M(\omega)}{M(\omega)} = 0$$

Tolerancije elemenata

$$x = x_0(1 + \gamma_x)$$

$$-\frac{x_t}{100} < \gamma_x < +\frac{x_t}{100}$$

Gausova
distribucija

$$x_t = 300\sigma(\gamma_x)\%$$

Temperaturne promene

$$x = x_0(1 + \alpha_x \Delta T)$$

Sobna
temperatura

$$T = T_0 + \Delta T$$

$$\alpha_x = 100 \cdot 10^{-6} \text{ 1/K}$$

temperature coefficient of 100 ppm/K

Efekti starenja

$$x = x_0(1 + \beta_x \sqrt{t})$$

β_x is in ppm/yr

Vrednost i relativna promena

$$x = x_0(1 + \gamma_x + \alpha_x \Delta T + \beta_x \sqrt{t})$$

Srednja
vrednost

$$\frac{\Delta x}{x_0} = \gamma_x + \alpha_x \Delta T + \beta_x \sqrt{t}$$

$$\mu\left(\frac{\Delta x}{x_0}\right) \approx \mu(\gamma_x) + \mu(\alpha_x) \Delta T + \mu(\beta_x) \sqrt{t}$$

Standardna
devijacija

$$\sigma\left(\frac{\Delta x}{x_0}\right) \approx \sqrt{(\sigma(\gamma_x))^2 + (\sigma(\alpha_x) \Delta T)^2 + (\sigma(\beta_x))^2 t}$$

Proizvod osetljivost-pojačanje

$$A(s) = A_0 \frac{1}{1 + \frac{s}{\omega_{3dB}}} = \frac{\omega_G}{s + \omega_{3dB}}$$

Model za opamp

$$|A(j\omega_G)| \approx 1$$

$$A_0/\sqrt{2}$$

$$\Gamma_A^F = A S_A^F$$

Najgori slučaj


$$\frac{\Delta F}{F} = \Gamma_A^F \frac{\Delta A}{A^2}$$

Za proračun osetljivosti

$$I_A = Q_p \Gamma_A^{\omega_p} + \frac{1}{2} \Gamma_A^{Q_p}$$

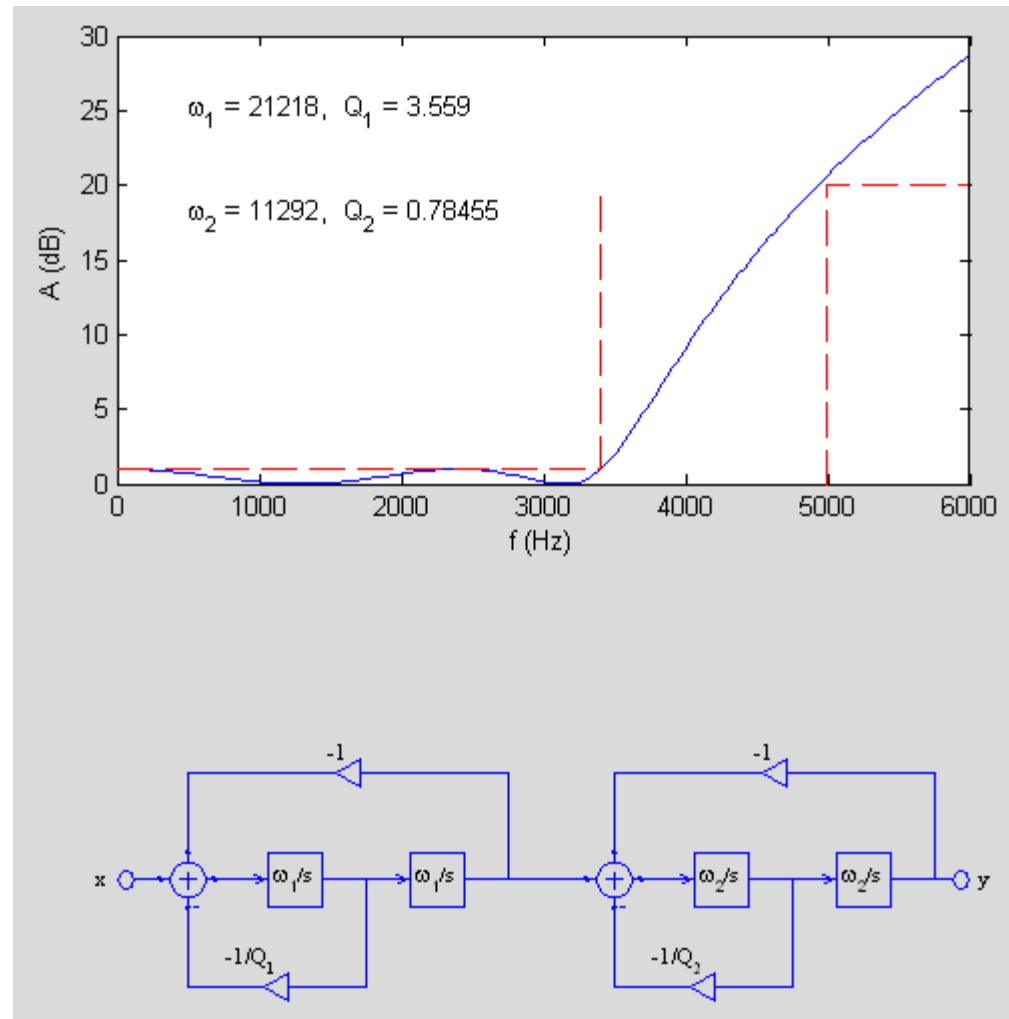Example specification and design

```
Fp = 3400; Fs = 5000;  
Ap = 1; As = 20;  
[n, Wn] = cheb1ord(Fp, Fs, Ap, As, 's')  
[z,p,k] = cheb1ap(n, Ap);  
Q = (-abs(p)./(2*real(p)));  
w = round(abs(p)*(2*pi*Fp));  
D1 = [1 w(1)/Q(1) w(1)^2];  
D2 = [1 w(2)/Q(2) w(2)^2];  
N1 = w(1)^2; N2 = w(2)^2;  
D = conv(D1,D2);  
N = 10^(-Ap/20)*conv(N1,N2);  
Fplot = 6000;  
f = 0:Fplot/200:Fplot;  
H = freqs(N,D,2*pi*f);  
M = -20*log10(abs(H));  
subplot(2,1,1)  
plot(f,M,[0 Fp Fp],[Ap Ap As],'r--',...  
[Fs Fs Fplot],[0 As As],'r--')  
xlabel('f (Hz)'); ylabel('A (dB)')  
subplot(2,1,2)  
drawschematic(0,0,4,5,8,'b')
```




Example sensitivity analysis


Pole magnitudes and Q-factors
decreased by 10%:
passband specification violated


Pole magnitudes and Q-factors
increased by 10%:
stopband specification violated

See the Matlab script
Lecture06sens.m

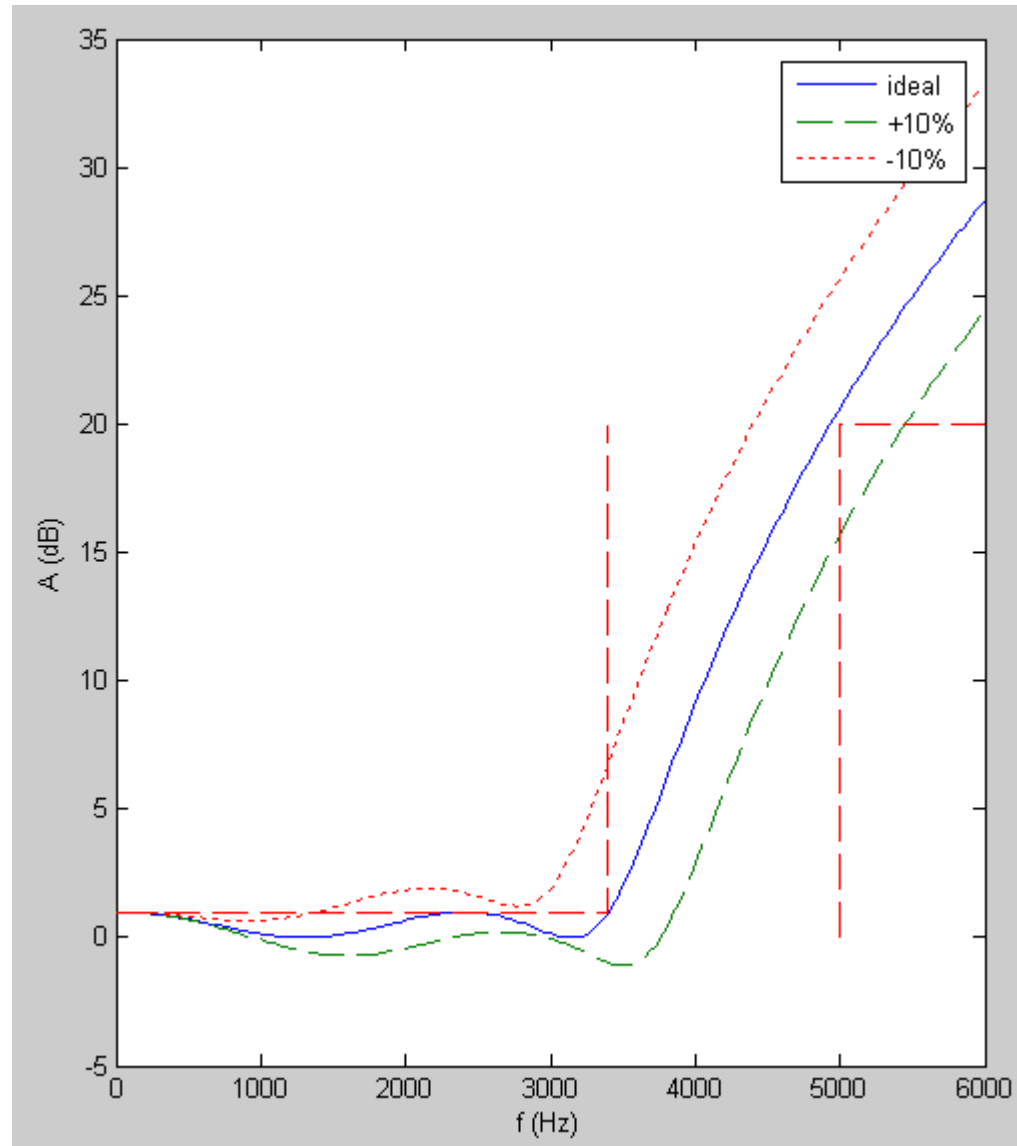


Anadigm chip

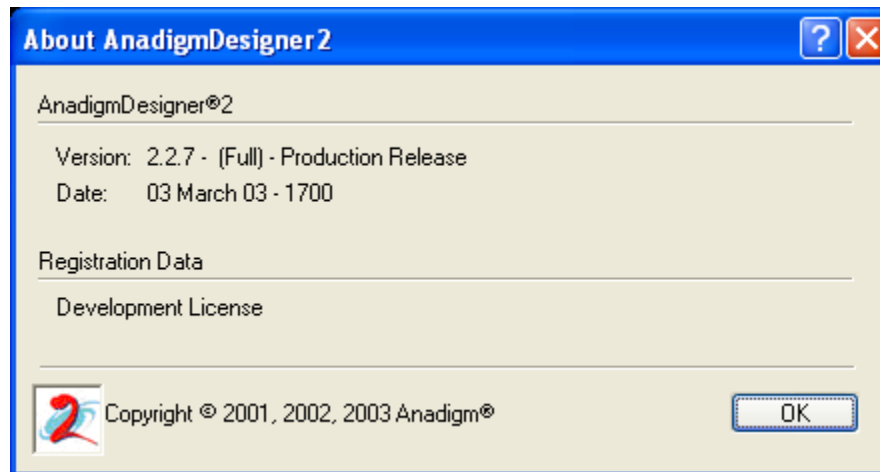

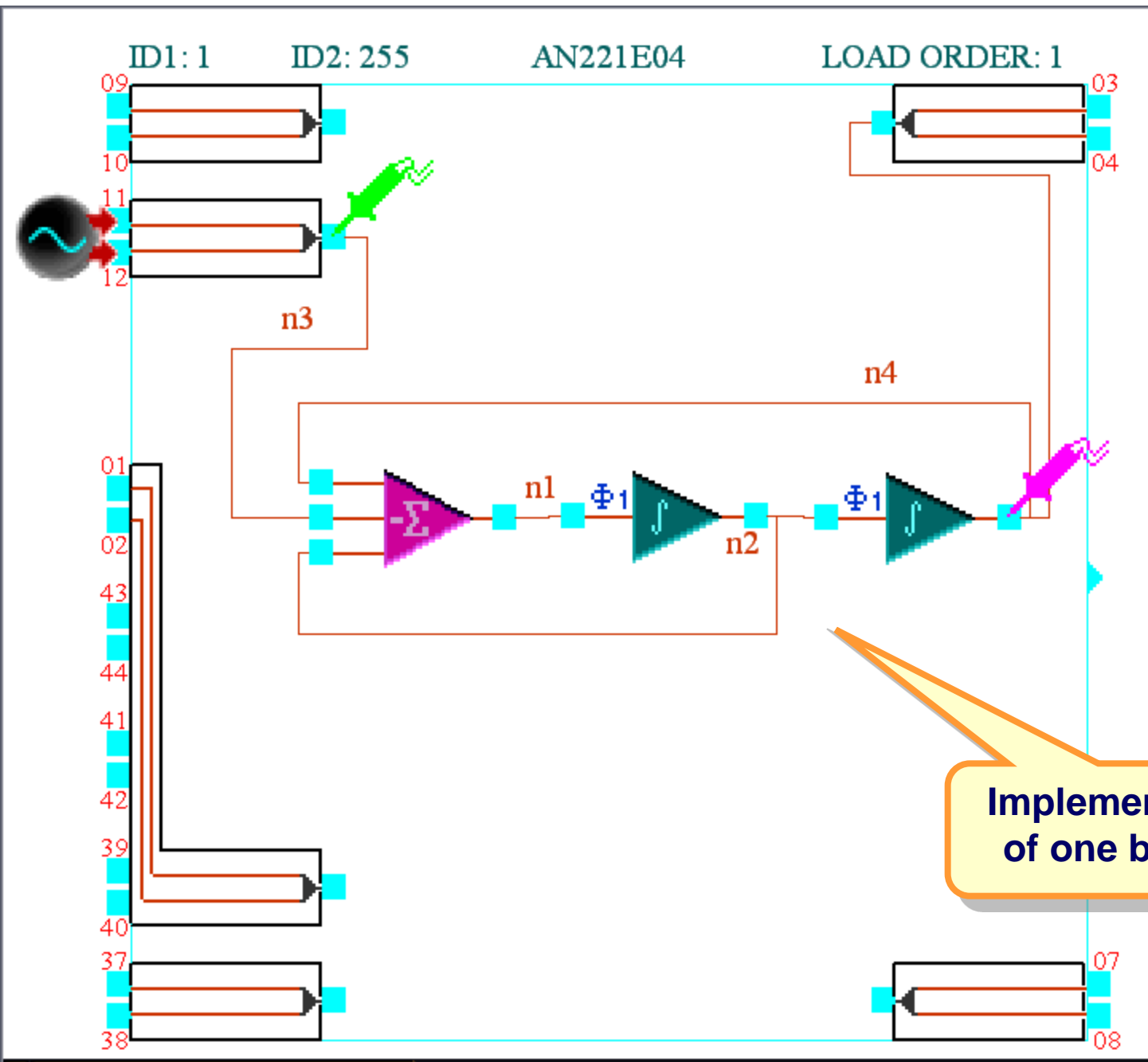

Signal Generator Control

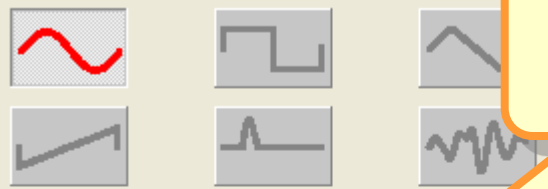

Output
 Differential Single

Signal Data
Peak Amplitude Differential Offset

2 Volts 0 Volts



Frequency Phase
2.3 k Hz 0 Degrees

Common Mode Offset
2 Volts


Passband simulation

AnadigmDesigner2 - Biquad.ad2

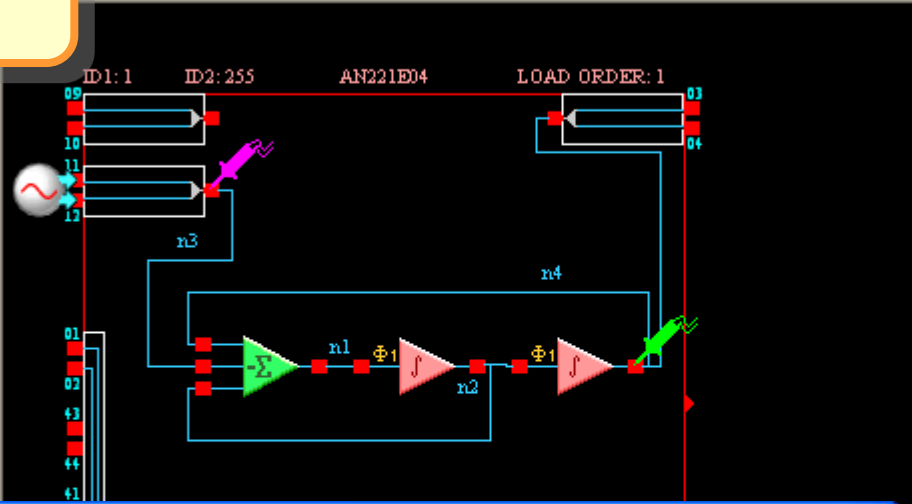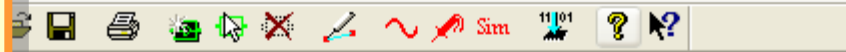Edit Simulate Configure Settings Dynamic Config. Target View Tools Help



Oscilloscope - Biquad.ad2

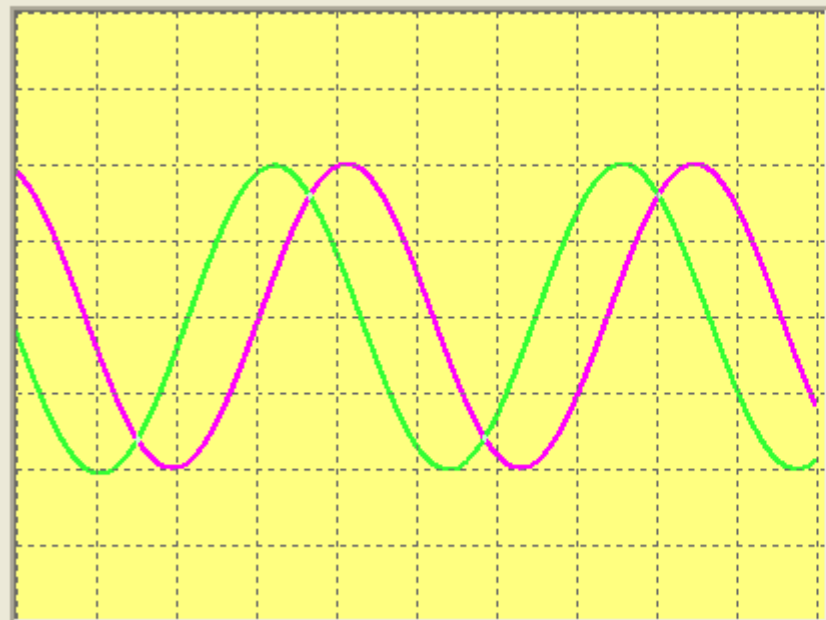

Start: 1.000 ms End: 2.000 ms


Display Data Volts Per Division Position Voltage

Display Data	Volts Per Division	Position	Voltage
Channel 1	1.0 V		
Channel 2	1.0 V		
Channel 3	1.0 V		
Channel 4	1.0 V		

Time Per Division: 100 μs Time:

Grid Cursor Close

Signal Generator Control

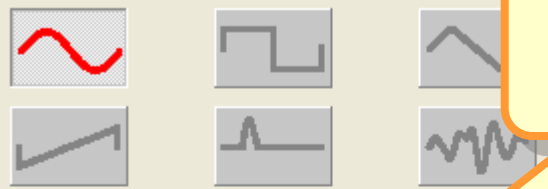

Stopband simulation

Output
 Differential Single

Signal Data
Peak Amplitude Differential Offset


2 Volts 0 Volts

Frequency Phase
10 k Hz 0 Degrees


Common Mode Offset
2 Volts

AnadigmDesigner2 - Biquad.ad2

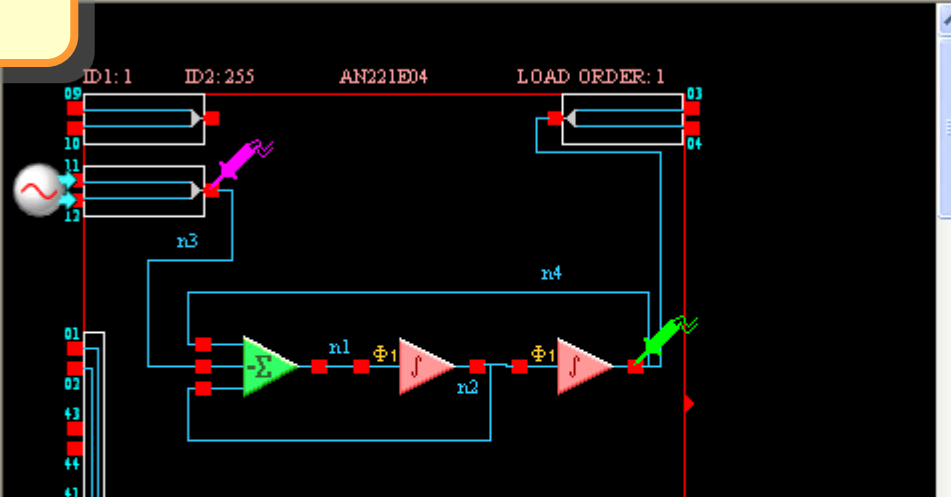File Edit Simulate Configure Settings Dynamic Config. Target View Tools Help



Oscilloscope - Biquad.ad2

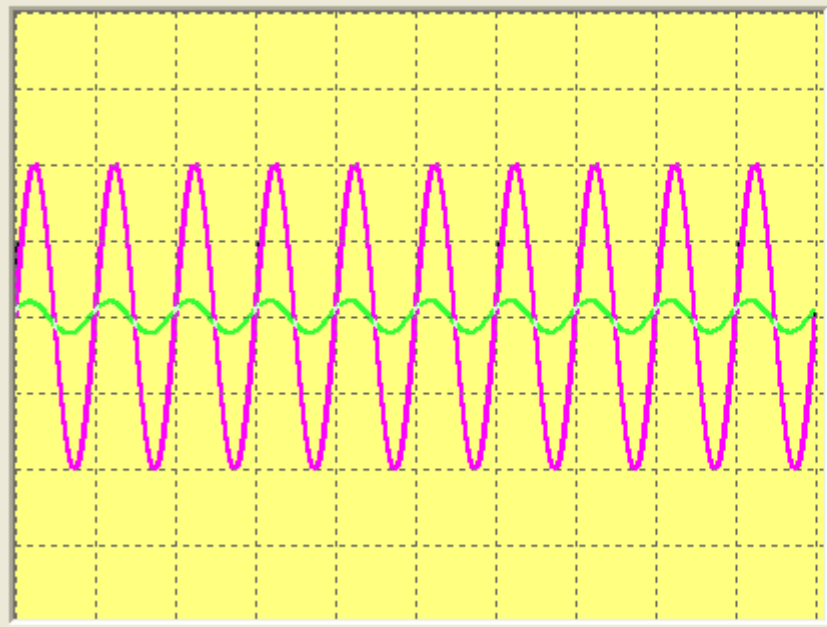

Display Data	Volts Per Division	Position	Voltage
Channel 1	1.0 V		
Channel 2	1.0 V		
Channel 3	1.0 V		
Channel 4	1.0 V		

Time Per Division: 100 μ s Time:

Start: 1.000 ms End: 2.000 ms Grid Cursor Close

Set CAM Parameters

ANx21 Standard (SumInv 1.1.0): Inverting Sum Stage

Anadigm Approved CAM

Instance name and clock frequency

Instance Name:
CLOCKA (kHz)

Notes

*****WARNING*****
It is not recommended to run this CAM's clock (CLOCKA)
at a frequency greater than 4 MHz.
*****WARNING*****

Symbol



OK

Cancel

Help

Documentation

C Code...

CAM Options

Input 3 Off On

Adder and gain implementation

CAM Parameters

Parameter:	Value:	Limits:	Realized
Gain 1 (UpperInput)	<input type="text" value="0.1"/>	0.0100 To 100	0.100
Gain 2 (MiddleInput)	<input type="text" value="0.5"/>	0.0100 To 25.5	0.500
Gain 3 (LowerInput)	<input type="text" value="1"/>	0.0100 To 25.5	1.00

Set CAM Parameters



ANx21 Standard (Integrator 2.0.1): Integrator

Anadigm Approved CAM


Instance name and clock frequency

Instance Name:
CLOCKA (kHz)

Notes

Notes area

Symbol

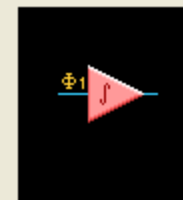

- OK
- Cancel
- Help
- Documentation
- C Code...


CAM Options

Reset: None Positive Signal Negative Signal
Polarity: Non-inverting Inverting
Input Sampling: Phase 1 Phase 2

Integrator implementation

CAM Parameters

Parameter:	Value:	Limits:	Realized
Integration Const. [1/us]	<input type="text" value="0.03"/>	0.02500 To 5.695	0.0300

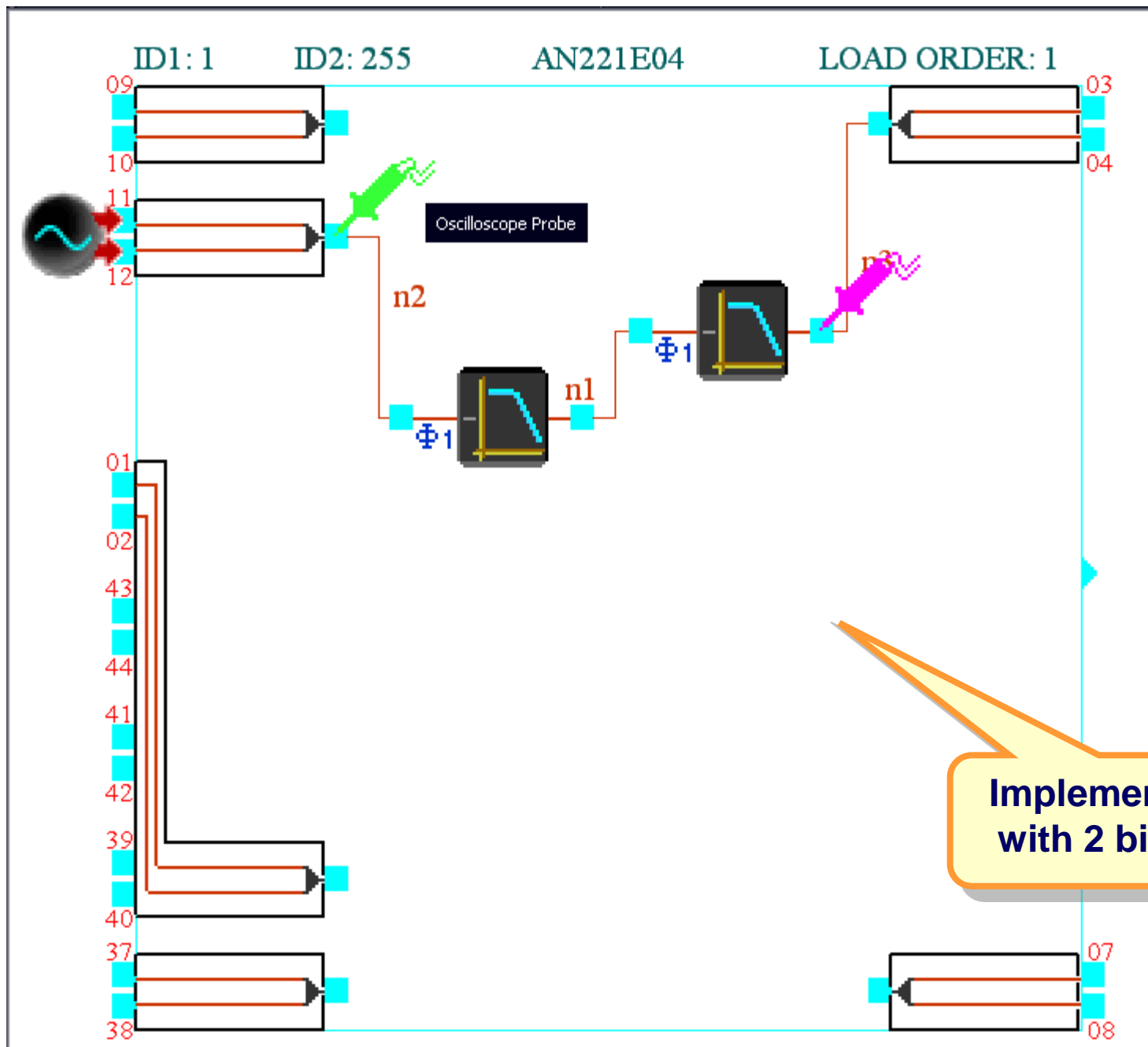

Signal Generator Control



Output

Differential Single Ended

Signal Data

Peak Amplitude

1 Volts

Differential Offset

0 Volts

Frequency

3.4 k Hz

Phase

0 Degrees


Common Mode Offset

2 Volts


**Passband
simulation**

adigmDesigner2 - Cheb_4.ad2

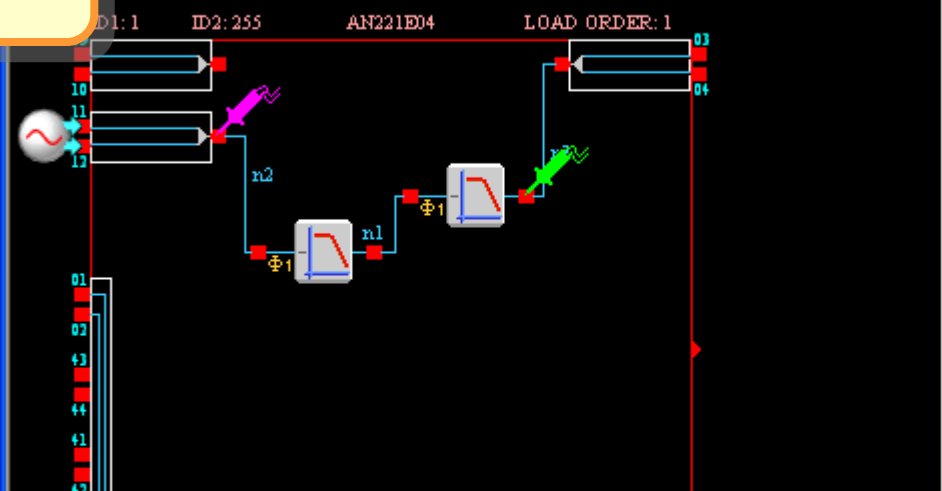Simulate Configure Settings Dynamic Config. Target View Tools Help



Oscilloscope - Cheb_4.ad2

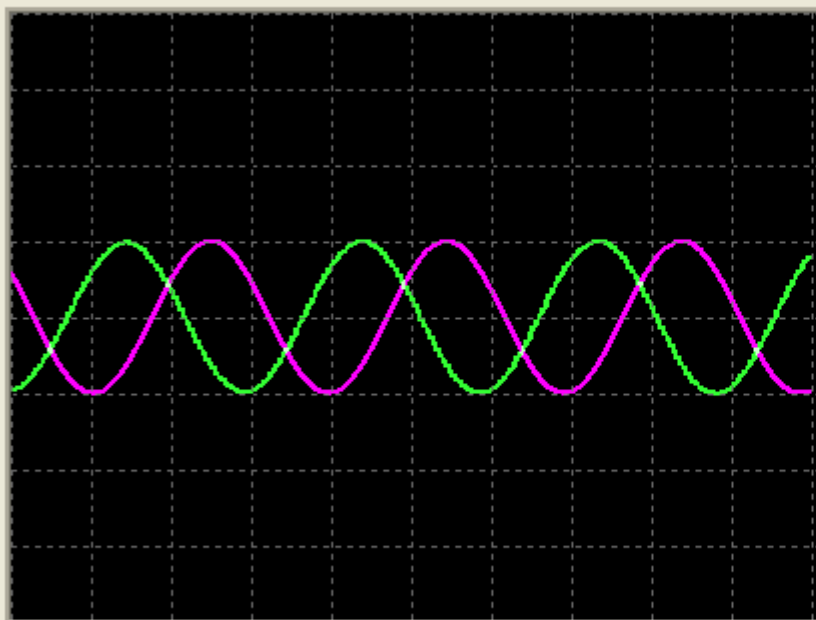


Display Data	Volts Per Division	Position	Voltage
Channel 1	1.0 V	0	
Channel 2	1.0 V	0	
Channel 3	1.0 V	0	
Channel 4	1.0 V	0	

Time Per Division: 100 μ s Time:

Grid Cursor Close

Signal Generator Control

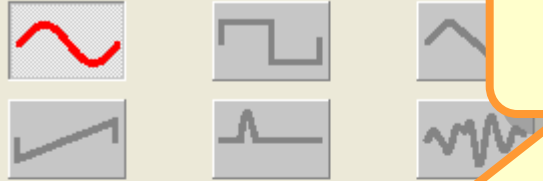

Stopband simulation

Output

Differential Single ended

Signal Data

Peak Amplitude

1 Volts

Differential Offset

0 Volts

Frequency

5 k Hz

Phase


0 Degrees

Common Mode Offset


2 Volts

AnadigmDesigner2 - Cheb_4.ad2

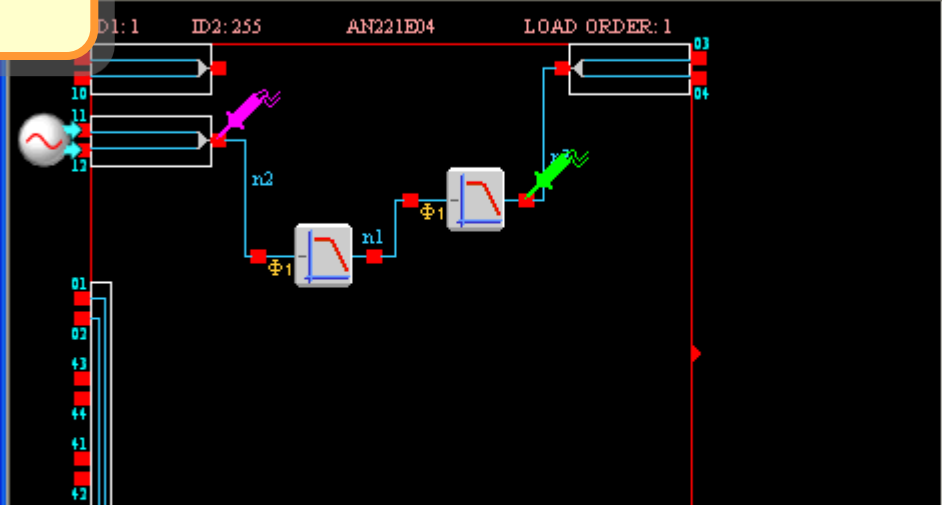File Edit Simulate Configure Settings Dynamic Config. Target View Tools Help



Oscilloscope - Cheb_4.ad2

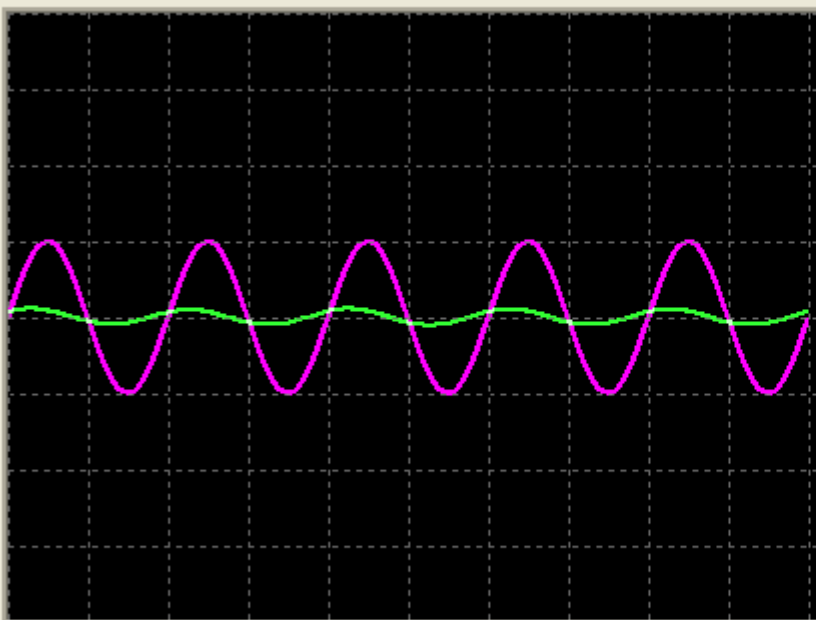

Start: 1.000 ms End: 2.000 ms

Display Data Volts Per Division Position Voltage

Display Data	Volts Per Division	Position	Voltage
Channel 1	1.0 V	0	
Channel 2	1.0 V	0	
Channel 3	1.0 V	0	
Channel 4	1.0 V	0	

Time Per Division: 100 μ s Time:

Grid Cursor Close

Set CAM Parameters

ANx21 Standard (FilterBiquad 1.4.0): Biquadratic Filter

Anadigm Approved CAM


Instance name and clock frequency

Instance Name:
CLOCKA (kHz)

Notes

This is an inverting filter. See the transfer function in the CAM Documentation.

Symbol

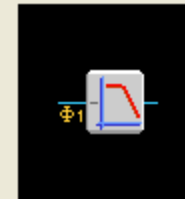

OK

Cancel

Help

Documentation

C Code...

CAM Options

Filter Type Low Pass High Pass Band Pass Band Stop
Input Sampling Phase 1 Phase 2

1st biquad implementation

CAM Parameters

Parameter:	Value:	Limits:	Realized
Corner Frequency [kHz]	<input type="text" value="3.3769"/>	0.500 To 25.0	3.38
Gain	<input type="text" value="1"/>	0.0740 To 100	1.00
Quality Factor	<input type="text" value="3.559"/>	0.0500 To 70.0	3.56

Set CAM Parameters ? X

ANx21 Standard (FilterBiquad 1.4.0): Biquadratic Filter Anadigm Approved CAM

Instance name and clock frequency


Instance Name:

CLOCKA (kHz)

Notes

This is an inverting filter. See the transfer function in the CAM Documentation.

Symbol

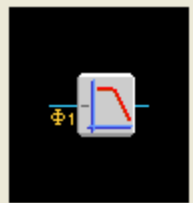

OK

Cancel

Help

Documentation

C Code...

CAM Options

Filter Type Low Pass High Pass Band Pass Band Stop

Input Sampling Phase 1 Phase 2

2nd biquad implementation

CAM Parameters

Parameter:	Value:	Limits:	Realized
Corner Frequency [kHz]	<input type="text" value="1.7972"/>	0.500 To 25.0	1.80
Gain	<input type="text" value="1"/>	0.139 To 100	1.00
Quality Factor	<input type="text" value="0.78455"/>	0.0835 To 70.0	0.784

