

Sinteza električnih filtara

Dr Miroslav Lutovac

Analog filter realizations

- After having accomplished the approximation step, the filter transfer function is known
- Next, the designer must choose a ***realization***, that is, an **electric circuit**
- Analog filters can be classified on the basis of their constituent components

Classification of analog filters

- **Passive RLC** filters
- **Operational amplifier RC** filters
(op amp active RC filters)
- Switched-capacitor (SC) filters
- Operational transconductance amplifier (OTA) filters
- Current-conveyor (CC) filters
- Microwave filters
- Electromechanical filters
- Crystal filters

Passive RLC filters

- Consist of passive macrocomponents: resistors, capacitors, and inductors (coils and transformers)
- Do not require a power supply
- Drawbacks:
 - Exhibit a significant passband loss,
 - Inductors cannot be miniaturized
- Practical at frequencies up to a few hundred MHz
- Important in deriving realizations of some active filters, such as active RC, OTA, and current-conveyor filters

Active RC filters

- Can be reduced in size and weight, especially when implemented as integrated circuits
- Manufacturing can be automated with high production yield
- Made out of resistors, capacitors, and operational amplifiers
- Disadvantages:
 - Require a power supply
 - Output signal can be distorted if the input signal is too large
 - Extra noise is generated in active devices
- Operate over the frequency range from 0.1 Hz to 500 kHz


Op amp active RC filters

Realizations

Classification of biquadratic realizations

- **Low Q -factor** realizations ($Q < 2$) exhibit no problems with tolerances, no need for tuning, minimal number of passive components, and only one operational amplifier
- **Medium Q -factor** realizations ($2 < Q < 20$) selected on the basis of minimum gain-sensitivity product, simple tuning, minimal number of passive components, and only one operational amplifier
- **High Q -factor** realizations ($20 < Q$) require two operational amplifiers, sensitivities are lower than the sensitivity of single-amplifier biquads

Lowpass low-Q-factor

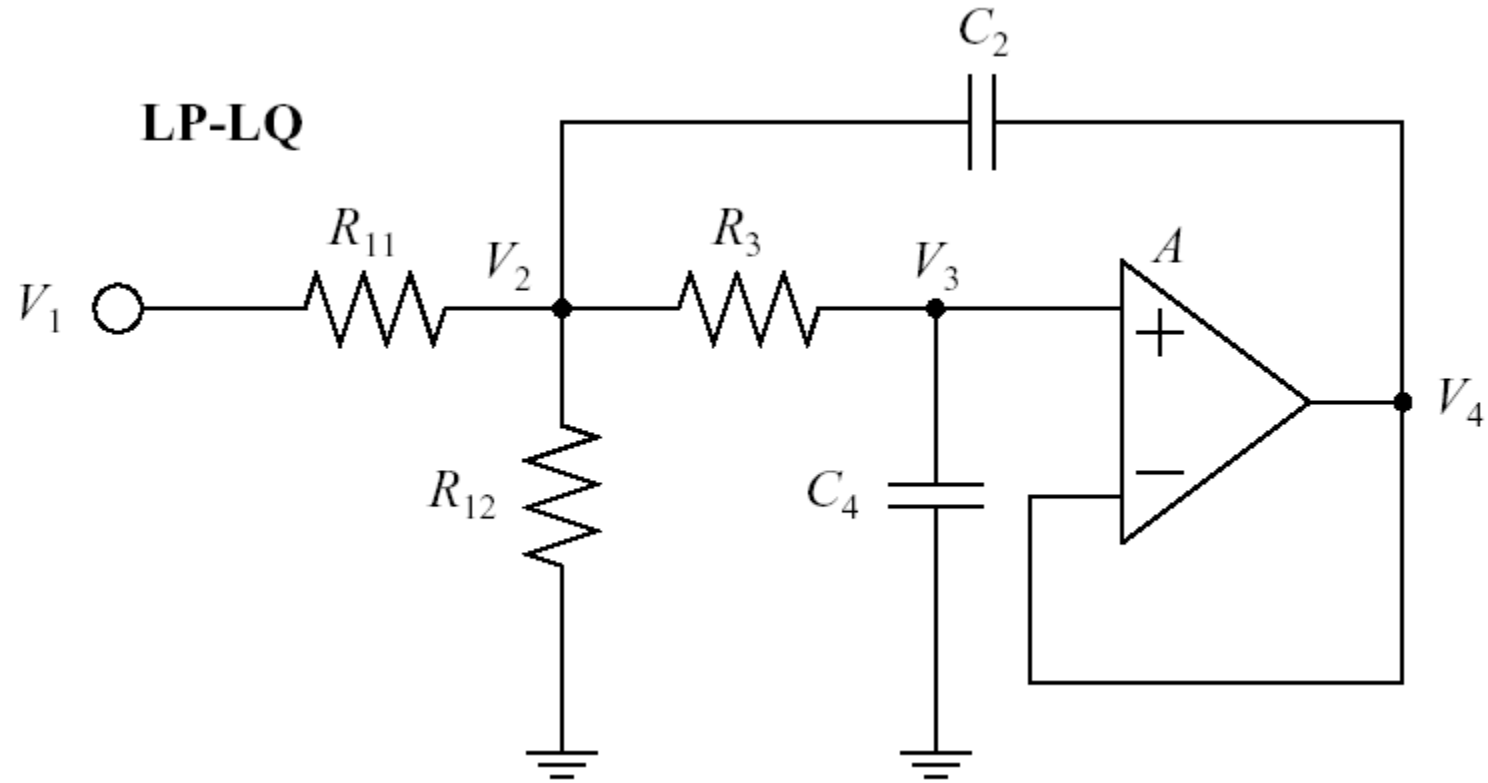

$$H_{LP}(s) = \frac{V_4}{V_1} = K \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun LP low-Q

$$P = R_3/R_1$$

$$0.1 < P < 10$$

$$K \leq 1$$


$$R_{11} = R_{11}(K, Q_p, \omega_p, C_x, P) = \frac{R_1}{K}$$

$$R_{12} = R_{12}(K, Q_p, \omega_p, C_x, P) = \frac{R_1}{1 - K}$$


$$C_2 = C_2(K, Q_p, \omega_p, C_x, P) = Q_p^2 C_x \frac{(1 + P)^2}{P}$$

$$R_3 = R_3(K, Q_p, \omega_p, C_x, P) = P R_1$$

$$C_4 = C_4(K, Q_p, \omega_p, C_x, P) = C_x$$
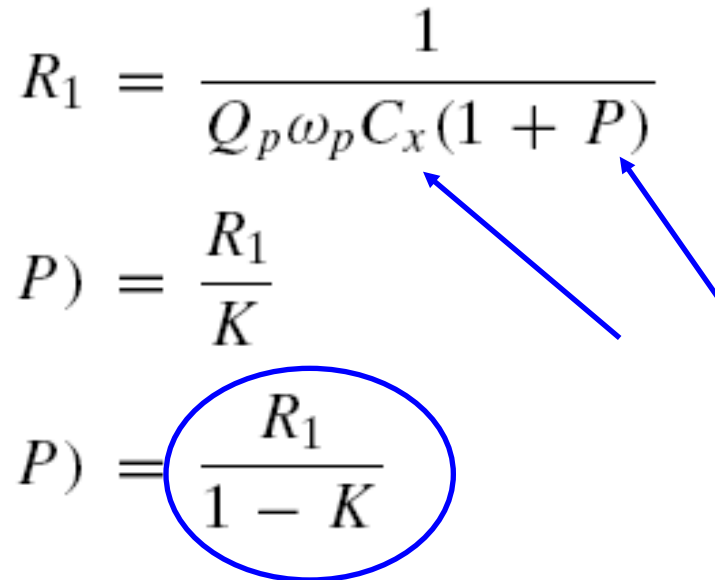
$$R_1 = \frac{1}{Q_p \omega_p C_x (1 + P)}$$


Matlab primer

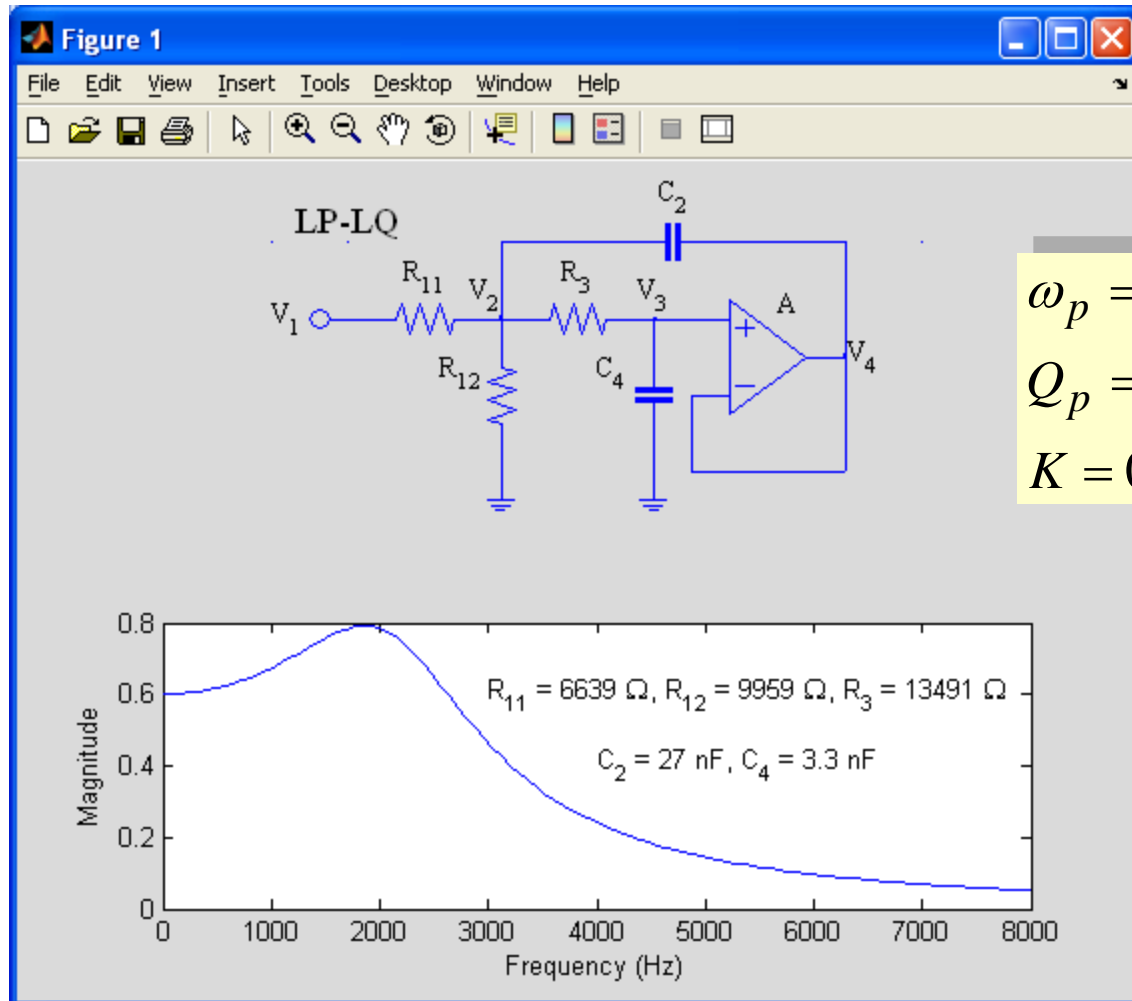

% Given a second-order lowpass transfer function we identify

fp = 2300;

wp = 2*pi*fp;

Qp = 1.2;

% Choose $K < 1$

K = 0.6;

% Choose $0.1 < P=R3/R1 < 10$

P = 3.3865;

% Choose C4

nano = 10⁽⁻⁹⁾; Cx = 3.3*nano;

C4 = Cx;

% Compute element values

C2 = 2*Qp²*Cx*(1+(1+P²)/(2*P));

R1 = 1/(wp*Cx*Qp*(1+P));

R3 = P*R1; R11 = R1/K; R12 = R1/(1-K);

% Generate transfer function in terms of element values

num = R12;


den = [(C2*C4*R11*R12*R3) (C4*R11*R12+C4*R11*R3+C4*R12*R3) (R11+R12)];

f = 0:80:8000; w = i*2*pi*f; H = num./polyval(den,w);

subplot(2,1,1); drawlplq(0,0,4,5,10,'b')

subplot(2,1,2); plot(f,abs(H))

Highpass Low-Q-factor

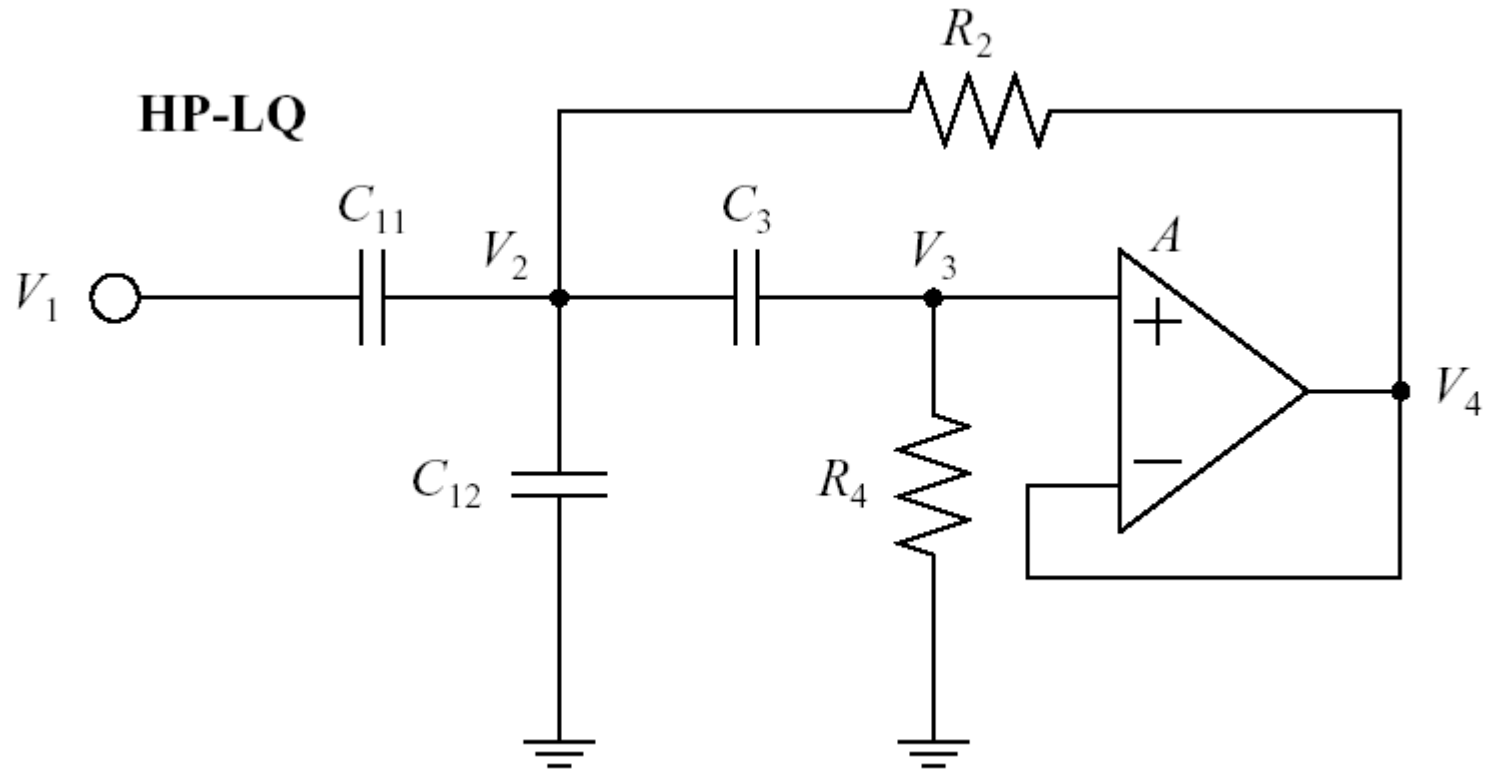

$$H_{HP}(s) = \frac{V_4}{V_1} = K \frac{s^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun HP Low-Q

$$K \leq 1$$

$$P = R_4/R_2$$

$$0.1 < P < 10$$

K, Q_p, ω_p, C_x, P

$$C_1 = C_x$$

$$C_{11} = C_{11}(K, Q_p, \omega_p, C_x, P) = K C_x$$


$$C_{12} = C_{12}(K, Q_p, \omega_p, C_x, P) = C_x - C_{11}$$

$$C_3 = C_3(K, Q_p, \omega_p, C_x, P) = C_x \frac{P - 2Q_p^2 - \sqrt{P^2 - 4PQ_p^2}}{2Q_p^2}$$

$$R_2 = R_2(K, Q_p, \omega_p, C_x, P) = \frac{1}{Q_p \omega_p (C_1 + C_3)}$$

$$R_4 = R_4(K, Q_p, \omega_p, C_x, P) = P R_2$$

Bandpass low-Q-factor

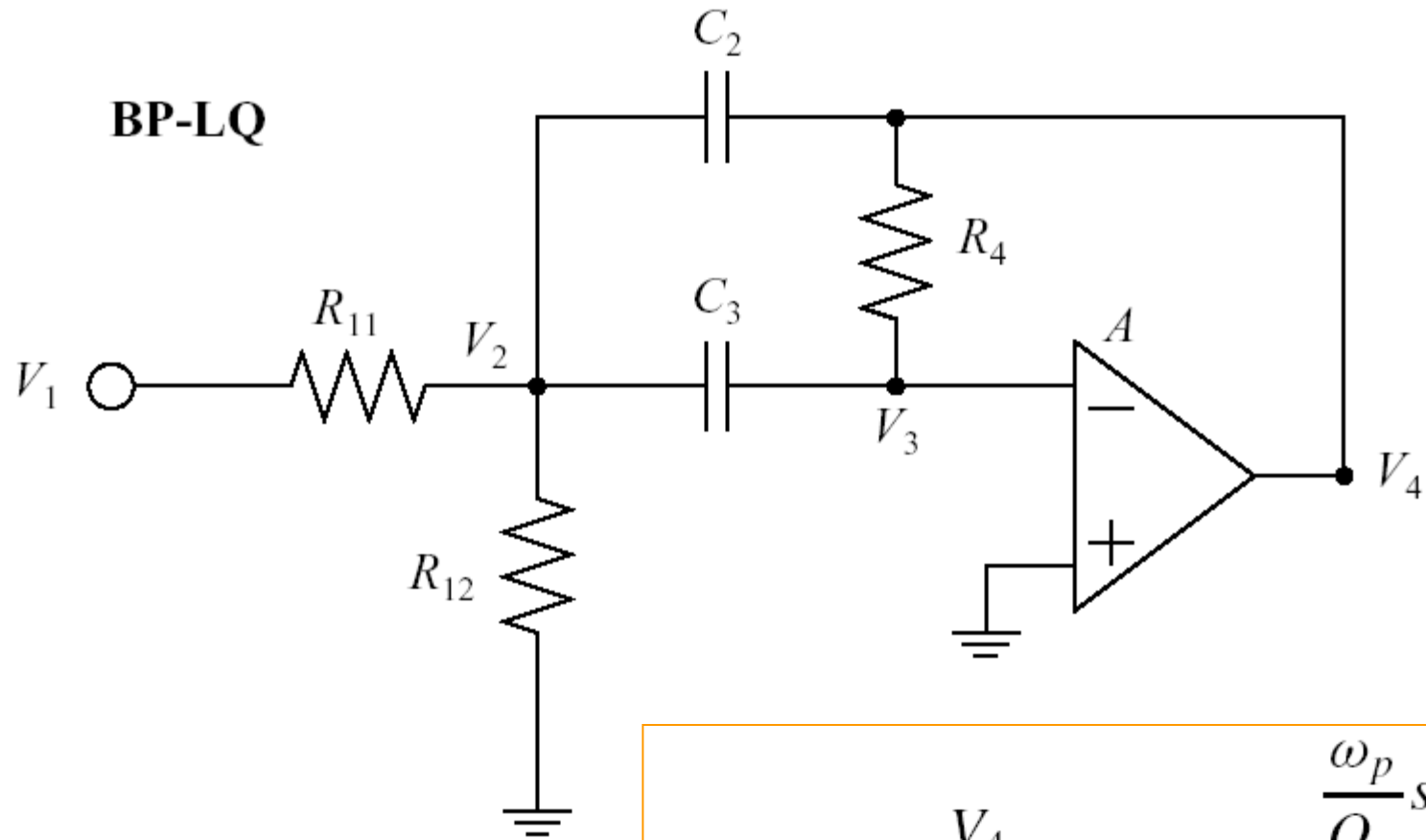

$$H_{BP}(s) = \frac{V_4}{V_1} = K \frac{\frac{\omega_p}{Q_p} s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun BP low-Q (1)

$$P = R_4/R_1$$

$$P \geq 4Q_p^2$$

$$C_2 = C_2(K, Q_p, \omega_p, C_x, P) = C_x$$

$$C_3 = C_3(K, Q_p, \omega_p, C_x, P) = C_x \frac{P - 2Q_p^2 - \sqrt{P^2 - 4PQ_p^2}}{2Q_p^2}$$

$$R_1 = \frac{1}{Q_p \omega_p (C_2 + C_3)}$$

$$R_4 = R_4(K, Q_p, \omega_p, C_x, P) = PR_1$$

$$R_{11} = R_{11}(K, Q_p, \omega_p, C_x, P) = \frac{C_3 R_4}{K(C_2 + C_3)}$$

$$R_{12} = R_{12}(K, Q_p, \omega_p, C_x, P) = \frac{C_3 R_1 R_4}{C_3 R_4 - R_1 K (C_2 + C_3)}$$


Proračun BP low-Q (2)

$$P = 4Q_p^2$$


$$C_2 = C_3$$

$$K = 2Q_p^2$$

~~R_{12}~~ BP-LQ

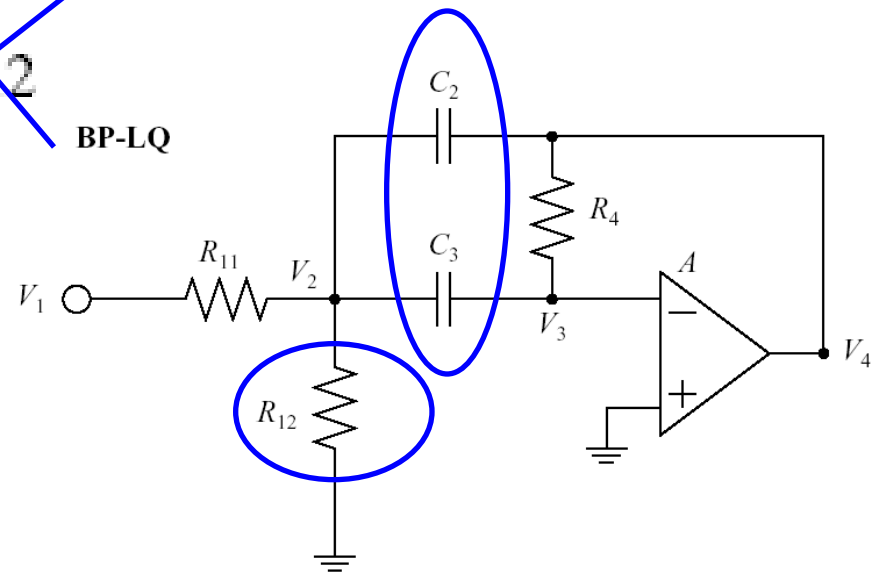

Bandreject low-Q-factor

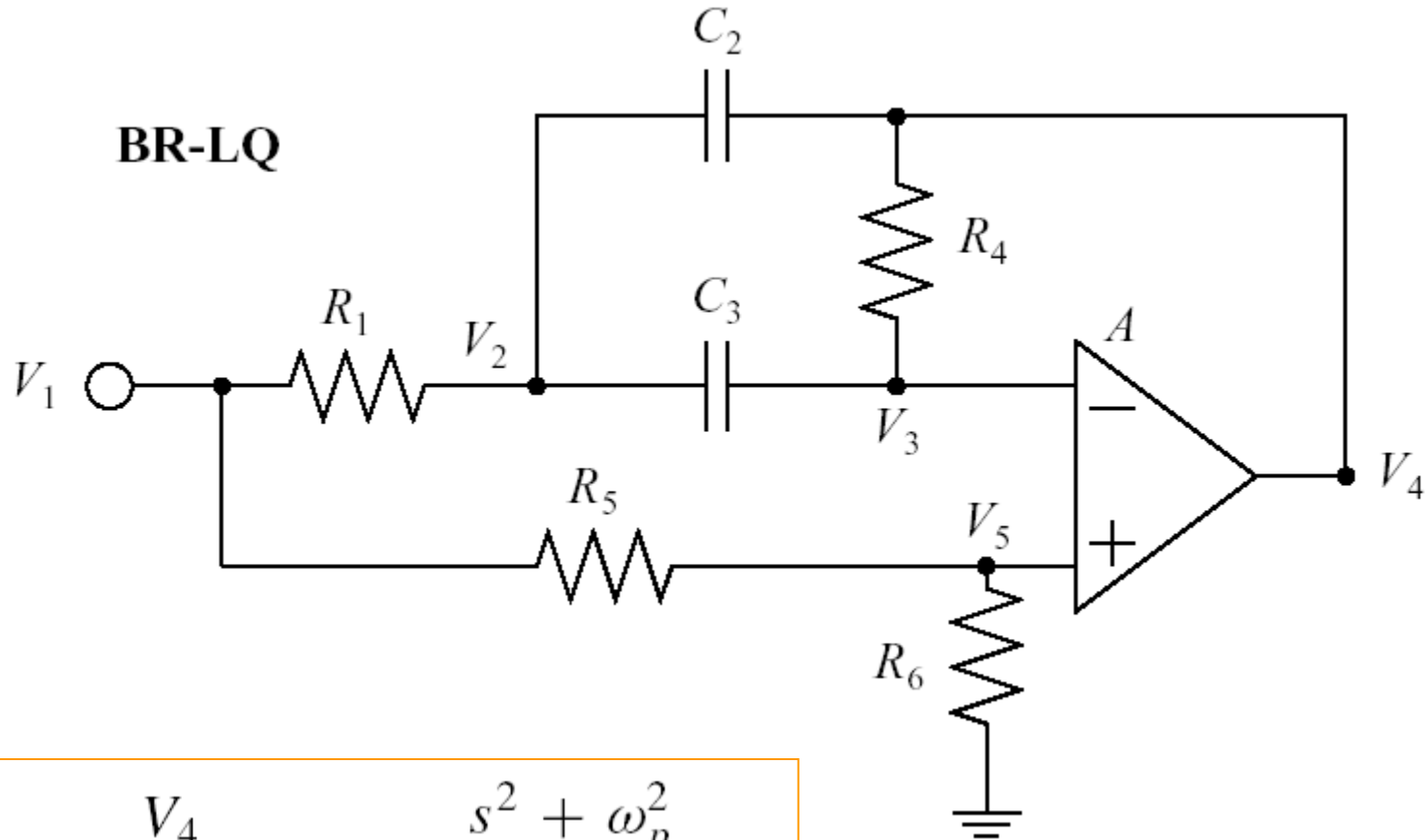

$$H_{BR}(s) = \frac{V_4}{V_1} = K \frac{s^2 + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun BR low-Q (1)

$$C_2 = C_2(K, Q_p, \omega_p, C_x, R_x) = C_x$$

$$P = \frac{4}{\left(\frac{1}{K} - 1\right) \left(2 - \left(\frac{1}{K} - 1\right) Q_p^2\right)}$$

$$C_3 = C_3(K, Q_p, \omega_p, C_x, P, R_x) = C_x \frac{P - 2Q_p^2 - \sqrt{P^2 - 4PQ_p^2}}{2Q_p^2}$$

$$R_1 = R_1(K, Q_p, \omega_p, C_x, P, R_x) = \frac{1}{Q_p \omega_p (C_2 + C_3)}$$

$$R_4 = R_4(K, Q_p, \omega_p, C_x, P, R_x) = PR_1$$

$$R_5 = R_5(K, Q_p, \omega_p, C_x, P, R_x) = R_x \left(\frac{1}{K} - 1\right)$$

$$R_6 = R_6(K, Q_p, \omega_p, C_x, P, R_x) = R_x$$

$$\frac{1}{1 + \frac{1}{Q_p^2}} < K < 1$$

$$Q_p < \frac{1}{\sqrt{\frac{1}{K} - 1}}$$

Proračun BR low-Q (2)

$$K = \frac{1}{1 + \frac{1}{2Q_p^2}}$$


$$P \geq 4Q_p^2$$

$$C_2 = C_3 = C_x$$

$$P = R_4/R_1$$

$$\omega_p = 1/(R_1 R_4 C_2 C_3)$$

Allpass low-Q-factor

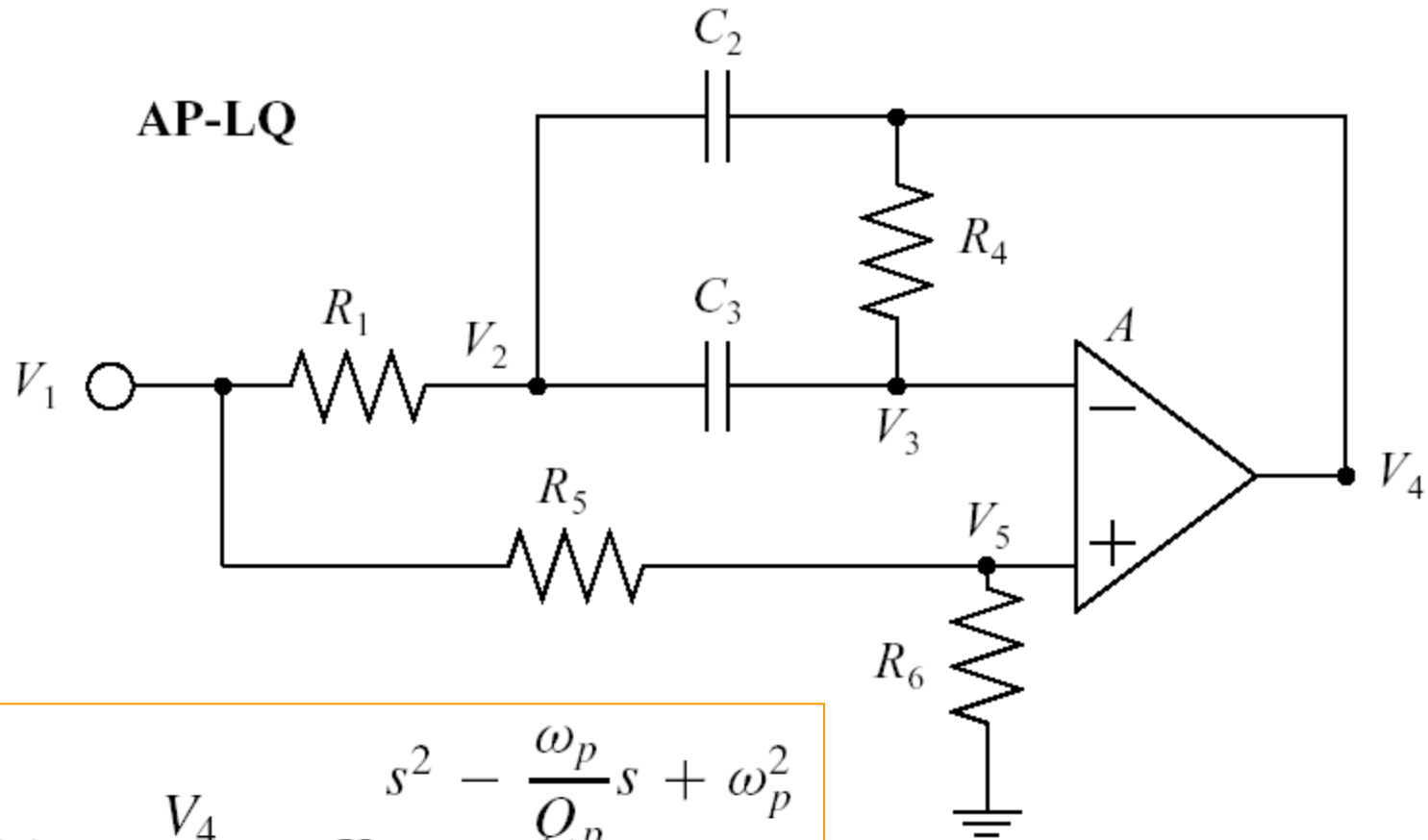

$$H_{AP}(s) = \frac{V_4}{V_1} = K \frac{s^2 - \frac{\omega_p}{Q_p}s + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun AP low-Q (1)

$$C_2 = C_2(K, Q_p, \omega_p, C_x, R_x) = C_x$$

$$P = \frac{4}{\left(\frac{1}{K} - 1\right) \left(2 - \left(\frac{1}{K} - 1\right) Q_p^2\right)}$$

$$C_3 = C_3(K, Q_p, \omega_p, C_x, P, R_x) = C_x \frac{P - 2Q_p^2 - \sqrt{P^2 - 4PQ_p^2}}{2Q_p^2}$$

$$R_1 = R_1(K, Q_p, \omega_p, C_x, P, R_x) = \frac{1}{Q_p \omega_p (C_2 + C_3)}$$

$$R_4 = R_4(K, Q_p, \omega_p, C_x, P, R_x) = PR_1$$

$$R_5 = R_5(K, Q_p, \omega_p, C_x, P, R_x) = R_x \left(\frac{1}{K} - 1\right)$$

$$R_6 = R_6(K, Q_p, \omega_p, C_x, P, R_x) = R_x$$

$$\frac{1}{1 + \frac{2}{Q_p^2}} < K < 1$$

Proračun AP low-Q (2)

$$K = \frac{1}{1 + \frac{1}{Q_p^2}}$$




$$C_2 = C_3 = C_x$$

R_x - C_x

- **1 kΩ ≤ R_x ≤ 100 kΩ**
- ✓ 15V napajanje
- ✓ 15*15 = 225
- 225 mW ≤ snaga ≤ 2 mW
- 1 MΩ ≤ R_x, tolerancije, šum

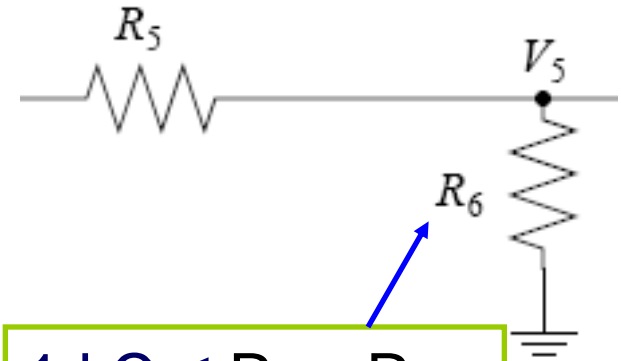- **100 pF ≤ C_x ≤ 1 μF**
- C_x ≤ 100 pF, parazitni efekti veza ...
- C_x ≥ 1 μF, tolerancije, gubici, ...




$$1 \text{ k}\Omega \leq R_5 + R_6$$

$$R_6 \leq 1 \text{ k}\Omega$$

$$0 \leq R_x$$

$$0 \leq C_x$$

Lowpass medium-Q-factor

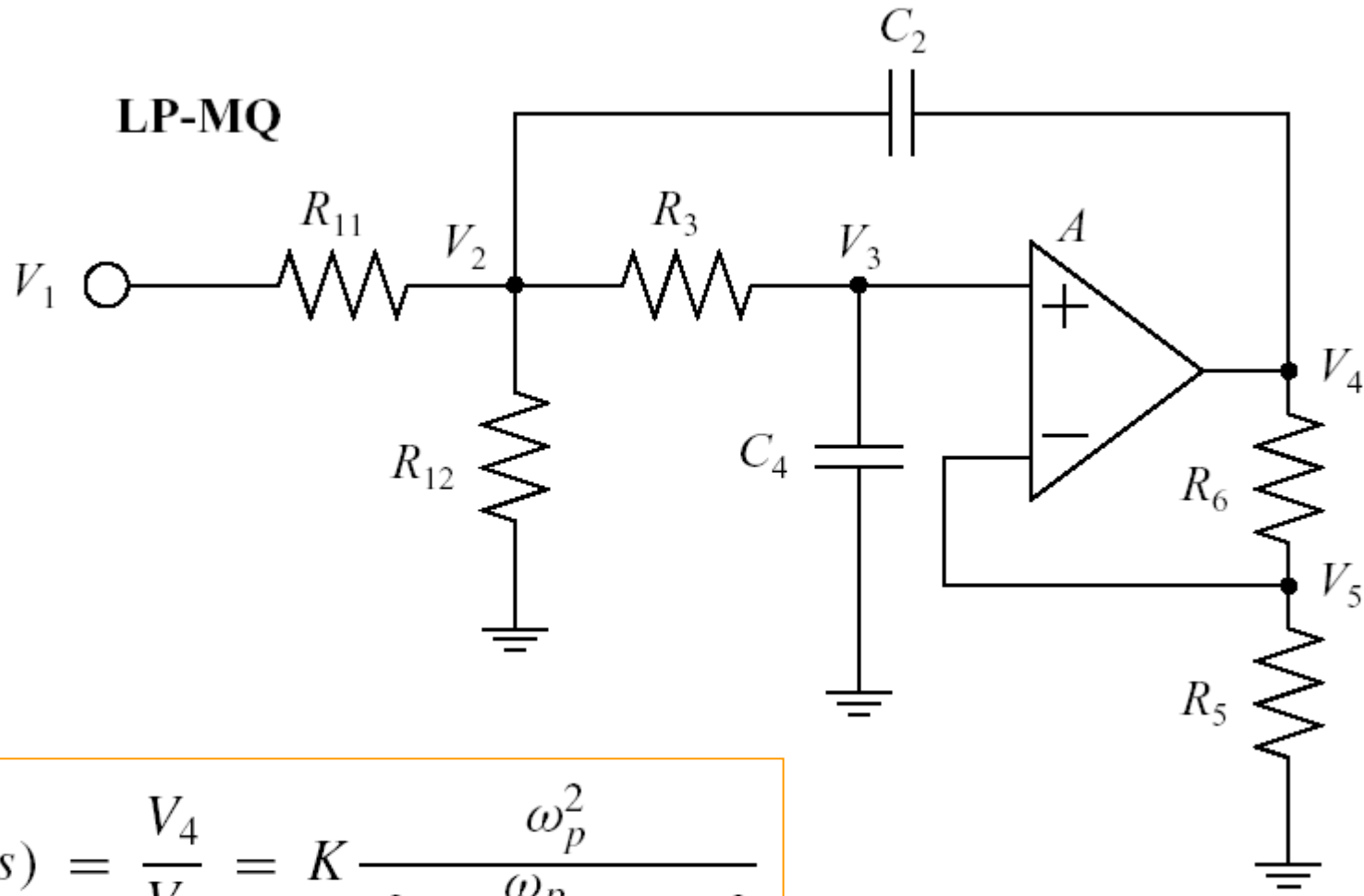

$$H_{LP}(s) = \frac{V_4}{V_1} = K \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun LP medium-Q

$$C_2 = C_2(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = C_{2x}$$

$$C_4 = C_4(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = C_{4x}$$

$$R_1 = \frac{1}{\omega_p \sqrt{C_{2x} C_{4x} P}}$$

$$R_3 = R_3(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = P R_1$$

$$R_5 = R_5(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = R_x$$

$$R_6 = R_6(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = R_x \left(\frac{C_4(1 + P)}{C_2} - \frac{\sqrt{P \frac{C_4}{C_2}}}{Q_p} \right)$$

$$K_0 = 1 + \frac{R_6}{R_x}$$

$$R_{11} = R_{11}(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = \frac{R_1 K_0}{K}$$



$$P = R_3 / R_1$$

$$R_{12} = R_{12}(K, Q_p, \omega_p, C_{2x}, C_{4x}, P, R_x) = \frac{R_1 K_0}{K_0 - K}$$


Proračun LP medium-Q

$$K_{LQ} \leq 1$$

$$1 \leq K_{MQ}$$

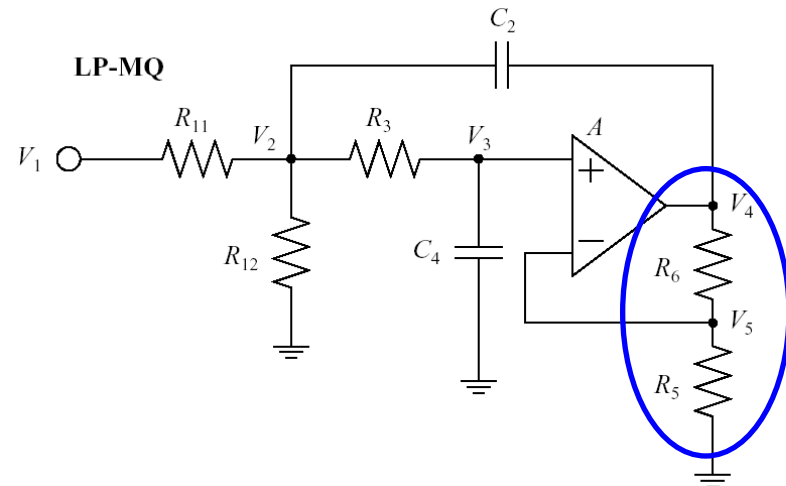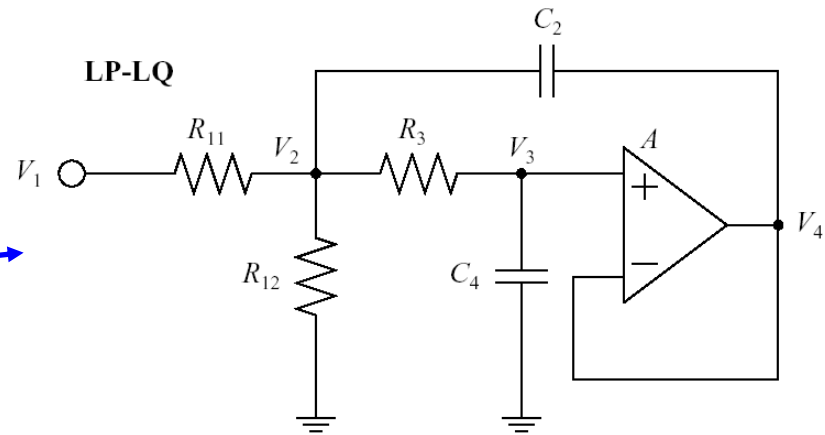

Highpass medium-Q-factor

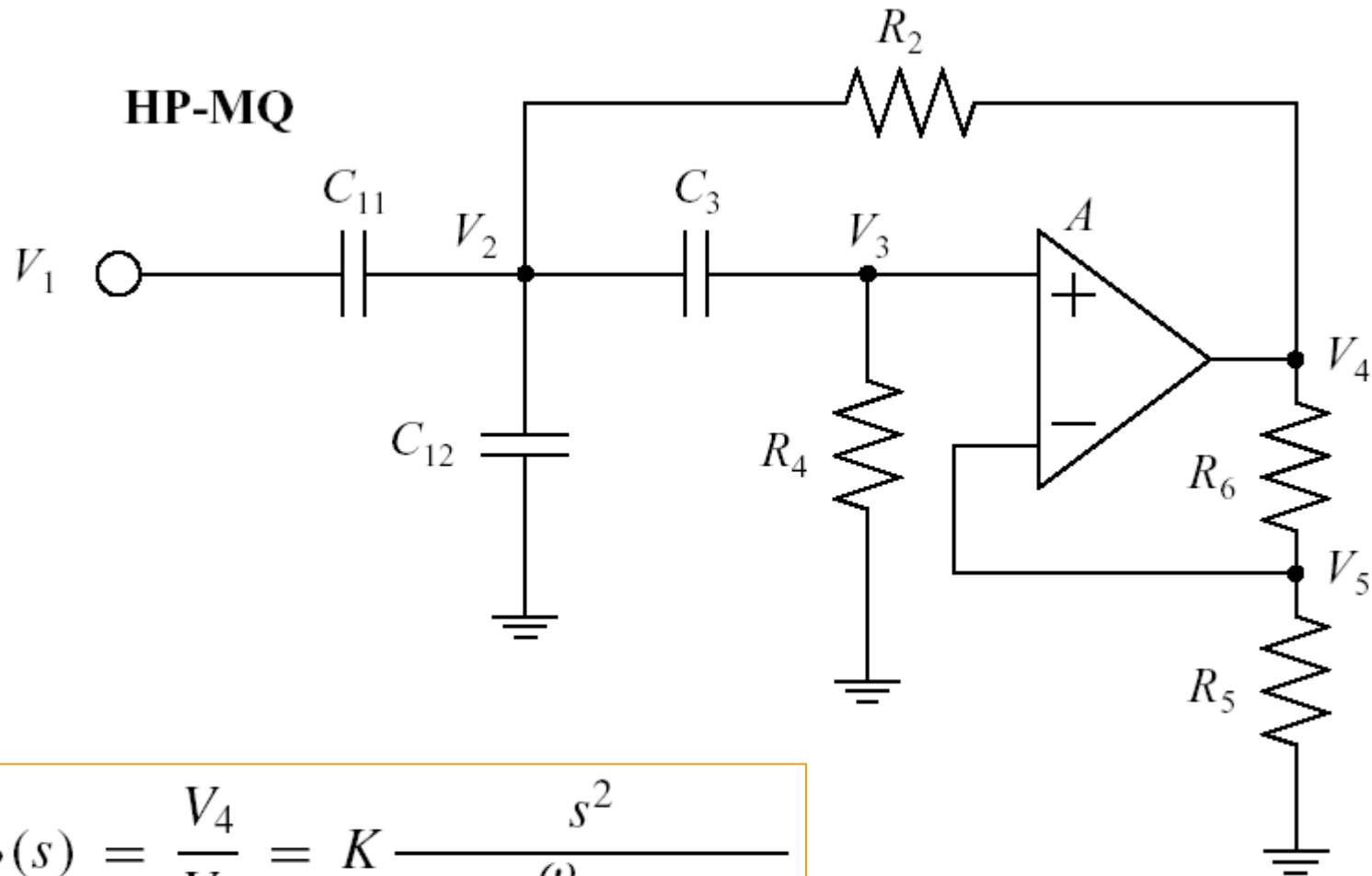

$$H_{HP}(s) = \frac{V_4}{V_1} = K \frac{s^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun HP medium-Q

$$C_1 = C_{1x}$$

$$C_3 = C_3(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = C_{3x}$$

$$R_2 = R_2(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = \frac{1}{\omega_p \sqrt{C_{1x} C_{3x} P}}$$

$$P = R_4 / R_2$$

$$R_4 = R_4(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = P R_2$$

$$R_5 = R_5(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = R_x$$

$$R_6 = R_6(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = R_x \left(\frac{1 + \frac{C_1}{C_3}}{P} - \frac{\sqrt{\frac{C_1}{PC_3}}}{Q_p} \right)$$



$$K_0 = 1 + \frac{R_6}{R_x}$$

$$C_{11} = C_{11}(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = \frac{C_1 K}{K_0}$$


$$C_{12} = C_{12}(K, Q_p, \omega_p, C_{1x}, C_{3x}, P, R_x) = C_1 - C_{11}$$

Proračun HP medium-Q

$$K_{LQ} \leq 1$$
$$1 \leq K_{MQ}$$

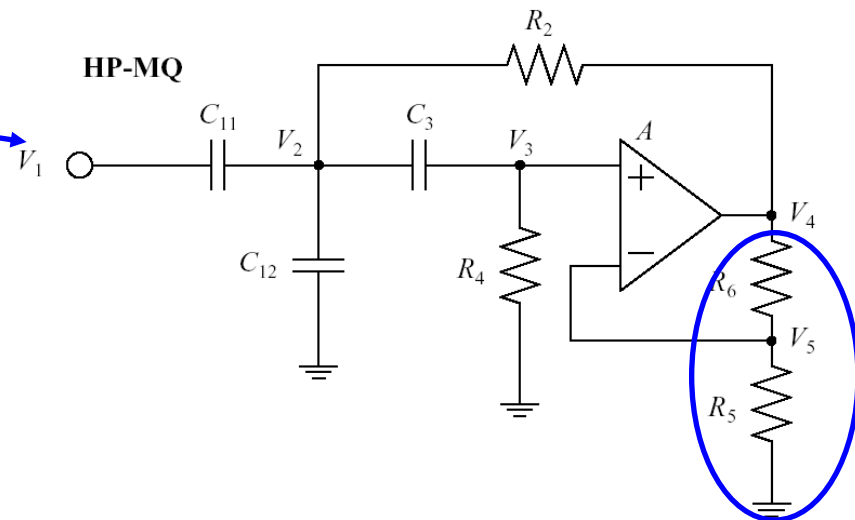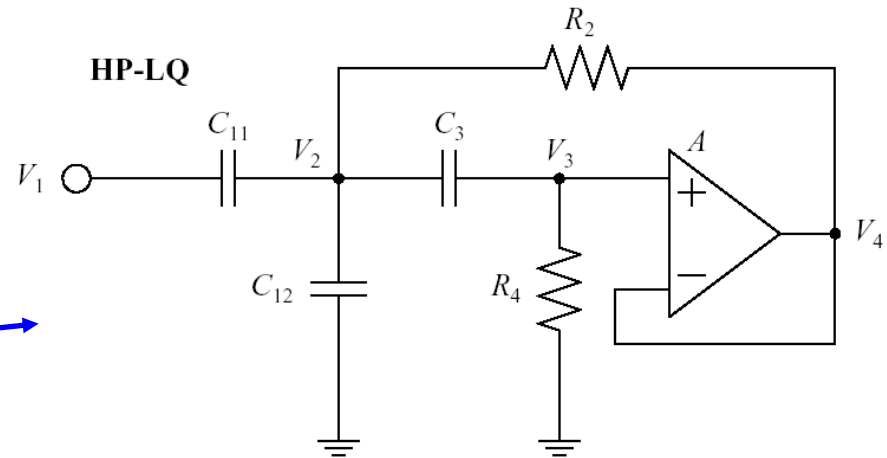

Bandpass medium-Q-factor

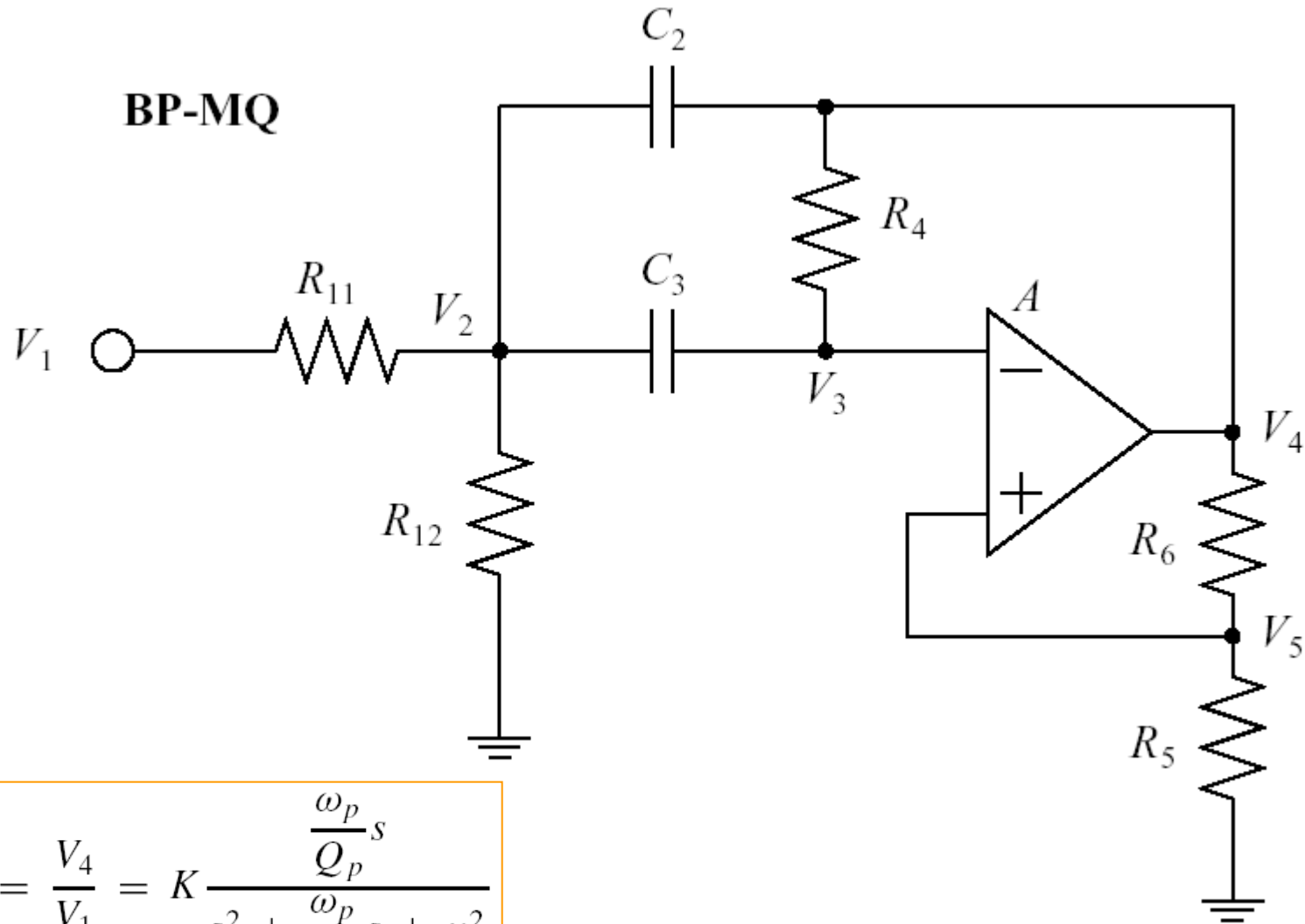

$$H_{BP}(s) = \frac{V_4}{V_1} = K \frac{\frac{\omega_p}{Q_p} s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun BP medium-Q

$$C_2 = C_2(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{2x}$$

$$C_3 = C_3(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{3x}$$

$$R_1 = \frac{1}{\omega_p \sqrt{C_{2x} C_{3x} P}}$$

$$P = R_4 / R_1$$

$$R_4 = R_4(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = P R_1$$

$$R_6 = R_6(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x$$


$$R_5 = R_5(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x \left(\frac{1 + \frac{C_2}{C_3}}{P} - \frac{\sqrt{\frac{C_2}{PC_3}}}{Q_p} \right)$$

$$K_0 = Q_p \left(1 + \frac{R_5}{R_x} \right) \sqrt{\frac{PC_3}{C_2}}$$

$$R_{11} = R_{11}(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_1 K_0}{K}$$


$$R_{12} = R_{12}(K, Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_1 K_0}{K_0 - K}$$

Proračun BP medium-Q

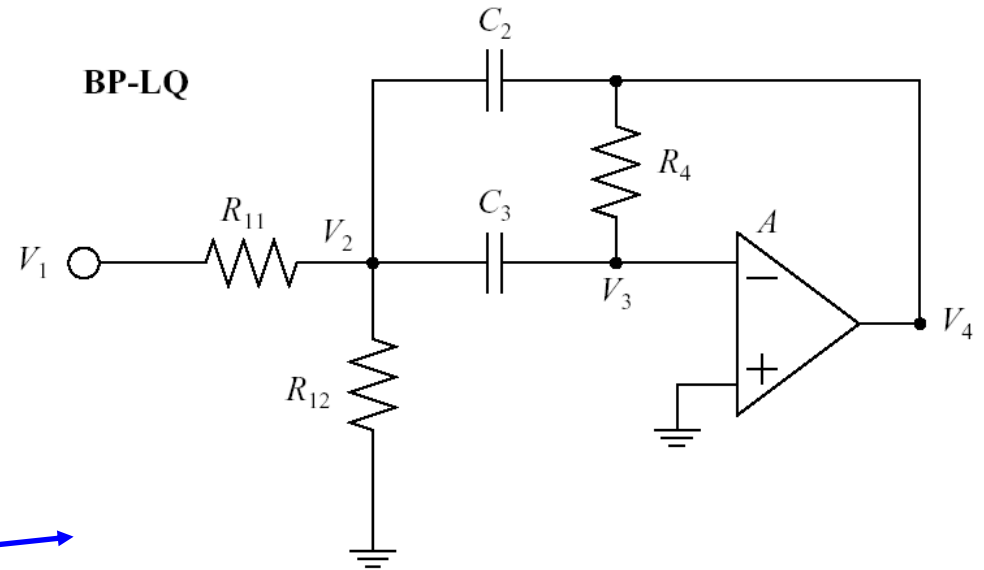


$$1 \leq K_{LQ}$$

$$1 \leq K_{MQ}$$

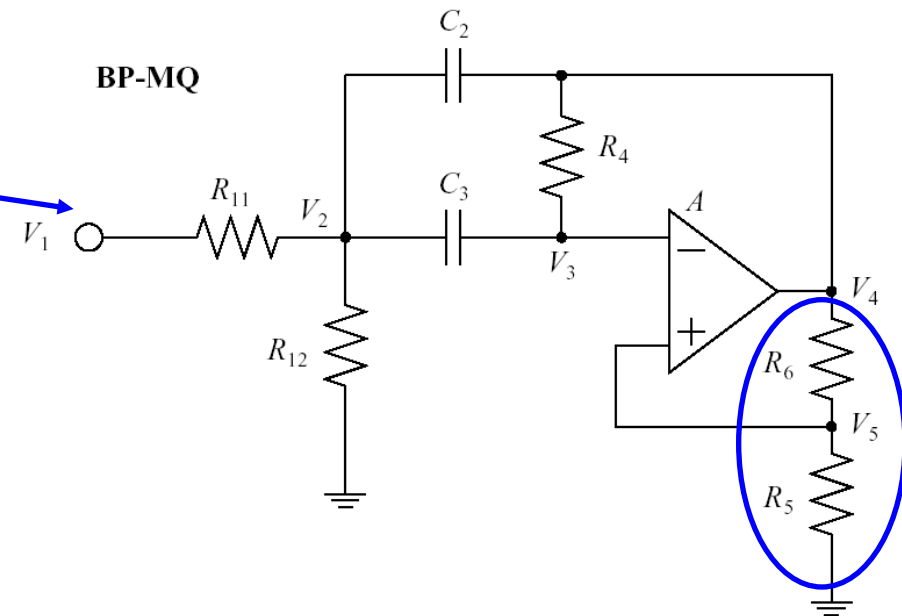

Bandreject medium-Q-factor

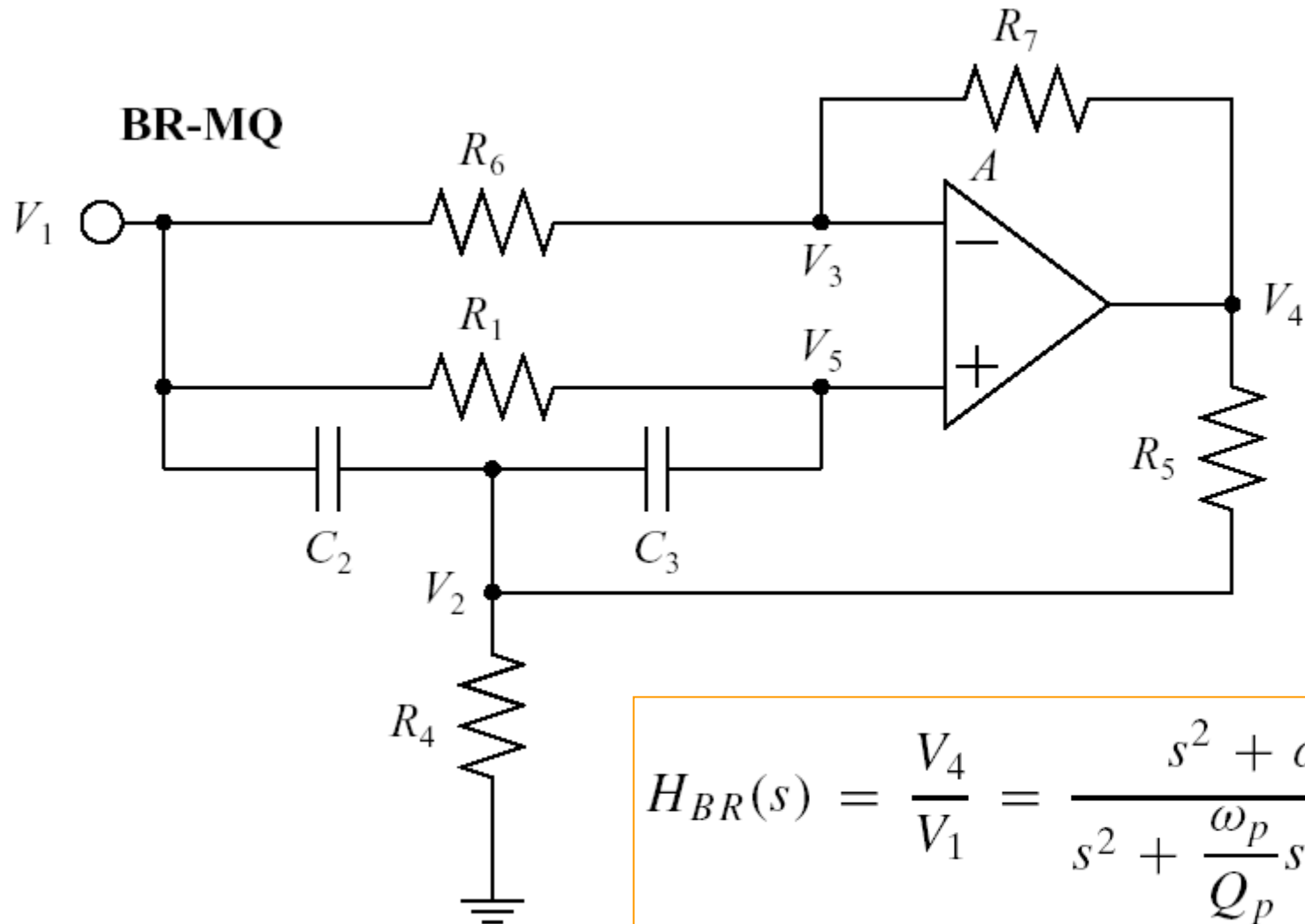

$$H_{BR}(s) = \frac{V_4}{V_1} = \frac{s^2 + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun BR medium-Q

$$C_2 = C_2(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{2x}$$

$$C_3 = C_3(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{3x}$$

$$R_1 = R_1(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{1}{\omega_p \sqrt{C_{2x} C_{3x} P}}$$

$$R_p = P R_1$$

$$R_6 = R_6(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x$$

$$R_7 = R_7(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x P \left(1 + \frac{C_2}{C_3}\right)$$


$$a = 1 - \frac{\sqrt{\frac{P C_2}{C_3}}}{Q_p \left(1 + \frac{R_7}{R_x}\right)}$$

$$R_5 = R_5(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_p}{a}$$

$$R_4 = R_4(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_p}{1 - a}$$

$$K_{MQ} = 1$$

Allpass medium-Q-factor

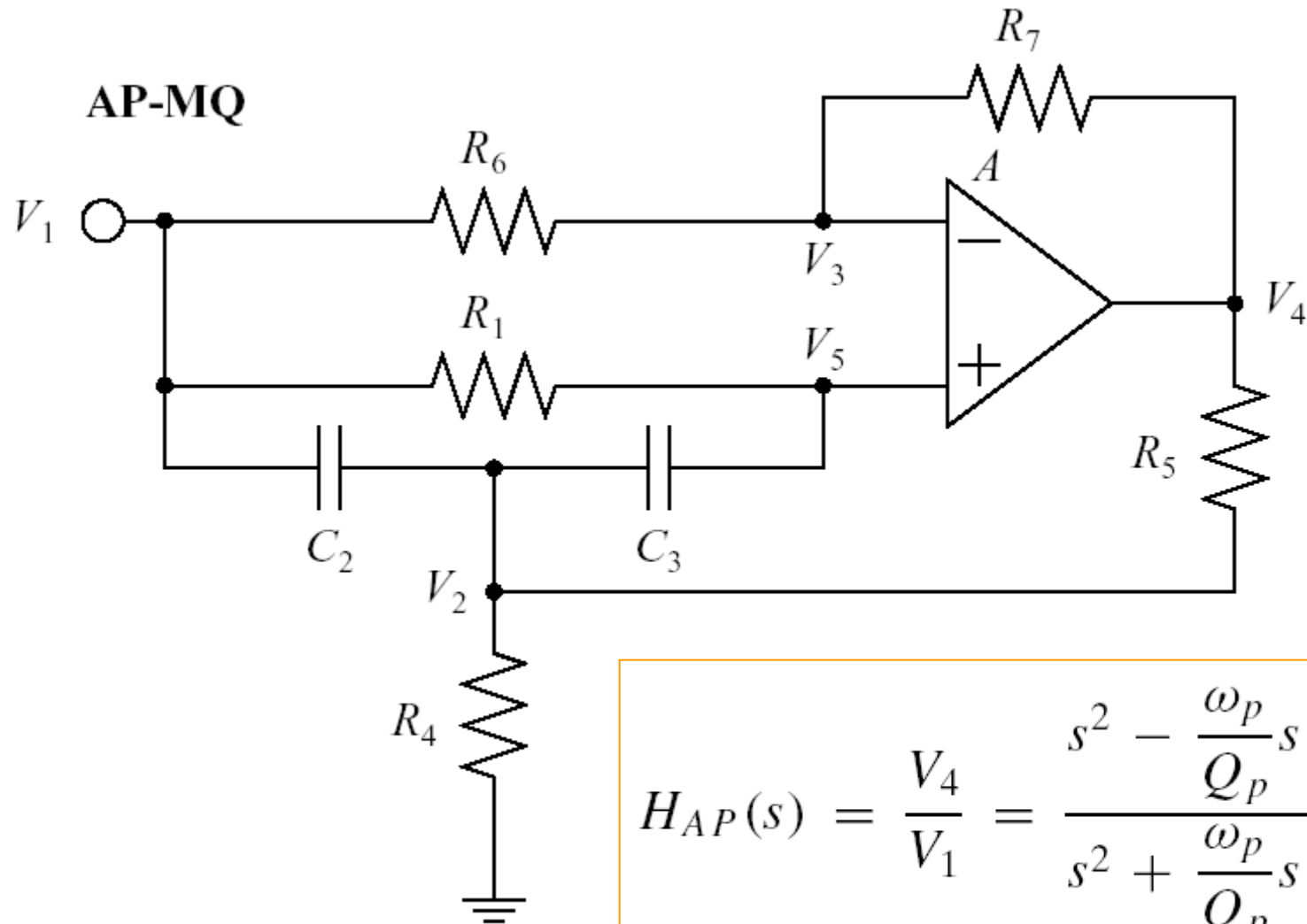

$$H_{AP}(s) = \frac{V_4}{V_1} = \frac{s^2 - \frac{\omega_p}{Q_p}s + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_2 = C_2(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{2x}$$

$$C_3 = C_3(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = C_{3x}$$

$$R_1 = R_1(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{1}{\omega_p \sqrt{C_{2x} C_{3x} P}}$$

$$R_p = P R_1$$

$$R_6 = R_6(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x$$

$$R_7 = R_7(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = R_x \left(P \left(1 + \frac{C_2}{C_3} \right) + \frac{\sqrt{P \frac{C_2}{C_3}}}{Q_p} \right)$$


$$a = 1 - \frac{2 \sqrt{\frac{P C_2}{C_3}}}{Q_p \left(1 + \frac{R_7}{R_x} \right)}$$

$$R_5 = R_5(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_p}{a}$$

$$R_4 = R_4(Q_p, \omega_p, C_{2x}, C_{3x}, P, R_x) = \frac{R_p}{1 - a}$$

$$K_{MQ} = 1$$

Lowpass notch medium-Q-factor

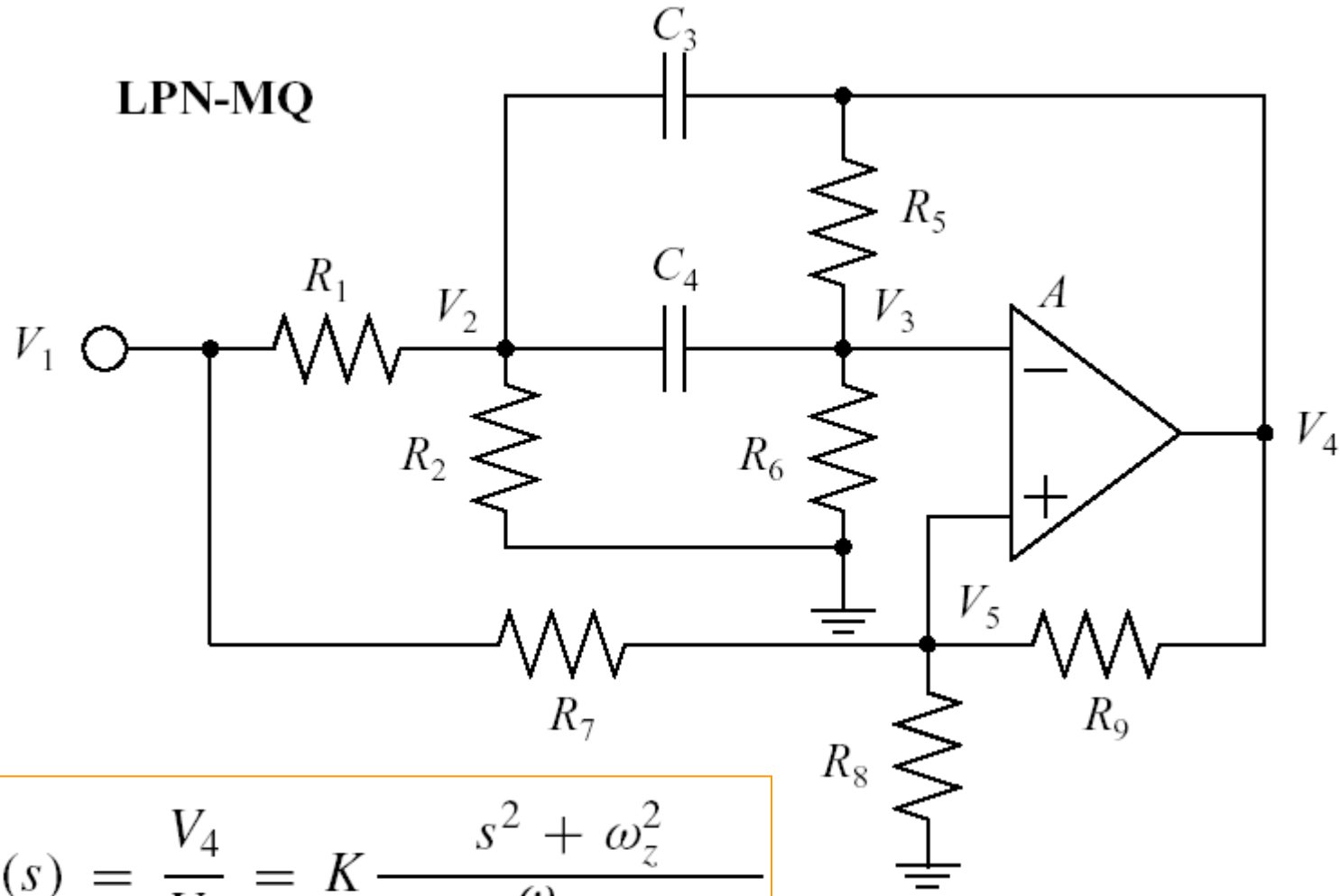

$$H_{LPN}(s) = \frac{V_4}{V_1} = K \frac{s^2 + \omega_z^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_3 = C_3(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = C_{3x}$$

$$C_4 = C_4(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = C_{4x}$$

$$G = \frac{C_3 \omega_p}{2P Q_p} \left(\sqrt{1 + 4Q_p^2 P \left(1 + \frac{C_4}{C_3}\right)} - 1 \right)$$

$$K_0 = \frac{1 + P}{1 + \left(1 + \frac{C_4}{C_3}\right) \omega_z^2 \frac{C_3^2}{G^2}}$$

$$R_1 = R_1(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{K_0}{KG}$$

$$R_2 = R_2(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{K_0}{G(K_0 - K)}$$

$$R_6 = R_6(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{G(1 + P)}{C_3 C_4 (\omega_z^2 - \omega_p^2)}$$


$$R_5 = R_5(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{1}{\frac{C_3 C_4 \omega_p^2}{G} + \frac{P}{R_6}}$$

$$R_7 = R_7(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{P R_x}{K}$$

$$R_8 = R_8(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{P R_x}{1 - K}$$

$$R_9 = R_9(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = R_x$$

Highpass notch medium-Q factor

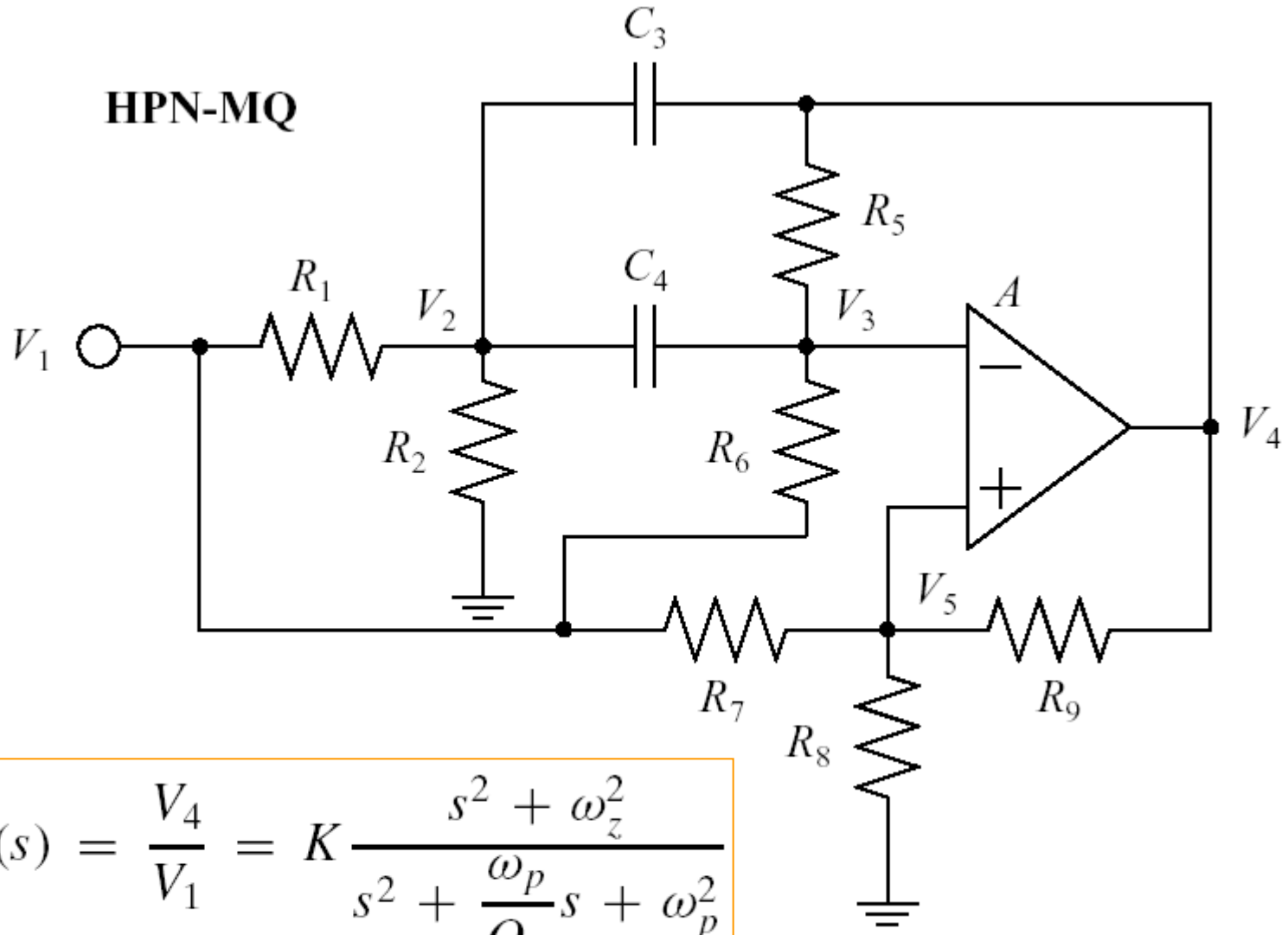

$$H_{HPN}(s) = \frac{V_4}{V_1} = K \frac{s^2 + \omega_z^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_3 = C_3(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = C_{3x}$$

$$C_4 = C_4(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = C_{4x}$$

$$G = \frac{C_3 \omega_p}{2P Q_p} \left(\sqrt{1 + 4Q_p^2 P \left(1 + \frac{C_4}{C_3}\right)} - 1 \right)$$

$$K_0 = \frac{1 + P}{1 + \left(1 + \frac{C_4}{C_3}\right) \omega_z^2 \frac{C_3^2}{G^2}}$$

$$R_1 = R_1(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{K_0}{KG}$$

$$R_2 = R_2(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{K_0}{G(K_0 - K)}$$

$$R_6 = R_6(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{G(1 + P)\left(1 - \frac{1}{K}\right)}{C_3 C_4 (\omega_z^2 - \omega_p^2)}$$


$$R_5 = R_5(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{1}{\frac{C_3 C_4 \omega_p^2}{G} + \frac{P}{R_6}}$$

$$R_7 = R_7(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{P R_x}{K}$$

$$R_8 = R_8(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = \frac{P R_x}{1 - K}$$

$$R_9 = R_9(K, Q_p, \omega_p, \omega_z, P, C_{3x}, C_{4x}, R_x) = R_x$$

Lowpass high-Q-factor

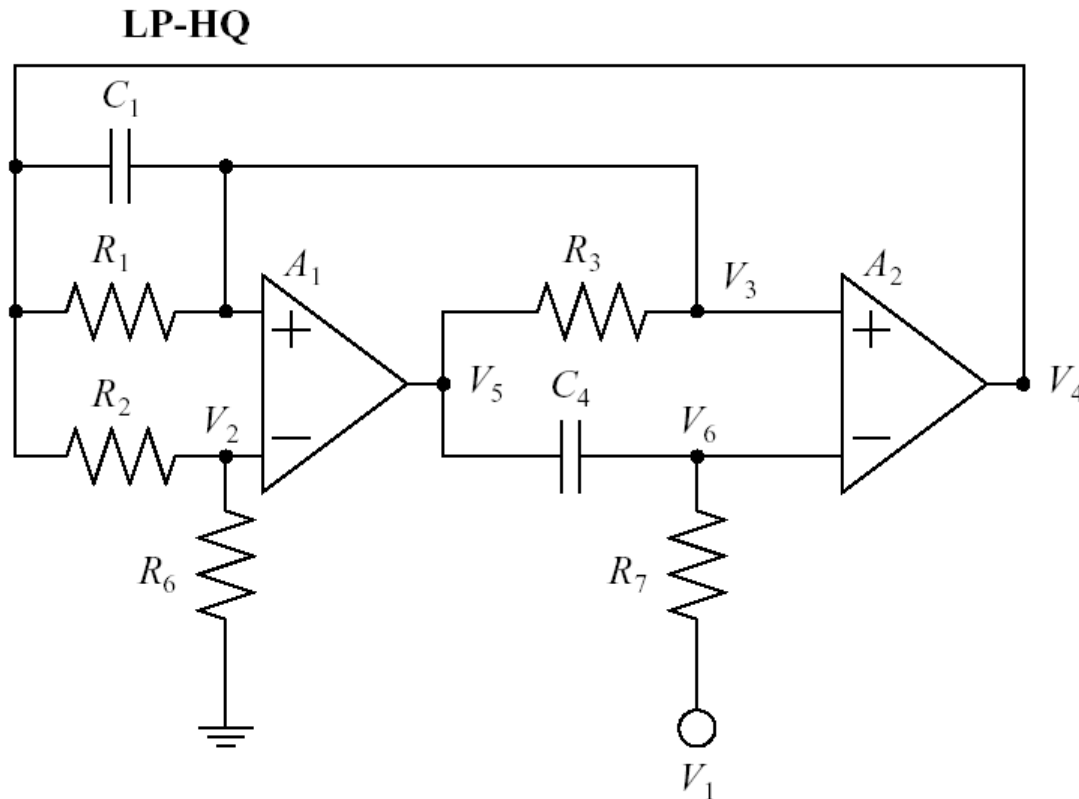

$$H_{LP}(s) = \frac{V_5}{V_1} = \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_1 = C_1(Q_p, \omega_p, C_x, R_x) = C_x$$

$$C_4 = C_4(Q_p, \omega_p, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_2 = R_2(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_3 = R_3(Q_p, \omega_p, C_x, R_x) = R_x$$


$$R_6 = R_6(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_1 = R_1(Q_p, \omega_p, C_x, R_x) = Q_p R_0$$

$$R_7 = R_7(Q_p, \omega_p, C_x, R_x) = \frac{R_0^2}{R_x}$$

Highpass high-Q-factor

HP-HQ

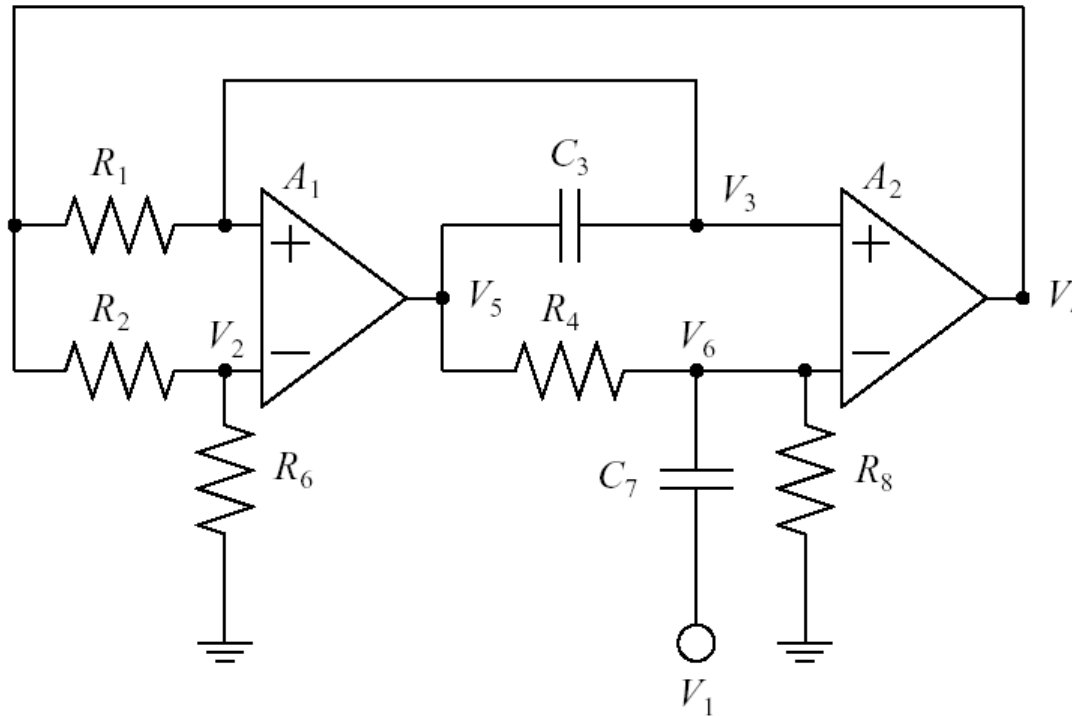

$$H_{HP}(s) = \frac{V_4}{V_1} = \frac{s^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_3 = C_3(Q_p, \omega_p, C_x, R_x) = C_x$$

$$C_7 = C_7(Q_p, \omega_p, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_2 = R_2(Q_p, \omega_p, C_x, R_x) = R_x$$


$$R_6 = R_6(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_8 = R_8(Q_p, \omega_p, C_x, R_x) = Q_p R_0$$

$$R_4 = R_4(Q_p, \omega_p, C_x, R_x) = \frac{R_0^2}{R_x}$$

Bandpass high-Q-factor

BP-HQ

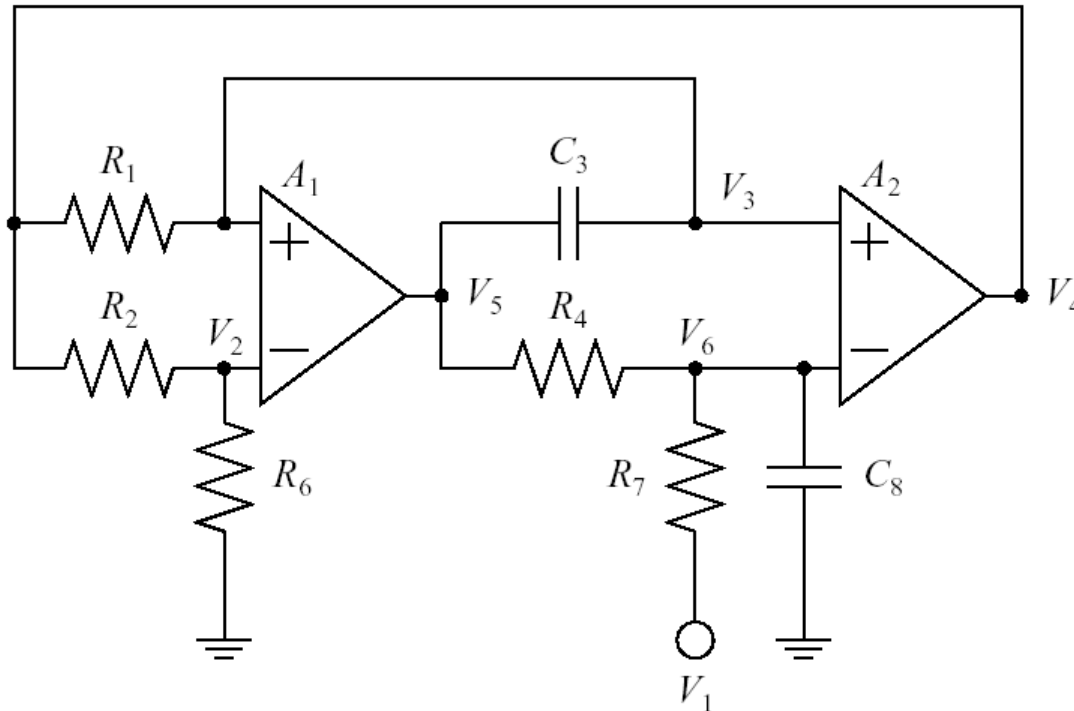

$$H_{BP}(s) = \frac{V_4}{V_1} = \frac{\frac{\omega_p}{Q_p} s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun

$$C_3 = C_3(Q_p, \omega_p, C_x, R_x) = C_x$$

$$C_8 = C_8(Q_p, \omega_p, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, C_x, R_x) = R_x$$


$$R_2 = R_2(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_6 = R_6(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_7 = R_7(Q_p, \omega_p, C_x, R_x) = Q_p R_0$$

$$R_4 = R_4(Q_p, \omega_p, C_x, R_x) = \frac{R_0^2}{R_x}$$

Bandreject high-Q-factor

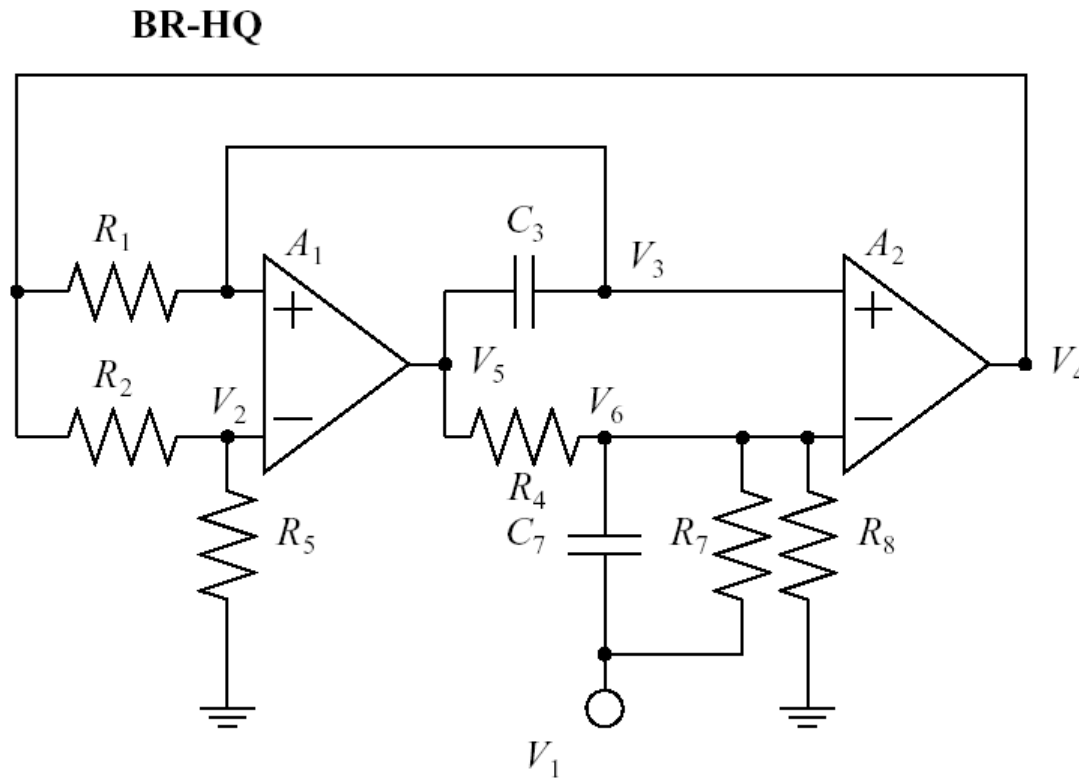

$$H_{BR}(s) = \frac{V_4}{V_1} = \frac{s^2 + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_3 = C_3(Q_p, \omega_p, C_x, R_x) = C_x$$

$$C_7 = C_7(Q_p, \omega_p, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_2 = R_2(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_5 = R_5(Q_p, \omega_p, C_x, R_x) = R_x$$


$$R_7 = R_7(Q_p, \omega_p, C_x, R_x) = 2Q_p R_0$$

$$R_8 = R_8(Q_p, \omega_p, C_x, R_x) = 2Q_p R_0$$

$$R_4 = R_4(Q_p, \omega_p, C_x, R_x) = \frac{R_0^2}{R_x}$$

Lowpass notch high-Q-factor

LPN-HQ

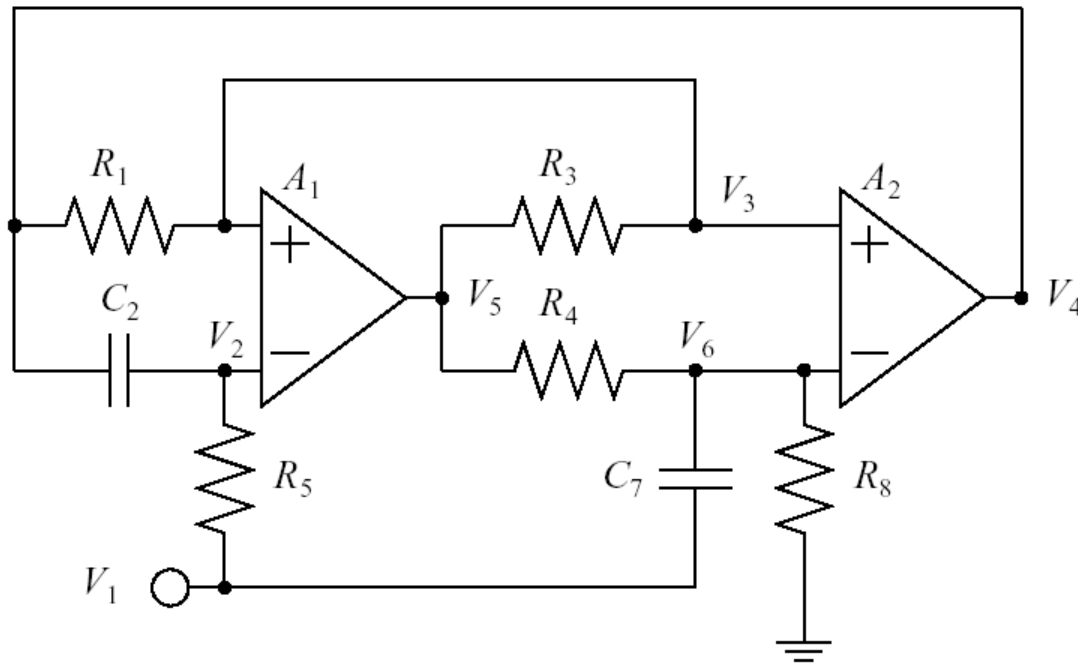

$$H_{LPN}(s) = \frac{V_5}{V_1} = \frac{s^2 + \omega_z^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_2 = C_2(Q_p, \omega_p, \omega_z, C_x, R_x) = C_x$$

$$C_7 = C_7(Q_p, \omega_p, \omega_z, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, \omega_z, C_x, R_x) = R_x$$

$$R_3 = R_3(Q_p, \omega_p, \omega_z, C_x, R_x) = R_x$$


$$R_8 = R_8(Q_p, \omega_p, \omega_z, C_x, R_x) = Q_p R_0$$

$$R_4 = R_4(Q_p, \omega_p, \omega_z, C_x, R_x) = R_8 \left(\frac{\omega_z^2}{\omega_p^2} - 1 \right)$$

$$R_5 = R_5(Q_p, \omega_p, \omega_z, C_x, R_x) = \frac{R_0^2}{R_4}$$

Highpass notch high-Q-factor

HPN-HQ

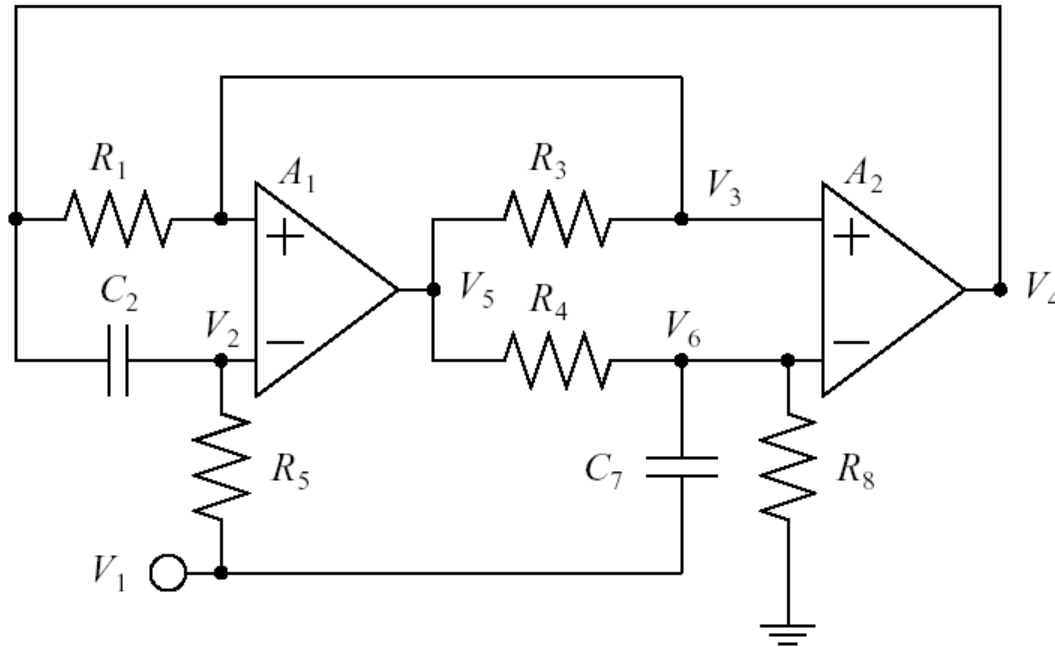

$$H_{HPN}(s) = \frac{V_4}{V_1} = \frac{s^2 + \omega_z^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Proračun

$$C_2 = C_2(Q_p, \omega_p, \omega_z, C_x, R_x) = C_x$$

$$C_7 = C_7(Q_p, \omega_p, \omega_z, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, \omega_z, C_x, R_x) = R_x$$


$$R_3 = R_3(Q_p, \omega_p, \omega_z, C_x, R_x) = R_x$$

$$R_8 = R_8(Q_p, \omega_p, \omega_z, C_x, R_x) = Q_p R_0$$

$$R_4 = R_4(Q_p, \omega_p, \omega_z, C_x, R_x) = R_8 \left(1 - \frac{\omega_z^2}{\omega_p^2} \right)$$

$$R_5 = R_5(Q_p, \omega_p, \omega_z, C_x, R_x) = \frac{R_0^2}{R_4}$$

General-purpose realization

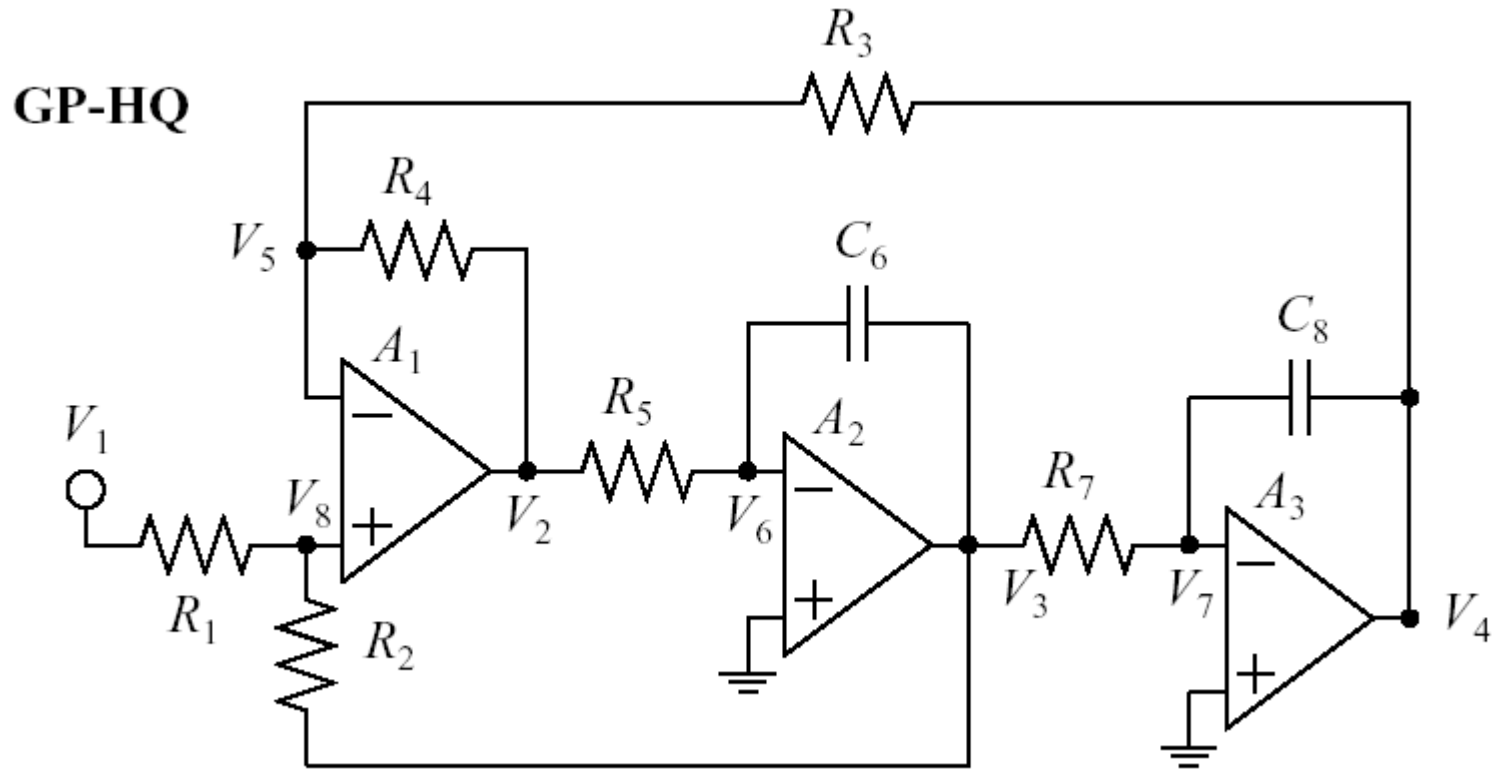

KHN filter (Kerwin-Huelsman-Newcomb)

Proračun

$$C_6 = C_6(Q_p, \omega_p, C_x, R_x) = C_x$$

$$C_8 = C_8(Q_p, \omega_p, C_x, R_x) = C_x$$

$$R_0 = \frac{1}{\omega_p C_x}$$

$$R_1 = R_1(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_3 = R_3(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_5 = R_5(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_7 = R_7(Q_p, \omega_p, C_x, R_x) = R_x$$

$$R_4 = R_4(Q_p, \omega_p, C_x, R_x) = \frac{R_x^3}{R_0^2}$$

$$R_2 = R_2(Q_p, \omega_p, C_x, R_x) = R_x \left(\frac{Q_p \left(1 + \frac{R_4}{R_x} \right)}{\sqrt{\frac{R_4}{R_x}}} - 1 \right)$$

$$H_{LP}(s) = \frac{V_4}{V_1} = K_{LP} \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

$$H_{HP}(s) = \frac{V_2}{V_1} = K_{HP} \frac{s^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

$$H_{BP}(s) = \frac{V_3}{V_1} = K_{BP} \frac{\frac{\omega_p}{Q_p} s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Proračun

$$K_{LP} = \frac{R_2(R_3 + R_4)}{R_4(R_1 + R_2)}$$

$$K_{HP} = \frac{R_2(R_3 + R_4)}{R_3(R_1 + R_2)}$$

$$K_{BP} = -\frac{R_2}{R_1}$$

$$H_{LP}(s) = \frac{V_4}{V_1} = K_{LP} \frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$
$$H_{HP}(s) = \frac{V_2}{V_1} = K_{HP} \frac{s^2}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$
$$H_{BP}(s) = \frac{V_3}{V_1} = K_{BP} \frac{\frac{\omega_p}{Q_p}s}{s^2 + \frac{\omega_p}{Q_p}s + \omega_p^2}$$

Simbolički proračun (1)


A.5 Lowpass-Medium-Q-Factor Active RC Filter Analysis and Design

Miroslav D. Lutovac, Dejan V. Tosić and Brian L. Evans

Simbolički proračun (2)

A.5.3 Schematic

DrawLPMQ[0,0,1/2,1/0.8];

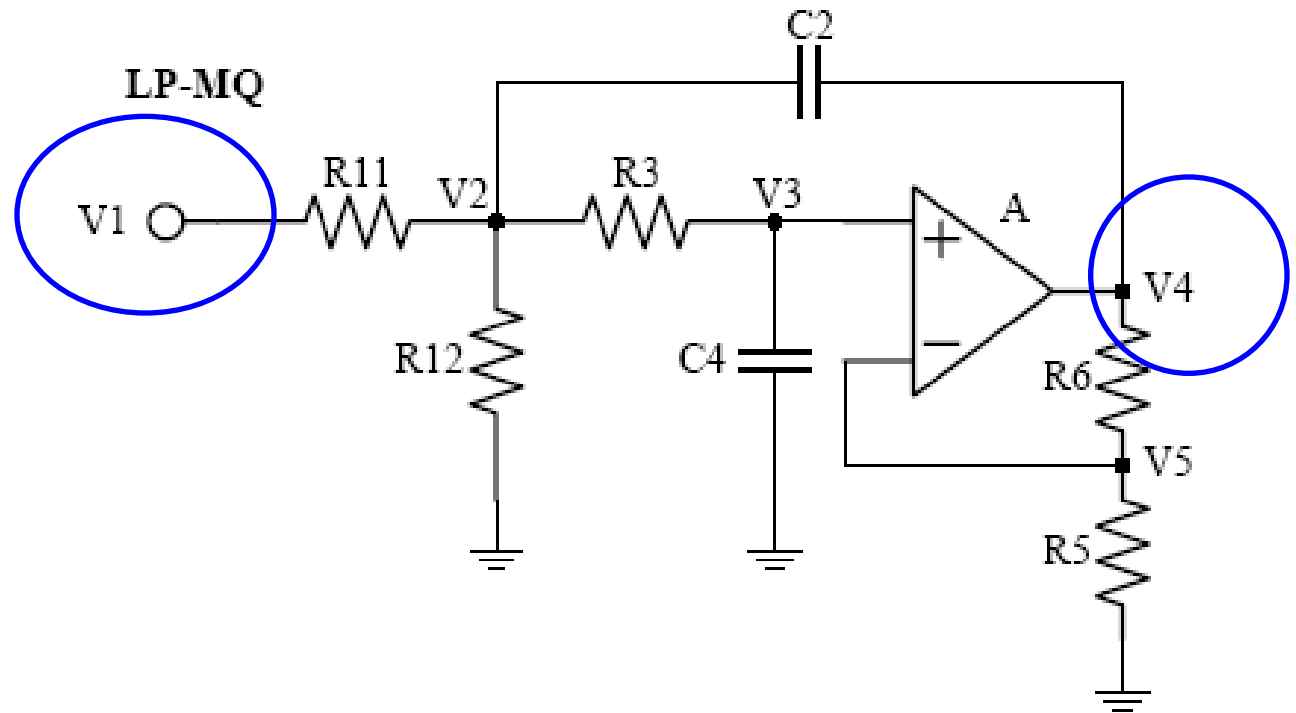

Simbolički proračun (3)

■ A.5.4 Circuit Analysis

■ Reduced Modified Nodal Analysis

```
CircuitEquations = {V1 == Vg  
  , (V2-V1)/R11 + V2/R12 + (V2-V3)/R3 + (V2-V4)/(1/(s*C2)) == 0  
  , (V3-V2)/R3 + V3/(1/(s*C4)) == 0  
  , (V5-V4)/R6 + V5/R5 == 0  
  , (V3-V5)*A == V4};  
NodeVoltages = {V1,V2,V3,V4,V5};  
CircuitResponse = Together[Flatten[  
  Solve[CircuitEquations,NodeVoltages]  
  ]];
```

Simbolički proračun (4)

$$V1 = Vg$$

$$V4 = \frac{-((A R12 R3 R5 Vg) / 2 (A C2 R11 R12 R3 R5 s - (-R5 - A R5 - R6) (1 + C4 R3 s) (R11 R12 + R11 R3 + R12 R3 + C2 R11 R12 R3 s) + (-R5 - A R5 - R6) (R11 R12 + A C2 R11 R12 R3 s))) - (A R12 R3 (-R5 - A R5 - R6) Vg) / 2 (A C2 R11 R12 R3 R5 s - (-R5 - A R5 - R6) (1 + C4 R3 s) (R11 R12 + R11 R3 + R12 R3 + C2 R11 R12 R3 s) + (-R5 - A R5 - R6) (R11 R12 + A C2 R11 R12 R3 s))$$

Simbolički proračun (5)

A.5.5 Voltage Transfer Function

```
H = V4/V1 /. CircuitResponse //Together //Simplify;
```

```
Ha = Limit[H, A->Infinity];
```

```
Print["H(s) = ",
```

```
Collect[Numerator[Ha],s]/Collect[Denominator[Ha],s]]
```

```
H(s) = (R12 (R5 + R6)) /
```

```
(R11 R5 + R12 R5 + (C4 R11 R12 R5 + C4 R11 R3 R5 + C4 R12 R3 R5 - C2 R11 R12 R6) s +
```

```
2
```

```
C2 C4 R11 R12 R3 R5 s )
```

Simbolički proračun (6)

■ A.5.6 Definitions and Procedures

```
PoleQpole[H_,s_] := Module[{den,fp,Qp},
  den = Denominator[H];
  fp = Sqrt[Coefficient[den,s,0]/Coefficient[den,s,2]]/(2*Pi);
  Qp = (Coefficient[den,s,2]/Coefficient[den,s,1])*(2*Pi*fp);
  Simplify[{fp, Qp}]];
ZeroQzero[H_,s_] := Module[{fz,num,Qz0},
  num = Numerator[H];
  Qz0 = (Coefficient[num,s,2]/Coefficient[num,s,1]);
  fz = Sqrt[Coefficient[num,s,0]/Coefficient[num,s,2]]/(2*Pi);
  Simplify[{fz, Qz0*fz}]];
Sensitivity[F_,x_] := (x/F)*D[F,x];
GSP[F_,A_] := Limit[A*Sensitivity[F,A],A->Infinity]//Simplify;
PrintLabeledList[expressions_List,labels_List] := Map[
  Print#[[1]]," = ",#[[2]]]&
,Transpose[{labels,expressions}]
];
```

Simbolički proračun (7)

■ A.5.7 Poles, Zeros, Q-Factors

```
{fp,Qp} = Simplify[PoleQpole[H,s]];
PrintLabeledList[{fp,Qp},{ "fp", "Qp"}];
```

$$fp = \frac{\text{Sqrt}\left[\frac{R11 + R12}{C2 C4 R11 R12 R3}\right]}{2 \text{ Pi}}$$

$$Qp = \frac{(C2 C4 R11 R12 \text{ Sqrt}\left[\frac{R11 + R12}{C2 C4 R11 R12 R3}\right] R3 (R5 + A R5 + R6))}{C2 C4 R11 R12 R3}$$

$$(C2 R11 R12 R5 + C4 R11 R12 R5 + A C4 R11 R12 R5 + C4 R11 R3 R5 + A C4 R11 R3 R5 + C4 R12 R3 R5 + A C4 R12 R3 R5 + C2 R11 R12 R6 - A C2 R11 R12 R6 + C4 R11 R12 R6 + C4 R11 R3 R6 + C4 R12 R3 R6)$$

Simbolički proračun (8)

■ A.5.8 Gain-Sensitivity Product (GSP)

$GSP_{fp} = GSP[fp, A];$

$GSP_{Qp} = GSP[Qp, A];$

$PrintLabeledList[\{GSP_{fp}, GSP_{Qp}\}, \{"GSP_{fp}", "GSP_{Qp}"\}];$

$GSP_{fp} = 0$

$$GSP_{Qp} = \frac{C2 R11 R12 (R5 + R6)^2}{R5 (C4 R11 R12 R5 + C4 R11 R3 R5 + C4 R12 R3 R5 - C2 R11 R12 R6)}$$

Simbolički proračun (9)

■ A.5.9 Design

■ Find Element Values

```
DesignLPMQ[K_, Qp_, wp_, P_, C2x_, C4x_, R5x_] := Module[
  {C2, C4, R1, R11, R12, R3, R5, R6, Ko},
  C2 = C2x;
  C4 = C4x;
  R1 = 1/(wp*Sqrt[C2x*C4x*P]);
  R3 = P*R1;
  R5 = R5x;
  R6 = R5*((1+P)*C4/C2-Sqrt[P*C4/C2]/Qp);
  Ko = 1+R6/R5;
  R11 = R1*Ko/K;
  R12 = R1*Ko/(Ko-K);
  {R11, R12, C2, R3, C4, R5, R6}
];
{R11, R12, C2, R3, C4, R5, R6} = Together[DesignLPMQ[K, Q, W, P, C2x, C4x, R5x]];
```


Simbolički proračun (10)

■ A.5.10 Design Example

```
values = {K -> 1., Q -> 7.5, W -> 2*Pi*2500., P -> 1.5333078
, C2x -> 33.*10^(-9), C4x -> 10.*10^(-9), R5x -> 6800.} //N;
PrintLabeledList[N[{K,Q,W/(2*Pi),P} /. values]
,{"K","Qp","fp (Hz)","P"} ];
Print["-----"]
PrintLabeledList[Together[{R11,R12,C2*10^9,R3,C4*10^9,R5,R6} /. values],
{"R11 (ohm)","R12 (ohm)","C2 (nF)","R3 (ohm)","C4 (nF)","R5 (ohm)","R6 (ohm)"}];
```

K = 1.

Qp = 7.5

fp (Hz) = 2500.

P = 1.53331

R11 (ohm) = 4745.54

R12 (ohm) = 7011.9

C2 (nF) = 33.

R3 (ohm) = 4339.48

C4 (nF) = 10.

R5 (ohm) = 6800.

R6 (ohm) = 4602.13

Simbolički proračun (11)

■ A.5.11 Optimization


■ Find P for Low Gain-Sensitivity Product

```
values = {K -> 1.476288, Q -> 7.5, W -> 2*Pi*2500.  
  , C2x -> 100.*10^(-9), C4x -> 15.*10^(-9), R5x -> 10000.} //N;  
gspQp = Together[Simplify[GSPQp] /. values]
```

$$\frac{0.435711 (7.66667 - 0.344265 \sqrt{P} + 1. P)^2}{\sqrt{P}}$$

Simbolički proračun (12)
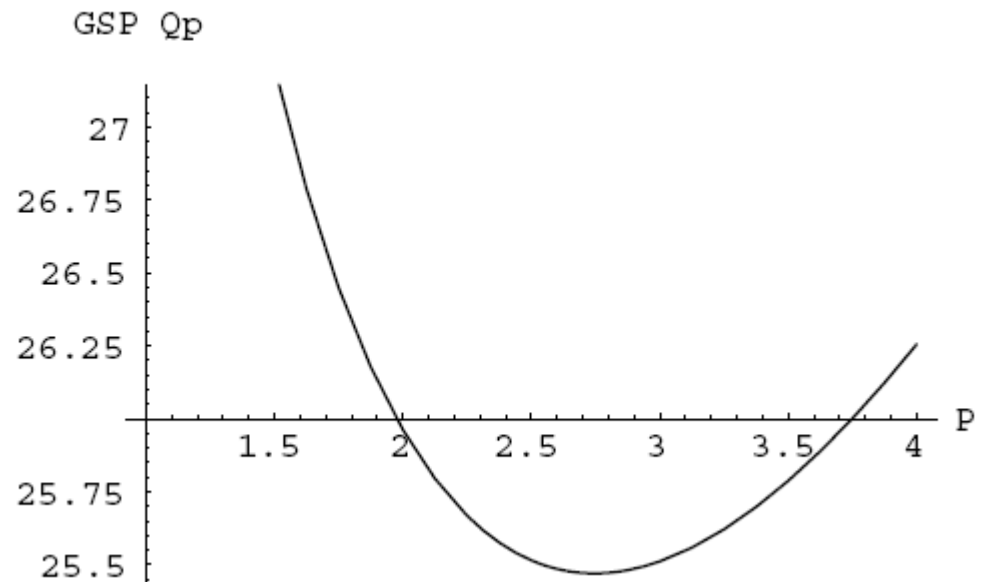
```
P1 = 1.;  
P2 = 4.;  
Plot[gspQp /. values  
  , {P, P1, P2}  
  , AxesLabel -> {"P", "GSP Qp"}  
  ];
```



```
{GSPmin, Pset} = FindMinimum[gspQp, {P, P1, P2}]
```

```
{25.4701, {P -> 2.74571}}
```

Simbolički proračun (13)

```
PrintLabeledList[N[{K,Q,W/(2*Pi),P} /. values /.Pset]
, {"K", "Qp", "fp (Hz)", "P"} ];
Print["-----"]
PrintLabeledList[Together[{R11,R12,C2*10^9,R3,C4*10^9,R5,R6} /. values /.Pset],
{"R11 (ohm)", "R12 (ohm)", "C2 (nF)", "R3 (ohm)", "C4 (nF)", "R5 (ohm)", "R6 (ohm)"}];
```

```
K = 1.47629
Qp = 7.5
fp (Hz) = 2500.
P = 2.74571
-----
R11 (ohm) = 991.99
```

```

          9
R12 (ohm) = 1.81368 10
C2 (nF) = 100.
R3 (ohm) = 2723.72
C4 (nF) = 15.
R5 (ohm) = 10000.
R6 (ohm) = 4762.89
```


Simbolički proračun (14)

```
Hhpmq = Together[Ha /.Pset/. values] ;  
num = Numerator[Hhpmq];  
den = Denominator[Hhpmq];  
numlist = CoefficientList[num,s];  
denlist = CoefficientList[den,s];  
Hhpmq = (1/denlist[[3]]) * num/(den/denlist[[3]])//Factor
```

$$\frac{3.64259 \cdot 10^8}{2.4674 \cdot 10^8 + 2094.4 s + 1. s^2}$$

Simbolički proračun (15)
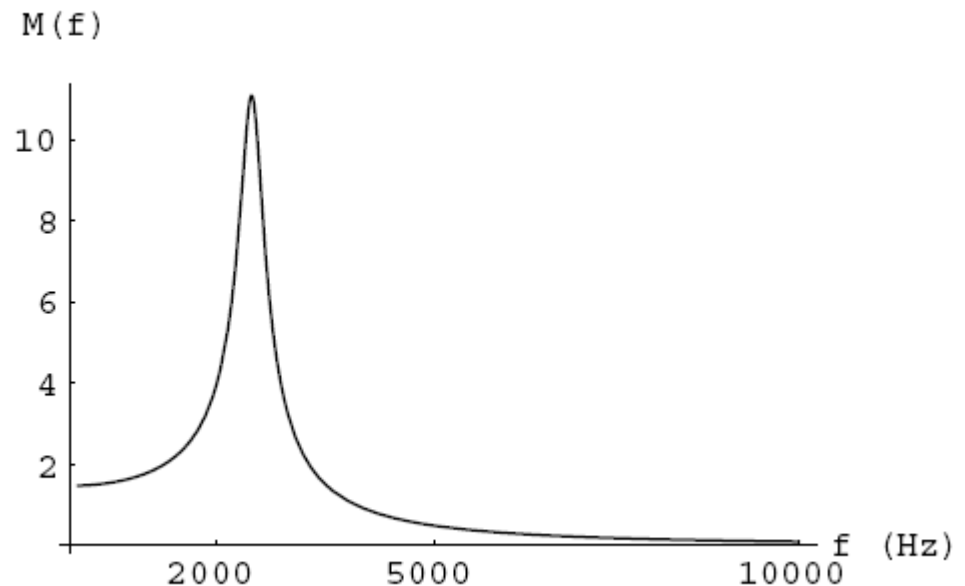
```
Plot[{Abs[Hhpmq] /. s -> N[I*2*Pi*f]}  
, {f, 100, 10000}  
, PlotRange -> All  
, Ticks -> {{0,2000,5000,10000},{0,2,4,6,8,10}}  
, AxesLabel -> {"f (Hz)","M(f)"}];
```



Simbolički proračun (16)

- Remark

We choose $P=2.7457$ as a good choice because we obtain small GSP and $1/R_{12}=0$.

We choose $P=2.7457$ as a good choice because we obtain small GSP and $1/R_{12}=0$.

LowPass Low-Q-factor Active RC Second-order Filter, Analysis and Design
(caflplq.ma)

HighPass Low-Q-factor Active RC Filter, Analysis and Design (cafhplq.ma)

BandPass Low-Q-factor Active RC Filter, Analysis and Design (cafbplq.ma)

BandReject Low-Q-factor Active RC Filter, Analysis and Design (cafbrlq.ma)

AllPass Low-Q-factor Active RC Filter, Analysis and Design (cafaplq.ma)

LowPass Medium-Q-factor Active RC Filter, Analysis and Design (caflpmq.ma)

HighPass Medium-Q-factor Active RC Filter, Analysis and Design (cafhpmq.ma)

BandPass Medium-Q-factor Active RC Filter, Analysis and Design (cafbpmq.ma)

BandReject Medium-Q-factor Active RC Filter, Analysis and Design (cafbrmq.ma)

AllPass Medium-Q-factor Active RC Filter, Analysis and Design (cafapmq.ma)

Lowpass Notch Medium-Q-factor Active RC Filter, Analysis and Design
(caflnmq.ma)

Highpass Notch Medium-Q-factor Active RC Filter, Analysis and Design
(cafhnmq.ma)

LowPass High-Q-factor Active RC Filter, Analysis and Design (caflphq.ma)

HighPass High-Q-factor Active RC Filter, Analysis and Design (cafhphq.ma)

BandPass High-Q-factor Active RC Filter, Analysis and Design (cafbphq.ma)

BandReject High-Q-factor Active RC Filter, Analysis and Design (cafbrhq.ma)

AllPass High-Q-factor Active RC Filter, Analysis and Design (cafaphq.ma)

Lowpass-Notch High-Q-factor Active RC Filter, Analysis and Design (caflnhq.ma)

Highpass-Notch High-Q-factor Active RC Filter, Analysis and Design (cafhnhq.ma)

General Purpose Active RC Filter, Analysis and Design (cafghq.ma)