
 


Switch-level modeli u Verilog-u

- Switch-level primitive

MOS transistor switches	MOS pull gates	MOS Bi-directional switches
nmos	pullup	tran
pmos	pulldown	tranif0
cmos		tranif1
rnmos		rtran
rpmos		tranif0
rcmos		rtranif1

MOS transistori

 


		ctrl			
		in			
		out			
		control			
		0	1	x	z
pmos	rpmos	0	1	x	z
	input	0	z	L	L
nmos	rnmos	0	1	x	z
	input	0	z	0	L
pmos	rpmos	1	z	H	H
	input	1	z	1	H
nmos	rnmos	x	z	x	x
	input	x	z	x	x
pmos	rpmos	z	z	z	z
	input	z	z	z	z

Statička CMOS kola


- Pull-up logika implementirana pomoću PMOS tranzistora
- Pull-down logika implementirana pomoću NMOS tranzistora
- PMOS i NMOS tranzistori se uključuju komplementarnim signalima
- Kada je tranzistor u on stanju, ponaša se kao kratak spoj, ili otpornost
- Kada je tranzistor u off stanju ponaša se kao otvorena veza
- Ne postoji put između napajanja i mase, pa je statička disipacija jednaka nuli

Verilog model CMOS invertora

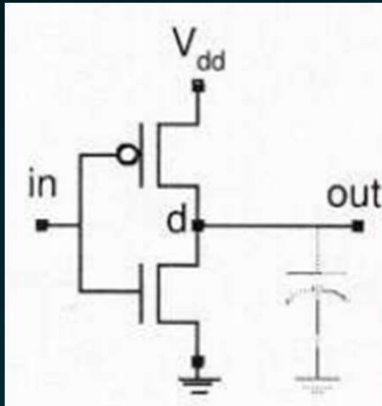

```
module cmos_inv (out, in);  
  output out;  
  input in;  
  supply0 GND;  
  supply1 PWR;  
  pmos (out, PWR, in);  
  nmos (out, GND, in);  
endmodule
```


Verilog model 3-ulaznog NI kola

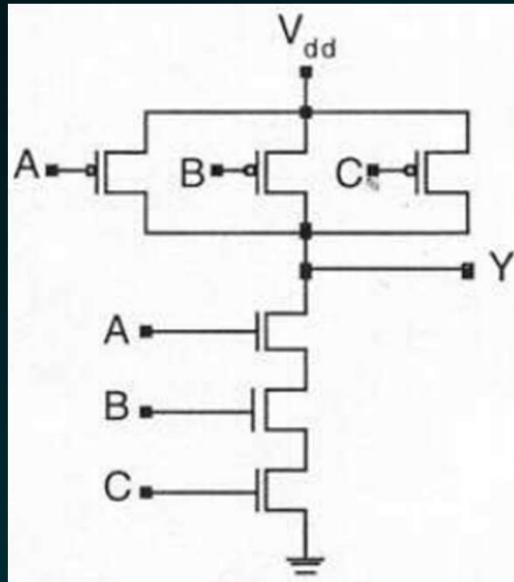

```
module nand_3 (Y, A,B,C);  
  output Y;  
  input A, B, C;  
  supply0 GND;  
  supply1 PWR;  
  wire w1,w2;  
  pmos (Y, PWR, A);  
  pmos (Y, PWR, B);  
  pmos (Y, PWR, C);  
  nmos (Y, w1, A);  
  nmos (w1, w2, B);  
  nmos (w2, GND, C);  
endmodule
```

Bidirekcionni prekidači

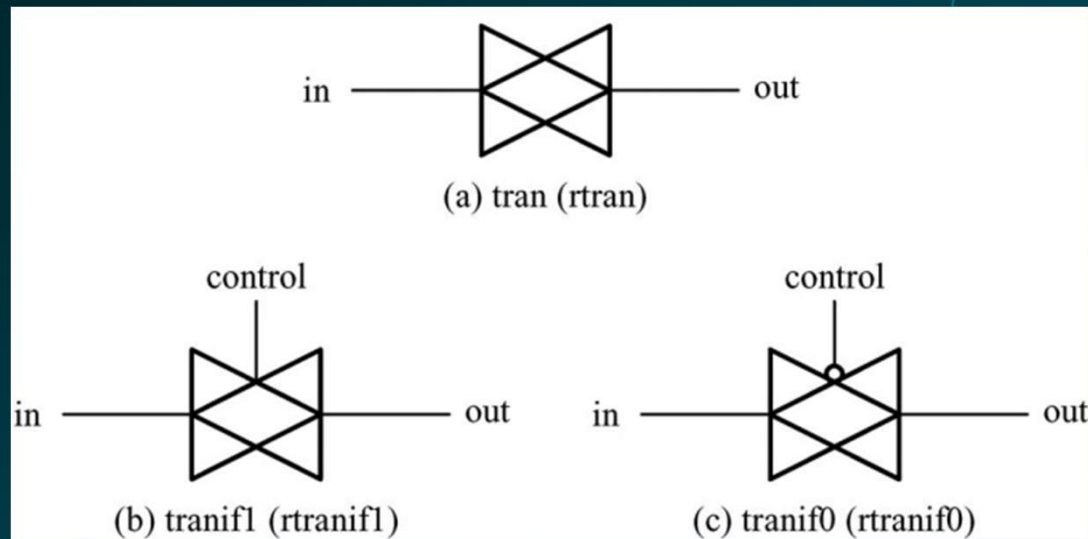- tran [instance_name] (in, out);
- tranif0 [instance_name] (in, out, control);
- tranif1 [instance_name] (in, out, control);




Kašnjenje : Unidirekcionni prekidači

- Specify no delay :
`mos_sw [instance_name](output, input, ...);`
 - Specify propagation delay only :
`mos_sw #(prop_delay)[instance_name](output, input, ...);`
 - Specify both rise and fall times :
`mos_sw #(t_rise, t_fall)[instance_name](output, input, ...);`
- Specify rise, fall, and turn-off times :
- `mos_sw #(t_rise, t_fall, t_off)[instance_name](output, input, ...);`

Kašnjenje : Bidirekcionni prekidači


- Ne unose kašnjenje signala koji prolazi kroz bidirekcionni prekidač. Umesto toga ovi prekidači unose turn-on, ili turn-off kašnjenja
 - Specify no delay :
`bds_w name [instance name](in, out, control);`
 - Specify a turn-on and turn-off delay :
`bds_w name #(t_on_off)[instance name](in, out, control);`
- Specify separately turn-on and turn-off delays :
- `bds_w name #(t_on, t_off)[instance name](in, out, control);`

CMOS transmisioni gejt

 


```
module Tgate (data_in, data_out, n_ena, p_ena);  
  Input data_in, n_ena, p_ena;  
  output data_out;  
  pmos (data_out, data_in, p_ena);  
  nmos (data_out, data_in, n_ena);  
endmodule
```



Multiplexer 2 u 1

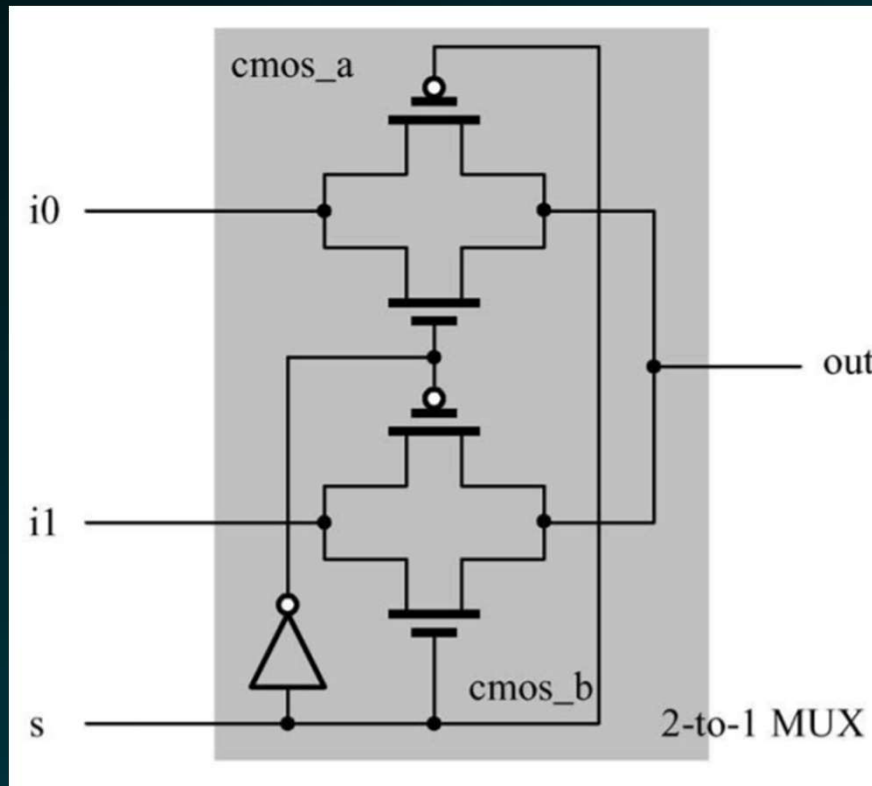


```
module my_mux21(out,s, i0,i1)
output out;
Input s, i0, i1;
wire sbar;
not (sbar,s);
cmos(out, i0, sbar, s);
cmos(out, i1, s, sbar);
endmodule
```

Master-Slave D FF sa active-low clear-om

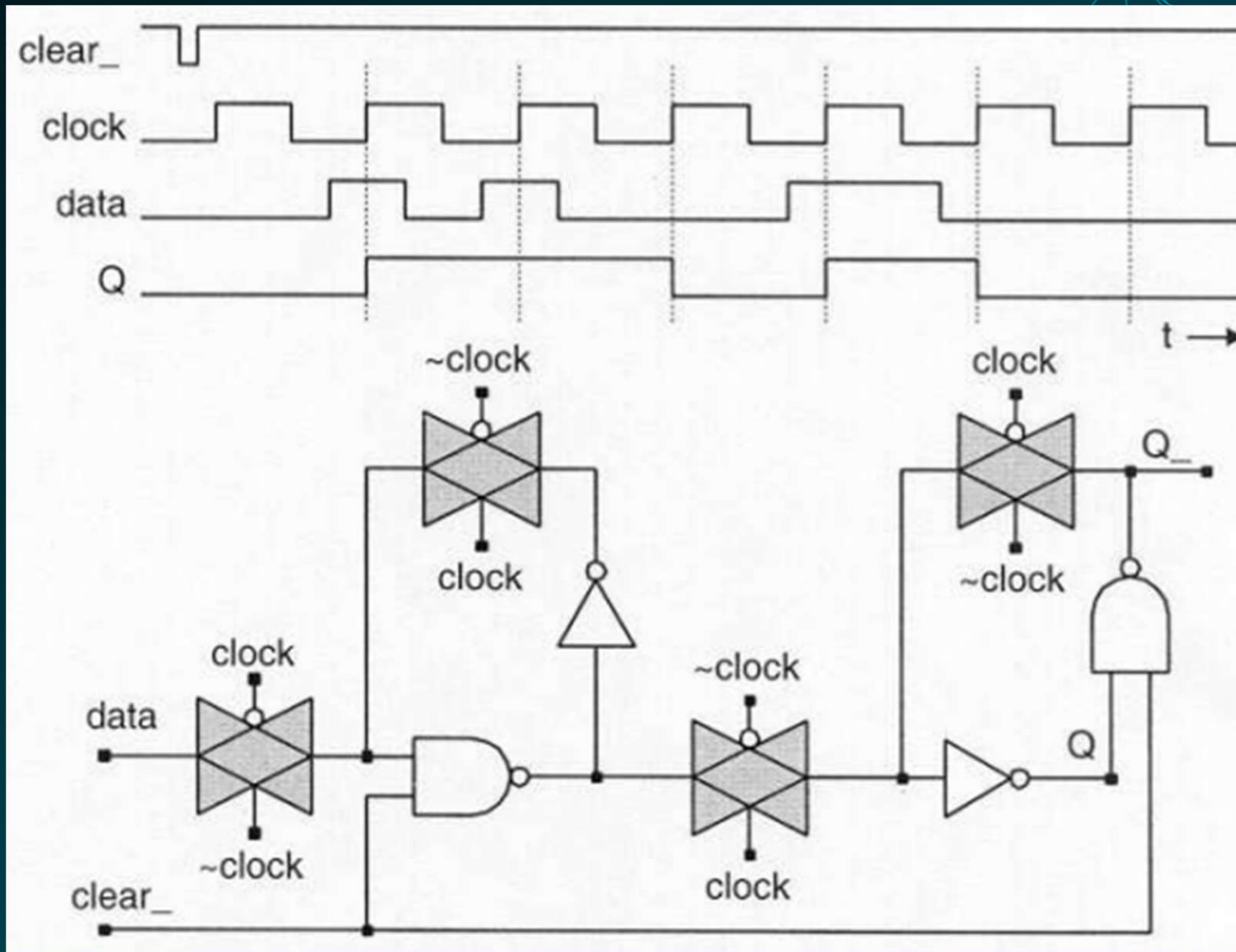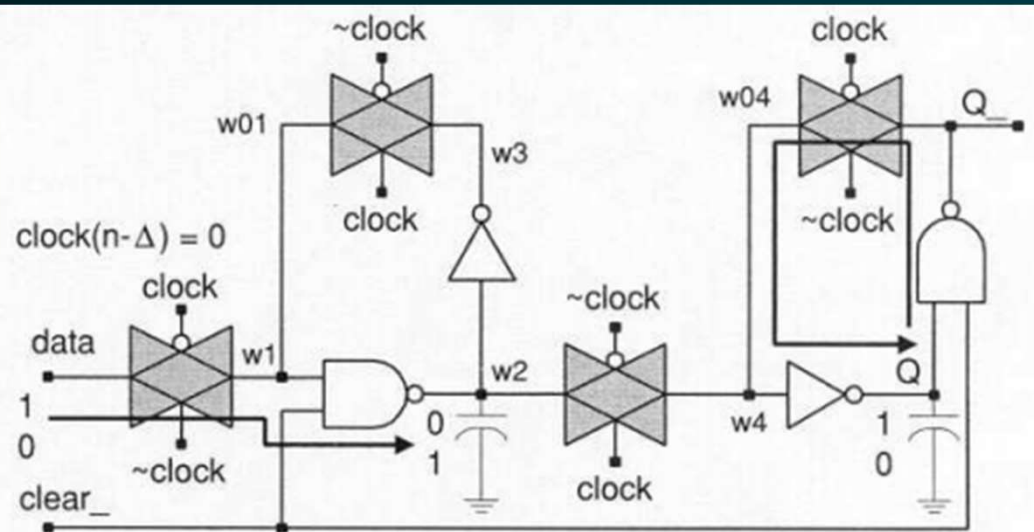



(a)

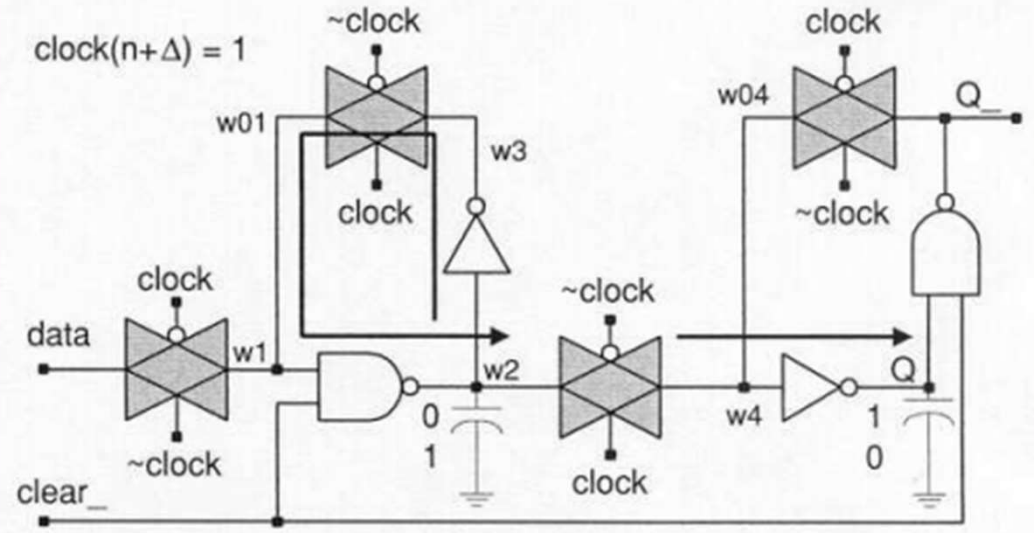


(b)

```
module tgate_dff (Q, Q_, data, clk, clk_, clear_);  
  Input data, clk, clk_, clear_;  
  output Q, Q_;  
  wire wO1, w1, w2, w3, wO4, W4;  
  assign w1=wO1;  
  assign w4=wO4;  
  cmos (w1, data, clk_, clk);  
  nand #1 (w2,w1, clear_);  
  not #1 (w3,w2);  
  cmos (wO1, w3, clk, clk_);  
  cmos (w4, w2, clk, clk_);  
  not #1 (Q, w4);  
  nand #1 (Q_, Q, clear_);  
  cmos (wO4, Q_, clk_, clk);  
endmodule
```

trireg Nets, states: Driven, Capacitive

At simulation time 0

 - a, b, and c = 1
- x = 0
- y -> 0
- z -> driven state and = strong0




At simulation time 10

- b = 0
- y -> a high-impedance
- z -> capacitive state and = medium0

trireg Nets, states: Driven, Capacitive

At simulation time 0

 - $a = 0$
- $b = c = 1$
- $x, y,$ and $z = \text{strong}1$



At simulation time 10

- $b = 0$
- $y \rightarrow$ capacitive state and = large1
- $z \rightarrow$ driven state and = large1

At simulation time 20

- $c = 0$
- $z \rightarrow$ capacitive state and = small1


At simulation time 30

- $c = 1$ again,
- y and z share the charge

At simulation time 40

- $c = 0$
- $z \rightarrow$ capacitive state and = small1

Statička RAM ćelija

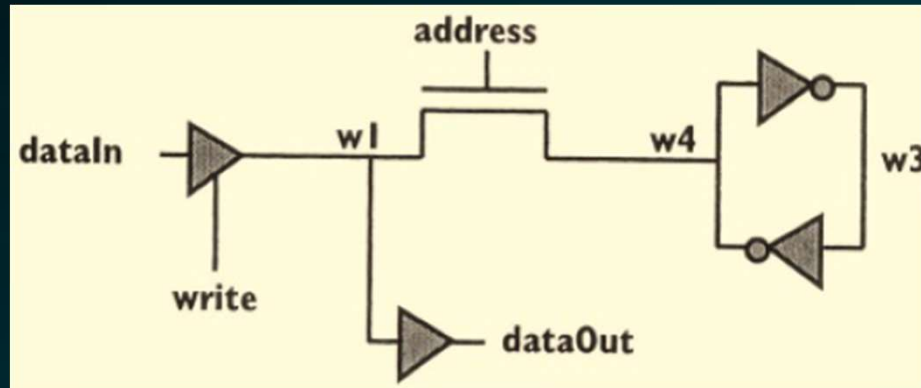

```
module sram (dataOut, address, dataIn, write);  
output dataOut;  
input address, dataIn, write;  
tri w1, w3, w4, w43;  
bufif1 g1(w1, dataIn, write);  
tranif1 g2(w4, w1, address);  
not (pull0, pull1) g3(w3, w4), g4(w4, w3);  
buf g5(dataOut, w1);  
endmodule
```

```
module wave_sram; //waveform for testing the static RAM cell
#(parameter d = 100);
wire dataOut;
reg address, dataIn, write;
sram cell (dataOut, address, dataIn, write);
initial begin
#d dis;
#d address = 1; #d dis;
#d dataIn = 1; #d dis;
#d write = 1; #d dis;
#d write = 0; #d dis;
#d write = 'bx; #d dis;
#d address = 'bx; #d dis;
#d address = 1; #d dis;
#d write = 0; #d dis;
end
task dis; //display the circuit state
"addr=%v d_in=%v write=%v d_out=%v", address, dataIn, write, dataOut, "
(134)=%b%b%b", cell.w1, cell.w3, cell.w4, " w134=%v %v %v", cell.w1, cell.w3,
cell.w4);
endtask
endmodule
```


Testbench-statički RAM

time	addr	d_in	wr	d_out	134	Comments
100	x	x	x	x	xxx	
300	1	x	x	x	xxx	
500	1	1	x	x	xxx	
700	1	1	1	1	101	write function
900	1	1	0	1	101	read function
1100	1	1	x	1	101	
1300	x	1	x	x	x01	ram holds value
1500	1	1	x	1	101	
1700	1	1	0	1	101	read function