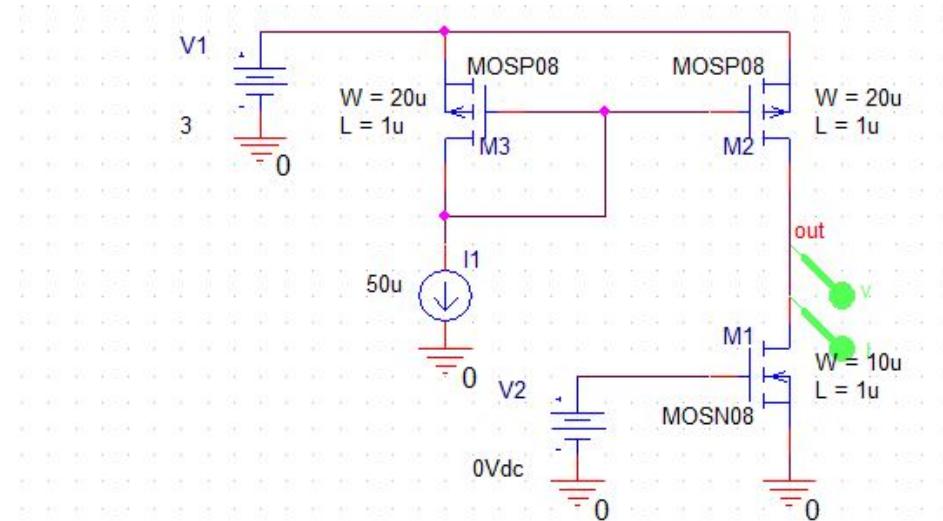


LABOE-18.3.2020.



```
.model MOSN08 NMOS vto=0.7 kp=110u lambda=0.04
.model MOSP08 PMOS vto=-0.7 kp=50u lambda=0.05
```

DC Sweep

V2 0.5V 1.5V 1m




Trace

Add Trace

Izvod funkcije $V(\text{out})$ u funkciji ulaznog napona=naponsko pojačanje, $dV(\text{out})/dV_2$: D($V(\text{out})$)



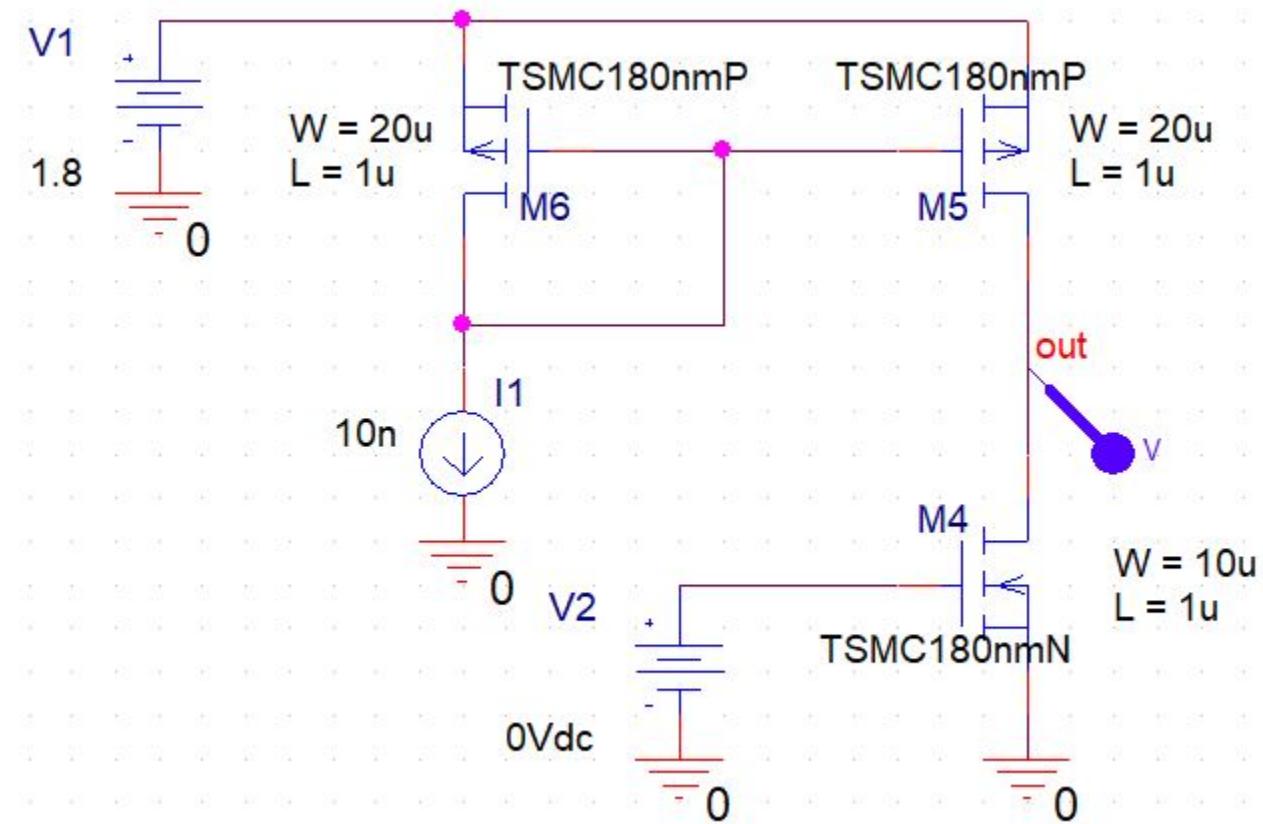CMOS pojačavač sa tranzistorima u TSMC 180nm tehnologiji:



Modele tranzistora iskopirati sa site-a predmeta, http://tnt.etf.bg.ac.rs/~laboe/index_files/2015/tsmc180nmcmos.lib

```

.MODEL TSMC180nmN NMOS (
    LEVEL = 7
+VERSION = 3.1          TNOM   = 27           TOX     = 4.1E-9
+XJ      = 1E-7          NCH    = 2.3549E17    VTH0    = 0.354505
+K1      = 0.5733393     K2     = 3.177172E-3   K3      = 27.3563303
+K3B     = -10           W0     = 2.341477E-5   NLX     = 1.906617E-7
+DVTOW   = 0             DVT1W   = 0            DVT2W   = 0
+DVT0    = 1.6751718     DVT1   = 0.4282625    DVT2   = 0.036004
+U0      = 327.3736992    UA     = -4.52726E-11  UB     = 4.46532E-19
+UC      = -4.74051E-11   VSAT   = 8.785346E4   A0      = 1.6897405
+AGS     = 0.2908676     BO     = -8.224961E-9  B1      = -1E-7
+KETA    = 0.021238      A1     = 8.00349E-4   A2      = 1
+RDSW   = 105           PRWG   = 0.5           PRWB   = -0.2
+WR      = 1              WINT   = 0            LINT   = 1.351737E-8
*+XL     = -2E-8         XW     = -1E-8
+ DWG    = 1.610448E-9
+DWB    = -5.108595E-9   VOFF   = -0.0652968  NFACTOR = 2.4901845
+CIT    = 0              CDSC   = 2.4E-4        CDSCD   = 0
+CDSCB   = 0             ETA0   = 0.0231564   ETAB   = -0.058499
+DSUB   = 0.9467118     PCLM   = 0.8512348   PDIBLC1 = 0.0929526
+PDIBLC2 = 0.01         PDIBLCB = -0.1        DROUT   = 0.5224026
+PSCBE1 = 7.979323E10  PSCBE2 = 1.522921E-9  PVAG   = 0.01
+DELTA   = 0.01          RSH    = 6.8           MOBMOD  = 1
+PRT    = 0              UTE    = -1.5          KT1    = -0.11
+KT1L   = 0              KT2    = 0.022          UA1    = 4.31E-9
+UB1    = -7.61E-18      UC1    = -5.6E-11     AT     = 3.3E4
+WL     = 0              WLN    = 1            WW     = 0
+WWN    = 1              WWL    = 0            LL     = 0
+LLN    = 1              LW     = 0            LWN    = 1
+LWL    = 0              CAPMOD = 2            XPART  = 0.5
+CGDO   = 7.7E-10        CGSO   = 7.7E-10      CGBO   = 1E-12
+CJ     = 1.010083E-3    PB     = 0.7344298   MJ     = 0.3565066
+CJSW   = 2.441707E-10   PBSW   = 0.8005503   MJSW   = 0.1327842
+CJSWG  = 3.3E-10        PBSWG  = 0.8005503   MJSWG  = 0.1327842
+CF     = 0              PVTH0  = 1.307195E-3  PRDSW  = -5
+PK2    = -1.022757E-3   WKETA  = -4.466285E-4  LKETA  = -9.715157E-3
+PU0    = 12.2704847    PUA    = 4.421816E-11  PUB    = 0
+PVSAT  = 1.707461E3    PETAO  = 1E-4          PKETA  = 2.348777E-3 )
```

*


```

.MODEL TSMC180nmP PMOS (
    LEVEL      = 7
+VERSION = 3.1          TNOM     = 27           TOX      = 4.1E-9
+XJ      = 1E-7          NCH      = 4.1589E17   VTH0     = -0.4120614
+K1      = 0.5590154     K2       = 0.0353896   K3       = 0
+K3B     = 7.3774572     W0       = 1E-6         NLX      = 1.103367E-7
+DVT0W   = 0              DVT1W    = 0            DVT2W    = 0
+DVT0    = 0.4301522     DVT1    = 0.2156888   DVT2    = 0.1
+U0      = 128.7704538    UA       = 1.908676E-9 UB      = 1.686179E-21
+UC      = -9.31329E-11   VSAT    = 1.658944E5  A0       = 1.6076505
+AGS     = 0.3740519     B0       = 1.711294E-6 B1       = 4.946873E-6
+KETA    = 0.0210951     A1       = 0.0244939   A2       = 1
+RDSW   = 127.0442882    PRWG    = 0.5           PRWB    = -0.5
+WR      = 1              WINT    = 5.428484E-10 LINT    = 2.468805E-8
*+XL     = -2E-8          XW       = -1E-8
+DWG    = -2.453074E-8   VOFF    = -0.0974174  NFACTOR = 1.9740447
+DWB    = 6.408778E-9    CDSC    = 2.4E-4        CDSCD   = 0
+CIT     = 0              CDSCD   = 0            ETAB    = -0.2531172
+CDSCB   = 0              ETA0    = 0.1847491   PDIBLC1 = 0.0156227
+DSUB   = 1.5             PCLM    = 4.8842961   PDIBLCB = -1E-3
+PDIBLC2 = 0.1            PDIBLCB = -1E-3        DROUT   = 0
+PSCBE1  = 1.733878E9   PSCBE2 = 5.002842E-10 PVAG    = 15
+DELTA   = 0.01            RSH     = 7.7           MOBMOD  = 1
+PRT     = 0              UTE     = -1.5          KT1     = -0.11
+KT1L    = 0              KT2     = 0.022         UA1     = 4.31E-9
+UB1     = -7.61E-18       UC1     = -5.6E-11     AT      = 3.3E4
+WL      = 0              WLN     = 1             WW      = 0
+WWN    = 1               WWL     = 0             LL      = 0
+LLN     = 1               LW      = 0             LWN     = 1
+LWL     = 0               CAPMOD = 2            XPART   = 0.5
+CGDO   = 7.11E-10         CGSO    = 7.11E-10    CGBO    = 1E-12
+CJ      = 1.179334E-3    PB      = 0.8545261   MJ      = 0.4117753
+CJSW   = 2.215877E-10   PBSW    = 0.6162997   MJSW    = 0.2678074
+CJSWG  = 4.22E-10         PBSWG  = 0.6162997   MJSWG   = 0.2678074
+CF      = 0              PVTH0   = 2.283319E-3 PRDSW   = 5.6431992
+PK2     = 2.813503E-3    WKETA   = 2.438158E-3 LKETA   = -0.0116078
+PU0     = -2.2514581     PUA     = -7.62392E-11 PUB     = 4.502298E-24
+PVSAT  = -50              PETAO   = 1E-4         PKETA   = -1.047892E-4 )
*|


```

I1=50u, V1 parametar sa listom vrednosti 1.8V 0.9V i 0.5V


DC sweep

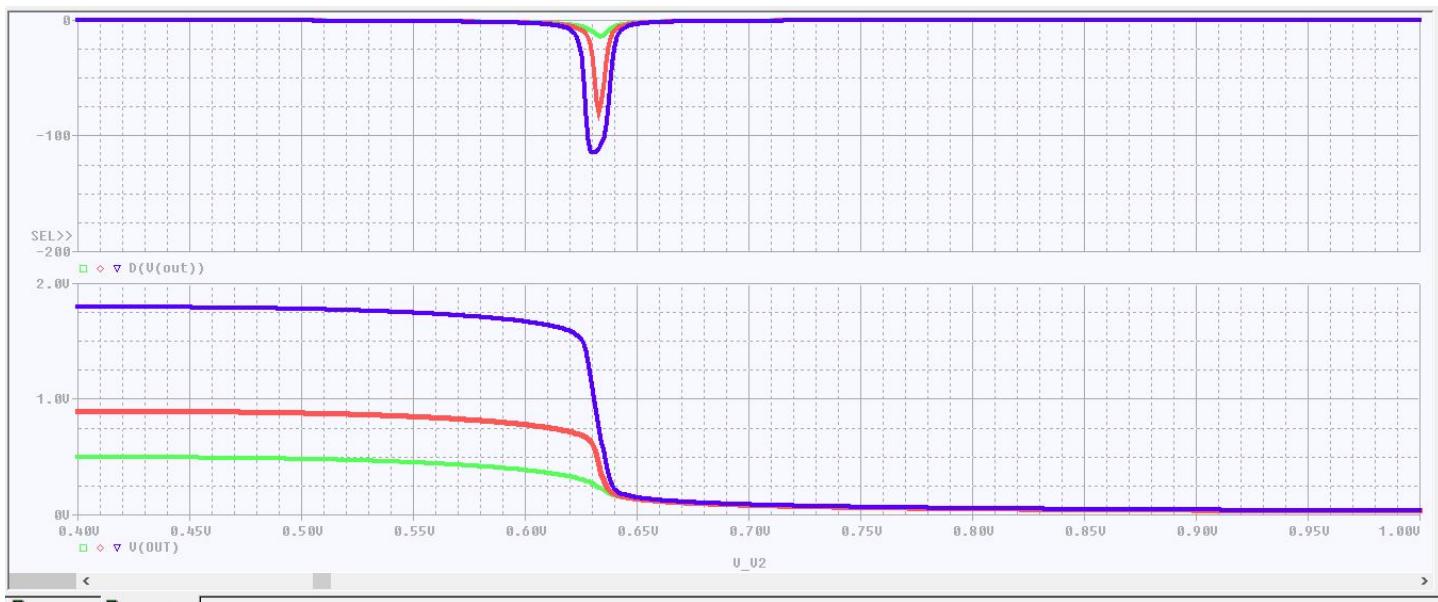

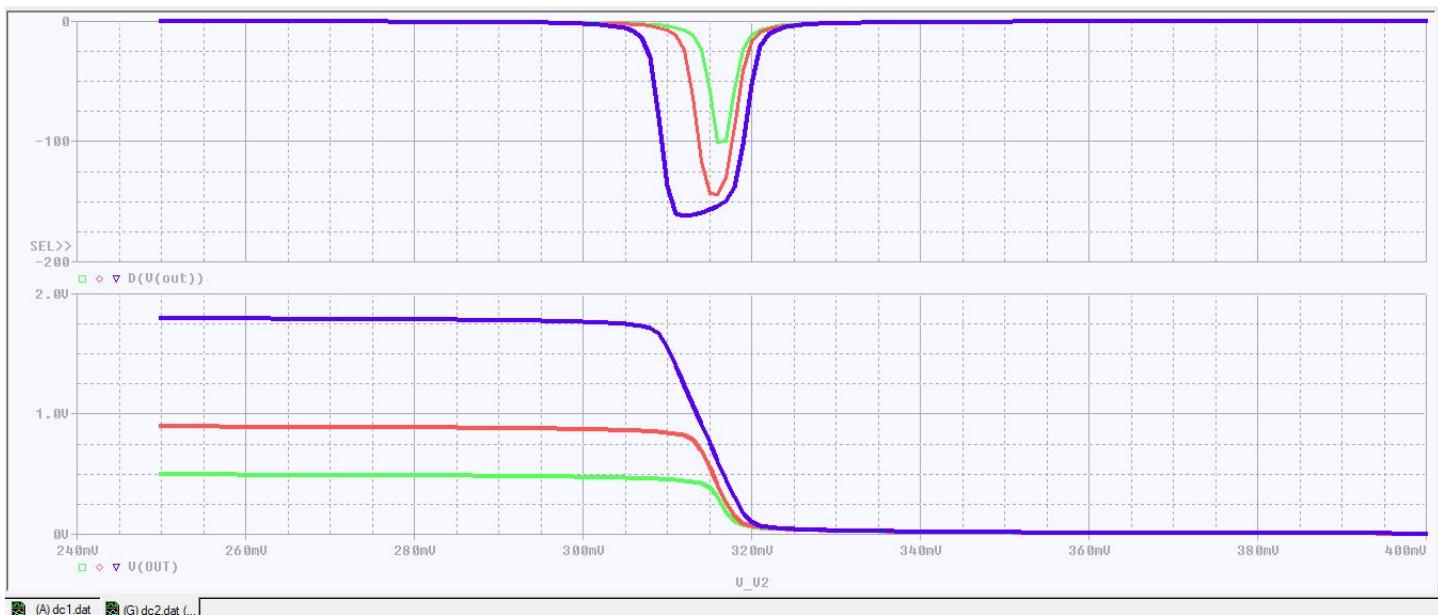
$I_1=100n$, V_1 parametar sa listom vrednosti 1.8V 0.9V i 0.5V
DC sweep



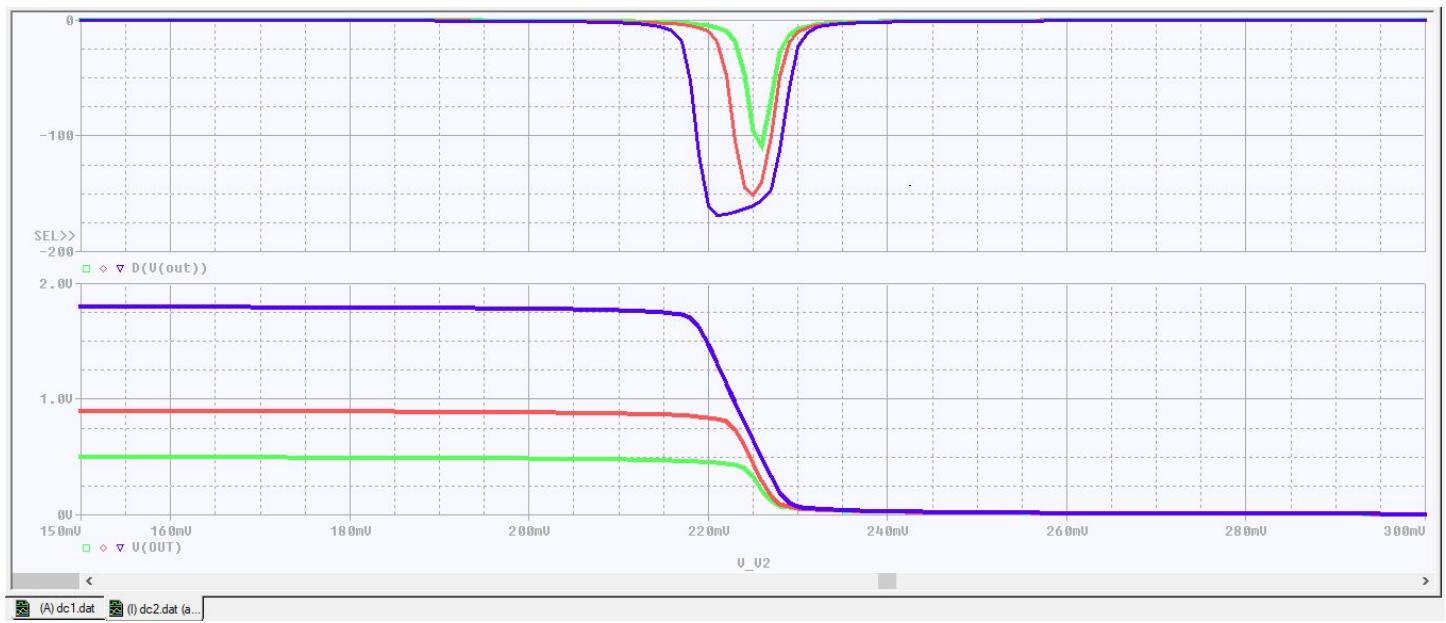$I_1=10n$, V_1 parametar sa listom vrednosti 1.8V 0.9V i 0.5V
DC sweep



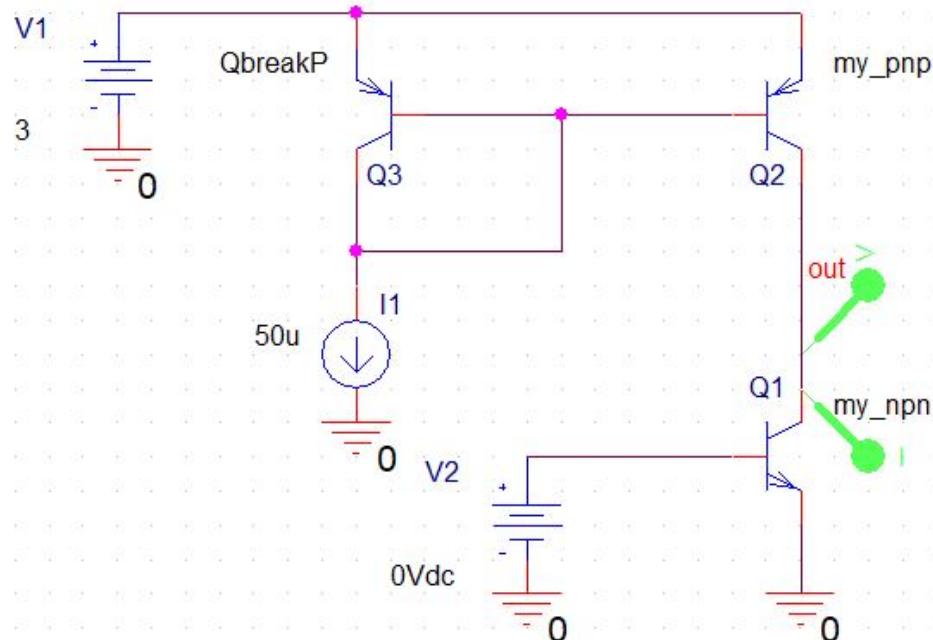Pojačavač sa integrisanim bipolarnim tranzistorima



```
.model my_npn NPN is=6e-18 bf=100 Vaf=35
.model my_pnp PNP is=6e-18 bf=50 Vaf=30
```

DC sweep V2 600m 800m 0.1mV

