


# OTA-1

### ❖ OVA-Operational Voltage Amplifier


- Ideally a voltage-controlled voltage source
- Typically contains an output stage that can drive “arbitrary” loads, including small resistances
- Predominantly used for board-level circuitry
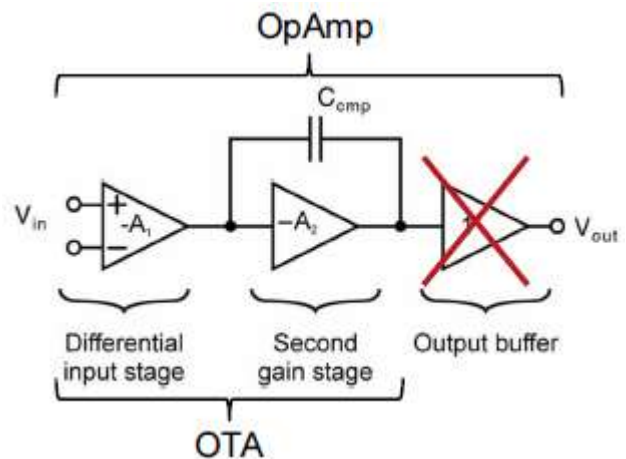
### ❖ OTA-Operational Transconductance Amplifier


- Ideally a voltage controlled current source
- Typically restricted to capacitive (or moderate resistive) loads
- Primarily used in integrated circuits



OpAmp Symbol

 


OTA Symbol  
(Fully Differential)

 

- The op-amp (OVA and OTA) is a fundamental building block in Mixed Signal design.
- Employed profusely in data converters, filters, sensors, drivers etc.
- Continued scaling in CMOS technology has been challenging the established paradigms for op-amp design.

- With downscaling in channel length (L)
  - ✓Transition frequency increases (more speed)
  - ✓Open-loop gain reduces (lower intrinsic gain)
  - ✓Supply voltage is scaled down (lower headroom)
  - ✓VDD is scaling down but  $V_{TH}$  is almost constant (Design headroom is shrinking faster)
  - ✓Random offsets due to device mismatches
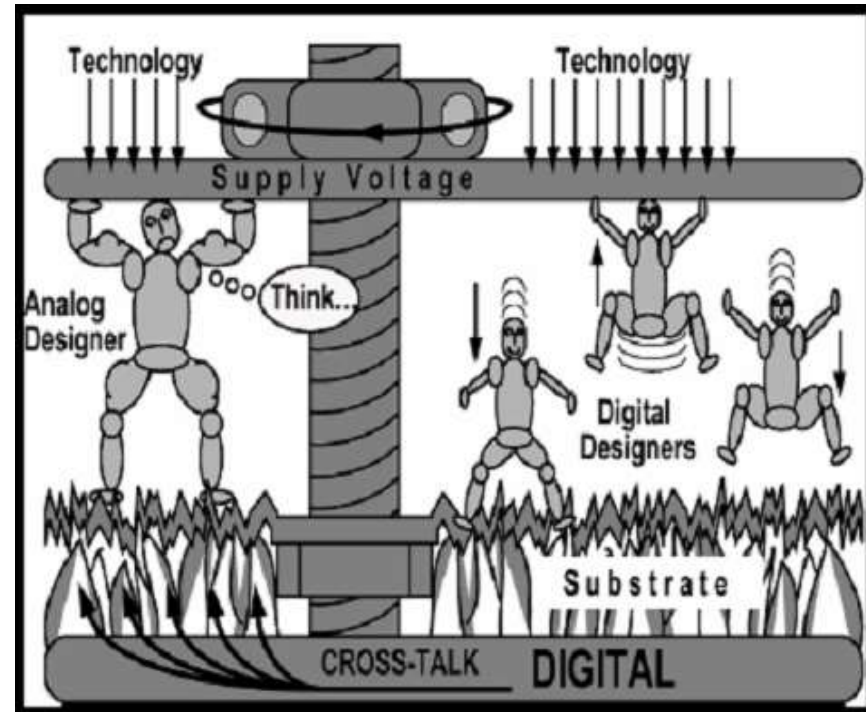
$$\sigma_{\Delta V_{TH}} \propto \frac{1}{\sqrt{WL}}$$



- Integration of Analog into Nano-CMOS?
  - ✓Design low-VDD op-amps.
  - ✓Replace vertical stacking (cascode) by horizontal cascading of gain stages
  - ✓Explore more effective op-amp compensation techniques.
  - ✓Offset tolerant designs.
  - ✓Also minimize power and layout area to keep up with the digital trend.
  - ✓Better power supply noise rejection (PSRR)
- Even if we employ wide-swing biasing for low-voltage designs, three- or higher stage opamps will be indispensable in realizing large open-loop DC gain.

The op amp (operational amplifier) is a high gain, dc coupled amplifier designed to be used with negative feedback to precisely define a closed loop transfer function.

The basic requirements for an op amp:

- Sufficiently large gain (the accuracy of the signal processing determines this)
- Differential inputs
- Frequency characteristics that permit stable operation when negative feedback is applied


Other requirements:

- High input impedance
- Low output impedance
- High speed/frequency

## ❖ OP AMP CHARACTERIZATION
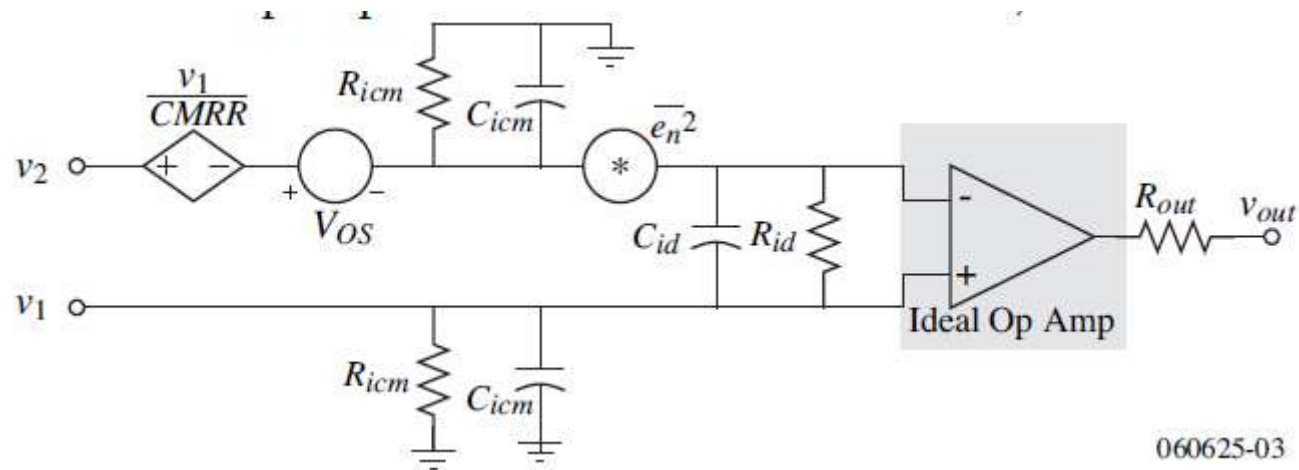
### • Linear and Static Characterization of the CMOS Op Amp

A model for a nonideal op amp that includes some of the linear, static nonidealities:



where

$R_{id}$  = differential input resistance

$C_{id}$  = differential input capacitance

$R_{icm}$  = common mode input resistance

$C_{icm}$  = common mode input capacitance

$V_{OS}$  = input-offset voltage

CMRR = common-mode rejection ratio (when  $v_1=v_2$  an output results)

$e_n^2$  = voltage-noise spectral density (mean-square volts/Hertz)

### ▪ Linear and Dynamic Characteristics of the Op Amp

Differential and common-mode frequency response:

$$V_{out}(s) = A_v(s)[V_1(s) - V_2(s)] \pm A_c(s) \frac{V_1(s) + V_2(s)}{2}$$

Differential-frequency response:

$$A_v(s) = \frac{A_{v0}}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \left(1 - \frac{s}{p_3}\right) \dots}$$

$$p_i = -\omega_i$$

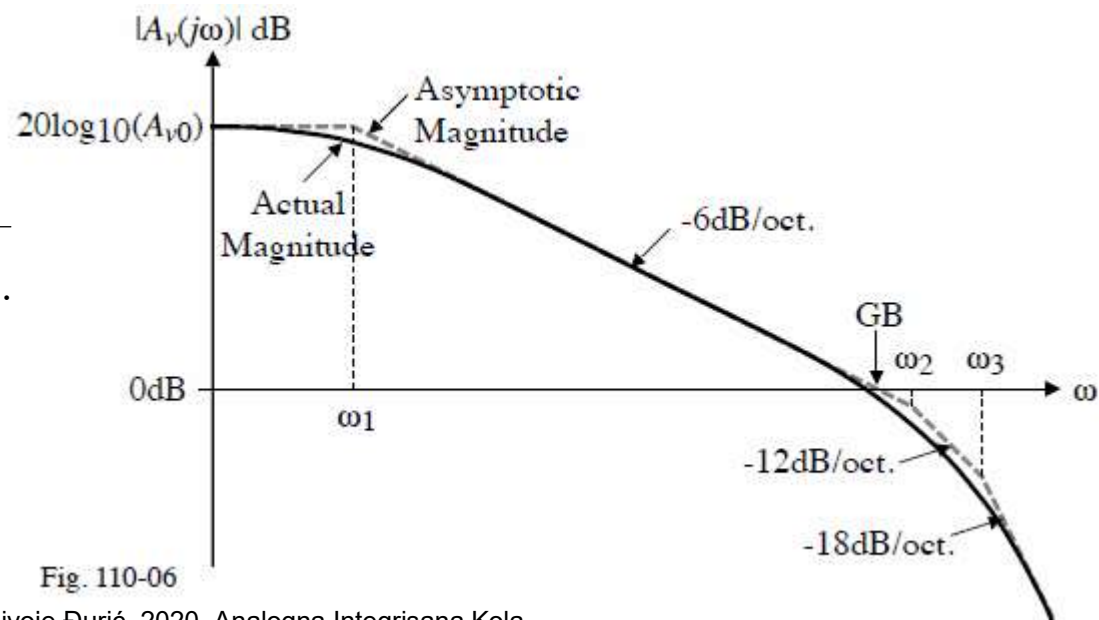


Fig. 110-06

Radivoje Đurić, 2020, Analogni Integrirana Kola

## Other Characteristics of the Op Amp

- Power supply rejection ratio (*PSRR*):

$$PSRR = \frac{V_{out}(s) / V_{in}(s) \Big|_{V_{dd}(s)=0}}{V_{out}(s) / V_{dd}(s) \Big|_{V_{in}(s)=0}}$$


- Input common mode range (*ICMR*):

*ICMR = the voltage range over which the input common-mode signal can vary without influence the differential performance*

- Slew rate (*SR*): *maximum current available to charge and discharge a capacitance*

*SR = output voltage rate limit of the op amp*

 
- Settling time ( $T_s$ ): *the time needed for the output of the output of the op amp to reach a final value value when excited by a small signal (SR is a large-signal phenomenon). Small-signal settling time can be completely determined from the location of the poles and zeros in the small-signal equivalent circuit.*




## ❖ OP AMP CATEGORIZATION

Amplifiers generally consist of a cascade of V-I (transconductance stage) or I-V (load stage)

### •Classification of CMOS Op Amps

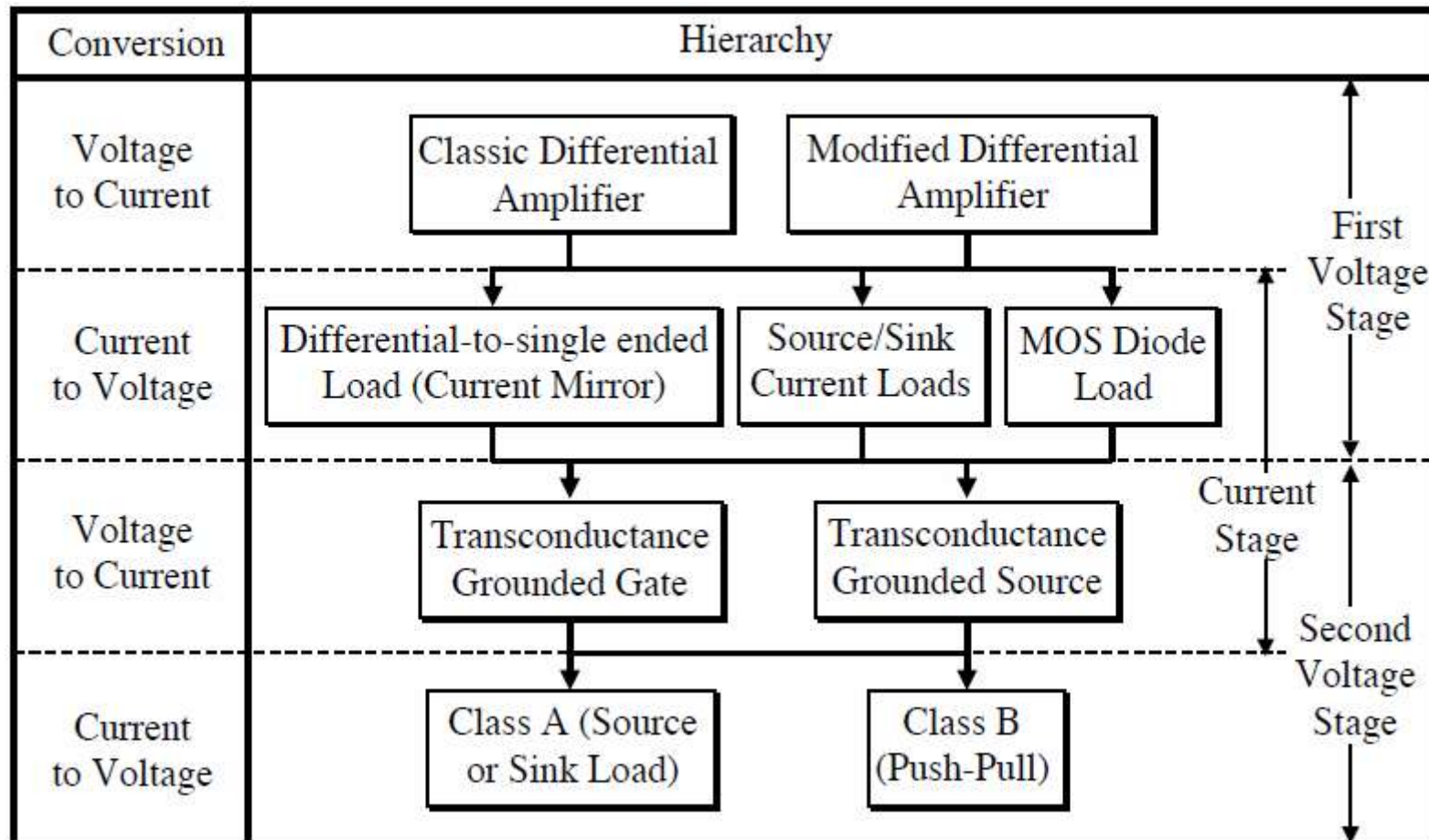

- Output configuration
  - Single ended
  - Differential
    - Predominantly used for integrated high-performance or high precision amplifiers
    - Requires common mode feedback circuit
  - Class-A
    - Output cannot source/sink currents larger than quiescent point bias current
  - Class-AB
    - Output can provide large drive currents “on demand”
  - Dynamic, comparator-based
    - Still a research topic
- ✓ Two-stage single ended Miller CMOS OTA

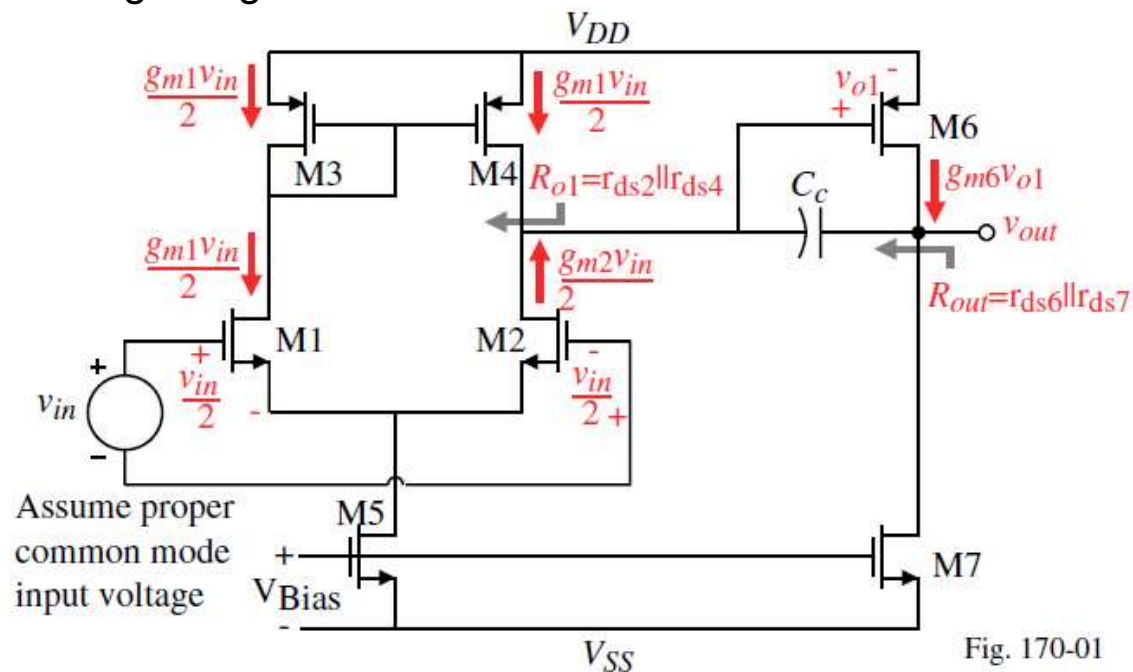

$$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \left( \frac{-g_{m6}}{g_{ds6} + g_{ds7}} \right)$$

Fig. 170-01



- Classical two-stage CMOS op amp broken into voltage-to-current and current-to-voltage stages:


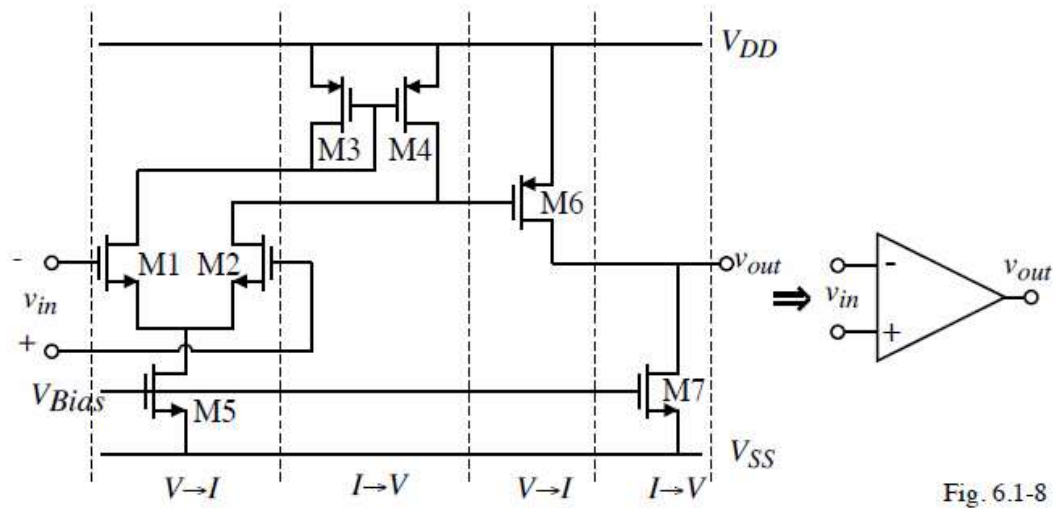



Fig. 6.1-8

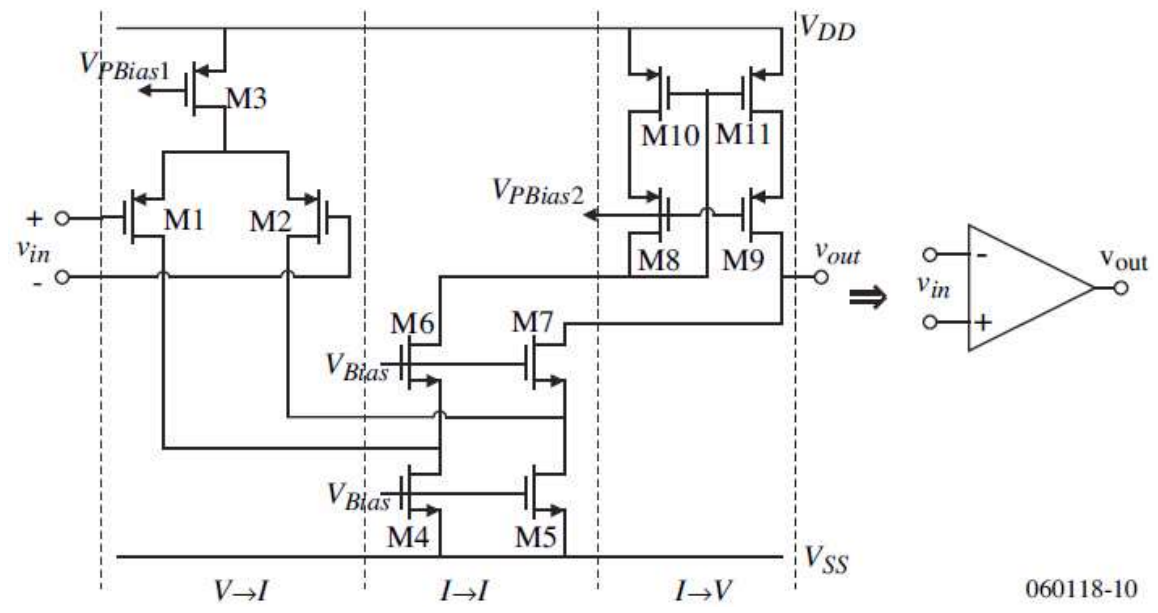- Folded cascode CMOS op amp broken into stages:



060118-10

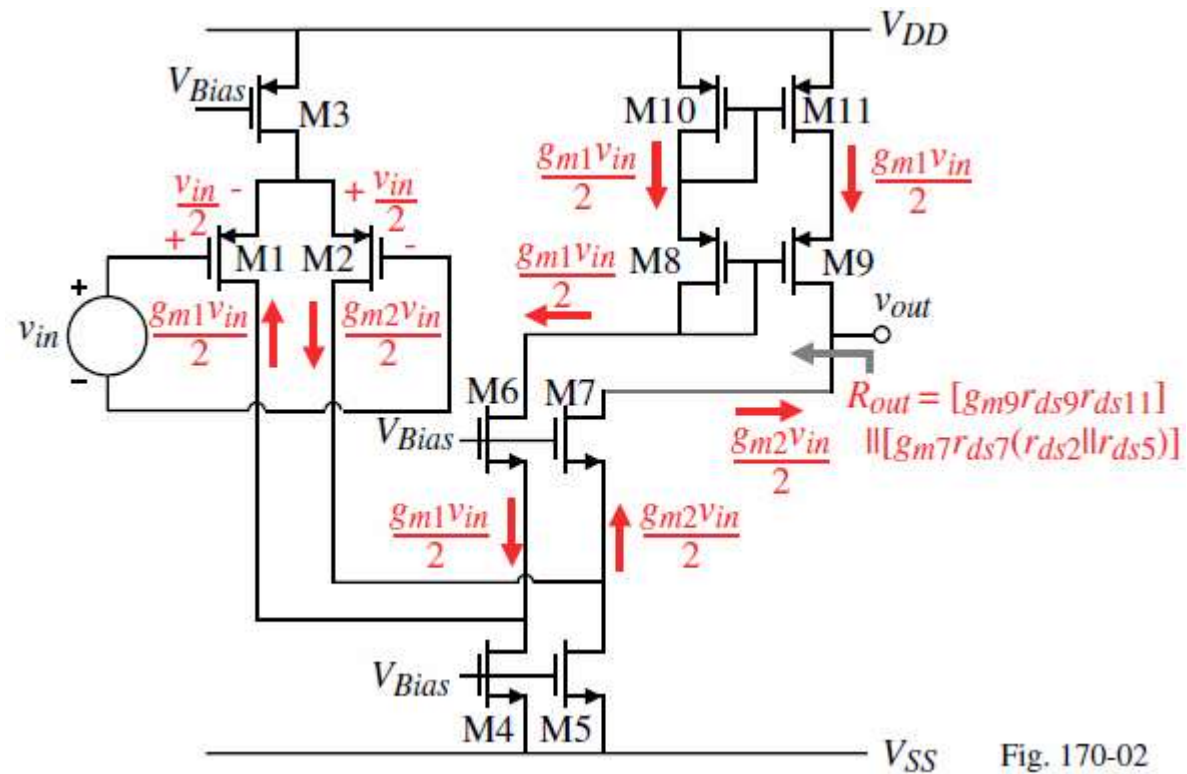
✓Two-stage Single ended Folded-Cascode CMOS OTA



$$\frac{v_{out}}{v_{in}} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \right) R_{out} = g_{m1} \{ (g_{m9}r_{ds9}r_{ds11}) \parallel [g_{m7}r_{ds7}(r_{ds2} \parallel r_{ds5})] \}$$
 
## ➤ COMPENSATION OF OP AMPS


- Objective of compensation is to achieve stable operation when negative feedback is applied around the op amp.



$$L(s) = -A(s)F(s)$$

$$CLG(s) = \frac{A(s)}{1 + A(s)F(s)}$$


$$|A(j\omega_{0dB})F(j\omega_{0dB})| = |L(j\omega_{0dB})| = 1 \Rightarrow \omega_0$$

 

$$\begin{aligned} \phi_M &= 2\pi - \arg[-A(j\omega_{0dB})F(j\omega_{0dB})] \\ &= 2\pi - \arg[L(j\omega_{0dB})] \end{aligned}$$
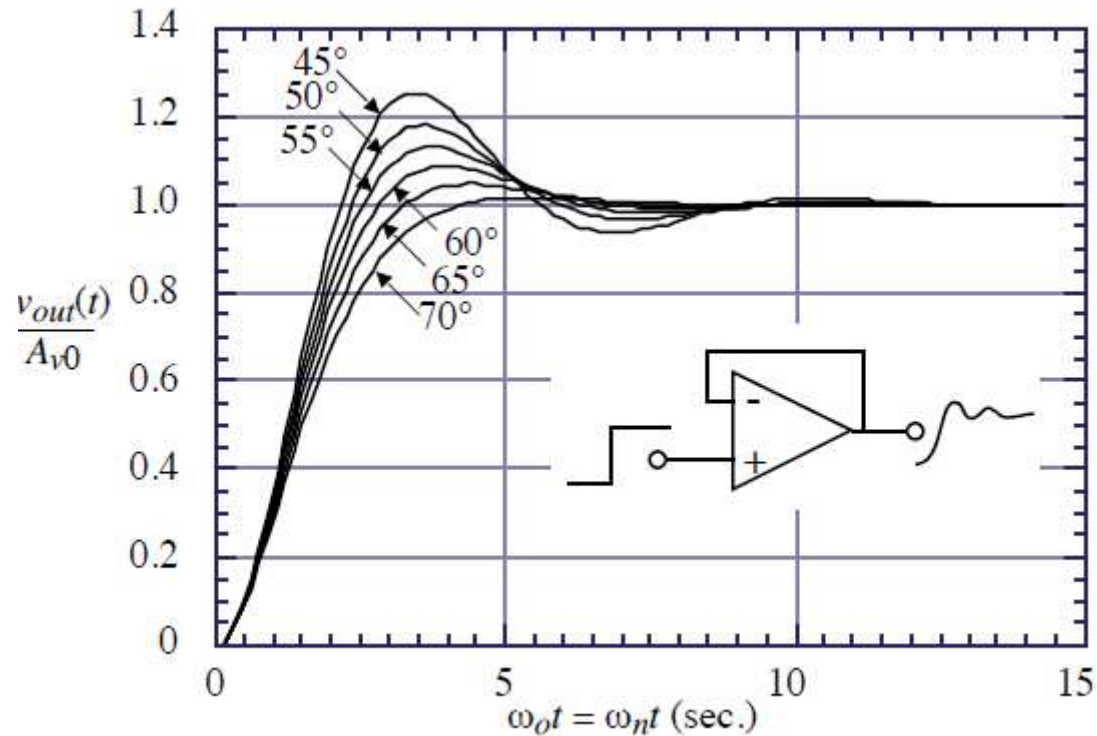
## Why Do We Want Good Stability?


- Consider the step response of second-order system which closely models the closed-loop gain of the op amp connected in unity gain.



- A “good” step response is one that quickly reaches its final value.
- Therefore, we see that phase margin should be at least 45° and preferably 60° or larger.  
(A rule of thumb for satisfactory stability is that there should be less than three rings.)
- Note that good stability is not necessarily the quickest rise time.

## Root Locus

➤ 1st order feedback system

 

• A so-called “root locus” plot shows the movement of the poles in the s plane as we vary the low-frequency loop gain  $T_0$

➤ 2nd order feedback system


$$H(s) = \frac{1}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

$$\text{for } Q > 0.5 \quad s_{1,2} = -\frac{\omega_0}{2Q} \left( 1 \pm j\sqrt{4Q^2 - 1} \right)$$

$$\text{for } Q \leq 0.5 \quad s_{1,2} = -\frac{\omega_0}{2Q} \left( 1 \pm \sqrt{1 - 4Q^2} \right)$$

$$\omega_0 = \sqrt{(1 + T_0)\omega_{p1}\omega_{p2}}$$
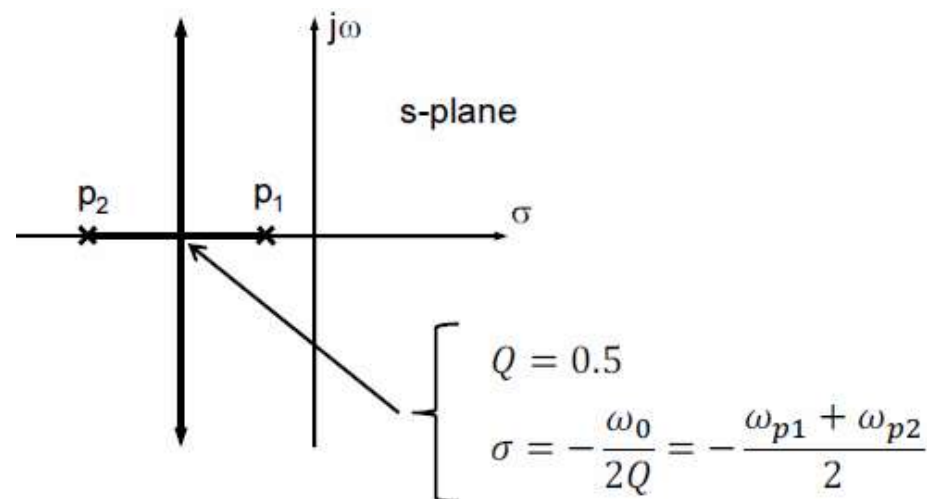
$$Q = \frac{\sqrt{(1 + T_0)\omega_{p1}\omega_{p2}}}{\omega_{p1} + \omega_{p2}}$$




➤ 3rd order feedback system

- Consider a feedback network consisting of a forward amplifier with three identical poles, and a feedback network with a constant transfer function  $f$

$$a(s) = \frac{a_0}{\left(1 - \frac{s}{p_1}\right)^3} \quad T_0 = a_0 f$$
 
$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{\frac{a_0}{\left(1 - \frac{s}{p_1}\right)^3}}{1 + a \frac{a_0}{\left(1 - \frac{s}{p_1}\right)^3} f} = \frac{a_0}{\left(1 - \frac{s}{p_1}\right)^3 + T_0}$$



The poles of  $A(s)$  are therefore the solution to

$$\left(1 - \frac{s}{p_1}\right)^3 + T_0 = 0 \quad \left(1 - \frac{s}{p_1}\right)^3 = -T_0$$

$$\left(1 - \frac{s}{p_1}\right) = \sqrt[3]{-T_0} = -\sqrt[3]{T_0} \quad \text{or} \quad \left(1 - \frac{s}{p_1}\right) = \sqrt[3]{T_0} e^{j60^\circ} \quad \text{or} \quad \left(1 - \frac{s}{p_1}\right) = \sqrt[3]{T_0} e^{-j60^\circ}$$

$$s_1 = p_1 \left(1 + \sqrt[3]{T_0}\right) \quad s_2 = p_1 \left(1 - \sqrt[3]{T_0} e^{j60^\circ}\right) \quad s_3 = p_1 \left(1 - \sqrt[3]{T_0} e^{-j60^\circ}\right)$$

$$0 = 1 - \text{Re}\left(\sqrt[3]{T_0} e^{j60^\circ}\right) \quad 0 = 1 - \sqrt[3]{T_0} \cos(60^\circ) \Rightarrow T_0 = 8$$

MATLAB:


The transfer function with three poles

```
s = tf('s');
```

```
p1=-1; p2=-2; p3=-4;
```

```
T = 1 / [(1-s/p1)*(1-s/p2)*(1-s/p3)];
```

```
rlocus(T)
```

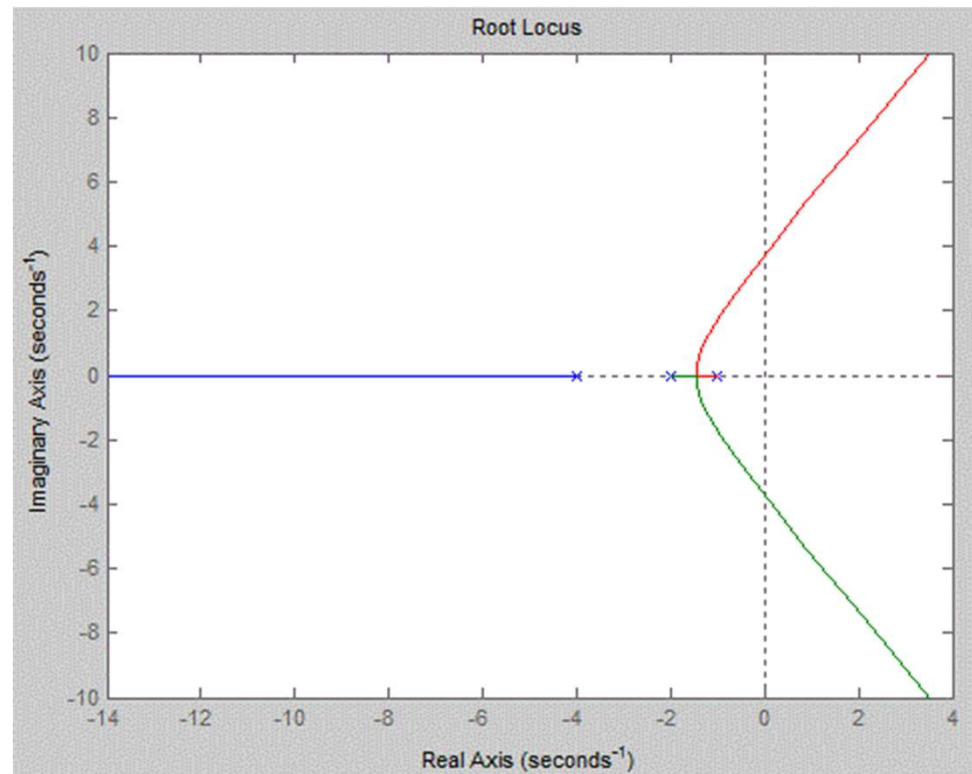


Adding a Zero:

```
s = tf('s');
```

```
z=-5; p1=-1; p2=-2; p3=-4;
```

```
T = (1-s/z) / [(1-s/p1)*(1-s/p2)*(1-s/p3)];
```

```
rlocus(T)
```

 



## ▪ Benchmarking

- In order to compare the merit of various compensation techniques, it makes sense to inspect the loop's unity gain frequency before and after the compensation is applied
- Rationale: The maximum bandwidth we can possibly expect from a feedback amplifier is the unity gain frequency of the loop
  - ✓ Regardless of the order of the feedback system, the closed-loop response departs from  $1/f$  as  $|T(s)|$  crosses unity

$$A(s) = \frac{a(s)}{1 + a(s)f(s)} \begin{cases} \cong \frac{1}{f(s)} & \text{for } |T(s)| \gg 1 \\ \cong a(s) & \text{for } |T(s)| \ll 1 \end{cases}$$

- ✓ Consider a loop transfer function with  $n$  “dominant” poles that occur before the unity crossover



$$T(s) = \frac{T_0}{\left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) \dots \left(1 - \frac{s}{p_n}\right)} = \frac{T_0}{1 + \dots + \frac{s^n}{p_1 p_2 \dots p_n}}$$

$$\omega_u \cong \sqrt[n]{T_0 |p_1| |p_2| \dots |p_n|} = \sqrt[n]{LP}$$



- ✓ The product of the low frequency loop gain and all dominant poles is called the loop gain pole product (LP product)
- ✓ Note that in a first-order system, the LP product is simply the gain bandwidth product

▪ **Feedback Zero Compensation**

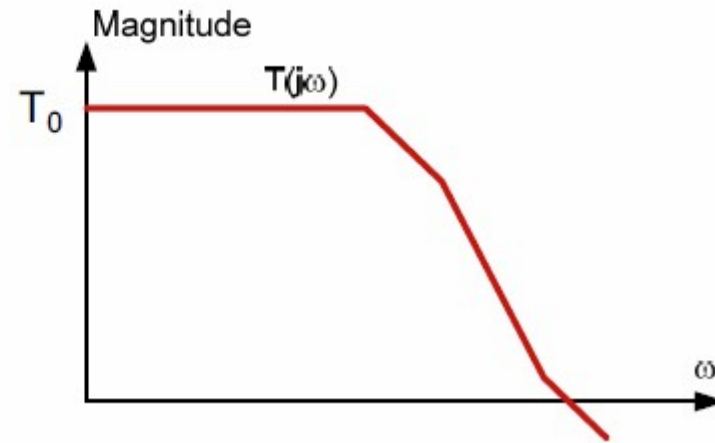 ✓ Leave amplifier poles unchanged and introduce a zero in the feedback network




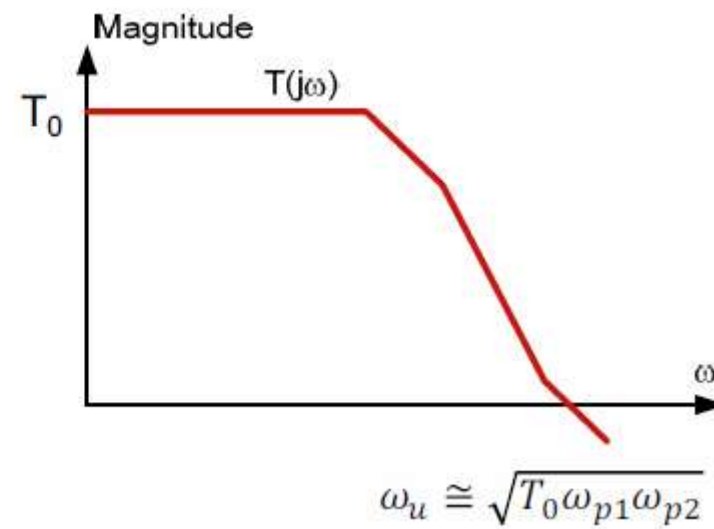 • **Efficiency of Feedback Zero Compensation**




- ✓ To first order, since we do not change the poles, the LP product and  $\omega_u$  are (approximately) unchanged.
- ✓ Feedback zero compensation is therefore bandwidth efficient, since we do not need to sacrifice bandwidth to stabilize the circuit.
- ✓ To second order, the LP product will change slightly due to loading from the capacitance added in the feedback network

▪ **Narrowbanding Compensation**

 

Idea: Make one of the loop poles dominant, leave other poles unchanged

• **Efficiency of Narrowbanding**

 

$\omega_{p1}$  that gives a maximally flat magnitude response for the closed-loop amplifier?


$$\omega_{p1} = \frac{1}{2} \frac{\omega_{p2}}{T_0}$$

$$\omega_u \cong \sqrt{T_0 \omega_{p1} \omega_{p2}}$$

$$\omega'_u \cong T_0 \omega_{p1} \cong \frac{1}{2} \omega_{p2}$$


- ✓ The crossover and bandwidth is limited to some fraction of  $\omega_{p2}$
- ✓ At first glance, this makes narrowbanding appear to be inefficient
- ✓ However, provided that  $\omega_{p2}$  is close to the transit frequency of the process technology, this compensation approach is acceptable and hard to surpass in terms of absolute achievable closed-loop speed

 ❖ Example: Single Gain Stage with Current Buffer




- $C_{gs}$  introduces a non-dominant pole at high frequencies  $\omega_{p2} = \omega_T$
- $C_L$  is adjusted until the circuit achieves the desired phase margin
- This type of narrowbanding is called “load compensation,” since stability is ensured by properly sizing the load capacitance  $C_L$

✓ Example Realizations

 
 
## Two-Stage OTA

- The two-stage amplifier shown below has two comparable poles, assuming that there is no additional significant pole from the feedback network




- ✓ If the feedback network is resistive, we may be able to compensate the amplifier by introducing a feedback zero
- ✓ What can we do if the feedback is capacitive?

- ✓ Narrowbanding is not a good idea, since both poles are at low frequencies
 
## Miller Compensation

- ✓ Purposely connect a capacitor across the second transconductor!



- Two interesting things happen
  - ✓ Low frequency input capacitance of second stage becomes large – moves the first pole to a lower frequency
  - ✓ Qualitatively speaking, at high frequencies,  $C_c$  turns the second stage into a “diode connected device” – low impedance, i.e. large  $\omega_{p2}$

- Using the dominant pole approximation:

$$p_1 \cong -\frac{1}{R_1[C_1 + C_c(1 + g_{m2}R_2)] + R_2(C_2 + C_c)} \quad p_2 \cong -\frac{R_1[C_1 + C_c(1 + g_m R_2)] + R_2(C_2 + C_c)}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)}$$


RHP zero:  $z = +\frac{g_{m2}}{C_c}$

- ✓We can approximate further as shown below

$$\omega_{p1} \cong \frac{1}{g_{m2} R_2 R_1 C_c} \quad a_0 \omega_{p1} \cong \frac{g_{m1} R_1 g_{m2} R_2}{g_{m2} R_2 R_1 C_c} = \frac{g_{m1}}{C_c} \quad \text{GBW set by } g_{m1} \text{ and } C_c$$


$$\omega_{p2} \cong \frac{g_{m2} C_c}{C_1 C_2 + C_c (C_1 + C_2)} \quad \frac{1}{\omega_{p2}} \cong \left( \frac{C_1}{g_{m2}} + \frac{C_2}{g_{m2}} \right) \left( 1 + \frac{C_1 C_2}{C_1 + C_2} \right)$$

 - ✓“Pole Splitting”: Increasing  $C_c$  reduces  $\omega_{p1}$ , and increases  $\omega_{p2}$



✓ A very nice “knob” for adjusting the phase margin of the circuit!

• Graphical View of Pole Splitting

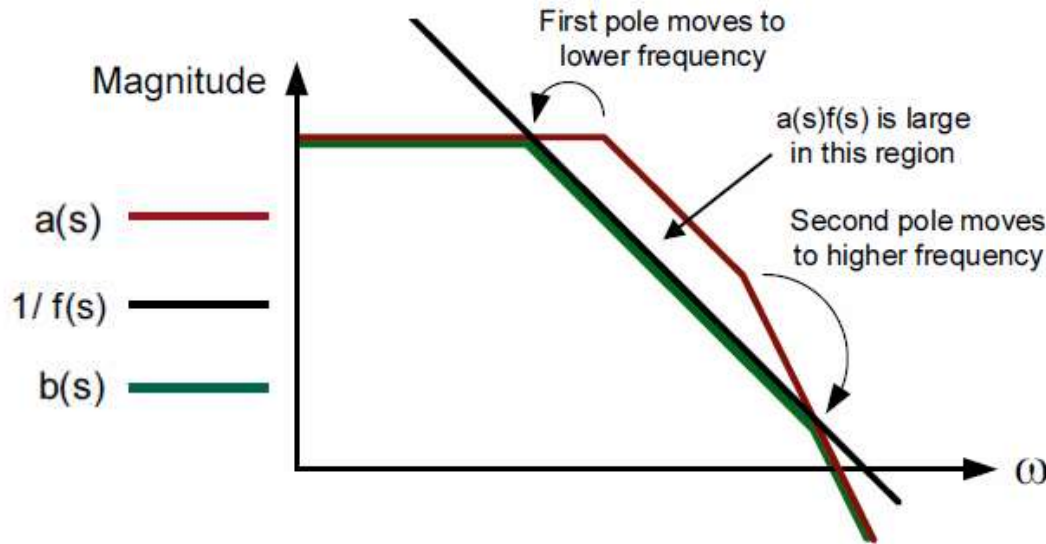

$$b(s) = \frac{a(s)}{1 + a(s)f(s)} \cong \begin{cases} a(s) & \text{when } |a(s)f(s)| \ll 1 \\ \frac{1}{f(s)} & \text{when } |a(s)f(s)| \gg 1 \end{cases}$$

➤ Miller Compensation of the Two-Stage Op Amp


The various capacitors are:

$C_c$  = accomplishes the Miller compensation

$C_M$  = capacitance associated with the first-stage mirror (mirror pole)

$C_I$  = output capacitance to ground of the first-stage

 $C_{II}$  = output capacitance to ground of the second-stage



➤ Compensated Two-Stage, Small-Signal Frequency Response Model Simplified

Use the CMOS op amp to illustrate:

- Assume that:

$$C_C \gg C_{gd6}, g_{m3} \gg g_{ds3} + g_{ds1}, \frac{g_{m3}}{C_M} \gg \omega_u = GB$$

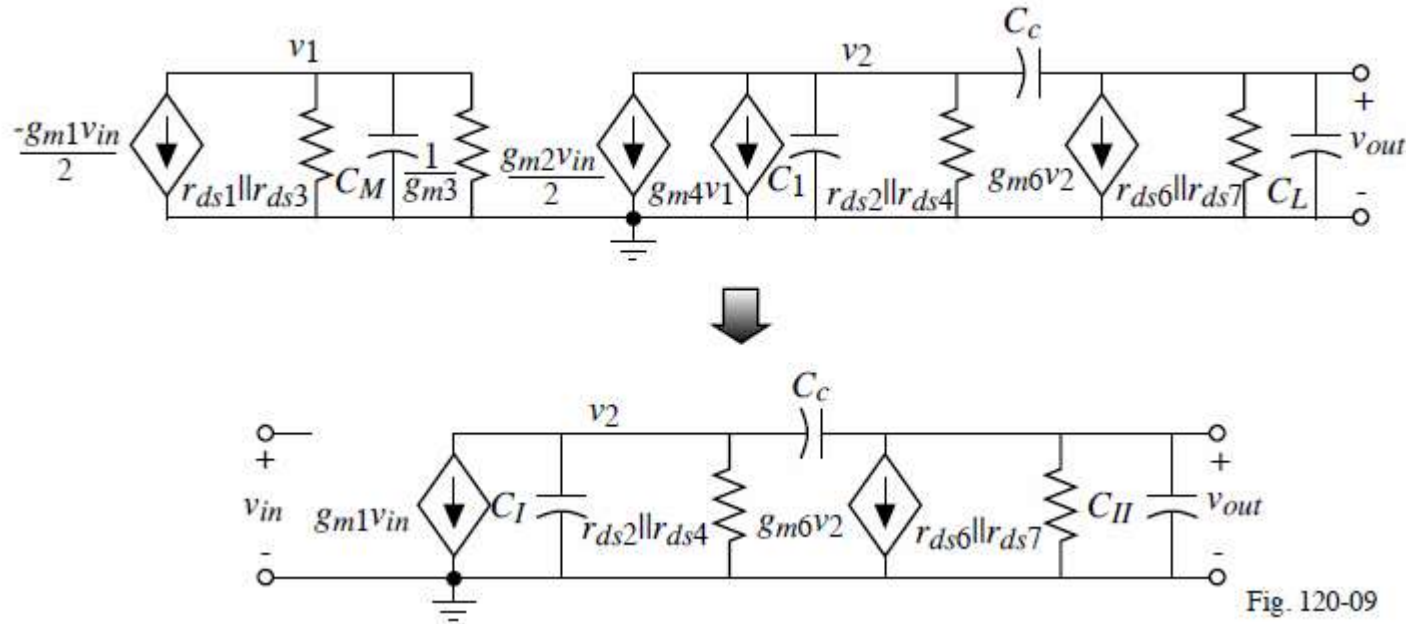


Fig. 120-09

$$g_{m1} = g_{mI}, g_{m6} = g_{mII}$$

$$\frac{1}{g_{ds2} + g_{ds4}} = R_I, \frac{1}{g_{ds6} + g_{ds7}} = R_{II}$$

$$C_I = C_{db2} + C_{db4} + C_{gs6}, C_{II} = C_L + C_{db6} + C_{db7} + C_{gd7}$$



Nodal Equations:

$$[G_I + s(C_I + C_c)]V_2 - sC_c V_{out} = -g_{mI}V_{in}$$

$$[g_{mII} - sC_c]V_2 + [G_{II} + s(C_{II} + C_c)]V_{out} = 0$$

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{g_{mI}(g_{mII} - sC_c)}{G_I G_{II} + s[G_{II}(C_I + C_{II}) + G_I(C_{II} + C_c) + g_{mII}C_c] + s^2[C_I C_{II} + C_c C_I + C_c C_{II}]}$$

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{A_0 \left(1 - \frac{s}{g_{mII}/C_c}\right)}{1 + s[R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c] + s^2 R_I R_{II}[C_I C_{II} + C_c C_I + C_c C_{II}]}$$

$$A_0 = \frac{g_I g_{II}}{G_I G_{II}} = \frac{g_{m1}}{g_{ds2} + g_{ds4}} \frac{g_{m6}}{g_{ds6} + g_{ds7}}$$

$$D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right) = 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

$$|p_2| \gg |p_1| \Rightarrow D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2} = 1 + as + bs^2$$

$$\Rightarrow p_1 = -\frac{1}{a}, p_2 = -\frac{a}{b}$$

$$p_1 = -\frac{1}{R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c} \approx -\frac{1}{g_{mII}R_I R_{II}C_c} = -\frac{g_{ds2} + g_{ds4}}{g_{m6}} \frac{g_{ds6} + g_{ds7}}{C_c}$$

$$C_I < C_c < C_{II}$$


$$p_2 = -\frac{a}{b} = -\frac{R_I(C_I + C_{II}) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c}{R_I R_{II}[C_I C_{II} + C_c C_I + C_c C_{II}]} \approx -\frac{g_{mII}}{C_{II}} = -\frac{g_{m6}}{C_L}$$

✓ Right-half plane zero:  $z_1 = +\frac{g_{mII}}{C_c} = \frac{g_{m6}}{C_c}$

✓ The unity gain bandwidth:  $GB = A_0 |p_1| = \frac{g_I g_{II}}{G_I G_{II}} \frac{1}{g_{mII} R_I R_{II} C_c} = \frac{g_{mI}}{C_c} = \frac{g_{m1}}{C_c}$

✓  $\omega_{p2}$  must be greater than unity-gainbandwidth or satisfactory phase margin will not be achieved.

• Influence of the Mirror Pole

 


The transfer function from the input to the output voltage of the first stage

$$\frac{V_{o1}(s)}{V_{in}(s)} = -\frac{g_{m1}/2}{g_{ds2} + g_{ds4}} \left[ \frac{g_{m3} + g_{ds1} + g_{ds3}}{g_{m3} + g_{ds1} + g_{ds3} + sC_3} + 1 \right] \approx -\frac{g_{m1}}{g_{ds2} + g_{ds4}} \frac{1 + \frac{s}{2g_{m3}/C_3}}{1 + \frac{s}{g_{m3}/C_3}}$$

$$z_3 = -2g_{m3} / C_3$$

$$p_3 = -g_{m3} / C_3$$

 

- The requirement for  $45^\circ$  phase margin is:

$$\Phi_M = \pm 180^\circ - \arg[A(j\omega)F(j\omega)] = \pm 180^\circ - \arctg\left(\frac{\omega}{\omega_{p1}}\right) - \arctg\left(\frac{\omega}{\omega_{p2}}\right) - \arctg\left(\frac{\omega}{\omega_{z1}}\right) = 45^\circ$$

$$\omega_{pi} = -p_i, i = 1, 2, \omega_{z1} = -z_1$$

- ✓Let  $\omega = GB$  and assume that  $\omega_{z1} \geq 10GB$ ,

$$45^\circ = \pm 180^\circ - \arctg\left(\frac{GB}{\omega_{p1}}\right) - \arctg\left(\frac{GB}{\omega_{p2}}\right) - \arctg(0.1)$$

Radivoje Đurić, 2020, Analognna Integrisana Kola

$$\Rightarrow 135^\circ \approx \arctg(A_0) + \arctg\left(\frac{GB}{\omega_{p2}}\right) + \arctg(0.1), A_0 \gg 1$$

$$\Rightarrow 135^\circ \approx 90^\circ + \arctg\left(\frac{GB}{\omega_{p2}}\right) + 5.7^\circ \Rightarrow 135^\circ \approx 90^\circ + \arctg\left(\frac{GB}{\omega_{p2}}\right) + 5.7^\circ$$

$$\Rightarrow \arctg\left(\frac{GB}{\omega_{p2}}\right) \approx 39.3^\circ \Rightarrow \frac{GB}{\omega_{p2}} = 0.818 \Rightarrow \omega_{p2} \geq 1.22 \cdot GB$$

✓ If 60° phase margin is required, then the following relationships apply:

$$\omega_{z1} \geq 10GB \Rightarrow \omega_{p2} \geq 2.2 \cdot GB$$


$$\frac{g_{m6}}{C_c} > \frac{10g_{m1}}{C_c} \Rightarrow g_{m6} > 10g_{m1}$$

$$\frac{g_{m6}}{C_c} > \frac{2.2g_{m1}}{C_c} \Rightarrow C_c > 0.22C_2$$

### ➤ CMOS op amp Slew Rate (SR)

• Slew rate occurs when currents flowing in a capacitor become limited and is given as

$$I_{\text{lim}} = C \frac{dv_C}{dt}$$

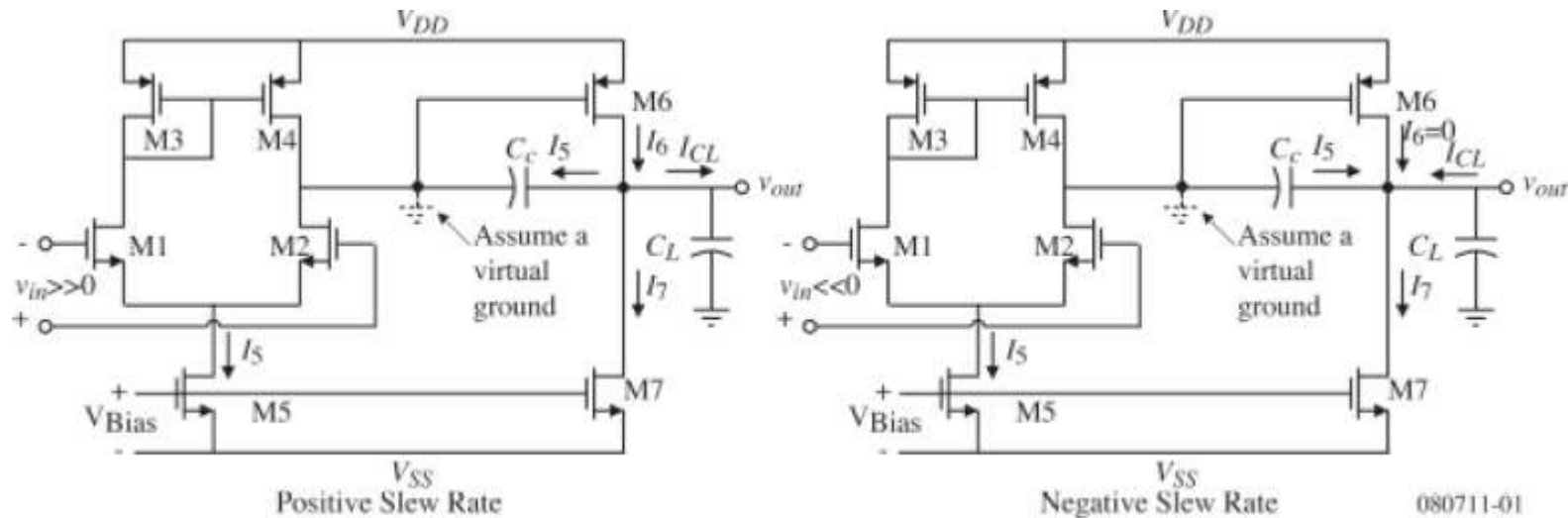

$$SR^+ = \min \left[ \frac{I_5}{C_c}, \frac{I_6 - I_5 - I_7}{C_L} \right] = \frac{I_5}{C_c}, I_6 \gg I_5 \quad SR^- = \min \left[ \frac{I_5}{C_c}, \frac{I_7 - I_5}{C_L} \right] = \frac{I_5}{C_c}, \text{if } I_7 \gg I_5$$

✓ Therefore, if  $C_L$  is not too large and if  $I_7$  is significantly greater than  $I_5$ , then the slew rate of the two-stage op amp should be,  $I_5/C_c$ .

## ➤ RIGHT-HALF PLANE ZERO

### ▪ Controlling the Right-Half Plane Zero

Why is the RHP zero a problem?

✓ Because it boosts the magnitude but lags the phase - the worst possible combination for stability.

✓ Solution of the problem: The compensation comes from the feedback path through  $C_c$ , but the RHP zero comes from the feedforward path through  $C_c$  so eliminate the feedforward path!

➤ Use of Buffer to Eliminate the Feedforward Path through the Miller Capacitor

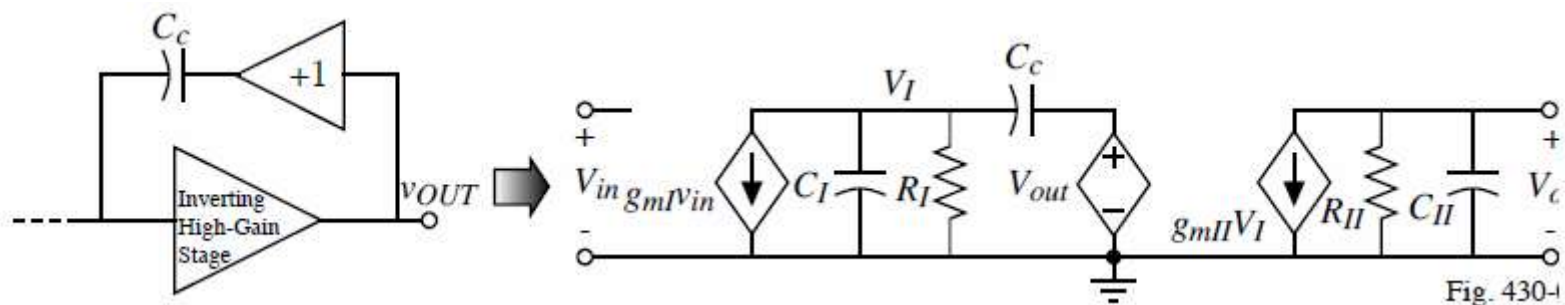


Fig. 430-1

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{A_0}{1 + s[R_I(C_I + C_{II}) + R_{II}C_{II} + g_{mII}R_I R_{II}C_c] + s^2 R_I R_{II}C_{II}(C_I + C_c)}$$

$$p_1 = -\frac{1}{R_I(C_I + C_{II}) + R_{II}C_{II} + g_{mII}R_I R_{II}C_c} \approx -\frac{1}{g_{mII}R_I R_{II}C_c} = -\frac{g_{ds2} + g_{ds4}}{g_{m6}} \frac{g_{ds6} + g_{ds7}}{C_c}$$


$$C_I < C_c < C_{II}$$

$$p_2 = -\frac{a}{b} = -\frac{R_I(C_I + C_{II}) + R_{II}C_{II} + g_{mII}R_I R_{II}}{R_I R_{II}C_{II}(C_I + C_c)} \approx -\frac{g_{mII}C_c}{C_{II}(C_I + C_c)}$$

- ✓ Poles are approximately what they were before with the zero removed
- ✓ For 45° phase margin,  $\omega_{p2}$  must be greater than  $GB$
- ✓ For 60° phase margin,  $\omega_{p2}$  must be greater than  $1.73GB$

➤ Use of Buffer with Finite Output Resistance to Eliminate the RHP Zero

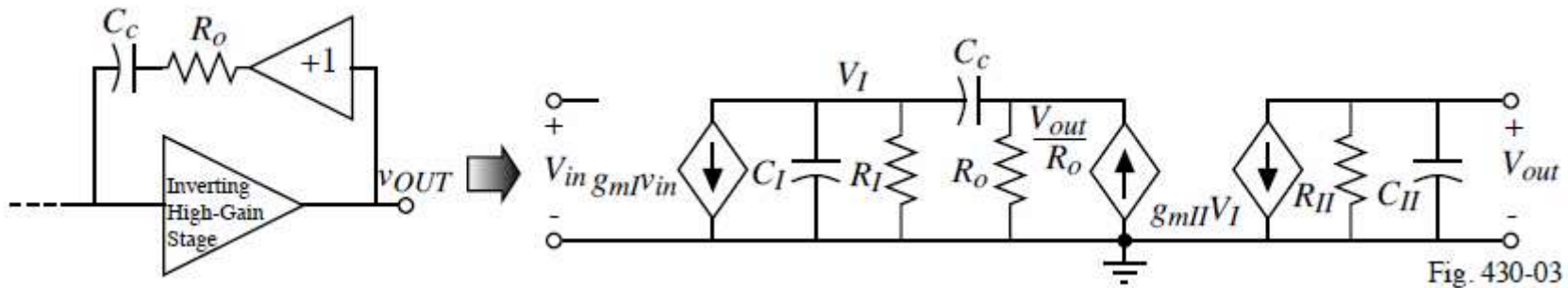• Assume that the unity-gain buffer has an output resistance of  $R_o$



• It can be shown that if the output resistance of the buffer amplifier,  $R_o$ , is not neglected that another pole occurs at,


$$p_4 \approx -\frac{1}{R_o [(C_I C_c)(C_I + C_c)]}$$

and a LHP zero at

$$z_2 \approx -\frac{1}{R_o C_c}$$

✓ Although the LHP zero can be used for compensation, the additional pole makes this method less desirable than the following method.

 ➤ Use of Nulling Resistor to Eliminate the RHP Zero (or turn it into a LHP zero)



Nodal Equations:

$$g_{mI}V_{in} + \frac{V_I}{R_I} + sC_I V_I + \left( \frac{sC_c}{1 + sC_c R_z} \right) (V_I - V_{out}) = 0$$

$$g_{mI}V_I + \frac{V_I}{R_{II}} + sC_{II}V_{out} + \left( \frac{sC_c}{1 + sC_c R_z} \right) (V_{out} - V_I) = 0$$

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = \frac{g_{mI}g_{mII}R_I R_{II} \left( 1 - s \left[ \frac{C_c}{g_{mII}} - R_z C_c \right] \right)}{1 + bs + cs^2 + ds^3}$$

$$b = R_I(C_I + C_c) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c + R_z C_c$$

$$c = R_I R_{II}(C_I C_{II} + C_c C_I + C_c C_{II}) + R_z C_c (R_I C_I + R_{II} C_{II})$$

$$d = R_I R_{II} C_I C_{II} C_c R_z$$

✓ If  $R_z$  is assumed to be less than  $R_I$  or  $R_{II}$  and the poles widely spaced, then the roots of the above transfer function can be approximated as

$$p_1 = -\frac{1}{R_I(C_I + C_c) + R_{II}(C_{II} + C_c) + g_{mII}R_I R_{II}C_c + R_z C_c} \approx -\frac{1}{(1 + g_{mII}R_{II})R_I C_c} \approx -\frac{1}{g_{mII}R_{II}R_I C_c}$$


$$p_2 \approx -\frac{g_{mII}C_c}{C_c C_I + C_I C_{II} + C_c C_{II}} \approx -\frac{g_{mII}}{C_{II}}$$

$$z_1 = \frac{1}{C_c \left( \frac{1}{g_{mII}} - R_z \right)}$$

$$p_4 \approx -\frac{1}{R_z C_I}$$



 - ✓ Note that the zero can be placed anywhere on the real axis!
- ✓ We desire that  $z_1 = p_2$  in terms of the previous notation



$$p_2 = z_1 \Rightarrow C_c \left( \frac{1}{g_{mII}} - R_z \right) = -\frac{C_{II}}{g_{mII}} \Rightarrow R_z = \frac{C_c + C_{II}}{C_c} \frac{1}{g_{mII}}$$

- ✓ With  $p_2$  canceled, the remaining roots are  $p_1$  and  $p_4$  (the pole due to  $R_z$ ). For unity-gain stability, all that is required is that

$$\omega_{p4} > A_0 \omega_{p1} = \frac{A_0}{g_{mII} R_{II} R_I C_c} = GB$$


$$\frac{1}{R_z C_I} > \frac{g_{mI}}{C_c} = GB$$

- ✓ Substituting  $R_z$  into the above inequality and assuming  $C_{II} \gg C_c$  results in

$$C_c > \sqrt{\frac{g_{mI}}{g_{mII}} C_I C_{II}}$$

- ✓ This procedure gives excellent stability for a fixed value of  $C_{II}$  ( $\approx C_L$ ).
- ✓ Unfortunately, as  $C_L$  changes,  $p_2$  changes and the zero must be readjusted to cancel  $p_2$ !

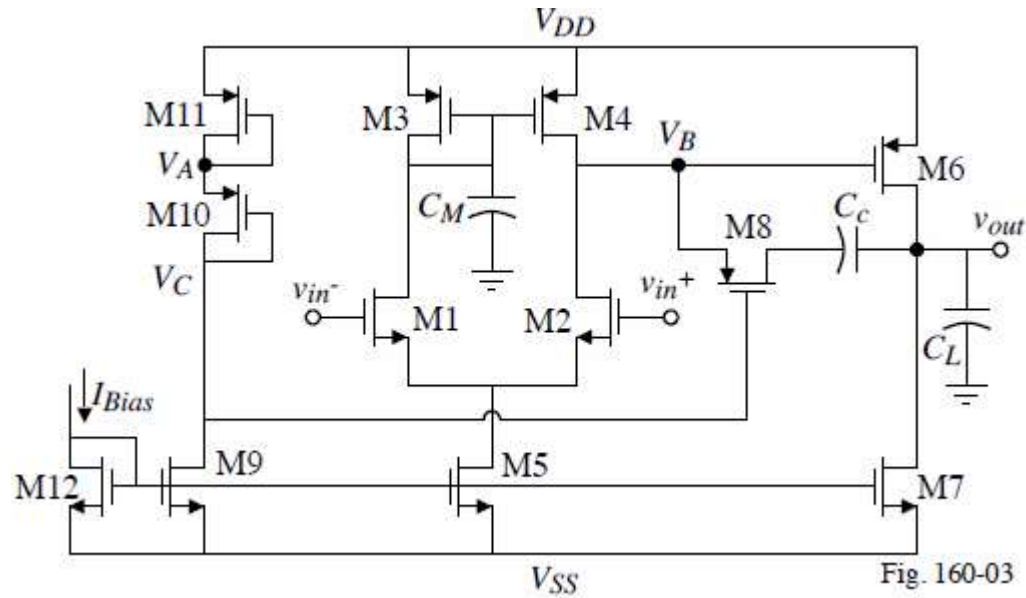➤ Incorporating the Nulling Resistor into the Miller Compensated Two-Stage Op Amp



$$p_1 \approx -\frac{1}{g_{mII} R_{II} R_I C_c} = -\frac{g_{mI}}{(g_{mII} g_{mI} R_{II} R_I) C_c} = -\frac{g_{mI}}{A_0 C_c} \quad p_2 \approx -\frac{g_{mII}}{C_{II}} \approx -\frac{g_{m6}}{C_L}$$

$$p_4 \approx -\frac{1}{R_z C_I} \quad z_1 = \frac{1}{C_c \left( \frac{1}{g_{m6}} - R_z \right)}$$

• Design of the Nulling Resistor (M<sub>8</sub>)

✓ For the zero to be on top of the second pole (p<sub>2</sub>), the following relationship must hold

$$R_z = \frac{C_c + C_{II}}{C_c} \frac{1}{g_{mII}} \approx \frac{C_c + C_L}{C_c} \frac{1}{g_{m6}} = \frac{C_c + C_L}{C_c} \frac{1}{\sqrt{2I_{D6} \mu_p C_{ox} (W/L)_6}}$$

Radioje Đurić, 2020, Analogni Integrirana Kola

✓The resistor,  $R_z$ , is realized by the transistor M8 which is operating in the triode region because the dc current through it is zero. Therefore,  $R_z$ , can be written as

$$R_z = \frac{1}{\partial i_{D8} / \partial v_{DS8}} \Big|_{V_{DS8}=0} = \frac{1}{\mu_p C_{ox} (W/L)_8 (V_{SG8} - |V_{THP}|)}$$

✓The bias circuit is designed so that voltage VA is equal to VB. As a result

$$|V_{GS10} - V_{THP}| = \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} (W/L)_{10}}} = |V_{GS8} - V_{THP}|$$

✓Equating the two expressions for  $R_z$  gives


$$R_z = \frac{1}{\mu_p C_{ox} (W/L)_8 \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} (W/L)_{10}}}} = \frac{1}{(W/L)_8} \sqrt{\frac{(W/L)_{10}}{2\mu_p C_{ox} I_{D10}}}$$

$$R_z = \frac{C_c + C_L}{C_c} \frac{1}{\sqrt{2I_{D6} \mu_p C_{ox} (W/L)_6}} = \frac{1}{(W/L)_8} \sqrt{\frac{(W/L)_{10}}{2\mu_p C_{ox} I_{D10}}}$$

$$\Rightarrow (W/L)_8 = \frac{C_c}{C_c + C_L} \sqrt{(W/L)_{10} (W/L)_6 \frac{I_{D6}}{I_{D10}}}$$

$$V_{GS11} = V_{GS6} \Rightarrow \left(\frac{W}{L}\right)_{11} = \frac{I_{D10}}{I_{D6}} \left(\frac{W}{L}\right)_6 \Rightarrow (W/L)_8 = \frac{C_c}{C_c + C_L} \sqrt{\frac{(W/L)_{10} (W/L)_6^2}{(W/L)_{11}}}$$

•An Alternate Form of Nulling Resistor

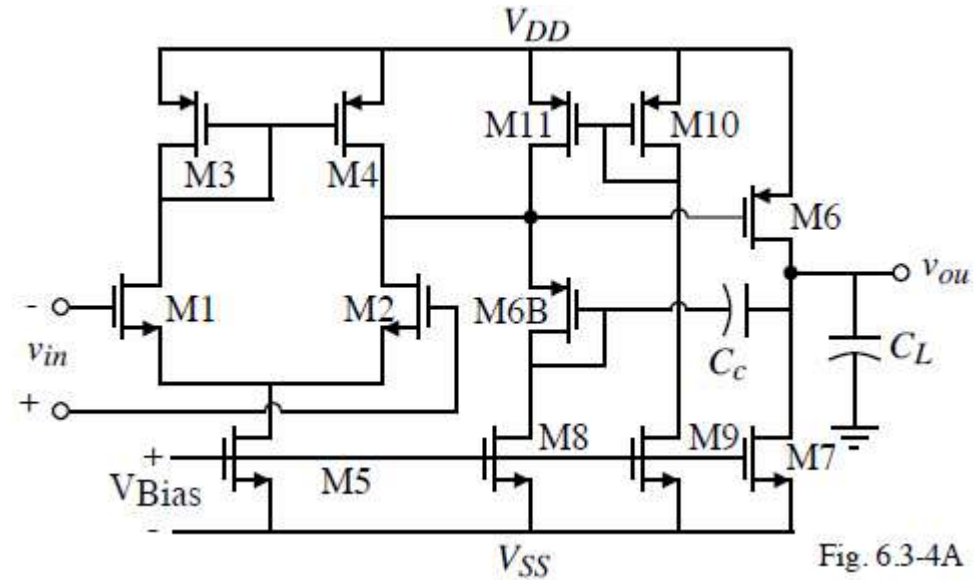


✓To cancel p2,

$$R_z \approx \frac{C_c + C_L}{C_c} \frac{1}{g_{m6}} = \frac{1}{g_{m6B}} \Rightarrow g_{m6} = g_{m6B} \left( 1 + \frac{C_L}{C_c} \right)$$

$$\sqrt{\frac{2I_{D6}}{\mu_p C_{ox} (W/L)_6}} = \sqrt{\frac{2I_{D6B}}{\mu_p C_{ox} (W/L)_{6B}}} \left( 1 + \frac{C_L}{C_c} \right)$$
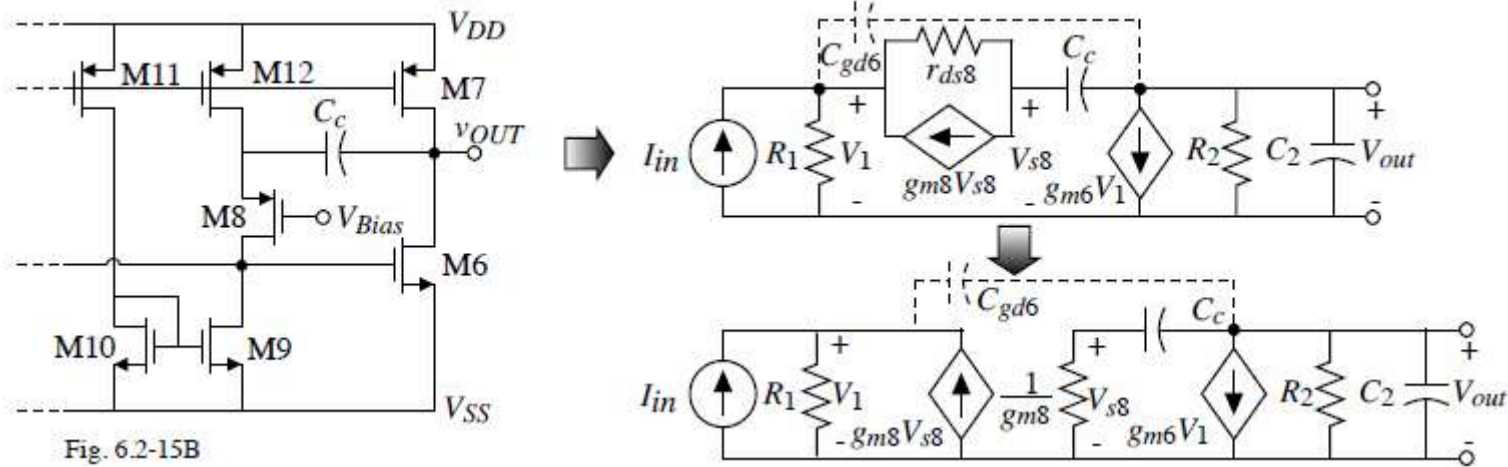
## ➤ Increasing the Magnitude of the Output Pole



$$R_1 = \frac{1}{g_{ds2} + g_{ds4} + g_{ds9}} \quad R_2 = \frac{1}{g_{ds6} + g_{ds7}}$$

Nodal equations:

$$I_{in} = G_1 V_1 - g_{m8} V_{s8} = G_1 V_1 - \frac{g_{m8} s C_c}{g_{m8} + s C_c} V_{out}$$

$$0 = g_{m6} V_1 + \left( G_2 + s C_2 + \frac{g_{m8} s C_c}{g_{m8} + s C_c} \right) V_{out}$$

✓ Solving for the transfer function  $V_{out}/I_{in}$  gives

$$\frac{V_{out}(s)}{I_{in}(s)} = -\frac{g_{m6}}{G_1 G_2} \frac{1 + \frac{s C_c}{g_{m8}}}{1 + s \left( \frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6} C_c}{G_1 G_2} \right) + s^2 \frac{C_1 C_2}{g_{m8} G_2}}$$

✓Using the approximate method of solving for the roots of the denominator gives

$$p_1 = -\frac{1}{\frac{C_c}{g_{m8}} + \frac{C_2}{G_2} + \frac{C_c}{G_2} + \frac{g_{m6}C_c}{G_1G_2}} \approx -\frac{6}{g_{m6}r_{ds}^2C_c}$$


$$p_2 = -\frac{\frac{g_{m6}r_{ds}^2C_c}{6}}{\frac{C_cC_2}{g_{m8}G_2}} = -\frac{g_{m8}r_{ds}^2G_2}{6} \frac{g_{m6}}{C_2} = \frac{g_{m8}r_{ds}}{3} p_2' \quad z_2 = -\frac{g_{m8}}{C_c}$$

where all the various channel resistance have been assumed to equal  $r_{ds}$  and  $p_2'$  is the output pole for normal Miller compensation.

✓Result: Dominant pole is approximately the same and the output pole is increased by  $\approx g_{m6}r_{ds}$

✓In addition there is a LHP zero at  $-g_{m8}/sC_c$  and a RHP zero due to  $C_{gd6}$  (shown dashed in the previous model) at  $g_{m6}/C_{gd6}$ .

✓Roots are:

 

## ➤ FEEDFORWARD COMPENSATION

✓ Use two parallel paths to achieve a LHP zero for lead compensation purposes

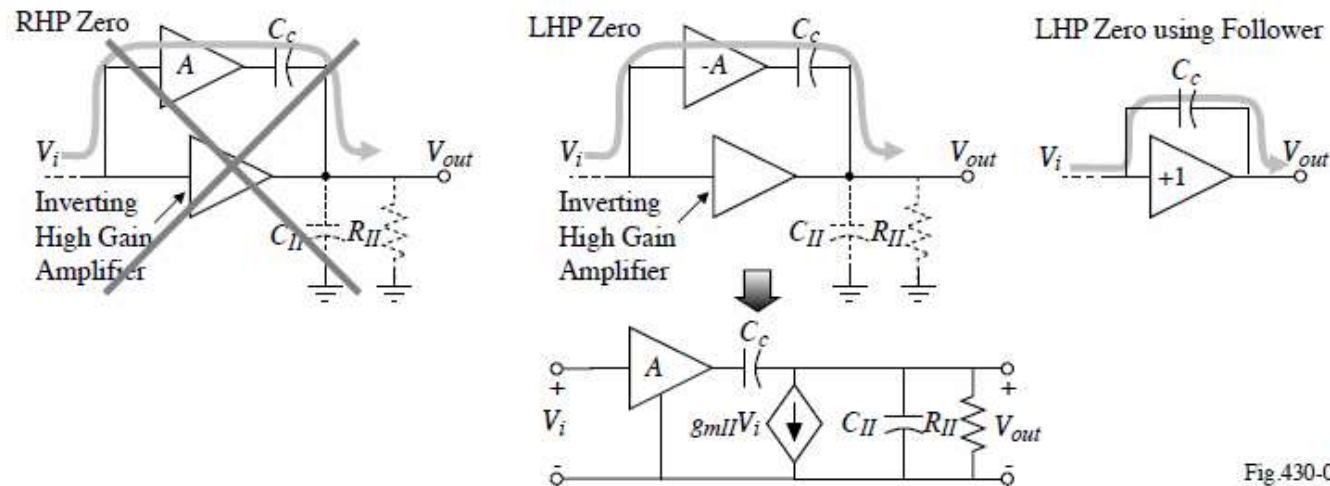



Fig.430-09

$$\frac{V_{out}(s)}{V_i(s)} = \frac{AC_c}{C_c + C_{II}} \frac{s + \frac{g_{mII}}{AC_c}}{s + \frac{1}{R_{II}C_c + C_{II}}}$$

- To use the LHP zero for compensation, a compromise must be observed
  - ✓ Placing the zero below GB will lead to boosting of the loop gain that could deteriorate the phase margin
  - ✓ Placing the zero above GB will have less influence on the leading phase caused by the zero
- Note that a source follower is a good candidate for the use of feedforward compensation
  - ✓ This type of compensation is often used in source followers. The capacitor will provide a path that bypasses the transistor at high frequencies

## ◆ POWER SUPPLY REJECTION RATIO OF THE TWO-STAGE OP AMP


What is *PSRR*?

 

$$PSRR^+ = \frac{A_v(v_{dd} = 0)}{A_{dd}(v_{in} = 0)}$$

$$PSRR^- = \frac{A_v(v_{ss} = 0)}{A_{ss}(v_{in} = 0)}$$

Method for calculating PSRR:

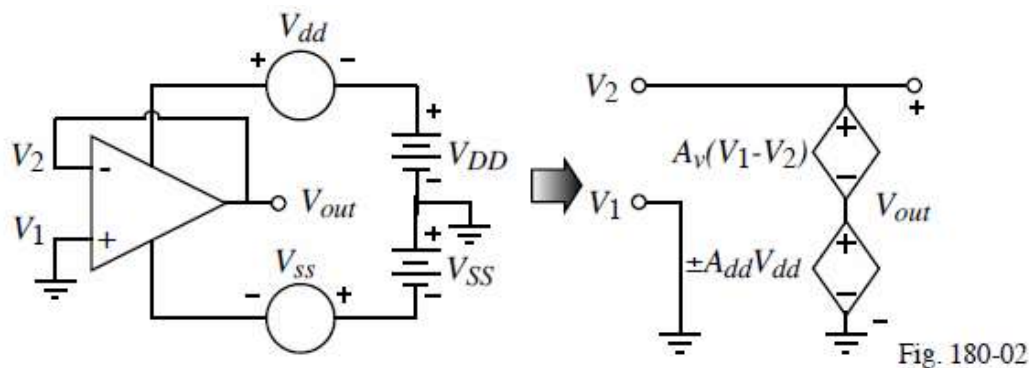

$$V_{out} = A_{dd}V_{dd} - A_vV_2 = A_{dd}V_{dd} - A_vV_{out}$$

$$V_{out} = \frac{A_{dd}}{1 + A_v}V_{dd} \approx \frac{A_{dd}}{A_v}V_{dd} = \frac{1}{PSRR^+}V_{dd}$$


$$\Rightarrow PSRR^+ = \frac{V_{dd}}{V_{out}} \quad \Rightarrow PSRR^- = \frac{V_{ss}}{V_{out}}$$

✓ If we connect the op amp in the unity-gain mode and input an AC signal of  $V_{dd}$  ( $V_{ss}$ ) in series with  $V_{DD}$  ( $V_{SS}$ ),  $PSRR$  will be equal

$$PSRR^+ = \frac{V_{dd}}{V_{out}} \quad PSRR^- = \frac{V_{ss}}{V_{out}}$$



## ❖ Negative PSRR

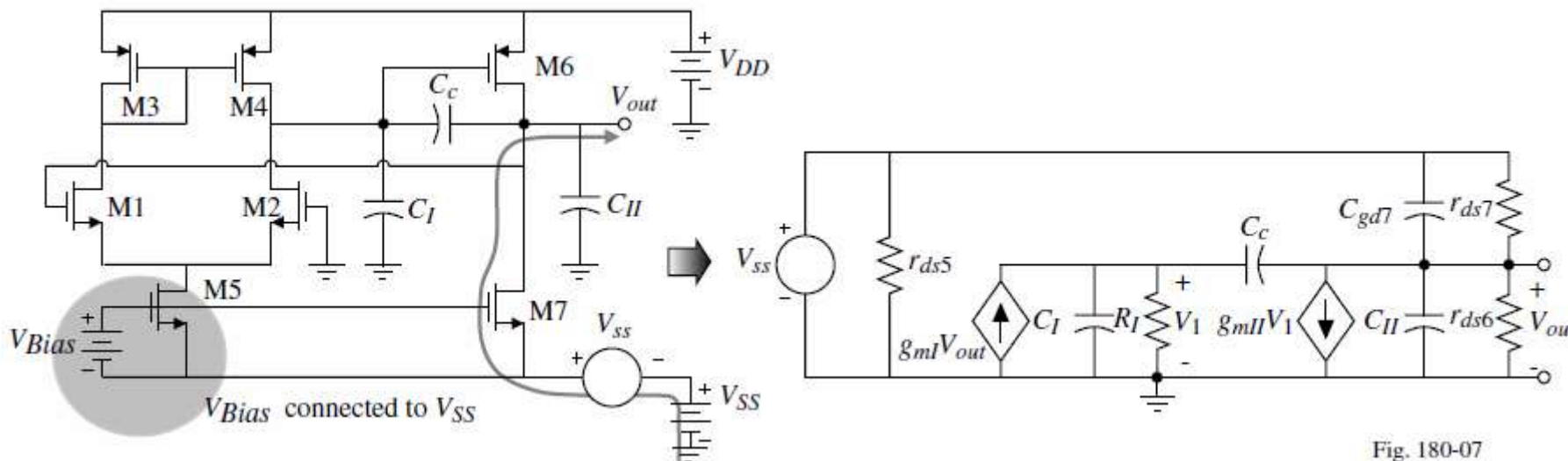

$$(G_I + sC_c + sC_I)V_1 - (g_{mI} + sC_c)V_{out} = 0$$

$$(g_{mII} - sC_c)V_1 + (G_{II} + sC_c + sC_{II} + sC_{gd7})V_{out} = (g_{ds7} + sC_{gd7})V_{ss}$$

Solving for  $V_{out}/V_{ss}$  and inverting:

$$\frac{V_{ss}}{V_{out}} = \frac{as^2 + bs + c}{g_{m7} [G_I + s(C_c + C_I)]}$$

$$a = C_c C_I + C_I C_{II} + C_{II} C_c + C_I C_{gd7} + C_c C_{gd7}$$

$$b = G_I (C_c + C_{II} + C_{gd7}) + G_{II} (C_c + C_I) + C_c (g_{mII} - g_{mI})$$

$$c = G_I G_{II} + g_{mII} g_{mI}$$


Solve for approximate roots:

$$PSRR^- = \frac{V_{ss}}{V_{out}} = \frac{g_{mII} g_{mI}}{G_I g_{ds7}} \frac{\left(1 + s \frac{C_c}{g_{mI}}\right) \left(1 + s \frac{(C_c C_I + C_c C_{II} + C_c C_{II})}{g_{mII} C_c}\right)}{\left(1 + s \frac{C_c + C_I}{G_I}\right) \left(1 + s \frac{C_{gd7}}{g_{ds7}}\right)}$$

$$PSRR^- = \frac{V_{ss}}{V_{out}} \approx \frac{g_{mII} g_{mI}}{G_I g_{ds7}} \frac{\left(1 + s \frac{C_c}{g_{mI}}\right) \left(1 + s \frac{C_{II}}{g_{mII}}\right)}{\left(1 + s \frac{C_{gd7}}{g_{ds7}}\right) \left(1 + s \frac{C_c}{G_I}\right)} = \frac{G_{II} A_v(0)}{g_{ds7}} \frac{\left(1 + \frac{s}{GB}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}{\left(1 + s \frac{C_{gd7}}{g_{ds7}}\right) \left(1 + \frac{s}{GB} \frac{g_{mI}}{G_I}\right)}$$

Comments:

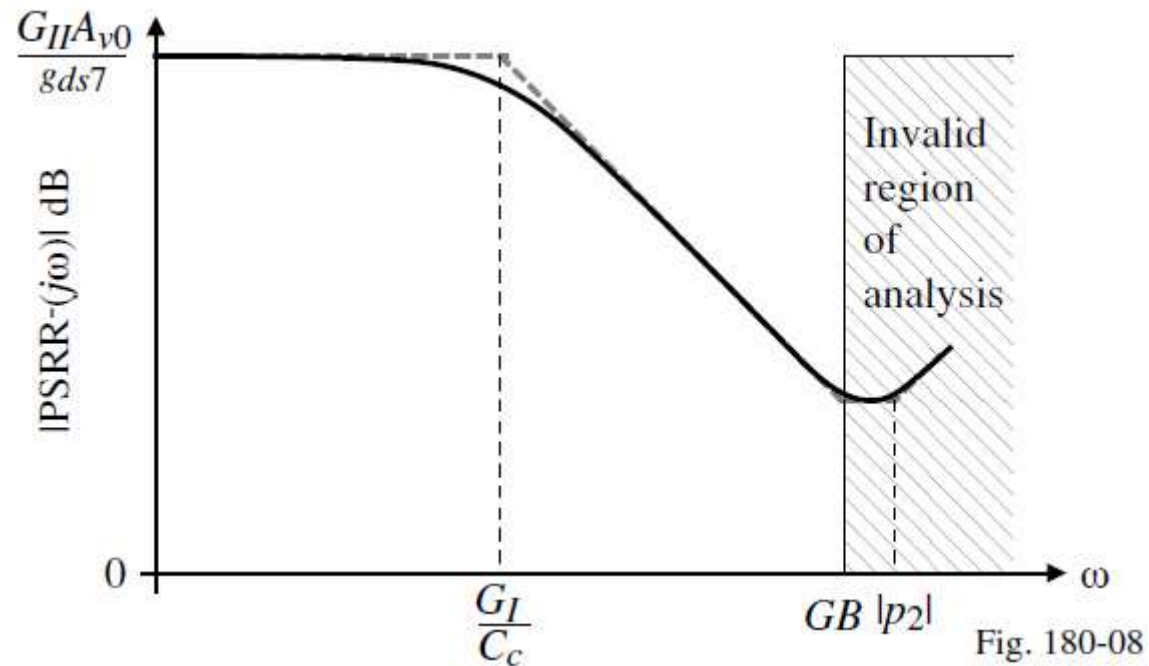- DC gain has been increased by the ratio of  $G_{II}$  to  $g_{ds7}$
- Two poles instead of one, however the pole at  $-g_{ds7}/C_{gd7}$  is large and can be ignored.



❖ Positive PSRR

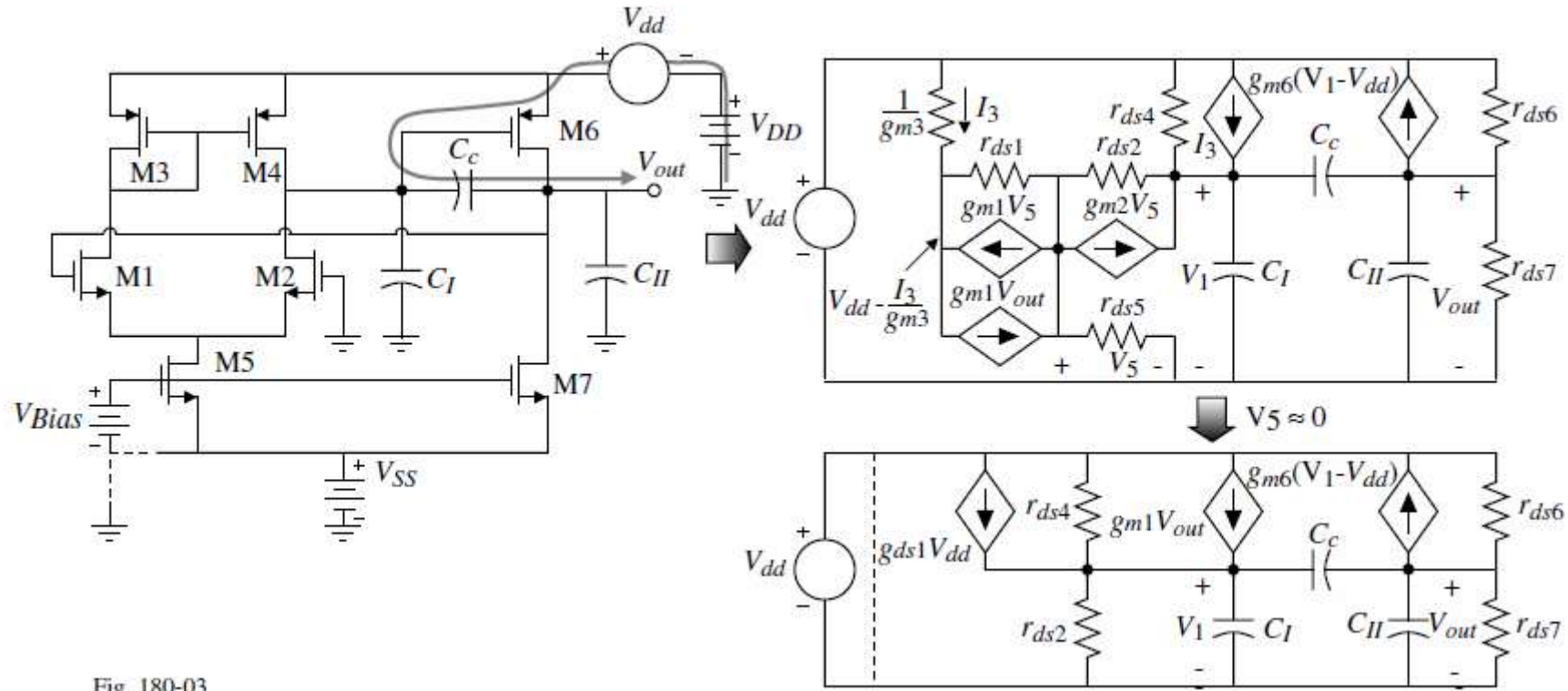


Fig. 180-03

$$(G_I + sC_c + sC_I)V_1 - (g_{mI} + sC_c)V_{out} = G_IV_{dd}$$

$$(g_{mII} - sC_c)V_1 + (G_{II} + sC_c + sC_{II})V_{out} = (g_{mII} + g_{ds6})V_{dd}$$

$$G_I = g_{ds1} + g_{ds4} = g_{ds2} + g_{ds4}, G_{II} = g_{ds6} + g_{ds7}, g_{mI} = g_{m1} = g_{m2}, g_{mII} = g_{m6}$$

Using Cramers rule to solve for the transfer function  $V_{out}/V_{dd}$ , and inverting the transfer function gives the following result

$$\frac{V_{ss}}{V_{out}} = \frac{as^2 + bs + c}{G_I g_{ds6} + s \left[ C_c (g_{mII} + G_I + g_{ds6}) + C_I (g_{mII} + g_{ds6}) \right]}$$

$$\begin{aligned}
 a &= C_c C_I + C_I C_{II} + C_{II} C_c \\
 b &= G_I (C_c + C_{II}) + G_{II} (C_c + C_I) + C_c (g_{mII} - g_{mI}) \\
 c &= G_I G_{II} + g_{mII} g_{mI}
 \end{aligned}$$


✓ We may solve for the approximate roots of numerator as

$$PSRR^+ = \frac{V_{dd}}{V_{out}} = \frac{g_{mII} g_{mI}}{G_I g_{ds6}} \frac{\left(1 + s \frac{C_c}{g_{mI}}\right) \left(1 + s \frac{(C_c C_I + C_c C_{II} + C_c C_{II})}{g_{mII} C_c}\right)}{\left[1 + s \frac{g_{mII} C_c}{G_I g_{ds6}}\right]}$$

Where  $g_{mII} > g_{mI}$  and that all transconductances are larger than the channel conductances:

$$PSRR^+ = \frac{V_{dd}}{V_{out}} = \frac{g_{mII} g_{mI}}{G_I g_{ds6}} \frac{\left(1 + s \frac{C_c}{g_{mI}}\right) \left(1 + s \frac{C_{II}}{g_{mII}}\right)}{\left[1 + s \frac{g_{mII} C_c}{G_I g_{ds6}}\right]} = \frac{G_{II} A_v(0)}{g_{ds6}} \frac{\left(1 + \frac{s}{GB}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}{\left[1 + \frac{s}{GB} \frac{G_{II} A_v(0)}{g_{ds6}}\right]}$$

 ✓ At approximately the dominant pole, the PSRR falls off with a -20dB/decade slope and degrades the higher frequency PSRR + of the two-stage op amp.



### Approximate Model for $PSRR+$

The M7 current sink causes VSG6 to act like a battery

2) Therefore, Vdd couples from the source to gate of M6

3) The path to the output is through any capacitance from gate to drain of M6

✓ Conclusion: The Miller capacitor  $C_c$  couples the positive power supply ripple directly to the output.

✓ **Must reduce or eliminate  $C_c$ !**

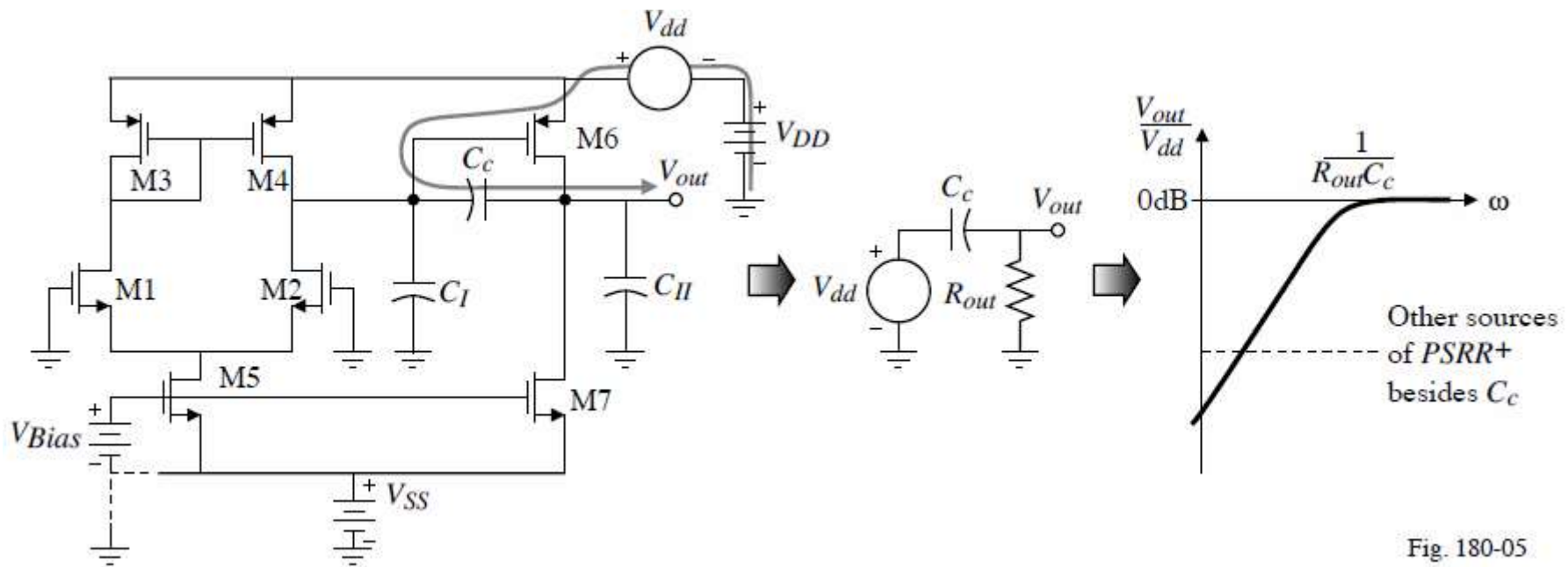


Fig. 180-05

Approximate Model for **Negative PSRR with VBias Connected to Ground**


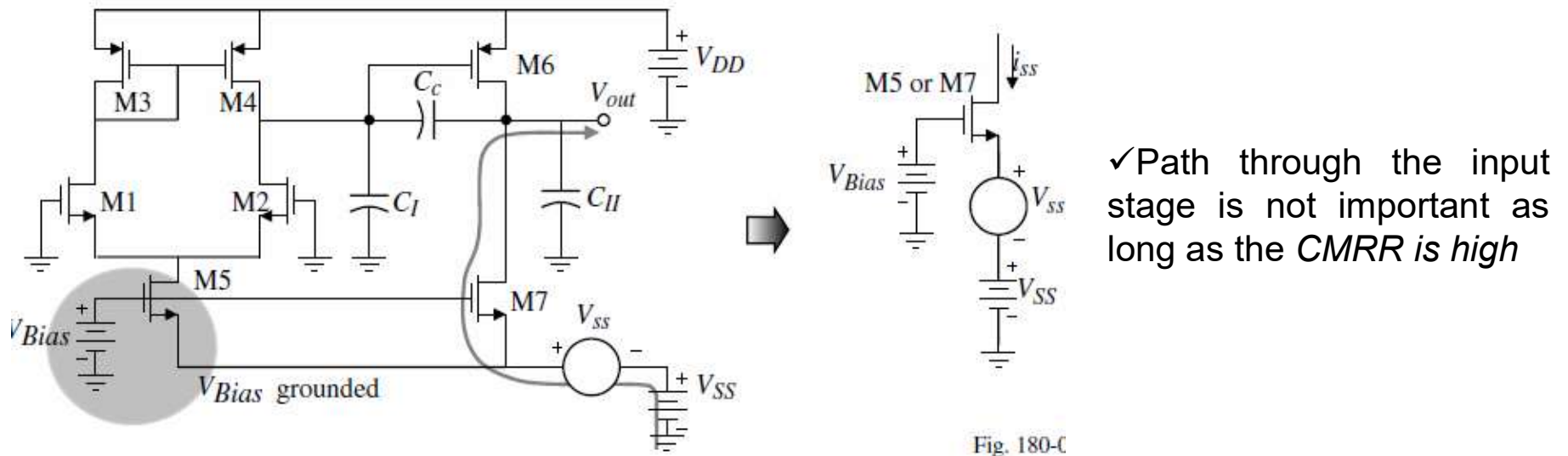


Fig. 180-C

 


Path through the output stage:

$$V_{out} \approx I_{ss} Z_{out} = g_{m7} V_{ss} Z_{out}$$

$$Z_{out} = R_{out} \parallel \frac{1}{sC_{out}} = \frac{R_{out}}{1 + sC_{out}R_{out}}$$

 
$$\frac{V_{out}}{V_{ss}} \approx \frac{g_{m7}R_{out}}{1 + sC_{out}R_{out}}$$



- ✓The two-stage op amp will never have good PSRR because of the Miller compensation
- ✓The two-stage op amp is a very general and flexible op amp
- ✓**Cascoding!**
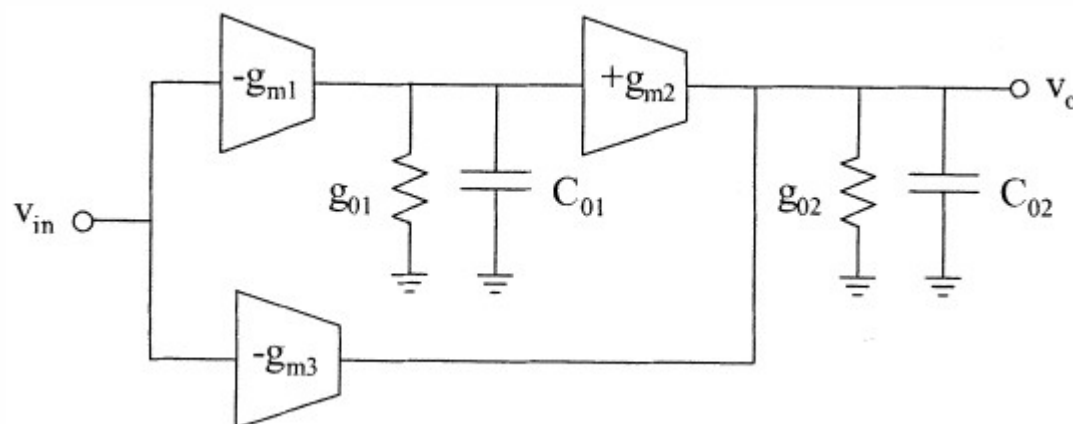
## ➤ Feedforward compensation without Miller Capacitor

- The compensation scheme used in this paper employs a feedforward path to create LHP zeros, but does not use any Miller capacitor.
- The dominant pole is not pushed to lower frequencies, resulting in a higher gain-bandwidth product with a fast step response.



$$A_{vi} = \frac{g_{mi}}{g_{0i}}, i = 1, 2, 3$$

$$\omega_{pj} = \frac{g_{0j}}{C_{0j}}, j = 1, 2$$

$$H(s) = -\frac{A_{v1}A_{v2} + A_{v3} \left(1 + \frac{s}{\omega_{p1}}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} = -(A_{v1}A_{v2} + A_{v3}) \frac{1 + \frac{A_{v3}s}{(A_{v1}A_{v2} + A_{v3})\omega_{p1}}}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$


✓The OTA transfer function has two poles and a LHP zero created by the feedforward path. The location of the LHP zero is

$$z_1 = -\left(1 + \frac{A_{v1}A_{v2}}{A_{v3}}\right)\omega_{p1} \approx -\frac{g_{m1} g_{m2}}{C_{01} g_{m3}}$$



✓The second and feedforward stages can be designed such that the negative phase shift due to  $\omega_{p2}$  is compensated by the positive phase shift of the LHP zero  
 When the frequency of  $\omega_{p2}$  exactly coincides with that of the LHP zero, the amplifier phase margin is 90 and the unity-gain frequency is given by
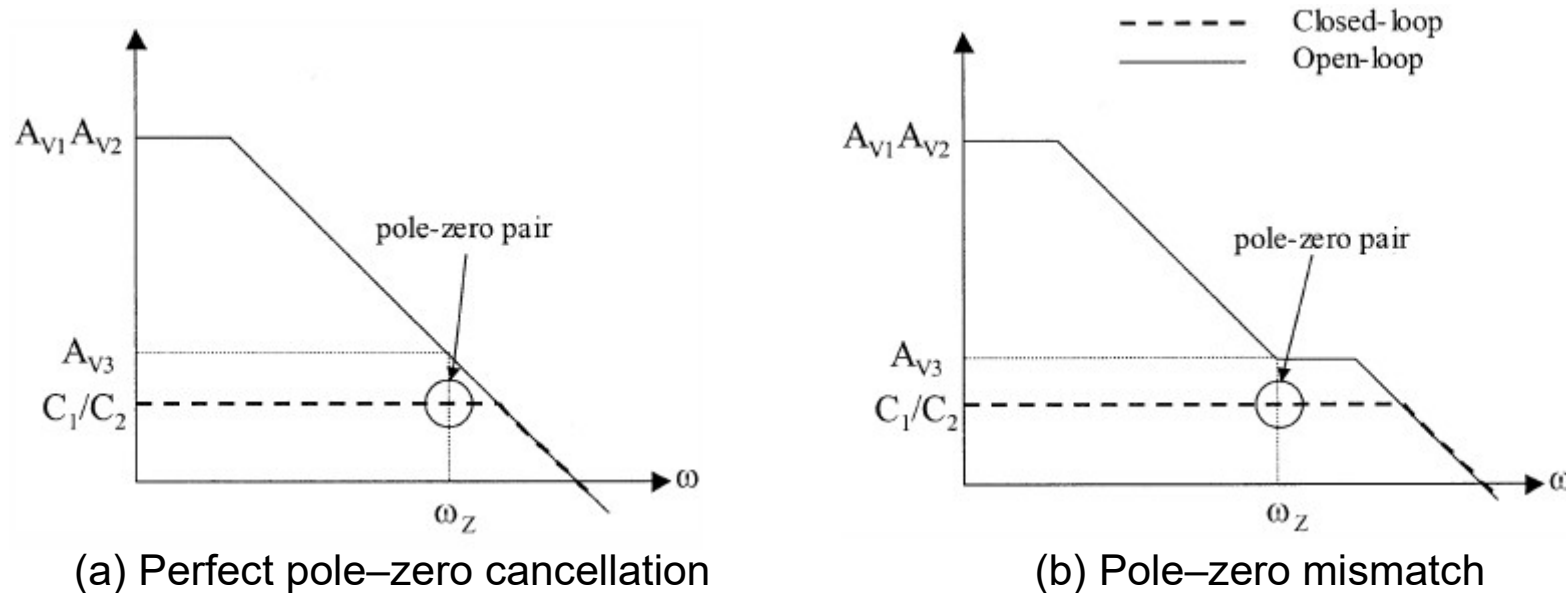
$$GB \approx (A_{v1}A_{v2} + A_{v3}) \approx A_{v1}A_{v2}\omega_{p1}$$



✓This compensation scheme results in an amplifier with high gain and fast response  
 ✓The bandwidth improvement is due to the fact that the poles are not split, as is the case in any amplifier with Miller compensation

## Two-Stage CMOS Unbuffered Op Amp-Design

### Relationships for the Two-Stage Op Amp:

- Slew rate  $SR = I_5 / C_c$  (Assuming  $I_7 \gg I_5$  and  $C_L > C_c$ )
- First-stage gain

$$A_{v1} = -\frac{g_{m1}}{g_{ds2} + g_{ds4}} = -\frac{2g_{m1}}{I_5(\lambda_2 + \lambda_4)}$$

- Second-stage gain

$$A_{v2} = -\frac{g_{m6}}{g_{ds6} + g_{ds7}} = -\frac{2g_{m6}}{I_5(\lambda_6 + \lambda_7)}$$

Gain bandwidth

$$GB = g_{m1} / C_c$$

- Output pole

$$p_2 = -g_{m6} / C_L$$

- RHP zero

$$z_1 = g_{m6} / C_c$$

- Positive ICM

$$V_{in\max} = V_{DD} - |V_{T03}|_{\max} + V_{T1\min} - \sqrt{I_5 / \beta_3}, \beta_3 = \mu_p C_{ox} (W / L)_3$$

- Negative ICM

$$V_{in\min} = V_{SS} + V_{DS5sat} + V_{T1\max} + \sqrt{I_5 / \beta_1}, \beta_1 = \mu_n C_{ox} (W / L)_1$$

- 60° phase margin requires that

$$C_c > 0.22C_L$$

 


Fig. 160-01

## DC Balance Conditions for the Two-Stage Op Amp

- For best performance, keep all transistors in saturation.
- M4 is the only transistor that cannot be forced into saturation by internal connections or external voltages. Therefore, we develop conditions to force M4 to be in saturation.

1. First *assume that  $V_{SG4} = V_{SG6}$* . This will cause “proper mirroring” in the M3-M4 mirror. Also, the gate and drain of M4 are at the same potential so that M4 is “guaranteed” to be in saturation.
2. *If  $V_{SG4} = V_{SG6}$ , then*

$$I_6 = (S_6 / S_4) I_4$$


3. *However,*

$$I_7 = (S_7 / S_5) I_5$$

4. For balance, *I6 must equal I7*

$$(S_6 / S_4) = 2(S_7 / S_5) \quad \text{“balance conditions”}$$

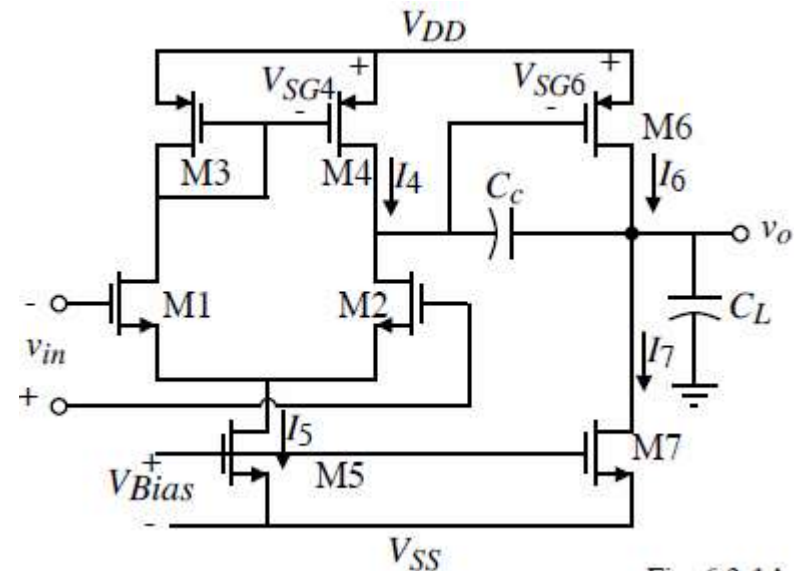5. So if the balance conditions are satisfied, then  *$V_{DG4} = 0$  and M4 is saturated*



## Op Amp Specifications:

The following design procedure assumes that specifications for the following parameters are given

1. Gain at dc,  $A_v(0)$
2. Gain-bandwidth,  $GB$
3. Phase margin (or settling time)
4. Input common-mode range, ICMR
5. Load Capacitance,  $CL$
6. Slew-rate,  $SR$
7. Output voltage swing
8. Power dissipation,  $P_{diss}$

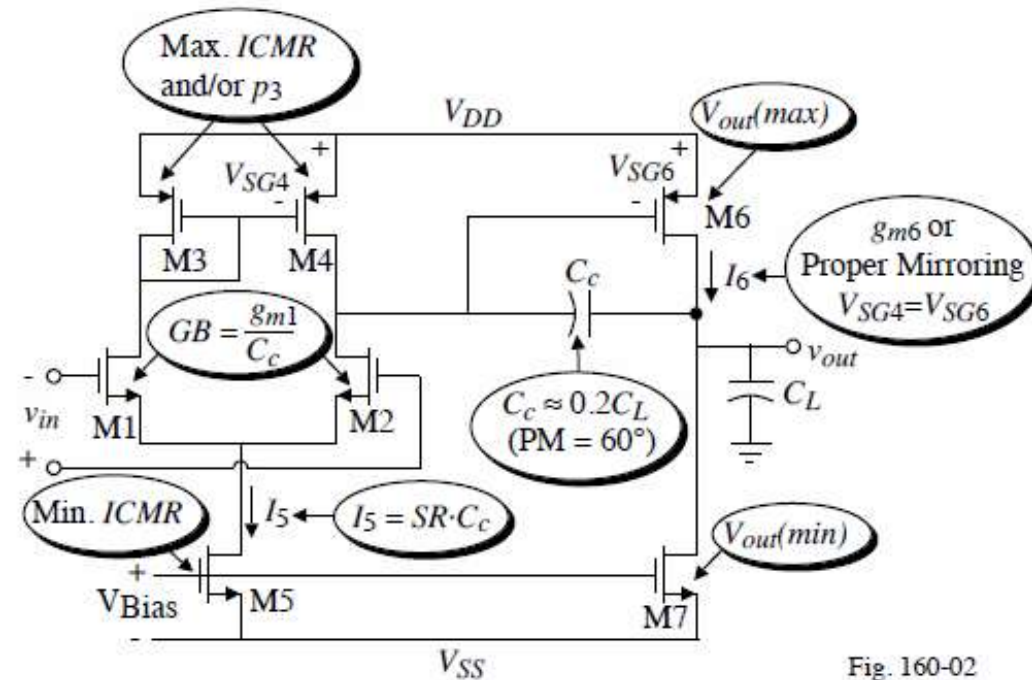


Fig. 160-02

## Unbuffered Op Amp Design Procedure:

1. From the desired phase margin, choose the minimum value for  $C_c$ , i.e. for a  $60^\circ$  phase margin we use the following relationship. This assumes that  $z \geq 10GB$ .

$$C_c > 0.22C_L$$

2. Determine the minimum value for the "tail current" ( $I_5$ )

$$I_5 = SR \cdot C_c$$

3. Design for S3 from the maximum input CM voltage specification.

$$S_3 = (W/L)_3 = \frac{I_5}{k_{pp} \left( V_{DD} - V_{in\max} - |V_{T03}|_{\max} + V_{T1\min} \right)^2}, k_{pp} = \mu_p C_{ox}$$

4. Verify that the pole of  $M_3$  due to  $C_{gs3}$  and  $C_{gs4}$  ( $= 0.67W_3L_3C_{ox}$ ) will not be dominant by assuming it to be greater than 10 GB

$$\frac{g_{m3}}{2C_{gs3}} > 10GB$$

5. Design for  $S_1$  ( $S_2$ ) to achieve the desired GB

$$g_{m1} = GB \cdot C_c \Rightarrow S_{1,2} = \frac{g_{m1}^2}{k_{pn}I_5}, k_{pn} = \mu_n C_{ox}$$

6. Design for  $S_5$  from the minimum input voltage. First calculate  $V_{DS5(sat)}$  then find  $S_5$ .

$$V_{DS5sat} = V_{inmin} - V_{SS} - V_{T1max} - \sqrt{I_5 / \beta_1} \geq 100 \text{ mV} \Rightarrow S_5 = \frac{2I_5}{k_{pn}V_{DS5sat}^2}$$

7. Find  $S_6$  by letting the second pole ( $p_2$ ) be equal to 2.2 times GB and assuming that  $V_{SG4} = V_{SG6}$

$$g_{m6} = 2.2g_{m2} \frac{C_L}{C_c}, \frac{g_{m6}}{g_{m4}} = \frac{\sqrt{S_6 I_6}}{\sqrt{S_4 I_4}} = \frac{S_6}{S_4} \Rightarrow S_6 = S_4 \frac{g_{m6}}{g_{m4}}$$

8. Calculate  $I_6$  from

$$I_6 = \frac{g_{m6}^2}{2k_{pp}S_6}$$

Check to make sure that  $S_6$  satisfies the  $V_{out(max)}$  requirement and adjust as necessary.

9. Design  $S_7$  to achieve the desired current ratios between  $I_5$  and  $I_6$ .

$$S_7 = (I_7 / I_5) S_5$$

Check the minimum output voltage requirements.

10. Check gain and power dissipation specifications

$$A_v = \frac{2g_{m2}g_{m6}}{I_5(\lambda_2 + \lambda_4)I_6(\lambda_6 + \lambda_7)} \quad P_{diss} = (V_{DD} + |V_{SS}|)(I_5 + I_6)$$

11. If the gain specification is not met, then the currents,  $I_5$  and  $I_6$ , can be decreased or the W/L ratios of M2 and/or M6 increased. The previous calculations must be rechecked to insure that they are satisfied.

If the power dissipation is too high, then one can only reduce the currents  $I_5$  and  $I_6$ . Reduction of currents will probably necessitate increase of some of the W/L ratios in order to satisfy input and output swings.

12. Simulate the circuit to check to see that all specifications are met.

### ❖ DESIGN EXAMPLE OF A TWO-STAGE OP AMP

If  $K_n = 120 \mu A/V^2$ ,  $K_p = 25 \mu A/V^2$ ,  $V_{TN} = |V_{TP}| = 0.5V$ ,  $\lambda_n = 0.06 V^{-1}$ , and  $\lambda_p = 0.08 V^{-1}$ , design a two-stage, CMOS op amp that meets the following specifications:  $A_v > 3000$ ,  $V_{DD} = 2.5V$ ,  $GB = 5MHz$ ,  $SR > 10V/\mu s$ ,  $60^\circ$  phase margin  $0.5V < V_{out\ range} < 2V$ ,  $I_{CMR} = 1.25V$  to  $2V$ ,  $P_{diss} \leq 2mW$ . Assume the channel length is to be  $0.5\mu m$  and the load capacitor is  $C_L = 10pF$ .

1) The first step is to calculate the minimum value of the compensation capacitor  $C_c$ ,

$$C_c > 0.22C_L = 2.2pF$$

2) Choose  $C_c$  as  $3pF$ . Using the slew-rate specification and  $C_c$  calculate  $I_5$ .

$$I_5 = SR \cdot C_c = 22 \mu A \Rightarrow I_5 = 30 \mu A$$

3) Next calculate  $(W/L)_3$  using *ICMR requirements (use worst case thresholds  $\pm 0.15V$ )*.

$$S_3 = (W/L)_3 = \frac{I_5}{k_{pp} (V_{DD} - V_{in\max} - |V_{T03}|_{\max} + V_{T1\min})^2} = 30$$

$$(W/L)_3 = (W/L)_4$$

4) Now we can check the value of the mirror pole,  $p_3$ , to make sure that it is in fact greater than 10GB. Assume the  $C_{ox} = 6fF/\mu m^2$ . The mirror pole can be found as

$$|p_3| = \frac{g_{m3}}{2\pi \cdot 2C_{gs3}} = \frac{1.25 \cdot 10^9}{2\pi} \text{ grad/s} = 199\text{MHz} > 10\text{GB} = 50\text{MHz}$$

5) The next step in the design is to calculate  $gm_1$  to get

$$g_{m1} = GB \cdot C_c = 94.25 \mu\text{S} \Rightarrow S_{1,2} = \frac{g_{m1}^2}{k_{pn} I_5} = 2.47 \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 3$$

6) Next calculate  $V_{DS5}$ ,

$$V_{DS5sat} = V_{in\min} - V_{SS} - V_{T1\max} - \sqrt{I_5 / \beta_1} = 0.31\text{V} > 100 \text{ mV} \Rightarrow S_5 = \frac{2I_5}{k_{pn} V_{DS5sat}^2} = 5.16 \Rightarrow \left(\frac{W}{L}\right)_5 = 6$$

7) For 60° phase margin, we know that

$$g_{m6} \geq 10g_{m1} = 942.5 \mu\text{S}$$

Assuming that  $gm_6 = 942.5\mu\text{S}$  and knowing that  $gm_4 = 150\mu\text{S}$ , we calculate  $(W/L)_6$  as

$$S_6 = S_4 \frac{g_{m6}}{g_{m4}} = 188.5 \Rightarrow \left( \frac{W}{L} \right)_6 = 190$$

8) Calculate  $I_6$  using the small-signal  $g_m$  expression:

$$I_6 = \frac{g_{m6}^2}{2k_{pp}S_6} = 94.2 \mu\text{A} \approx 95 \mu\text{A}$$

Calculating  $(W/L)_6$  based on  $V_{out(max)}$ , gives a value of 15. Since 190 exceeds the specification and gives better phase margin, we choose  $(W/L)_6 = 190$  and  $I_6 = 95 \mu\text{A}$ .

With  $I_6 = 95 \mu\text{A}$  the power dissipation is

$$P_{diss} = (V_{DD} + |V_{SS}|)(I_5 + I_6) = 2.5(30 + 95) \mu\text{W} = 312.5 \mu\text{W}$$

9) Finally, calculate  $(W/L)_7$

$$S_7 = (I_7 / I_5)S_5 = 19 \Rightarrow (W / L)_7 = 20$$

Let us check the  $V_{out(min)}$  specification although the  $W/L$  of  $M_7$  is so large that this is probably not necessary. The value of  $V_{out(min)}$  is

$$v_{OUT \min} = V_{DSsat7} = \sqrt{\frac{2I_{D7}}{\mu_n C_{ox} W / L}} = 281 \text{ mV}$$

which is less than required.

**At this point, the first-cut design is complete.**



10) Now check to see that the gain specification has been met

$$A_{v0} = \frac{2g_{m1}}{I_5(\lambda_2 + \lambda_4)} \frac{2g_{m6}}{I_6(\lambda_6 + \lambda_7)} = 3180$$



which barely exceeds the specifications. Since we are at  $2xL_{min}$ , it won't do any good to increase the channel lengths. Decreasing the currents or increasing  $W6/L6$  will help.

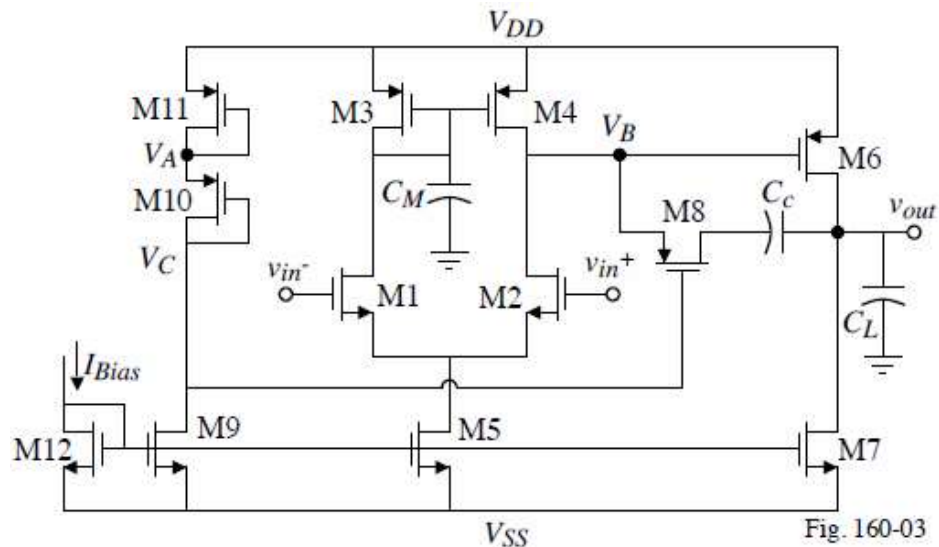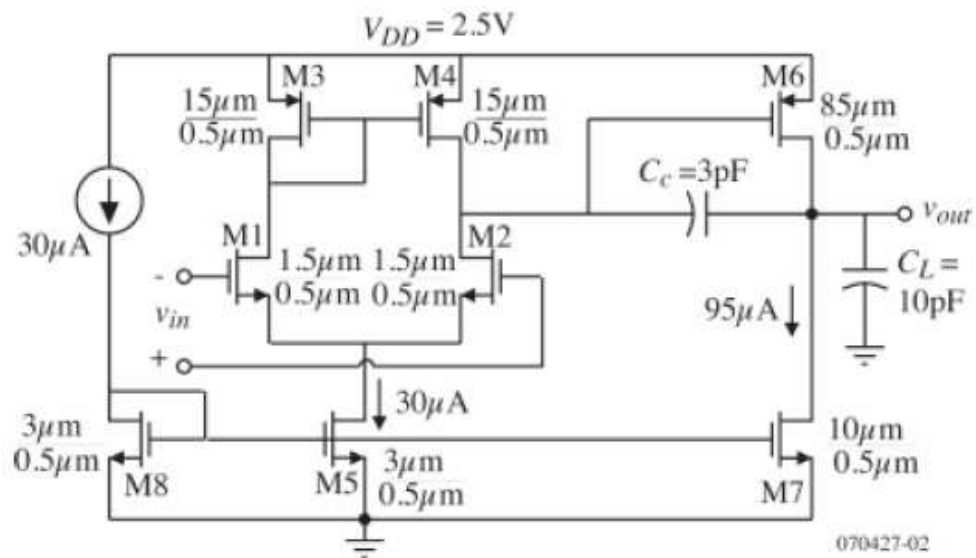•The figure below shows the results of the first-cut design. The W/L ratios shown do not account for the lateral diffusion discussed above. The next phase requires simulation.



### ➤ Incorporating the Nulling Resistor into the Miller Compensated Two-Stage Op Amp

•Design compensation circuitry so that the RHP zero is moved from the RHP to the LHP and placed on top of the output pole  $p_2$

•The task at hand is the design of transistors M8, M9, M10, M11, and bias current  $I_{10}$ . The first step in this design is to establish the bias components. In order to set  $V_A$  equal to  $V_B$ , then  $V_{SG11}$  must equal  $V_{SG6}$

$$S_{11} = (I_{11} / I_6) S_6$$

•Choose  $I_{11} = I_{10} = I_9 = 15\mu A$  which gives

$$S_{11} = (I_{11} / I_6) S_6 = (15 / 95) 190 = 30$$

- The aspect ratio of M10 is essentially a free parameter, and will be set equal to 1. There must be sufficient supply voltage to support the sum of  $V_{SG11}$ ,  $V_{SG10}$ , and  $V_{DS9}$ .

- The ratio of  $I_{10}/I_5$  determines the  $(W/L)$  of M9. This ratio is

$$(W/L)_9 = (I_{10}/I_5)(W/L)_5 = (15/30)6 = 3$$

- Now  $(W/L)_8$  is determined to be

$$R_z = \frac{C_c + C_L}{C_c} \frac{1}{\sqrt{2I_{D6}\mu_p C_{ox} (W/L)_6}} = \frac{1}{(W/L)_8} \sqrt{\frac{(W/L)_{10}}{2\mu_p C_{ox} I_{D10}}}$$


$$\Rightarrow (W/L)_8 = \frac{C_c}{C_c + C_L} \sqrt{(W/L)_{10} (W/L)_6 \frac{I_{D6}}{I_{D10}}} = \frac{3}{3+10} \sqrt{\frac{1 \cdot 190 \cdot 95}{15}} = 8$$

- It is worthwhile to check that the RHP zero has been moved on top of  $p_2$ . To do this, first calculate the value of  $R_z$ .  $V_{SG8}$  must first be determined. It is equal to  $V_{SG10}$ , which is

$$V_{SG10} = \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} S_{10}}} + |V_{TP}| = \sqrt{\frac{2 \cdot 15}{25 \cdot 1}} + 0.5 = 1.6 \text{ V}$$

- Next determine  $R_z$

$$R_z \approx \frac{1}{\mu_p C_{ox} S_8 (V_{SG10} - |V_{TP}|)} = 4.56 \text{ k}\Omega$$

 

- The location of  $z_1$  is calculated as

$$z_1 = \frac{1}{C_c \left( \frac{1}{g_{m6}} - R_z \right)} = -94.91 \text{ Mrad/s}$$

- The output pole,  $p_2$ , is

$$p_2 \approx -\frac{g_{m6}}{C_L} = -95 \text{ Mrad/s}$$


✓Thus, we see that for all practical purposes, the output pole is canceled by the zero that has been moved from the RHP to the LHP.

✓The results of this design are summarized below where  $L = 0.5\mu\text{m}$ ,  $W_8 = 4\mu\text{m}$ ,  $W_9 = 1.5\mu\text{m}$ ,  $W_{10} = 0.5\mu\text{m}$  and  $W_{11} = 15\mu\text{m}$

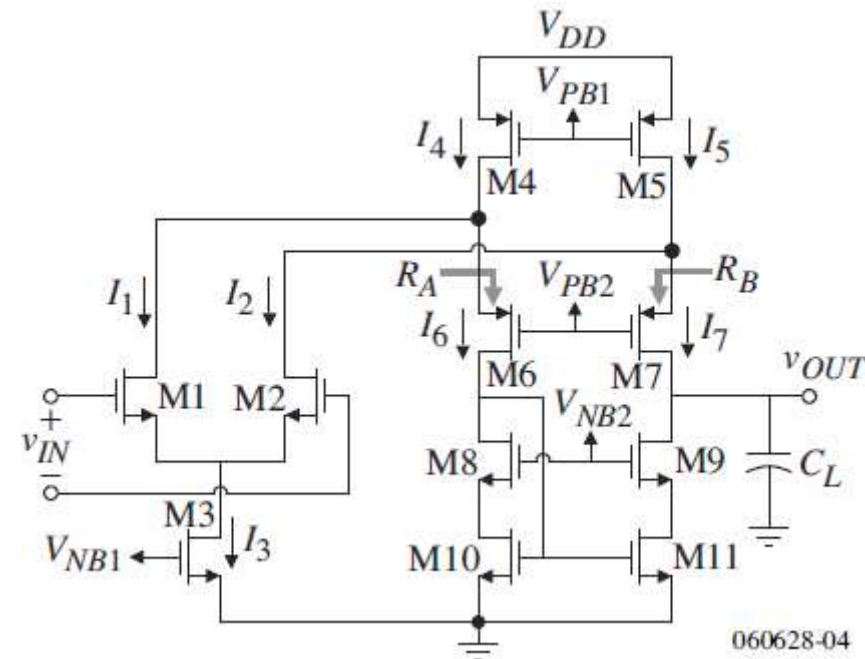
## ➤ The Folded Cascode Op Amp

Comments:

- $I_4$  and  $I_5$ , should be designed so that  $I_6$  and  $I_7$  never become zero (i.e.  $I_4=I_5=1.5I_3$ )
- This amplifier is nearly balanced (would be exactly if  $R_A$  was equal to  $R_B$ )
- Self compensating
- Poor noise performance, the gain occurs at the output so all intermediate transistors contribute to the noise along with the input transistors. (Some first stage gain can be achieved if  $R_A$  and  $R_B$  are greater than  $g_{m1}$  or  $g_{m2}$ ·


 
### ❖ Small-Signal Analysis of the Folded Cascode Op Amp



$$R_A = \frac{r_{ds6} + (1/g_{m10})}{1 + g_{m6}r_{ds6}} \approx \frac{1}{g_{m6}} \quad R_B = \frac{r_{ds7} + R_{II}}{1 + g_{m7}r_{ds7}} \approx \frac{R_{II}}{g_{m7}r_{ds7}} = \frac{g_{m9}r_{ds9}r_{ds11}}{g_{m7}r_{ds7}} \approx r_{ds}$$

$$i_{10} = -\frac{g_{m1}V_{in}}{2} \frac{r_{ds1} \parallel r_{ds4}}{R_A + r_{ds1} \parallel r_{ds4}} \approx -\frac{g_{m1}V_{in}}{2}$$

$$i_7 = \frac{g_{m2}V_{in}}{2} \frac{r_{ds2} \parallel r_{ds5}}{R_B + r_{ds2} \parallel r_{ds5}} \approx \frac{g_{m2}V_{in}}{2} \frac{r_{ds2} \parallel r_{ds5}}{\frac{R_{II}}{g_{m7}r_{ds7}} + r_{ds2} \parallel r_{ds5}} = \frac{g_{m2}V_{in}}{2} \frac{1}{\frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}} + 1}$$

$$\Rightarrow i_7 = \frac{g_{m2}V_{in}}{2} \frac{1}{k+1}, k = \frac{R_{II}(g_{ds2} + g_{ds5})}{g_{m7}r_{ds7}}$$

$$\frac{V_{out}}{V_{in}} = (i_7 + i_{10})R_{out} = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \frac{1}{k+1} \right) = \frac{1}{2} \frac{k+2}{k+1} g_{m1} R_{out}$$

$$R_{II} \approx g_{m9}r_{ds9}r_{ds11} \quad R_{out} \approx g_{m9}r_{ds9}r_{ds11} \parallel g_{m7}r_{ds7}(r_{ds5} \parallel r_{ds2})$$


### ❖ Intuitive Analysis of the Folded Cascode Op Amp

$$R_A \approx \frac{1}{g_{m6}} \quad R_B \approx r_{ds}$$

$$i_{10} \approx -\frac{g_{m1}V_{in}}{2} \quad i_7 \approx \frac{1}{2} \frac{g_{m2}V_{in}}{2} = \frac{g_{m2}V_{in}}{4}$$

$$\frac{V_{out}}{V_{in}} = (i_7 + i_{10})R_{out} = \left( \frac{g_{m1}V_{in}}{2} + \frac{g_{m2}V_{in}}{4} \right) R_{out}$$
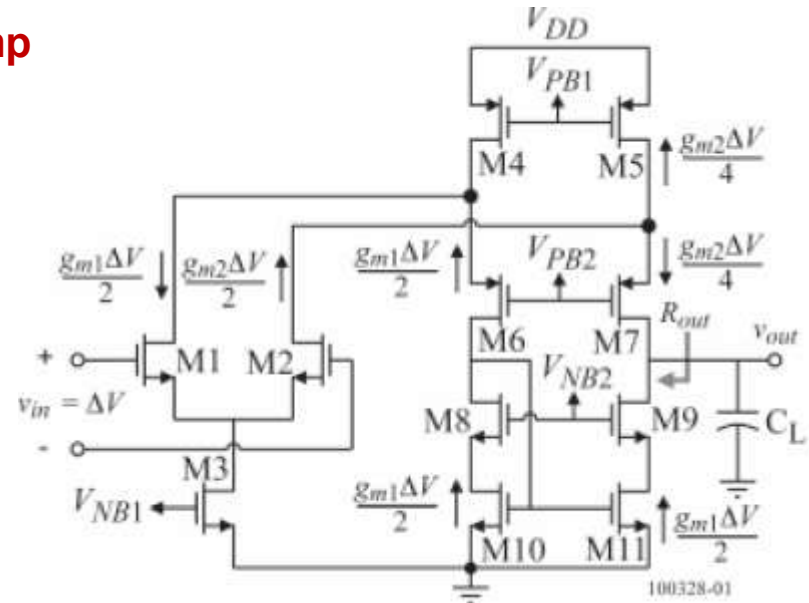
$$R_{out} \approx g_{m9}r_{ds9}^2 \parallel g_{m7}r_{ds7}^2 / 2 \approx g_{m7}r_{ds7}^2 / 3$$



## ❖ Frequency Response of the Folded Cascode Op Amp

• The frequency response of the folded cascode op amp is determined primarily by the output pole which is given as

$$p_{out} = -\frac{1}{R_{out}C_{out}}$$

where  $C_{out}$  is all the capacitance connected from the output of the op amp to ground.

• All other poles must be greater than  $GB = g_{m1}/C_{out}$ . The approximate expressions for each pole is

1) Pole at node A:

$$p_A = -\frac{1}{R_A C_A} \approx -\frac{g_{m6}}{C_{gs6} + C_{db1} + C_{db4}}$$

2) Pole at node B:

$$p_B = -\frac{1}{R_B C_B} \approx -\frac{1}{(C_{gs7} + C_{db2} + C_{db5})(r_{ds5} \parallel r_{ds7} \parallel r_{ds2})}$$

3) Pole at drain of  $M_6$ :

$$p_6 = -\frac{1}{R_6 C_6} \approx -\frac{g_{m10}}{(C_{gs10} + C_{gs11} + C_{db8} + C_{db10})}$$

4) Pole at source of  $M_8$ :

$$p_8 = -\frac{1}{R_8 C_8} \approx -\frac{g_{m8} r_{ds8} r_{ds10}}{(C_{gs8} + C_{db10})}$$

5) Pole at source of  $M_9$ :

$$p_9 = -\frac{1}{R_9 C_9} \approx -\frac{g_{m9}}{(C_{gs9} + C_{db11})}$$

•One might feel that because  $R_B$  is approximately  $r_{ds}/3$  that this pole also might be small. However, at frequencies where this pole has influence,  $C_{out}$ , causes  $R_{out}$  to be much smaller making  $p_B$  also nondominant.

❖ **PSRR of the Folded Cascode Op Amp**

•Consider the following circuit used to model the *PSRR*-:

 


Fig. 6.5

•This model assumes that gate, source and drain of  $M_{11}$  and the gate and source of  $M_9$  all vary with  $V_{SS}$ . We shall examine  $V_{out}/V_{SS}$  rather than *PSRR*- (Small  $V_{out}/V_{SS}$  will lead to large *PSRR*-)

•The transfer function of  $V_{out}/V_{SS}$  can be found as

$$\frac{V_{out}}{V_{SS}} \approx \frac{sC_{gd9}R_{out}}{1 + sC_{out}R_{out}}, C_{gd9} < C_{out}$$

 


Fig. 6.5-10A

- The positive PSRR is similar to the negative PSRR. The ripple appears at the gates of  $M_4$ ,  $M_5$ ,  $M_6$ ,  $M_7$ ,  $M_{13}$ , and  $M_{14}$ . The primary source of injection is through the gate/drain capacitor of  $M_7$ , which is the same situation as for the negative power-supply injection.
- The PSRR of the cascode op amp is much better than the two-stage op amp without any modifications to improve the PSRR!**



## ❖ Design Approach for the Folded-Cascode Op Amp

| Step # | Relationship/Requirement        | Design equation/Constraint  | Comments  |
|--------|---------------------------------|---|---|
| 1      | SR                              | $I_3 = SR \cdot C_L$  |   |
| 2      | Bias current at output cascodes | $I_4 = I_5 = (1.2 - 1.5) I_3$   | Avoid zero current in cascodes                          |
| 3      | $V_{outmax}$                    | $S_5 = \frac{2I_5}{k_{pp}V_{SD5}^2}, S_7 = \frac{2I_7}{k_{pp}V_{SD7}^2}, S_4 = S_5, S_6 = S_7$                        | $V_{SD5sat} = V_{SD7sat} = 0.5(V_{DD} - V_{outmax})$    |
| 4      | $V_{outmin}$                    | $S_{11} = \frac{2I_{11}}{k_{pn}V_{DS11}^2}, S_9 = \frac{2I_9}{k_{pn}V_{DS9}^2}, S_{10} = S_{11}, S_8 = S_9$           | $V_{DS9sat} = V_{DS11sat} = 0.5(V_{outmin} - V_{SS})$   |
| 5      | $GB = g_{m1}/C_L$               | $S_1 = S_2 = \frac{g_{m1}^2}{k_{pn}I_3} = \frac{(GB \cdot C_L)^2}{k_{pn}I_3}$   |   |
| 6      | Minimum input CM voltage        | $S_3 = \frac{2I_3}{k_{pn} \left( V_{inmin} - V_{SS} - \sqrt{I_3 / (k_{pn}S_1)} - V_{T1} \right)^2}$                   |   |
| 7      | Maximum input CM voltage        | $S_4 = S_5 = \frac{2I_4}{k_{pp} (V_{DD} - V_{inmax} + V_{T1})^2}$   | S4 and S5 must meet or exceed value in step 3           |
| 8      | Differential voltage gain       | $A_v = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \frac{1}{k+1} \right) = \frac{1}{2} \frac{k+2}{k+1} g_{m1} R_{out}$ | $k = \frac{R_{II} (g_{ds2} + g_{ds5})}{g_{m7} r_{ds7}}$ |
| 9      | Power Dissipation               | $P_{diss} = (V_{DD} + V_{SS})(I_3 + I_{11} + I_{10})$   |   |

## ❖ Design of a Folded-Cascode Op Amp

Design a folded-cascode op amp if the slew rate is  $10\text{V}/\mu\text{s}$ , the load capacitor is  $10\text{pF}$ , the maximum and minimum output voltages are  $2\text{V}$  and  $0.5\text{V}$  for a  $2.5\text{V}$  power supply, the  $GB$  is  $10\text{MHz}$ , the minimum input common mode voltage is  $+1\text{V}$  and the maximum input common mode voltage is  $2.5\text{V}$ . The differential voltage gain should be greater than  $3000$  and the power dissipation should be less than  $5\text{mW}$ . Use  $K_{pn}'=120\mu\text{A}/\text{V}^2$ ,  $K_{pp}'= 25\mu\text{A}/\text{V}^2$ ,  $V_{TN} = |V_{TP}| = 0.5\text{V}$ ,  $\lambda_n = 0.06(1/\text{V})$ , and  $\lambda_p = 0.08(1/\text{V})$ . Let  $L = 0.5 \mu\text{m}$ .

*Solution:*

Following the approach outlined above we obtain the following results

$$I_3 = SR \cdot C_L = 100 \mu\text{A}$$

Select  $I_4 = I_5 = 125\mu\text{A}$ .

Next, we see that the value of  $0.5(V_{DD}-V_{out(max)})$  is  $0.5\text{V}/2$  or  $0.25\text{V}$ . Thus

$$S_4 = S_5 = \frac{2I_5}{k_{pp}V_{SD5}^2} = 160$$

and assuming worst case currents in  $M_6$  and  $M_7$  gives,

$$S_6 = S_7 = \frac{2I_7}{k_{pp}V_{SD7}^2} = 160$$

The value of  $0.5 \cdot V_{out(min)}$  is  $0.25\text{V}$  which gives the value of  $S_8, S_9, S_{10}$  and  $S_{11}$  as

$$S_{8-11} = \frac{2I_8}{k_{pp}V_{DS8}^2} = 20$$

In step 5, the value of GB gives  $S_1$  and  $S_2$  as

$$S_1 = S_2 = \frac{g_{m1}^2}{k_{pn}I_3} = \frac{(GB \cdot C_L)^2}{k_{pn}I_3} = 32.9 \approx 33$$

The minimum input common mode voltage defines  $S_3$  as

$$S_3 = \frac{2I_3}{k_{pn} \left( V_{in\min} - V_{SS} - \sqrt{I_3 / (k_{pn}S_1)} - V_{T1} \right)^2} = 14.3 \approx 15$$

We need to check that the values of  $S_4$  and  $S_5$  are large enough to satisfy the maximum input common mode voltage. The maximum input common mode voltage of 2.5V requires

$$S_4 = S_5 = \frac{2I_4}{k_{pp} (V_{DD} - V_{in\max} + V_{T1})^2} = 40$$

which is less than 160. In fact, with  $S_4 = S_5 = 160$ , the maximum input common mode voltage is 2.75V.

The power dissipation is found to be

$$P_{diss} = (V_{DD} + V_{SS})(I_3 + I_{11} + I_{10}) = 625 \mu\text{W}$$

The small-signal voltage gain requires the following values to evaluate:

- $g_{m5} = g_{m4} = 1000 \mu\text{S}$ ,  $g_{ds4} = g_{ds5} = 10 \mu\text{S}$
- $g_{m6} = g_{m7} = 774.6 \mu\text{S}$ ,  $g_{ds6} = g_{ds7} = 10 \mu\text{S}$
- $g_{m(8-11)} = 600 \mu\text{S}$ ,  $g_{ds(8-11)} = 4.5 \mu\text{S}$
- $g_{m1} = g_{m2} = 629 \mu\text{S}$ ,  $g_{ds1} = g_{ds2} = 3 \mu\text{S}$

Thus,

$$R_{II} \approx g_{m9} r_{ds9} r_{ds11} = 29.63 \text{M}\Omega$$

$$R_{out} \approx 7.44 \text{M}\Omega$$

$$k = \frac{R_{II} (g_{ds2} + g_{ds5})}{g_{m7} r_{ds7}} = 0.75$$

The small-signal, differential-input, voltage gain is

$$A_v = \left( \frac{g_{m1}}{2} + \frac{g_{m2}}{2} \frac{1}{k+1} \right) = \frac{1}{2} \frac{k+2}{k+1} g_{m1} R_{out} = 3678$$

The gain is slightly larger than the specified 3000.

### Comments on Folded Cascode Op Amps

- Good PSRR
- Good ICMR
- Self compensated
- Can cascade an output stage to get extremely high gain with lower output resistance (use Miller compensation in this case)
- Need first stage gain for good noise performance
- Widely used in telecommunication circuits where large dynamic range is required

