

Dynamic Models of Converters in the Discontinuous Conduction Mode

Predrag Pejović

May 9, 2016

1 Preliminaries

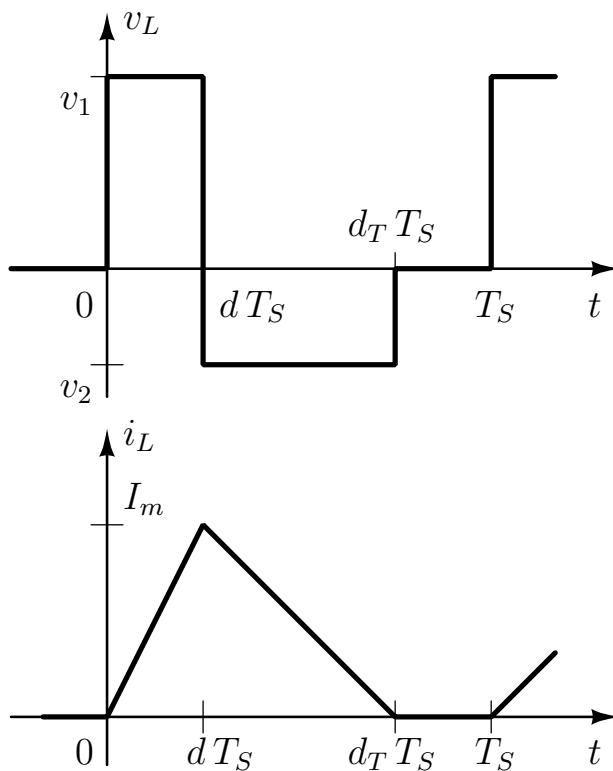


Figure 1: Waveforms of v_L and i_L , discontinuous conduction mode; $d_T = d + d_2$.

Table 1: Inductor Voltages and Average Current to the Capacitor and the Load

	buck	boost	buck-boost
v_1	$v_{IN} - v_{OUT}$	v_{IN}	v_{IN}
v_2	$-v_{OUT}$	$v_{IN} - v_{OUT}$	v_{OUT}
$\langle i_{CL} \rangle$	$\frac{1}{2} (d + d_2) I_m$	$\frac{1}{2} d_2 I_m$	$-\frac{1}{2} d_2 I_m$

In pulse-width modulation

$$I_m = \frac{v_1}{L} d T_S \quad (1)$$

while in the current mode control

$$d = \frac{f_S L I_m}{v_1}. \quad (2)$$

In both of the control methods

$$d_2 = -\frac{v_1}{v_2} d. \quad (3)$$

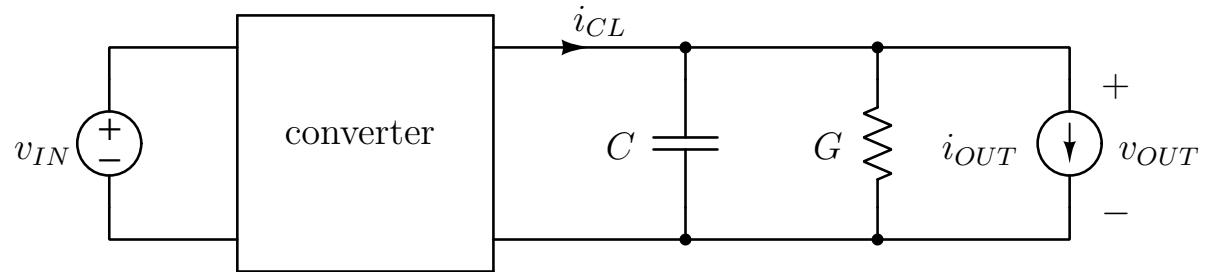


Figure 2: Assumed converter structure.

2 Pulse-Width Modulation

2.1 Nonlinear Dynamic Model

$$\frac{d v_{OUT}}{dt} = \frac{1}{C} i_{CL} - \frac{G}{C} v_{OUT} - \frac{1}{C} i_{OUT} \quad (4)$$

$$G_0 \triangleq \frac{1}{2 f_S L} \quad (5)$$

Table 2: Pulse-Width Modulation, Nonlinear Dynamic Model

converter	i_{CL}	nonlinear dynamic model
buck	$G_0 d^2 v_{IN} \frac{v_{IN} - v_{OUT}}{v_{OUT}}$	$\frac{d v_{OUT}}{dt} = \frac{G_0}{C} d^2 v_{IN} \frac{v_{IN} - v_{OUT}}{v_{OUT}} - \frac{G}{C} v_{OUT} - \frac{1}{C} i_{OUT}$
boost	$G_0 d^2 \frac{v_{IN}^2}{v_{OUT} - v_{IN}}$	$\frac{d v_{OUT}}{dt} = \frac{G_0}{C} d^2 \frac{v_{IN}^2}{v_{OUT} - v_{IN}} - \frac{G}{C} v_{OUT} - \frac{1}{C} i_{OUT}$
buck-boost	$G_0 d^2 \frac{v_{IN}^2}{v_{OUT}}$	$\frac{d v_{OUT}}{dt} = \frac{G_0}{C} d^2 \frac{v_{IN}^2}{v_{OUT}} - \frac{G}{C} v_{OUT} - \frac{1}{C} i_{OUT}$

2.2 Steady State Equations

Table 3: Pulse-Width Modulation, Steady State Equations

converter	steady state equations
buck	$G_0 D_0^2 V_{IN} \frac{V_{IN} - V_{OUT}}{V_{OUT}} - G V_{OUT} - I_{OUT} = 0$
boost	$G_0 D_0^2 \frac{V_{IN}^2}{V_{OUT} - V_{IN}} - G V_{OUT} - I_{OUT} = 0$
buck-boost	$G_0 D_0^2 \frac{V_{IN}^2}{V_{OUT}} - G V_{OUT} - I_{OUT} = 0$

2.3 Linearized Model

$$\frac{d \hat{v}_{OUT}}{dt} = a_1 \hat{v}_{OUT} + a_2 \hat{v}_{IN} + a_3 \hat{i}_{OUT} + a_4 \hat{d} \quad (6)$$

Table 4: Pulse-Width Modulation, Small-Signal Parameters

converter	buck	boost	buck-boost
a_1	$-\frac{G_0}{C} D_0^2 \frac{V_{IN}^2}{V_{OUT}^2} - \frac{G}{C}$	$-\frac{G_0}{C} D_0^2 \frac{V_{IN}^2}{(V_{OUT} - V_{IN})^2} - \frac{G}{C}$	$-\frac{G_0}{C} D_0^2 \frac{V_{IN}^2}{V_{OUT}^2} - \frac{G}{C}$
a_2	$\frac{G_0}{C} D_0^2 \left(\frac{2V_{IN}}{V_{OUT}} - 1 \right)$	$\frac{G_0}{C} D_0^2 \frac{V_{IN} (2V_{OUT} - V_{IN})}{(V_{IN} - V_{OUT})^2}$	$2 \frac{G_0}{C} D_0^2 \frac{V_{IN}}{V_{OUT}}$
a_3	$-\frac{1}{C}$	$-\frac{1}{C}$	$-\frac{1}{C}$
a_4	$2 \frac{G_0}{C} D_0 V_{IN} \frac{V_{IN} - V_{OUT}}{V_{OUT}}$	$2 \frac{G_0}{C} D_0 \frac{V_{IN}^2}{V_{OUT} - V_{IN}}$	$2 \frac{G_0}{C} D_0 \frac{V_{IN}^2}{V_{OUT}}$

3 Current Mode Control

3.1 Nonlinear Dynamic Model

$$C \frac{dv_{OUT}}{dt} = i_{CL} - G v_{OUT} - i_{OUT} \quad (7)$$

Table 5: Current Mode Control, Nonlinear Dynamic Model

converter	i_{CL}
buck	$\frac{1}{2} \frac{v_{IN}}{v_{OUT} (v_{IN} - v_{OUT})} f_s L I_m^2$
boost	$\frac{1}{2} \frac{1}{v_{OUT} - v_{IN}} f_s L I_m^2$
buck-boost	$\frac{1}{2} \frac{1}{v_{OUT}} f_s L I_m^2$

3.2 Steady State Equations

Table 6: Current Mode Control, Steady State Equations

converter	steady state equation
buck	$\frac{1}{2} \frac{V_{IN}}{V_{OUT} (V_{IN} - V_{OUT})} f_s L I_m^2 - G V_{OUT} - I_{OUT} = 0$
boost	$\frac{1}{2} \frac{1}{V_{OUT} - V_{IN}} f_s L I_m^2 - G V_{OUT} - I_{OUT} = 0$
buck-boost	$\frac{1}{2} \frac{1}{V_{OUT}} f_s L I_m^2 - G V_{OUT} - I_{OUT} = 0$

3.3 Linearized Model

$$\frac{d\hat{v}_{OUT}}{dt} = a_1 \hat{v}_{OUT} + a_2 \hat{v}_{IN} + a_3 \hat{i}_{OUT} + a_4 \hat{I}_m \quad (8)$$

Table 7: Current Mode Control, Small-Signal Parameters, Part 1

converter	a_1	a_2
buck	$\frac{f_s L}{2 C} \frac{V_{IN} (2 V_{OUT} - V_{IN})}{V_{OUT}^2 (V_{IN} - V_{OUT})^2} I_m^2 - \frac{G}{C}$	$-\frac{f_s L}{2 C} \frac{1}{(V_{IN} - V_{OUT})^2} I_m^2$
boost	$-\frac{f_s L}{2 C} \frac{1}{(V_{OUT} - V_{IN})^2} I_m^2 - \frac{G}{C}$	$\frac{f_s L}{2 C} \frac{1}{(V_{OUT} - V_{IN})^2} I_m^2$
buck-boost	$-\frac{f_s L}{2 C} \frac{1}{V_{OUT}^2} I_m^2 - \frac{G}{C}$	0

Table 8: Current Mode Control, Small-Signal Parameters, Part 2

converter	a_3	a_4
buck	$-\frac{1}{C}$	$\frac{f_S L}{C} \frac{V_{IN}}{V_{OUT}(V_{IN} - V_{OUT})} I_m$
boost	$-\frac{1}{C}$	$\frac{f_S L}{C} \frac{I_m}{V_{OUT} - V_{IN}}$
buck-boost	$-\frac{1}{C}$	$\frac{f_S L}{C} \frac{I_m}{V_{OUT}}$