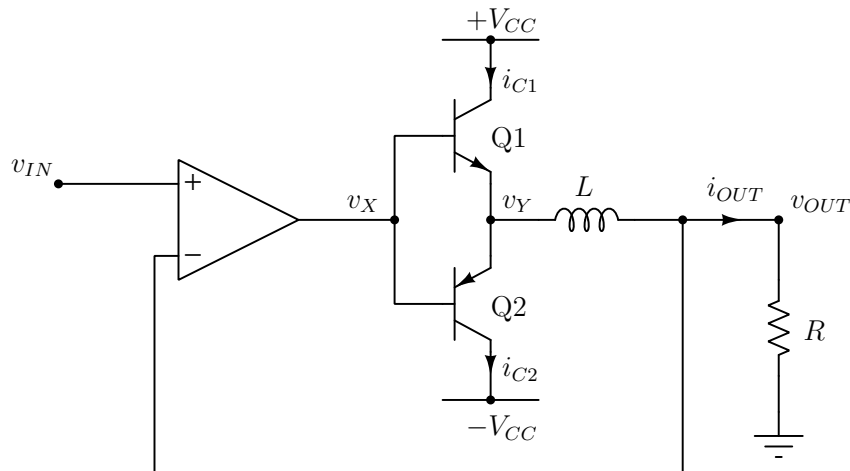


1. Na slici 1 je prikazan sistem za programiranje struje kalema primenom pojačavača snage u klasi B koji proširuje strujni kapacitet operacionog pojačavača. Poznato je  $V_{CC} = 15\text{ V}$ ,  $R = 10\ \Omega$ ,  $L = 10\text{ mH}$ ,  $\omega_0 = 1\ \frac{\text{krad}}{\text{s}}$ ,  $\beta_F \rightarrow \infty$ ,  $V_{BE} = 0.75\text{ V}$ , operacioni pojačavač je idealan,  $v_{IN} = 1\text{ V} \sin(\omega_0 t)$ .

- [6] Odrediti vremenske dijagrame napona  $v_{OUT}$ ,  $v_Y$  i  $v_X$ , kao i struja  $i_{OUT}$ ,  $i_{C1}$  i  $i_{C2}$ .
- [2] Koristeći zakon o održanju energije odrediti srednju snagu disipacije na tranzistorima Q1 i Q2,  $P_D = P_{D1} + P_{D2}$ .
- [2] Odrediti vremenski dijagram trenutne snage disipacije na tranzistoru Q1,  $p_{D1}(t)$ , i proceniti njenu maksimalnu trenutnu vrednost (greška u proceni od 20% se toleriše).



Slika 1

a) [6]

$$v_{OUT} = v_{IN} = 1\text{ V} \sin(\omega_0 t)$$

$$i_{OUT} = \frac{v_{OUT}}{R} = 100\text{ mA} \sin(\omega_0 t)$$

$$i_{C1} = \begin{cases} i_{OUT}, & i_{OUT} \geq 0 \\ 0, & i_{OUT} < 0 \end{cases}$$







$$i_{C2} = \begin{cases} -i_{OUT}, & i_{OUT} < 0 \\ 0, & i_{OUT} \geq 0 \end{cases}$$



$$v_L = L \frac{di_L}{dt} = \omega_0 L I_m \cos(\omega_0 t), \quad I_m = 100\text{ mA}$$

$$v_L = L \frac{di_L}{dt} = 1\text{ V} \cos(\omega_0 t)$$

$$v_Y = v_{OUT} + v_L = 1\text{ V} (\sin(\omega_0 t) + \cos(\omega_0 t)) \approx 1.41\text{ V} \sin\left(\omega_0 t + \frac{\pi}{4}\right)$$
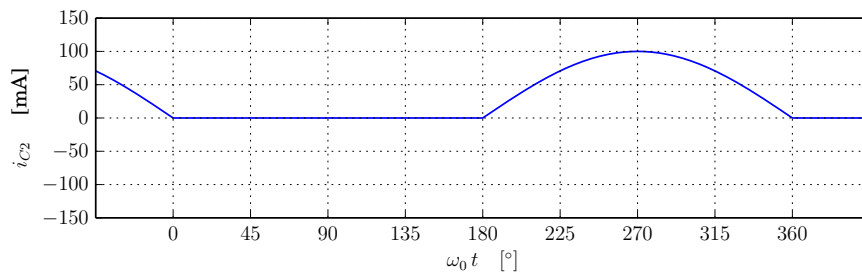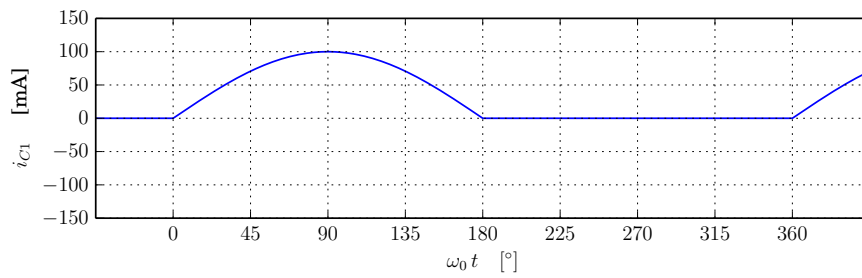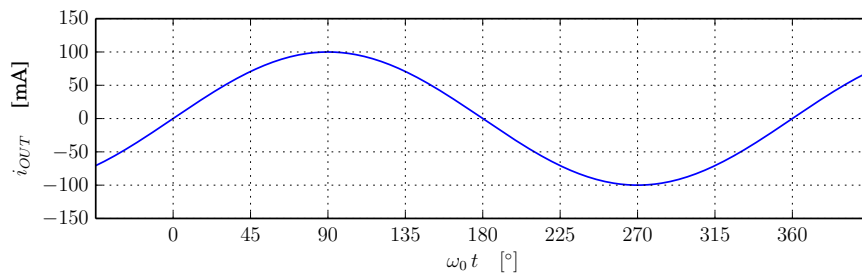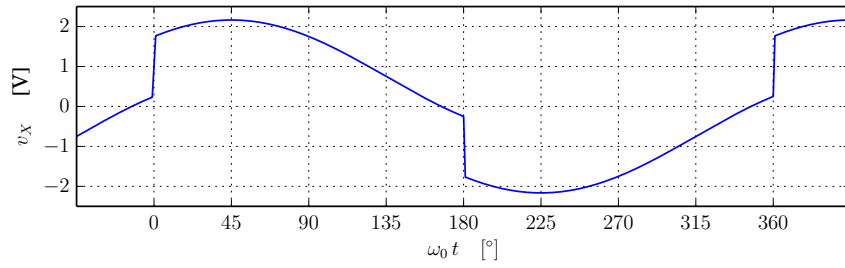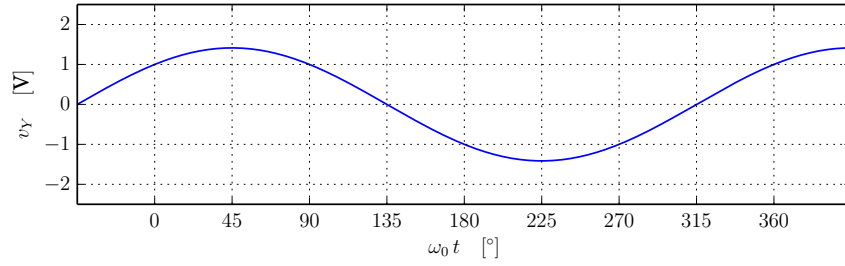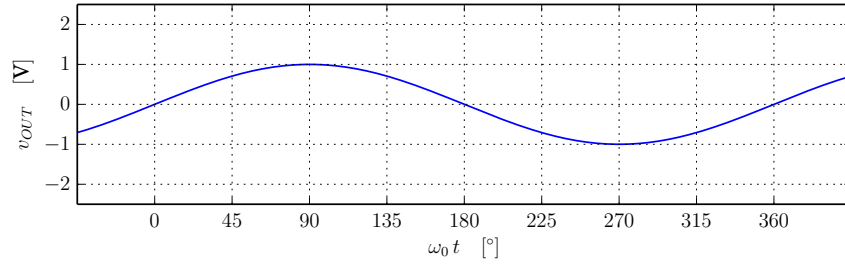
$$v_x = v_Y + V_D \operatorname{sgn}(i_{OUT}) \approx 1.41\text{ V} \sin\left(\omega_0 t + \frac{\pi}{4}\right) + 0.75\text{ V} \operatorname{sgn}(\sin(\omega_0 t))$$



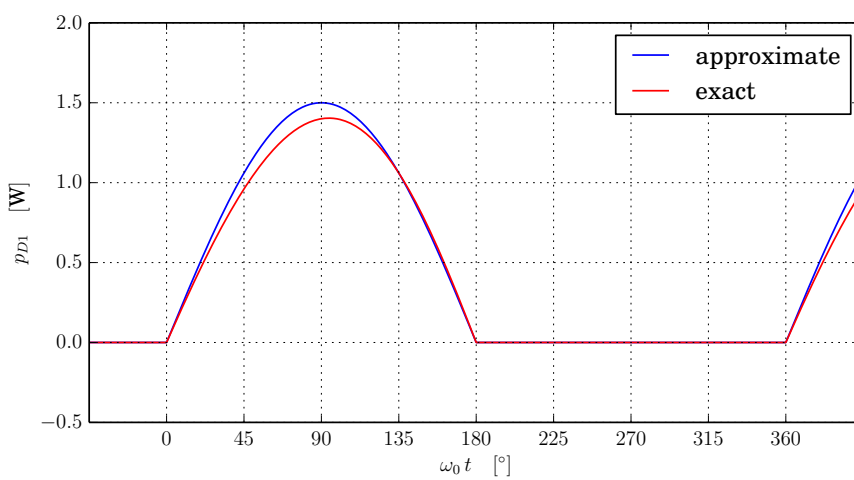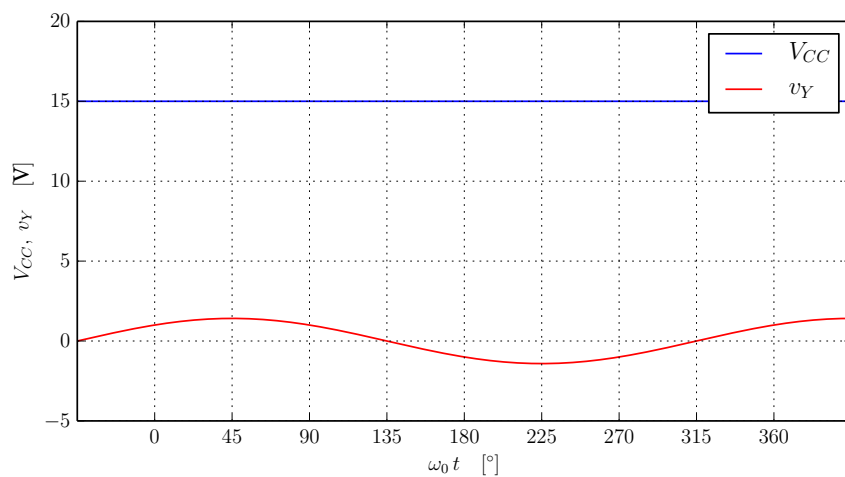

b) [2]

$$P_{CC} = \frac{2}{\pi} V_{CC} I_m = \frac{2}{\pi} 1.5 \text{ W} \approx 0.9549 \text{ W}$$

$$P_{OUT} = \frac{(V_{OUTm})^2}{2R} = 50 \text{ mW}$$

$$P_D = P_{CC} - P_{OUT} \approx 0.9049 \text{ W}$$

c) [2]

$$p_{D1} = (V_{CC} - v_Y) i_{C1} \approx V_{CC} i_{C1}$$

pošto je  $v_Y$  uvek manje od 20%  $V_{CC} = 3 \text{ V}$ , štaviše, manje je i od 10%  $V_{CC} = 1.5 \text{ V}$

$$p_{D1} \approx 1.5 \text{ W} \sin(\omega_0 t)$$

$$p_{D1max} \approx 1.5 \text{ W}$$

Numerički dobijen rezultat:

$$p_{D1max} = 1.404 \text{ W} \text{ za } \omega_0 t = 94^\circ$$