

### Elementi elektronike – JANUAR 2019 - REŠENJA

3.

$$v_i = \begin{cases} 0, & 0 \leq V_{CC} < V_{BE} = 0.6V, & T - OFF, DZ - OFF \\ \frac{1}{2}(V_{CC} - V_{BE}), & 0.6V \leq V_{CC} < 2V_Z - V_{BE} = 9.4V, & T - DAR, DZ - OFF \\ V_Z - V_{BE}, & 9.4V \leq V_{CC} \leq 12V, & T - DAR, DZ - Z \end{cases}$$

4.

a)

$$V_G = V_D = V_{DD} - R_D I_D$$

$$V_S = R_S I_D$$

$$V_{GS} = V_T + \sqrt{\frac{2I_D}{B}} = 4V = V_G - V_S = V_{DD} - R_D I_D - R_S I_D$$

$$R_S = \frac{V_{DD} - V_{GS} - R_D I_D}{I_D} = 3k\Omega$$

b) Naponsko pojačanje:


$$v_{gs} = v_u$$

$$i_i = -g_m v_{gs} - i_u = -g_m v_{gs} - \frac{v_i - v_u}{R_G}$$

$$v_i = i_i R_D || r_{ds} = -g_m R_D || r_{ds} v_u - R_D || r_{ds} \frac{v_i - v_u}{R_G}$$

$$v_i = \frac{-g_m R_D || r_{ds} + \frac{R_D || r_{ds}}{R_G}}{1 + R_D || r_{ds}} v_u$$

$$A_v = \frac{-g_m R_D || r_{ds} + \frac{R_D || r_{ds}}{R_G}}{1 + \frac{R_D || r_{ds}}{R_G}} = -5.7$$

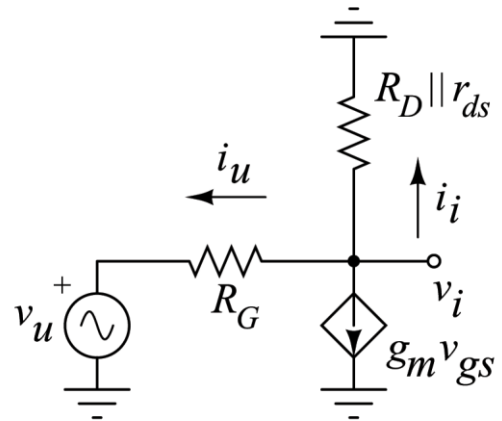

Ulazna otpornost:

$$i_t = -i_u = g_m v_{gs} + i_i = g_m v_t + \frac{v_i}{R_D || r_{ds}} = g_m v_t + \frac{A_v v_t}{R_D || r_{ds}}$$

$$R_U = \frac{1}{g_m + \frac{A_v}{R_D || r_{ds}}} \approx 1492\Omega$$

Izlazna otpornost:

$$v_{gs} = 0V$$

$$R_I = R_G \parallel |R_D| \parallel r_{ds} = 3k\Omega$$

7.

$$\text{Za } V_{EE} \leq v_U \leq \frac{V_{EE} + \frac{R_2 V_R}{R_1}}{1 + \frac{R_2}{R_1}} = -0.4V:$$

$$v_I = V_{EE}$$

$$\text{Za } -0.4V < v_U \leq V_R + \frac{R_1}{R_2} V_D = 2.15V:$$

$$v_I = v_U \left( 1 + \frac{R_2}{R_1} \right) - V_R \frac{R_2}{R_1}$$

$$\text{Za } 2.15V < v_U \leq \frac{R_1 \parallel R_2 \parallel R_3}{R_2 \parallel R_3} \left( V_{CC} + V_R \frac{R_2 \parallel R_3}{R_1} - V_D \frac{R_2}{R_2 + R_3} \right) \approx 6.18V$$

$$v_I = v_U \frac{R_2 \parallel R_3}{R_1 \parallel R_2 \parallel R_3} - V_R \frac{R_2 \parallel R_3}{R_1} + V_D \frac{R_2}{R_2 + R_3}$$

$$\text{Za } 6.18V < v_U \leq V_{CC}:$$

$$v_I = V_{CC}$$

8.

$$y_2 = a_1 a_0 b_0 + a_0 b_1 b_0 + a_1 b_1$$

$a_1 a_0 \backslash b_1 b_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	1
10	0	0	1	1

$$y_1 = \overline{a_1} \overline{a_0} b_1 + \overline{a_1} b_1 \overline{b_0} + a_1 \overline{b_1} \overline{b_0} + a_1 \overline{a_0} \overline{b_1} + \overline{a_1} a_0 \overline{b_1} b_0 + a_1 a_0 b_1 b_0$$

$b_1b_0$ \ $a_1a_0$	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	1	0	1	0
10	1	1	0	0

$$y_0 = a_0\bar{b}_0 + \bar{a}_0b_0$$

$b_1b_0$ \ $a_1a_0$	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	1	0	0	1
10	0	1	1	0

9.

Moduo brojanja je 5.