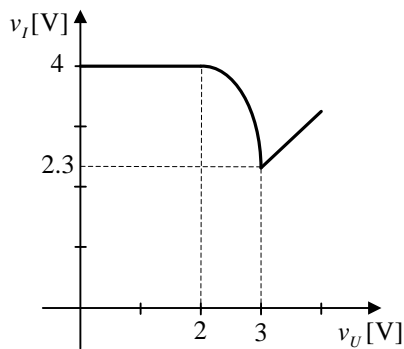


2.

$$v_I = \begin{cases} V_{DD} & 0 \leq v_U \leq V_t \\ V_{DD} - \frac{R_D k_n}{2} (v_U - V_t)^2 & V_t \leq v_U \leq 3V \\ v_U - V_D & 3V \leq v_U \leq 4V \end{cases}$$




3.

Sa šeme za male signale (Slika 1)

$$v_p = -(R_P \parallel R_C) g_m v_{be}$$

$$v_{be} = v_u - v_e$$

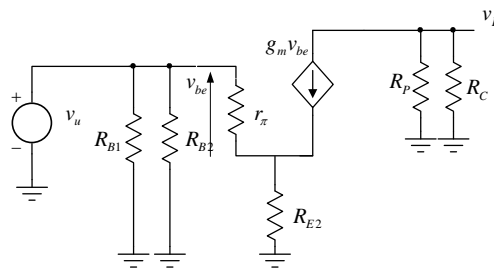

Slika 1

$$v_e = R_{E2} \left(\frac{v_{be}}{r_\pi} + g_m v_{be} \right) = R_{E2} \left(v_u \left(\frac{1}{r_\pi} + g_m \right) - v_e \left(\frac{1}{r_\pi} + g_m \right) \right)$$


$$v_e = \frac{\frac{R_{E2}}{r_\pi} + g_m R_{E2}}{1 + \frac{R_{E2}}{r_\pi} + g_m R_{E2}} v_u = \frac{R_{E2} (1 + g_m r_\pi)}{R_{E2} (1 + g_m r_\pi) + r_\pi} v_u$$

$$v_p = -(R_P \parallel R_C) g_m \frac{r_\pi}{R_{E2} (1 + \beta) + r_\pi} v_u$$

$$A_V = -(R_P \parallel R_C) \frac{\beta}{R_{E2} (1 + \beta) + r_\pi}$$

$$r_\pi = -(R_P \parallel R_C) \frac{\beta}{A_V} - R_{E2} (1 + \beta) = 6566.7 \Omega = \frac{\beta V_T}{I_C}$$

$$I_C = \frac{\beta V_T}{r_\pi} = 380.71 \mu A$$

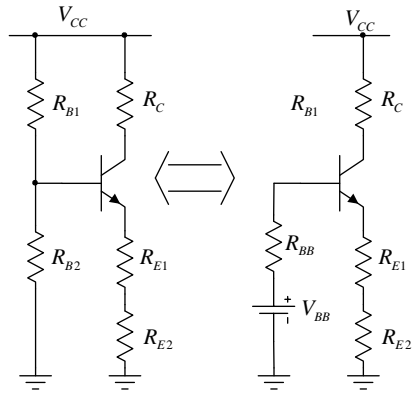

Slika 2

Sa šeme za veliki signal (Slika 2.):

$$V_{BB} = \frac{R_{B1}}{R_{B1} + R_{B2}} V_{CC} = 6V$$

$$R_{BB} = R_{B1} \parallel R_{B2} = 25k\Omega$$

$$V_{BB} = R_{BB} \frac{I_E}{1 + \beta} + V_{BE} + (R_{E1} + R_{E2}) I_E$$


$$I_E = \frac{V_{BB} - V_{BE}}{\frac{R_{BB}}{1 + \beta} + R_{E1} + R_{E2}}$$

$$I_C = \frac{\beta}{1 + \beta} I_E = \frac{\beta}{1 + \beta} \frac{V_{BB} - V_{BE}}{\frac{R_{BB}}{1 + \beta} + R_{E1} + R_{E2}}$$

$$R_{E1} = \frac{\beta}{1 + \beta} \frac{V_{BB} - V_{BE}}{I_C} - \frac{R_{BB}}{1 + \beta} - R_{E2} = 13.436k\Omega$$

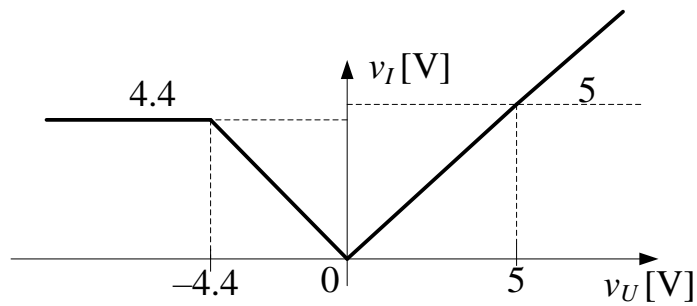6.





$$v_I = \begin{cases} V_{CC} - V_D & v_U \leq -V_{CC} + V_D \\ -v_U & -V_{CC} + V_D < v_U \leq 0 \\ v_U & 0 < v_U \end{cases}$$




7. a)

c	x_2	x_1	x_0	y_3	y_2	y_1	y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	1
0	1	1	0	0	1	1	0
0	1	1	1	0	1	1	1
1	0	0	0	1	0	0	0
1	0	0	1	0	1	1	1
1	0	1	0	0	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

c)

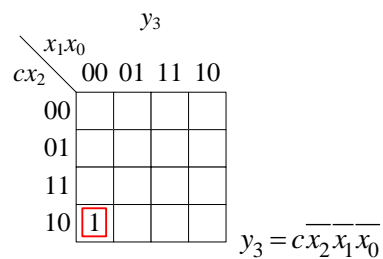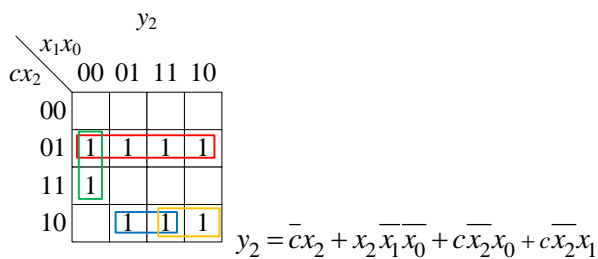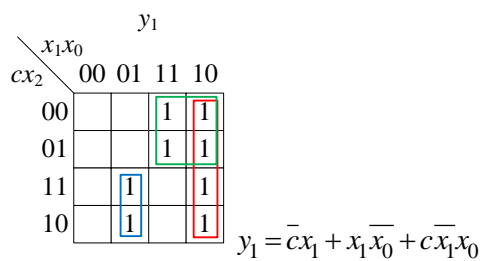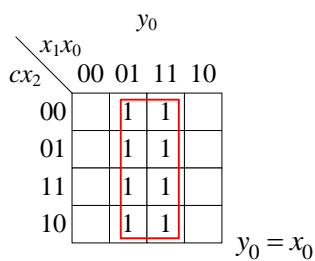

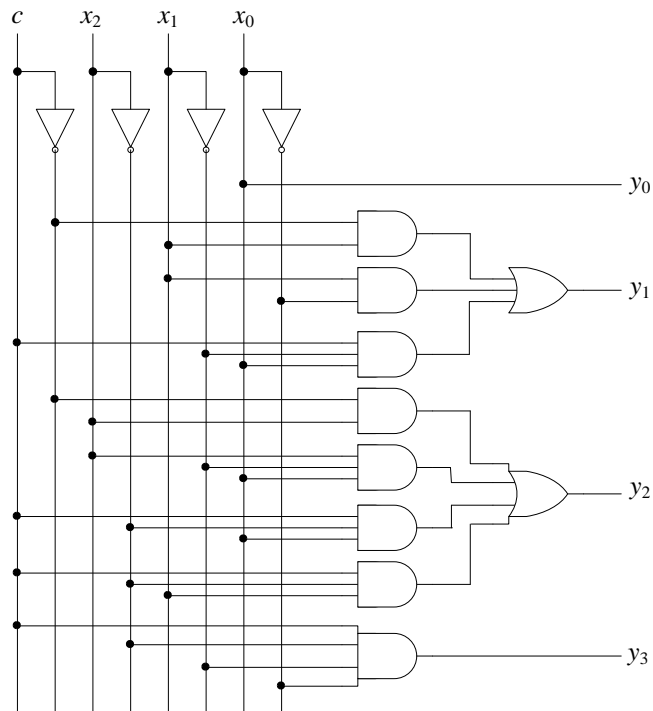


d)

$$y_0 = x_0$$

$$y_1 = \overline{c}x_1 + x_1\overline{x_0} + c\overline{x_1}x_0 = \overline{c}x_1 + x_1\overline{x_0} + c\overline{x_1}x_0 = \overline{c}x_1 \cdot x_1\overline{x_0} + c\overline{x_1}x_0 = \overline{c}x_1 \cdot x_1\overline{x_0} + c\overline{x_1}x_0$$

$$y_2 = \overline{c}x_2 + x_2\overline{x_1}x_0 + c\overline{x_2}x_0 + c\overline{x_2}x_1 = \overline{c}x_2 + x_2\overline{x_1}x_0 + c\overline{x_2}x_0 + c\overline{x_2}x_1 = \overline{c}x_2 \cdot x_2\overline{x_1}x_0 + c\overline{x_2}x_0 + c\overline{x_2}x_1 = \overline{c}x_2 \cdot x_2(\overline{x_1}x_0) + c(\overline{x_2}x_0) + c(\overline{x_2}x_1) = \overline{c}x_2 \cdot x_2 \cdot \overline{x_1} \cdot x_0 + c \cdot \overline{x_2} \cdot x_0 + c \cdot \overline{x_2} \cdot x_1$$
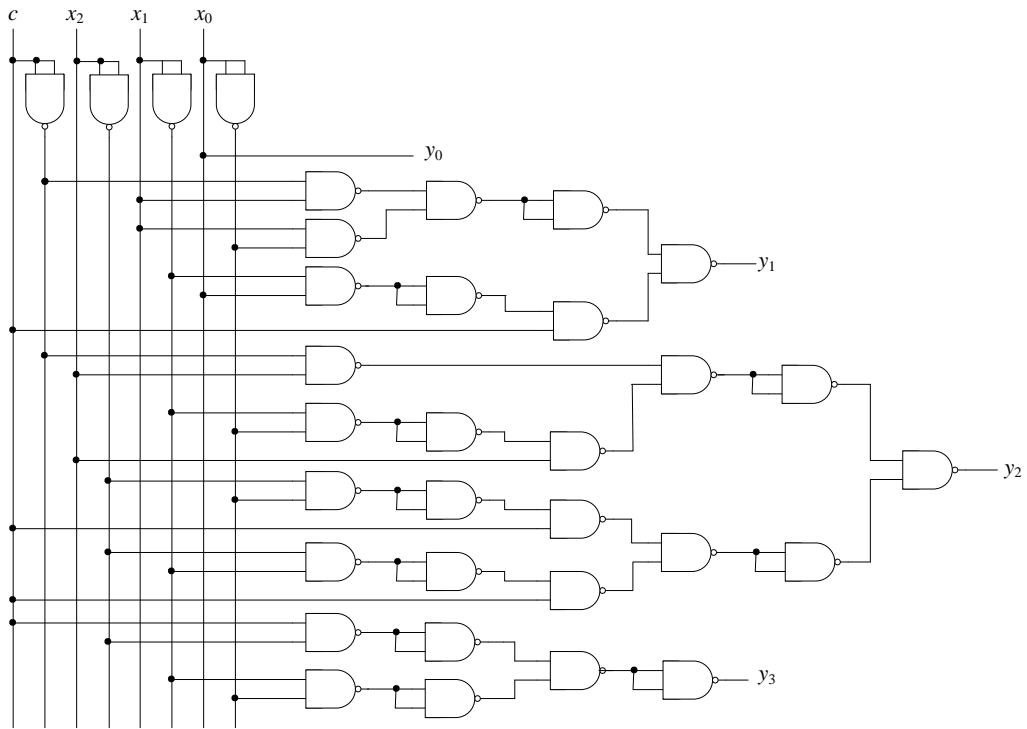
$$y_3 = \overline{c}x_2x_1x_0 = \overline{c}x_2x_1x_0 = (\overline{c}x_2)(x_1x_0) = \overline{c} \cdot x_2 \cdot x_1 \cdot x_0$$



8.

