

REŠENJA ZADATAKA

1. a)  $a_v = \frac{v_p}{v_g} = \frac{g_{m1} R_p}{1 + g_{m1} R_p} = 0,9936$

b)  $a_i = \frac{i_p}{i_g} = \frac{g_{m1} R_B}{1 + g_{m1} R_p} = 2,548$

c)  $V_p = 0$ ;

$v_{pMAX} = V_{CC} - V_{CES} + V_{BE} = 5,4V$  ( $Q_1$  na granici zasićenja);  $v_{pMIN} = -R_p I_{C1} = -3,9V$  ( $Q_1$  na granici zakočjenja);

$V_{pmmax} = 3,9V$ .

4. a)  $R_x = R_y \left( \frac{V_p}{V_z + V_{BE}} - 1 \right) = 6k\Omega$ .

b)  $v_p = V_p = 9V = const$ , za  $0 \leq i_p \leq I_{pMAX}$ ;

$v_p = \frac{R_s R_2}{R_1} i_p - \left( 1 + \frac{R_2}{R_1} \right) V_{BE}$ , za  $0 \leq v_p \leq 9V$ .

c)  $I_{pMAX} = \frac{R_1 + R_2}{R_s R_2} V_{BE} + \frac{R_1}{R_s R_2} V_p = 1,9A$ ;  $I_{PKS} = \frac{R_1 + R_2}{R_s R_2} V_{BE}$ ;  $R_s \approx 2\Omega$ .

d)  $R_{0max} = \frac{V_u - V_p - R_s I_{pMAX} - V_{BE}}{I_{Zmin} + \frac{I_{pMAX}}{\beta_{F1} + 1}} = 76,88\Omega$