

REŠENJA ZADATAKA

1. a) $I_{D1} = 103\mu\text{A}$; $V_I = 2.02\text{V}$ $I_{C2} = 1.1\text{mA}$.

b) $a = \frac{v_i}{v_u} = \frac{g_{m1}R_1}{1 + g_{m1}R_1} \cdot (-g_{m2}R_3) = -96.6$.

4. a) $R_2 = -R_1 \left(1 + \frac{V_P}{V_Z + V_{EB}} \right) = 1.25\text{k}\Omega$.

b) $v_p = -5\text{V} = \text{const}$, za $0 \leq i_p \leq I_{P\text{MAX}}$;
 $i_p = I_{P\text{MAX}} = \text{const}$, za $-5\text{V} \leq v_p \leq 0$.

c) $I_{P\text{MAX}} = -\frac{P_{DQ1\text{max}}}{V_{EB} + V_u} = 0.8\text{A}$; $R_S = \frac{V_{EB}}{I_{P\text{MAX}}} = 0.875\Omega$.

d) $R_{0\text{max}} = \frac{V_P - 2V_{EB} - V_u}{I_{Z\text{min}} + \frac{I_{P\text{MAX}}}{\beta_{F1}}} = 560\Omega$.