

REŠENJA ZADATAKA

1. a) $R_1 = 113\text{k}\Omega$; $R_2 = 7.78\text{k}\Omega$; $R_3 = 14.1\text{k}\Omega$; $R_4 = 1.2\text{k}\Omega$.

b) $a = \frac{v_i}{v_g} = [-g_{m1}(R_2 \parallel r_{\pi 2})] \cdot [-g_{m2}(R_3 \parallel (r_{\pi 3} + (\beta_0 + 1)R_4))] \cdot \frac{g_{m3}R_4}{1 + g_{m3}R_4} \approx 3825.1$.

c) $R_{ul} = r_{\pi 1} = 25\text{k}\Omega$; $R_{izl} = R_4 \parallel \frac{r_{\pi 3} + R_3}{\beta_0 + 1} = 127\Omega$.

4.

$v_I[\text{V}] = -0.75i_G[\text{mA}] + 0.9$, za $-5\text{mA} \leq i_G \leq -0.4\text{mA}$ (IOP-lin. režim, D-ON, T-DAR);

$v_I[\text{V}] = -3i_G[\text{mA}]$, za $-0.4\text{mA} \leq i_G \leq 4\text{mA}$ (IOP-lin. režim, D-OFF, T-OFF);

$v_I[\text{V}] = -12\text{V} = \text{const}$, za $4\text{mA} \leq i_G \leq 5\text{mA}$ (IOP-neg. zasićenje, D-OFF, T-OFF).