

**REŠENJA ZADATAKA**

1. a)  $I_{C1} \approx 162\mu\text{A}$ ;  $I_{C2} \approx 530\mu\text{A}$ .

$$\text{b) } a = \frac{v_i}{v_g} = \frac{R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1}}{R_1 + R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1}} g_{m1} [R_3 \parallel (r_{\pi 2} + (\beta_0 + 1)R_4)] \frac{g_{m2} R_4}{1 + g_{m2} R_4} \approx 15.73.$$

$$\text{c) } R_{ul} = R_1 + R_2 \parallel \frac{r_{\pi 1}}{\beta_0 + 1} \approx 100\Omega; \quad R_{izl} = R_4 \parallel \frac{r_{\pi 2} + R_3}{\beta_0 + 1} = 70\Omega.$$

**4.**

$v_I[\text{V}] = -12\text{V}$ , za  $-12\text{V} \leq v_G \leq -4.5\text{V}$  (IOP-neg. zasićenje, D-ON);

$v_I[\text{V}] = 2v_G[\text{V}] - 3$ , za  $-4.5\text{V} \leq v_G \leq -1.5\text{V}$  (IOP-lin. režim, D-ON);

$v_I[\text{V}] = 4v_G[\text{V}]$ , za  $-1.5\text{V} \leq v_G \leq 3\text{V}$  (IOP-lin. režim, D-OFF);

$v_I[\text{V}] = 12\text{V}$ , za  $3\text{V} \leq v_G \leq 12\text{V}$  (IOP-poz. zasićenje, D-OFF).