

REŠENJA ZADATAKA

1. M_1 - triodna oblast; M_2 - zasićenje;

$$V_1 = 0,232\text{V} \quad V_2 = 1,248\text{V}$$

4.

$v_I[\text{V}] = 12\text{V}$, za $-12\text{V} \leq v_G \leq -4.8\text{V}$ (IOP-poz. zasićenje, D_1 -OFF, D_2 -ON);

$v_I[\text{V}] = -2v_G[\text{V}] + 2.4$, za $-4.8\text{V} \leq v_G \leq -1.2\text{V}$ (IOP- lin. režim, D_1 -OFF, D_2 -ON);

$v_I[\text{V}] = -4v_G[\text{V}]$, za $-1.2\text{V} \leq v_G \leq 1.2\text{V}$ (IOP-lin. režim, D_1 -OFF, D_2 -OFF);

$v_I[\text{V}] = -2v_G[\text{V}] - 2.4$, za $1.2\text{V} \leq v_G \leq 4.8\text{V}$ (IOP-lin. režim, D_1 -ON, D_2 -OFF);

$v_I[\text{V}] = -12\text{V}$, za $4.8\text{V} \leq v_G \leq 12\text{V}$ (IOP-neg. zasićenje, D_1 -ON, D_2 -OFF).