

REŠENJA ZADATAKA

1. a)  $R_1 \approx 2.2\text{k}\Omega$ ;  $R_2 = 606\Omega$ ;  $R_3 = 5\text{k}\Omega$ .

b)  $a = \frac{v_i}{v_g} = g_{m3} R_3 \frac{g_{m1} (R_2 \parallel r_{\pi 3})}{1 + g_{m1} \left( R_1 \parallel \frac{r_{\pi 2}}{\beta_0 + 1} \right)} \approx 1972$ .

c)  $R_{ul} = r_{\pi 1} + (\beta_0 + 1) \cdot \left( R_1 \parallel \frac{r_{\pi 2}}{\beta_0 + 1} \right) \approx 4.97\text{k}\Omega$ ;  $R_{izl} = R_3 = 5\text{k}\Omega$ .

d)  $V_I = 0$ ;

$v_{IMAX} = 5\text{V}$  ( $Q_3$  na granici zakočenja);  $v_{IMIN} = -4.8\text{V}$  ( $Q_3$  na granici zasićenja);

$V_{im\max} = 4.8\text{V}$ .

4. a)  $R_2 = -R_1 \left( 1 + \frac{V_P}{V_Z + V_{EB}} \right) = 1.25\text{k}\Omega$ .

b)  $v_p = -5\text{V} = \text{const}$ , za  $0 \leq i_p \leq I_{PMAX}$ ;

$i_p = I_{PMAX} = \text{const}$ , za  $-5\text{V} \leq v_p \leq 0$ .

c)  $I_{PMAX} = -\frac{P_{DQ1\max}}{V_{EB} + V_u} = 0.8\text{A}$ ;  $R_S = \frac{V_{EB}}{I_{PMAX}} = 0.875\Omega$ .

d)  $R_{0\max} = \frac{V_P - 2V_{EB} - V_u}{I_{Z\min} + \frac{I_{PMAX}}{\beta_{F1}}} = 560\Omega$ .