

REŠENJA ZADATAKA

1.

$v_C[\text{V}] = V_{CC}$, za $0 \leq V_{CC} \leq 1.2\text{V}$ (D-OFF, Q-OFF);

$v_C[\text{V}] = -0,154V_{CC}[\text{V}] + 1.385$, za $1.2\text{V} \leq V_{CC} \leq 3.8\text{V}$ (D-ON, Q-DAR);

$v_C[\text{V}] = 0.8 = \text{const}$, za $3.8\text{V} \leq V_{CC} \leq 5\text{V}$ (D-ON, Q-zasićenje).