

REŠENJA ZADATAKA

1. a) $R_1 = 606\Omega$; $R_2 \approx 2.2k\Omega$; $R_3 = 5k\Omega$.

$$b) a = \frac{v_i}{v_u} = g_{m3}R_3 \frac{g_{m1}(R_1 \parallel r_{\pi3})}{1 + g_{m1}\left(R_2 \parallel \frac{r_{\pi2}}{\beta_0 + 1}\right)} \approx 1972.$$

$$c) R_{ul} = r_{\pi1} + (\beta_0 + 1) \cdot \left(R_2 \parallel \frac{r_{\pi2}}{\beta_0 + 1}\right) \approx 4.97k\Omega; \quad R_{izl} = R_3 = 5k\Omega.$$

d) $V_I = 0$;

$v_{IMAX} = 4.8V$ (Q_3 na granici zasićenja); $v_{IMIN} = -5V$ (Q_3 na granici zakočenja);

$V_{immax} = 4.8V$.

4.

$v_I[V] = 0$, za $-5V \leq v_G \leq 0$ (IOP-lin. režim, D_1 -ON, Q_1 -OFF);

$v_I[V] = -5v_G[V]$, za $0 \leq v_G \leq 2.88V$ (IOP-lin. režim, D_1 -OFF, Q_1 -DAR);

$v_I[V] = -14.4V$, za $2.88V \leq v_G \leq 5V$ (IOP-neg. zasićenje, D_1 -OFF, Q_1 -DAR).