

## REŠENJA ZADATAKA

1. a)  $I_{C1} = 1\text{mA}$ ,  $I_{C2} = 1\text{mA}$ ,  $R_1 = 1.6\text{k}\Omega$ ,  $R_2 = 4.4\text{k}\Omega$ .

b)  $a_v = \frac{v_p}{v_g} = (-g_{m1}(R_1 \parallel r_{\pi 2})) \cdot (-g_{m2}(R_4 \parallel R_p)) = 5203$

c)  $R_{ul} = r_{\pi 1} = 2.5\text{k}\Omega$                        $R_{izl} = R_4 = 5\text{k}\Omega$

d)  $v_{P\max} = 3.8\text{V}$  ( $Q_2$  na granici zasićenja)

$v_{P\min} = -3.33\text{V}$  ( $Q_2$  na granici zakočenja)

$V_P = 0$

$V_{pm\max} = \min\{v_{P\max} - V_P, V_P - v_{P\min}\} = 3.33\text{V}$

## 4.

$v_I[\text{V}] = V_D + |V_{BE}| = 1.4\text{V} = \text{const}$ , za  $-3\text{V} \leq v_G \leq -1.4\text{V}$  (IOP- lin. režim,  $D_1$ -OFF,  $Q_1$ -OFF,  $D_2$ -ON,  $Q_2$ -DAR);

$v_I[\text{V}] = -v_G[\text{V}]$ , za  $-1.4\text{V} \leq v_G \leq 1.4\text{V}$  (IOP-lin. režim,  $D_1$ -OFF,  $Q_1$ -OFF,  $D_2$ -OFF,  $Q_2$ -OFF);

$v_I[\text{V}] = -V_D - |V_{BE}| = -1.4\text{V} = \text{const}$ , za  $1.4\text{V} \leq v_G \leq 3\text{V}$  (IOP- lin. režim,  $D_1$ -ON,  $Q_1$ -DAR,  $D_2$ -OFF,  $Q_2$ -OFF).