

REŠENJA ZADATAKA

1. a) $R_1 = 606\Omega$; $R_2 \approx 2.2k\Omega$; $R_3 = 5k\Omega$.

b) $a = \frac{v_i}{v_u} = g_{m3}R_3 \frac{g_{m1}(R_1 \parallel r_{\pi3})}{1 + g_{m1}\left(R_2 \parallel \frac{r_{\pi2}}{\beta_0 + 1}\right)} \approx 1972$.

c) $R_{ul} = r_{\pi1} + (\beta_0 + 1) \cdot \left(R_2 \parallel \frac{r_{\pi2}}{\beta_0 + 1}\right) \approx 4.97k\Omega$; $R_{izl} = R_3 = 5k\Omega$.

d) $V_I = 0$;

$v_{IMAX} = 4.8V$ (Q_3 na granici zasićenja); $v_{IMIN} = -5V$ (Q_3 na granici zakočenja);

$V_{immax} = 4.8V$.

4.

$v_I[V] = -12V = const$, za $-12V \leq v_G \leq -4,5V$ (IOP-neg. zasićenje, D -ON);

$v_I[V] = 2v_G[V] - 3$, za $-4,5V \leq v_G \leq -1,5V$ (IOP-lin. režim, D -ON);

$v_I[V] = 4v_G[V]$, za $-1,5V \leq v_G \leq 3V$ (IOP-lin. režim, D -OFF);

$v_I[V] = 12V = const$, za $3V \leq v_G \leq 12V$ (IOP-poz. zasićenje, D -OFF).