

REŠENJA ZADATAKA

1. a) $I_{C1} = 0,98\text{mA}$; $I_{C2} = 0,94\text{mA}$; $I_{C3} = I_{C4} = 0,96\text{mA}$, $R_4 = 1,88\text{k}\Omega$.

b) $a_v = \frac{v_i}{v_g} = -g_{m1} [R_2 \parallel (r_{\pi 2} + (\beta_0 + 1)(R_4 + R_p))] \cdot \frac{g_{m2}(R_4 + R_p)}{1 + g_{m2}(R_4 + R_p)} \cdot \frac{R_p}{R_p + R_4} = -68,44$.

c) $R_{ul} = r_{\pi 1} = 1,276\text{k}\Omega$; $R_{izl} = R_4 + \frac{r_{\pi 2} + R_2}{\beta_0 + 1} = 1,96\text{k}\Omega$.

4. a) $V_I = 1,59\text{V}$.

b) $R_{ul} = 1,05\text{k}\Omega$.

c) $v_{I\min} = 0,7\text{V}$; $v_{I\max} = 2,3\text{V}$; $V_{im\max} = 0,71\text{V}$.