

**REŠENJA ZADATAKA**

1. a)  $I_{D1} = 500\mu\text{A}$ ;  $V_{S1} = -2\text{V}$ ;  $V_{D1} = 5\text{V}$ .

b)  $a = \frac{v_p}{v_u} = g_{m1}(R_D \parallel R_P) = 7.5$ ;  $g_{m1} = 1\text{mS}$

c)  $v_{P\min} = -V_D - V_T = -6\text{V}$ ;  $v_{P\max} = I_{D1}(R_D \parallel R_P) = 3.75\text{V}$ ;  $V_P = 0$ ;  
 $V_{p\max} = \min\{v_{P\max} - V_P; V_P - v_{P\min}\} = 3.75\text{V}$

**4.**

$v_I[\text{V}] = V_{EE} = -12\text{V} = \text{const}$ , za  $-12\text{V} \leq v_G \leq -4,5\text{V}$  (IOP- neg. zas.,  $D_1$ -ON,  $D_2$ -OFF);

$v_I[\text{V}] = 2v_G[\text{V}] - 3$ , za  $-4,5\text{V} \leq v_G \leq -1,5\text{V}$  (IOP- lin. režim,  $D_1$ -ON,  $D_2$ -OFF);

$v_I[\text{V}] = 4v_G[\text{V}]$ , za  $-1,5\text{V} \leq v_G \leq 1,5\text{V}$  (IOP- lin. režim,  $D_1$ -OFF,  $D_2$ -OFF);

$v_I[\text{V}] = 2v_G[\text{V}] + 3$ , za  $1,5\text{V} \leq v_G \leq 4,5\text{V}$  (IOP- lin. režim,  $D_1$ -OFF,  $D_2$ -ON);

$v_I[\text{V}] = V_{CC} = 12\text{V} = \text{const}$ , za  $4,5\text{V} \leq v_G \leq 12\text{V}$  (IOP- poz. zas,  $D_1$ -OFF,  $D_2$ -ON).