

REŠENJA ZADATAKA

$$1. a) I_{C1} \approx 0.5\text{mA}; \quad I_{C2} \approx 0.5\text{mA}, \quad V_I = 0.$$

$$b) a = \frac{v_i}{v_g} = -\frac{g_{m2}R_3}{1 + g_{m2}R_3} g_{m1} [R_1 \parallel (r_{\pi 2} + (\beta_0 + 1)R_3)] \approx -35.2,$$

$$R_{ul} = r_{\pi 1} = 5\text{k}\Omega,$$

$$R_{izl} = R_3 \parallel \frac{r_{\pi 2} + R_1}{\beta_0 + 1} \approx 66\Omega.$$

$$c) V_I = 0;$$

$$v_{iMAX} \approx 0.886\text{V} \quad (Q_1 \text{ na granici zakočjenja);} \quad v_{iMIN} = -1\text{V} \quad (Q_1 \text{ na granici zasićenja);}$$

$$V_{im\max} = 0.886\text{V}.$$

4. a)

$$v_I[\text{V}] = -v_G[\text{V}], \text{ za } -10\text{V} \leq v_G \leq 0 \text{ (IOP1 - lin. režim, IOP2 - lin. režim, } D_1\text{-OFF, } D_2\text{-ON);}$$

$$v_I[\text{V}] = v_G[\text{V}], \text{ za } 0 \leq v_G \leq 10\text{V} \text{ (IOP1 - lin. režim, IOP2 - lin. režim, } D_1\text{-ON, } D_2\text{-OFF).}$$

IOP1 - levi IOP

IOP2 - desni IOP