

REŠENJA ZADATAKA

1.

$v_C [V] = 0 = const$, za $0 \leq V_{CC} \leq 1.2V$ (Q-OFF, D-OFF)

$v_C [V] = 1.154V_{CC} [V] - 1.385$, za $1.2V \leq V_{CC} \leq 3.8V$ (Q-DAR, D-ON)

$v_C [V] = V_{CC} [V] - 0.8$, za $3.8V \leq V_{CC} \leq 5V$ (Q-zasićenje, D-ON)

4.

a)

$$a = \frac{v_p}{v_u} = \frac{g_m (R_D \parallel R_P)}{1 + g_m R_1} \approx 9.42.$$

b)

$$R_{ul} = R_1 + \frac{1}{g_m} = 796.3\Omega ; \quad R_{izl} = R_D = 10k\Omega .$$

c) $V_{pm\max}^{(1)} = I_D \cdot (R_P \parallel R_D) = 2.25V$ (M_1 na granici zakočenja);

$V_{pm\max}^{(2)} = |V_{TP}| - (V_{DD} + I_0 R_D) = 3V$ (M_1 na granici triodne oblasti);

$V_{pm\max} = 2.25V$.