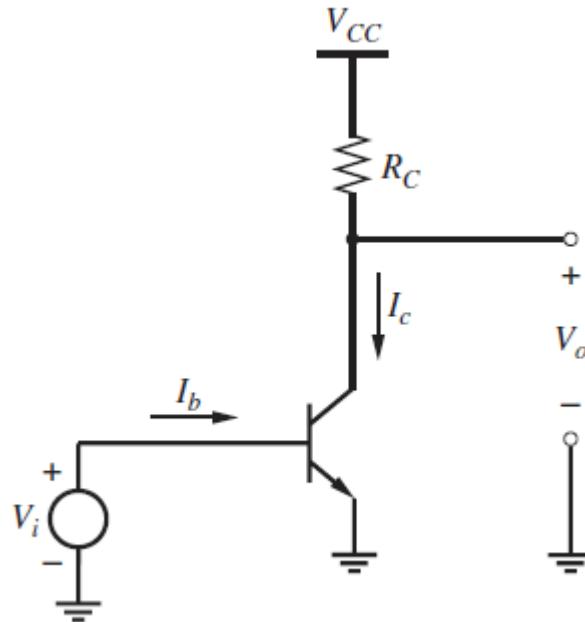


Osnove elektronike

III semestar

AKTIVNO OPTEREĆENJE



Ograničenje pojačanja pojačavača sa otpornim opterećenjem



$$A_n = -g_m R_C = -\frac{I_C R_C}{V_T} \approx -\frac{V_{CC}}{2V_T}$$

Naponsko pojačanje pojačavača sa otpornim opterećenjem je ograničeno naponom napajanja.

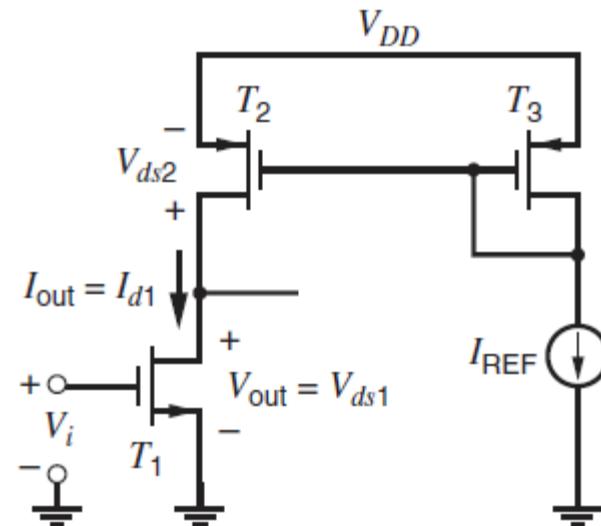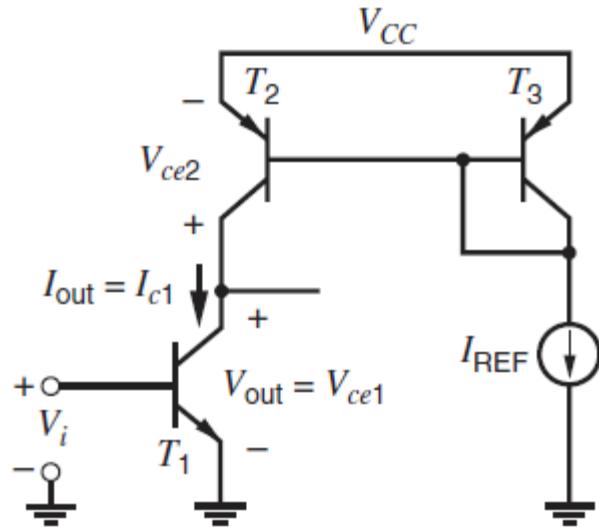Aktivno opterećenje sa bipolarnim i MOS tranzistorima



$$i_{c1} = i_{c2}$$

$$i_{c3} = I_{REF}$$

$$v_{BE1} = v_i$$

$$v_{EB2} = v_{EB3}$$

$$v_{CE1} = v_{out}$$

$$v_{EC3} = v_{EB3}$$

$$v_{EC2} = V_{CC} - v_{CE1}$$

$$I_{S2} = I_{S3}$$

Prenosna karakteristika pojačavača sa aktivnim opterećenjem

$$i_{C1} = I_{S1} \left(e^{\frac{v_{BE1}}{V_T}} - 1 \right) \left(1 + \frac{v_{CE1}}{V_{AN}} \right) = I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \left(1 + \frac{v_{out}}{V_{AN}} \right)$$

$$i_{C2} = I_{S2} \left(e^{\frac{v_{EB2}}{V_T}} - 1 \right) \left(1 + \frac{v_{EC2}}{V_{AP}} \right) = I_{S2} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{V_{CC} - v_{out}}{V_{AP}} \right)$$

$$i_{C3} = I_{S3} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{v_{EC3}}{V_{AP}} \right) = I_{S3} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{V_{EB3}}{V_{AP}} \right)$$

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \left(1 + \frac{v_{out}}{V_{AN}} \right) = I_{S2} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{V_{CC} - v_{out}}{V_{AP}} \right)$$

$$I_{REF} = I_{S3} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{V_{EB3}}{V_{AP}} \right) = I_{S2} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) \left(1 + \frac{V_{EB3}}{V_{AP}} \right)$$

$$I_{S2} \left(e^{\frac{v_{EB3}}{V_T}} - 1 \right) = \frac{I_{REF}}{1 + \frac{V_{EB3}}{V_{AP}}}$$

Prenosna karakteristika pojačavača sa aktivnim opterećenjem

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \left(1 + \frac{v_{out}}{V_{AN}} \right) = \frac{I_{REF}}{1 + \frac{V_{EB3}}{V_{AP}}} \left(1 + \frac{V_{CC} - v_{out}}{V_{AP}} \right)$$

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) = I_{REF} \frac{1 + \frac{V_{CC} - v_{out}}{V_{AP}}}{\left(1 + \frac{V_{EB3}}{V_{AP}} \right) \left(1 + \frac{v_{out}}{V_{AN}} \right)}$$

$$\frac{V_{EB3}}{V_{AP}} \ll 1 \quad \frac{v_{out}}{V_{AN}} \ll 1$$

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \approx I_{REF} \left(1 + \frac{V_{CC} - v_{out}}{V_{AP}} \right) \left(1 - \frac{V_{EB3}}{V_{AP}} \right) \left(1 - \frac{v_{out}}{V_{AN}} \right)$$

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \approx I_{REF} \left(1 + \frac{V_{CC} - v_{out}}{V_{AP}} - \frac{V_{EB3}}{V_{AP}} - \frac{v_{out}}{V_{AN}} \right)$$

$$I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right) \approx I_{REF} \left[1 + \frac{V_{CC} - V_{EB3}}{V_{AP}} - v_{out} \left(\frac{1}{V_{AP}} + \frac{1}{V_{AN}} \right) \right]$$

Prenosna karakteristika pojačavača sa aktivnim opterećenjem

$$\frac{I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right)}{I_{REF}} \approx 1 + \frac{V_{CC} - V_{EB3}}{V_{AP}} - v_{out} \left(\frac{1}{V_{AP}} + \frac{1}{V_{AN}} \right)$$

$$v_{out} \left(\frac{1}{V_{AP}} + \frac{1}{V_{AN}} \right) \approx 1 + \frac{V_{CC} - V_{EB3}}{V_{AP}} - \frac{I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right)}{I_{REF}}$$

$$v_{out} \approx \frac{\frac{V_{CC} - V_{EB3}}{V_{AP}} + 1 - \frac{I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right)}{I_{REF}}}{\frac{1}{V_{AP}} + \frac{1}{V_{AN}}}$$

$$v_{out} \approx \frac{\frac{V_{CC} - V_{EB3}}{V_{AP}} + 1 - \frac{I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right)}{I_{REF}}}{\frac{V_{AP} + V_{AN}}{V_{AP} V_{AN}}}$$

Naponsko pojačanje pojačavača sa aktivnim opterećenjem

$$v_{out} \approx (V_{CC} - V_{EB3}) \frac{V_{AN}}{V_{AP} + V_{AN}} + \frac{V_{AN}V_{AP}}{V_{AP} + V_{AN}} \left[1 - \frac{I_{S1} \left(e^{\frac{v_i}{V_T}} - 1 \right)}{I_{REF}} \right]$$

$$A_n = \frac{dv_{out}}{dv_i} \approx - \frac{V_{AN}V_{AP}}{V_{AP} + V_{AN}} \frac{I_{S1} e^{\frac{v_i}{V_T}}}{I_{REF}} \frac{1}{V_T}$$



$$\frac{I_{S1} e^{\frac{v_i}{V_T}}}{I_{REF}} = 1$$

$$A_n = \frac{dv_{out}}{dv_i} \approx - \frac{V_{AN}V_{AP}}{V_{AP} + V_{AN}} \frac{1}{V_T}$$



$$A_n = \frac{dv_{out}}{dv_i} \approx - \frac{1}{\frac{V_T}{V_{AP}} + \frac{V_T}{V_{AN}}}$$

Naponsko pojačanje pojačavača sa aktivnim opterećenjem je nezavisno od napona napajanja.

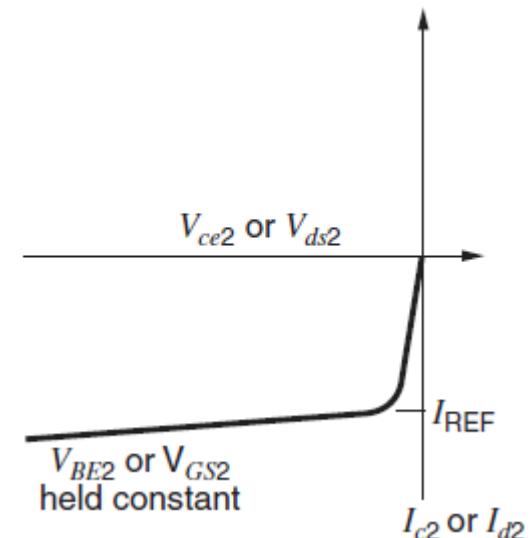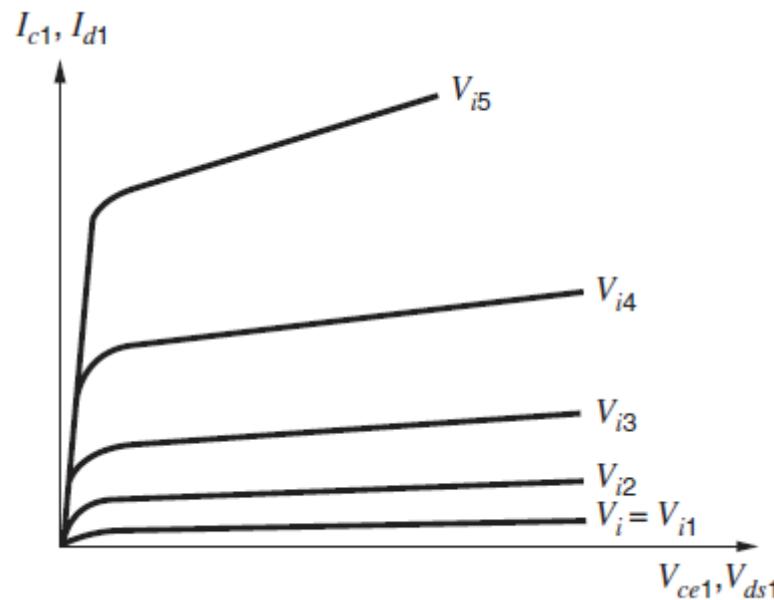
Strujno-naponska karakteristika ulaznog tranzistora i aktivnog opterećenja



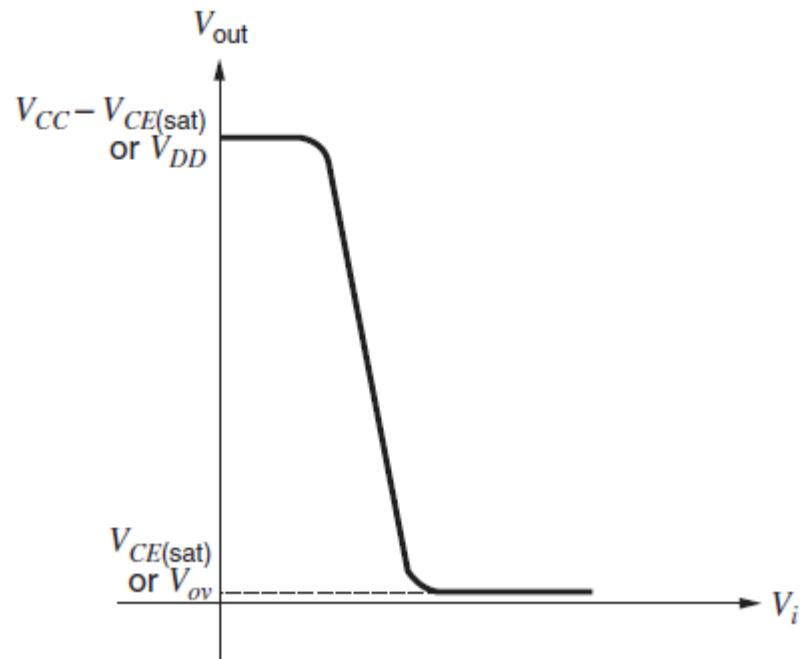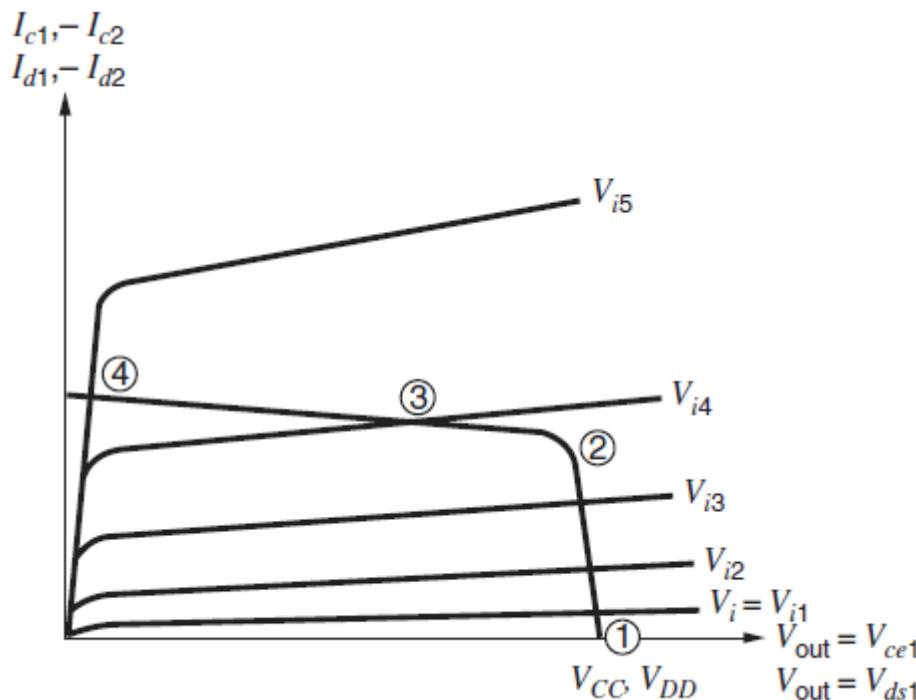Superponirane strujno-naponske karakteristike ulaznog tranzistora i aktivnog opterećenja, kao i prenosna karakteristika



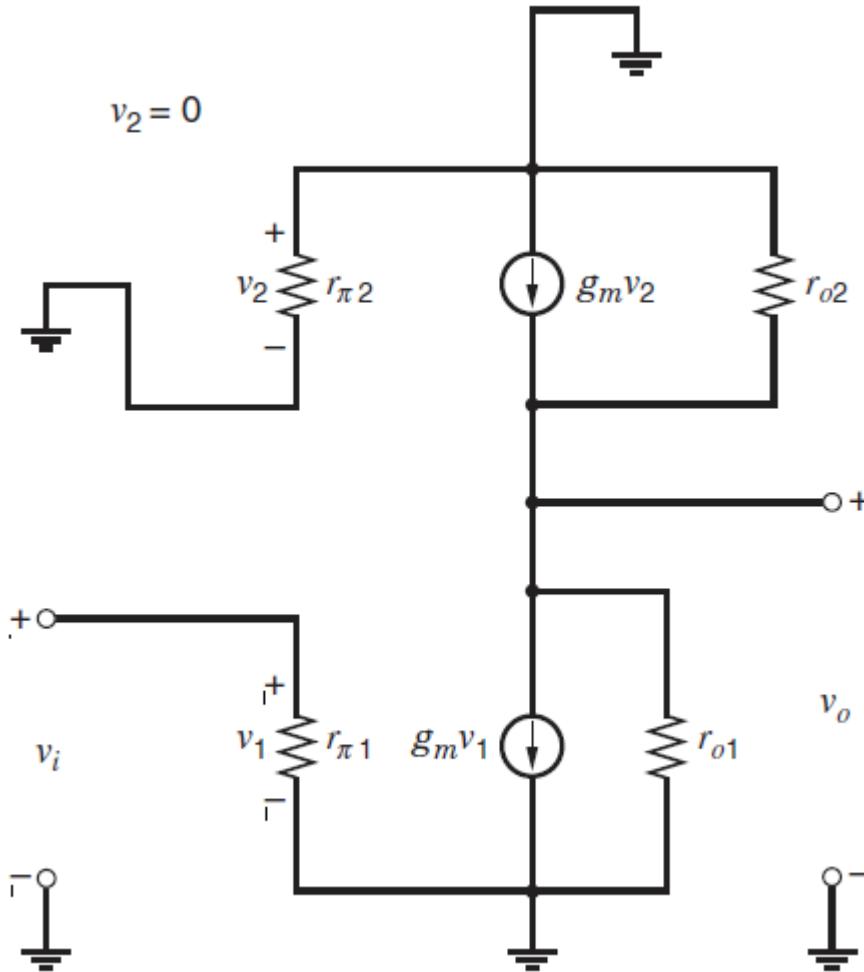Šema za male signale pojačavača sa aktivnim opterećenjem



$$R_o = r_{o1} || r_{o2}$$

$$A_v = -g_m v_2 (r_{o1} || r_{o2})$$



$$A_v = -\frac{1}{\frac{V_T}{V_{A1}} + \frac{V_T}{V_{A2}}}$$

Ista šema važi za MOSFET
ako se izbace ulazne
otpornosti:



$$r_{\pi 1} \rightarrow \infty$$

$$r_{\pi 2} \rightarrow \infty$$

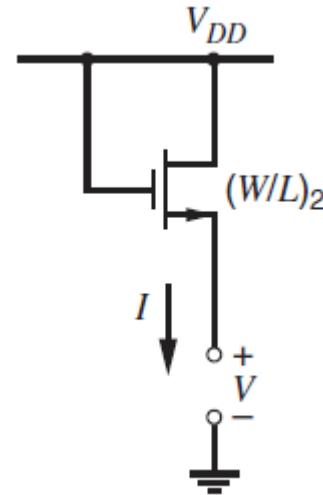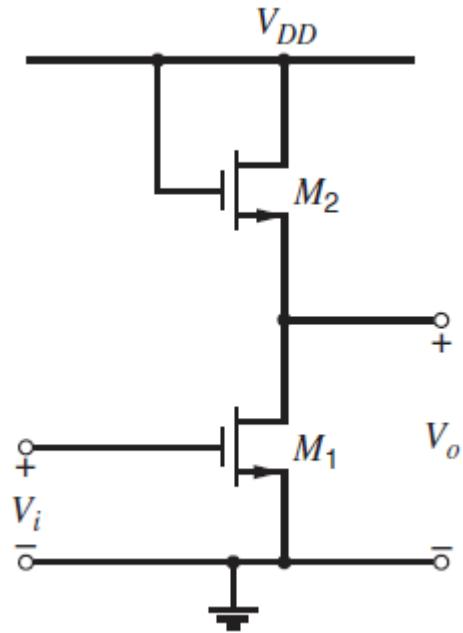Pojačavač sa MOSFET-om i kolo za određivanje struje



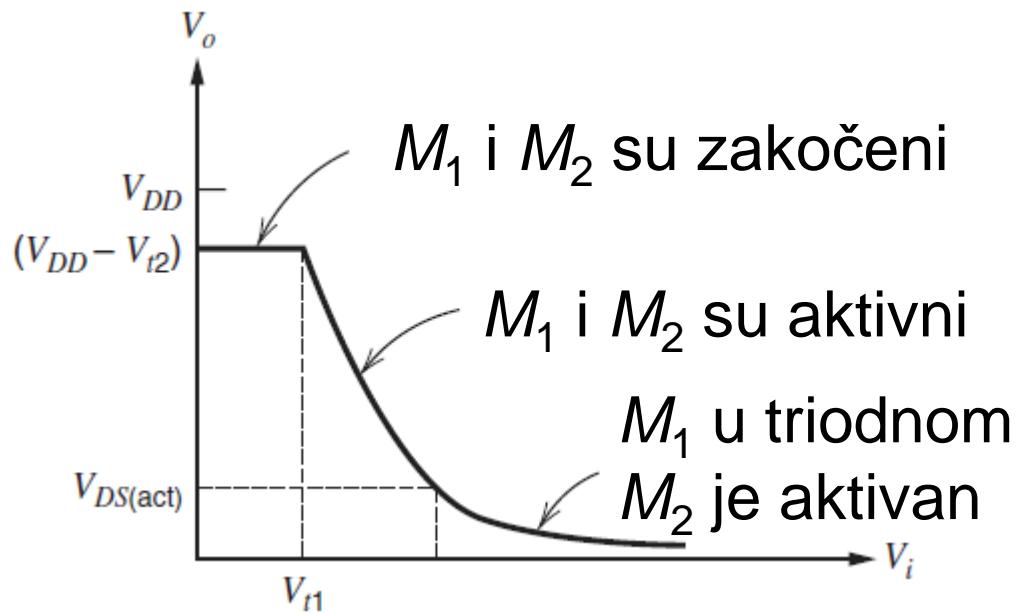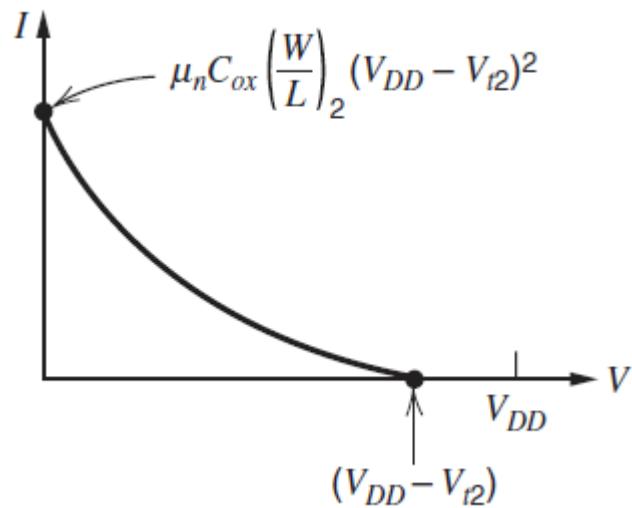Struja i prenosna karakteristika pojačavača sa MOSFET-om



Izlazni napon pojačavača sa MOSFET-om

$$i_{D1} = \frac{B_1}{2} (v_{GS1} - V_{T1})^2$$

$$B_1 = \frac{\mu_n C_{ox} W_1}{L_1}$$

$$v_{GS1} = V_{T1} + \sqrt{\frac{2i_{D1}}{B_1}}$$

$$i_{D2} = \frac{B_2}{2} (v_{GS2} - V_{T2})^2$$

$$B_2 = \frac{\mu_p C_{ox} W_2}{L_2}$$

$$v_{GS2} = V_{T2} + \sqrt{\frac{2i_{D2}}{B_2}}$$

$$v_o = V_{DD} - v_{GS2}$$

$$v_o = V_{DD} - V_{T2} - \sqrt{\frac{2i_{D2}}{B_2}}$$

$$i_{D2} = i_{D1}$$

$$v_o = V_{DD} - V_{T2} - \sqrt{\frac{2i_{D1}}{B_2}}$$


$$\sqrt{\frac{2i_{D1}}{B_1}} = v_{GS1} - V_{T1}$$

$$v_{GS1} = v_i$$

$$v_o = V_{DD} - V_{T2} - \sqrt{\frac{B_1}{B_2}} (v_{GS1} - V_{T1})$$

$$v_o = V_{DD} - V_{T2} - \sqrt{\frac{(W/L)_1}{(W/L)_2}} (v_i - V_{T1})$$

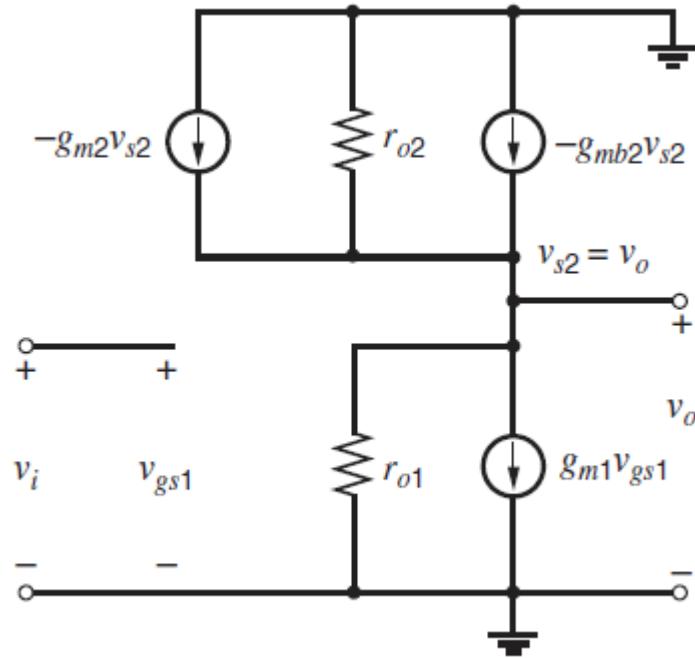Šema za male signale pojačavača sa MOSFET-om



Pojačanje za male signale pojačavača sa MOSFET-om

$$g_{m1}v_i + \frac{v_o}{r_{o1}} + \frac{v_o}{r_{o2}} + g_{m2}v_o + g_{mb2}v_o = 0$$

$$\frac{v_o}{v_i} = -g_{m1} \left(\frac{1}{g_{m2}} \left| \frac{1}{g_{mb2}} \right| r_{o1} r_{o2} \right) = -\frac{g_{m1}}{g_{m2}} \left(\frac{1}{1 + \frac{g_{mb2}}{g_{m2}} + \frac{1}{g_{m2}r_{o1}} + \frac{1}{g_{m2}r_{o2}}} \right)$$


$$g_{m2}/g_{mb2} \gg 1$$

$$g_{m2}r_{o1} \gg 1$$


$$g_{m2}r_{o2} \gg 1$$

$$\frac{v_o}{v_i} \simeq -\frac{g_{m1}}{g_{m2}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}}$$

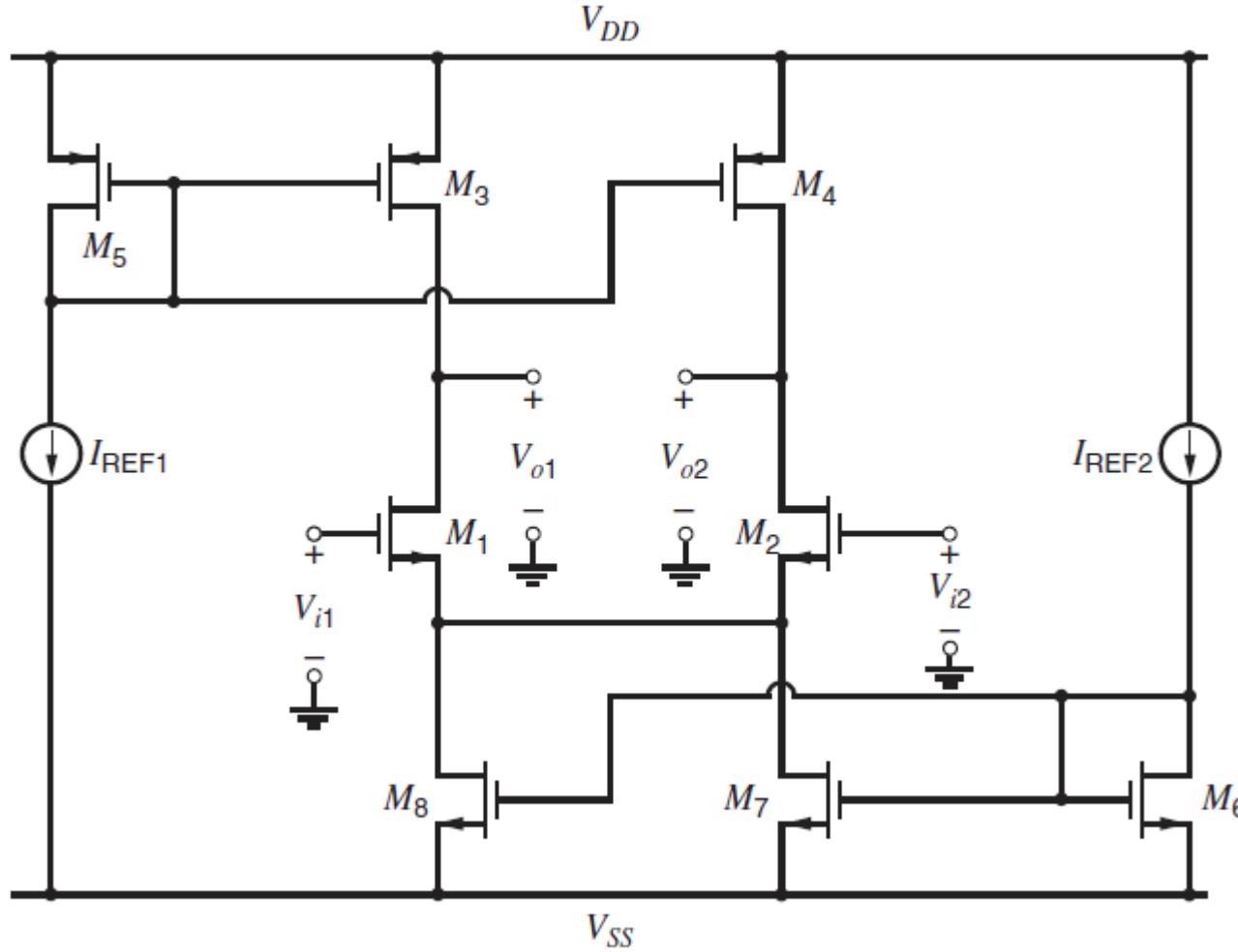
Diferencijalni par sa aktivnim opterećenjem



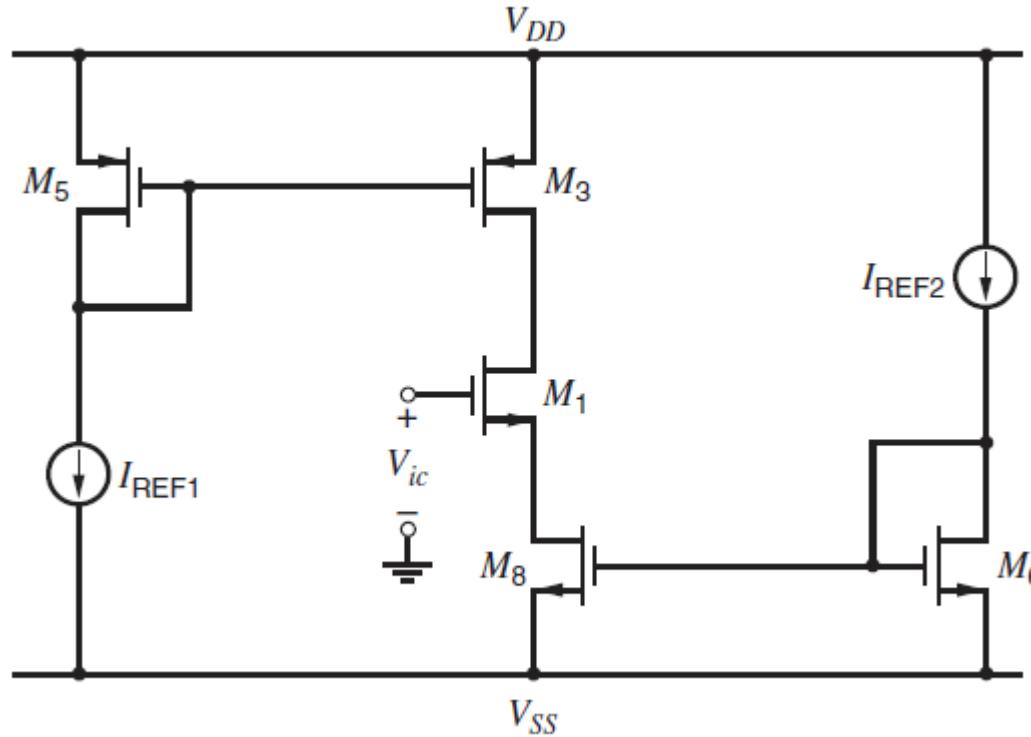
Polovina diferencijalnog para sa aktivnim opterećenjem



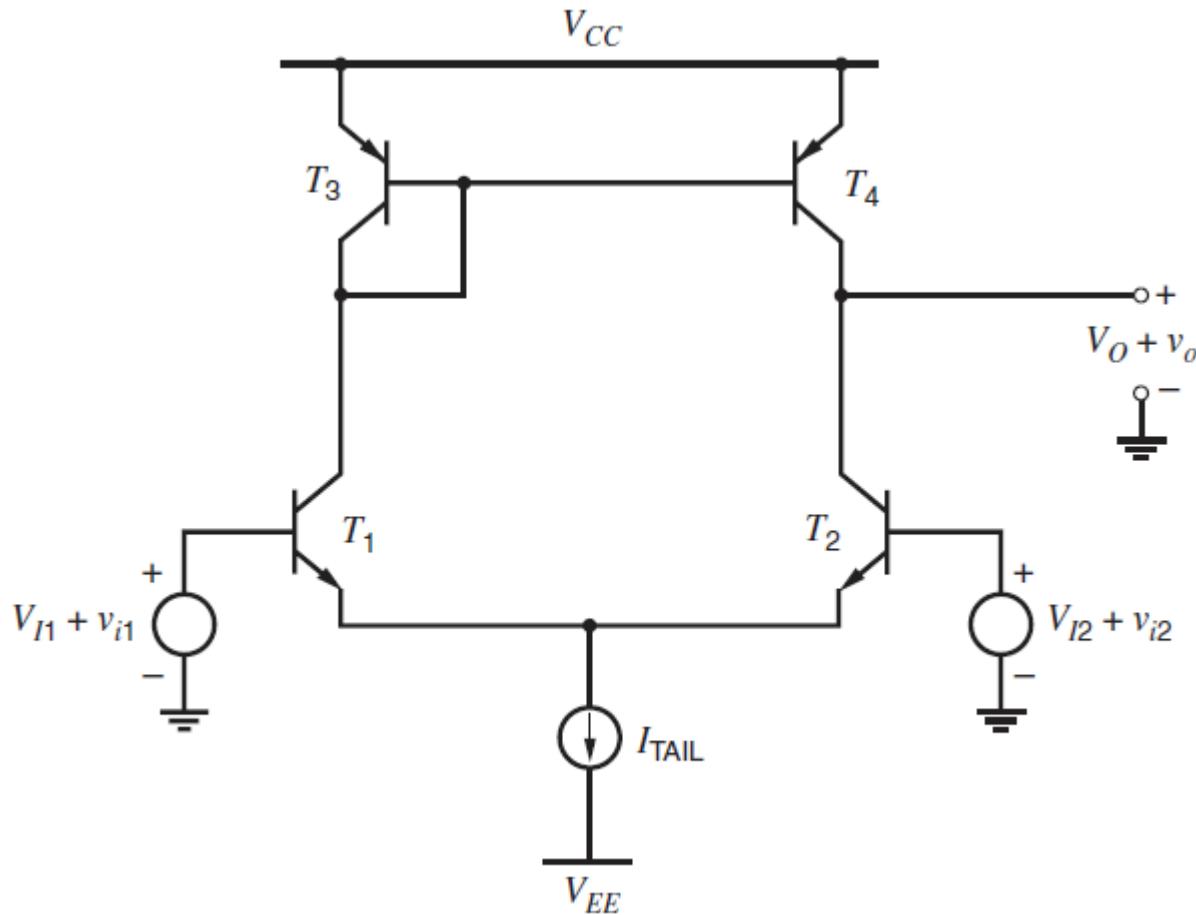Diferencijalni par sa aktivnim opterećenjem za svodenje na jednostruki izlaz



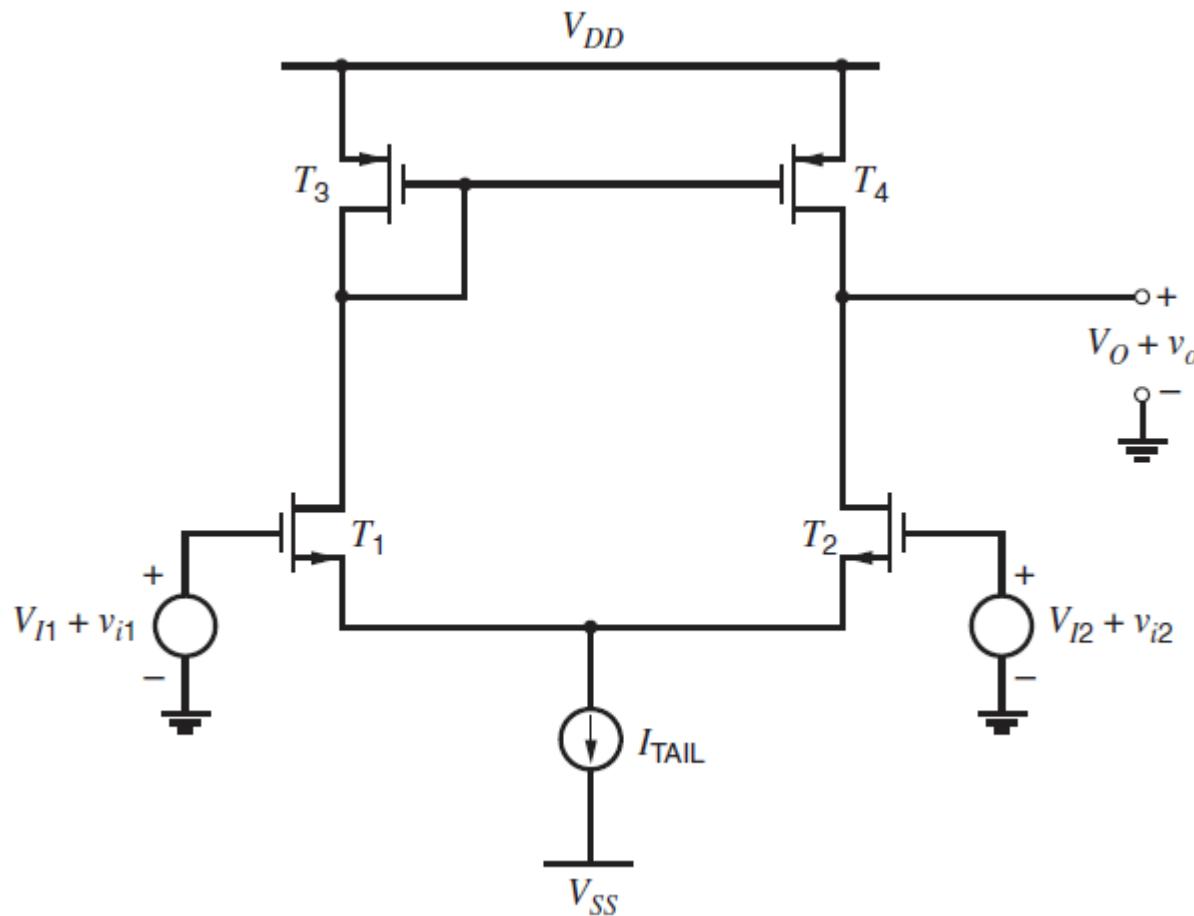Diferencijalni par sa aktivnim opterećenjem za svodenje na jednostruki izlaz



Šema za male signale diferencijalnog para sa aktivnim opterećenjem i jednostrukim izlazom

$$v_{id} = v_{i1} - v_{i2}$$

$$g_{m(dp)} = g_{m1} = g_{m2}$$

$$r_{\pi(dp)} = r_{\pi1} = r_{\pi2}$$

$$r_{o(dp)} = r_{o1} = r_{o2}$$

$$v_{i1} = v_{ic} + v_{id}/2$$


$$v_1 = \frac{v_{i1} + v_{i2}}{2} = v_{ic}$$

$$g_{m(mir)} = g_{m3} = g_{m4}$$

$$r_{\pi(mir)} = r_{\pi3} = r_{\pi4}$$

$$r_{o(mir)} = r_{o3} = r_{o4}$$

$$v_{i2} = v_{ic} - v_{id}/2$$

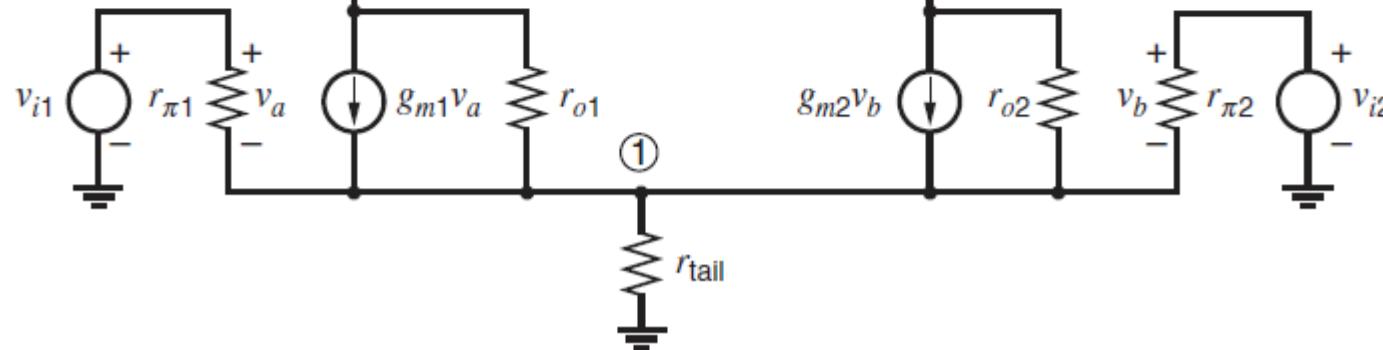


Šema za male signale diferencijalnog para sa aktivnim opterećenjem i jednostrukim izlazom

$$\beta_0 \gg 1$$

$$g_m r_o \gg 1$$

$$r_{tail} \rightarrow \infty$$

$$r_{o(dp)} \rightarrow \infty$$

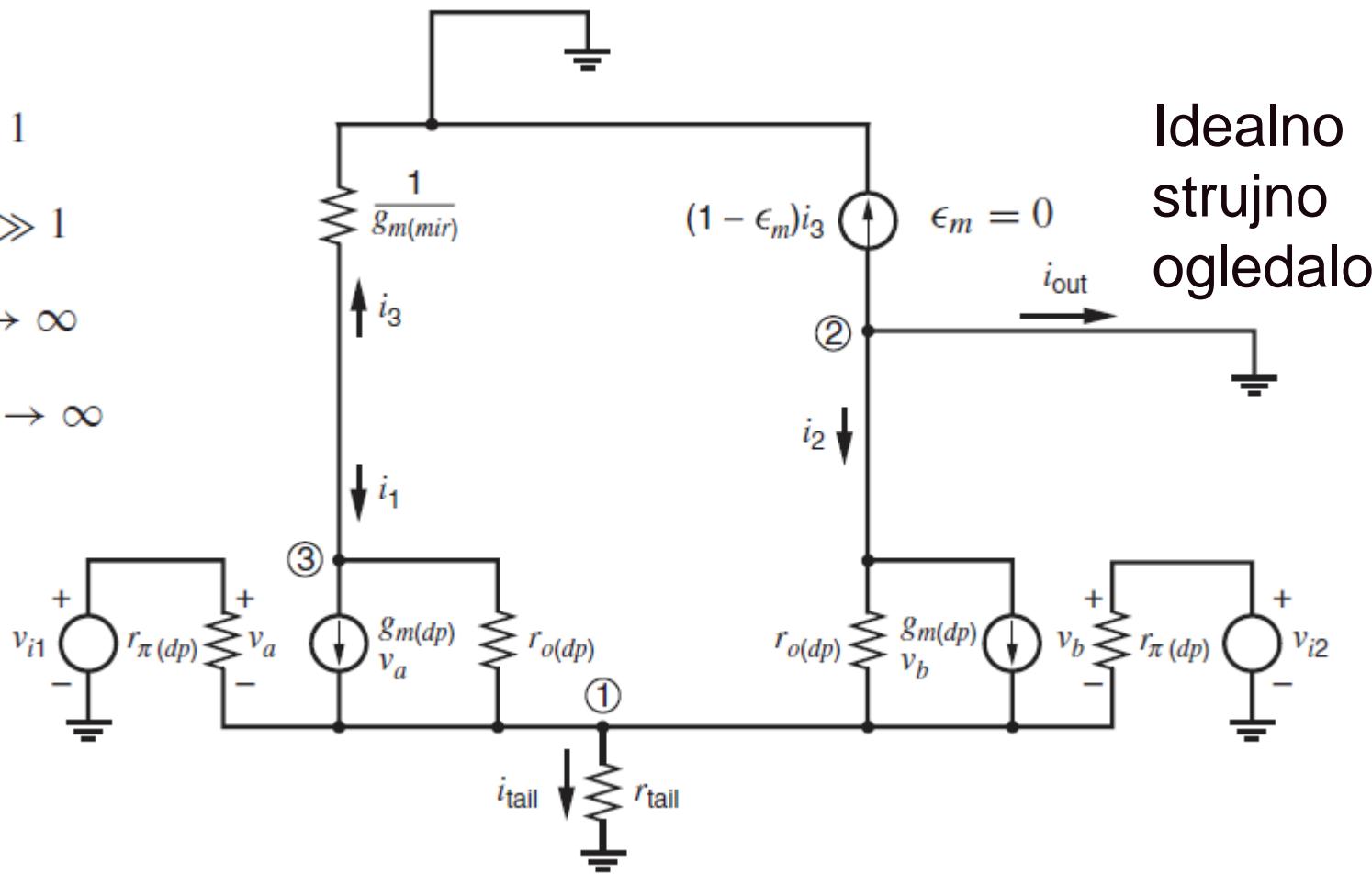

Pojačanje za male signale diferencijalnog para sa aktivnim opterećenjem i jednostrukim izlazom

$$v_3 = i_3 r_3 \simeq \frac{i_3}{g_{m3}}$$

$$(v_{i1} - v_1 + v_{i2} - v_1) \left(\frac{1}{r_{\pi(dp)}} + g_{m(dp)} \right) + \frac{v_3 - v_1}{r_{o(dp)}} - \frac{v_1}{r_{o(dp)} || r_{tail}} = 0$$

$$i_1 = g_{m(dp)}(v_{i1} - v_1) = \frac{g_{m(dp)} v_{id}}{2}$$

$$i_2 = g_{m(dp)}(v_{i2} - v_1) = -\frac{g_{m(dp)} v_{id}}{2}$$


$$i_{\text{out}} = -(1 - \epsilon_m) i_3 - i_2$$

$$\epsilon_m = 0$$

$$i_3 = -i_1$$

$$i_{\text{out}} = g_{m(dp)} v_{id}$$

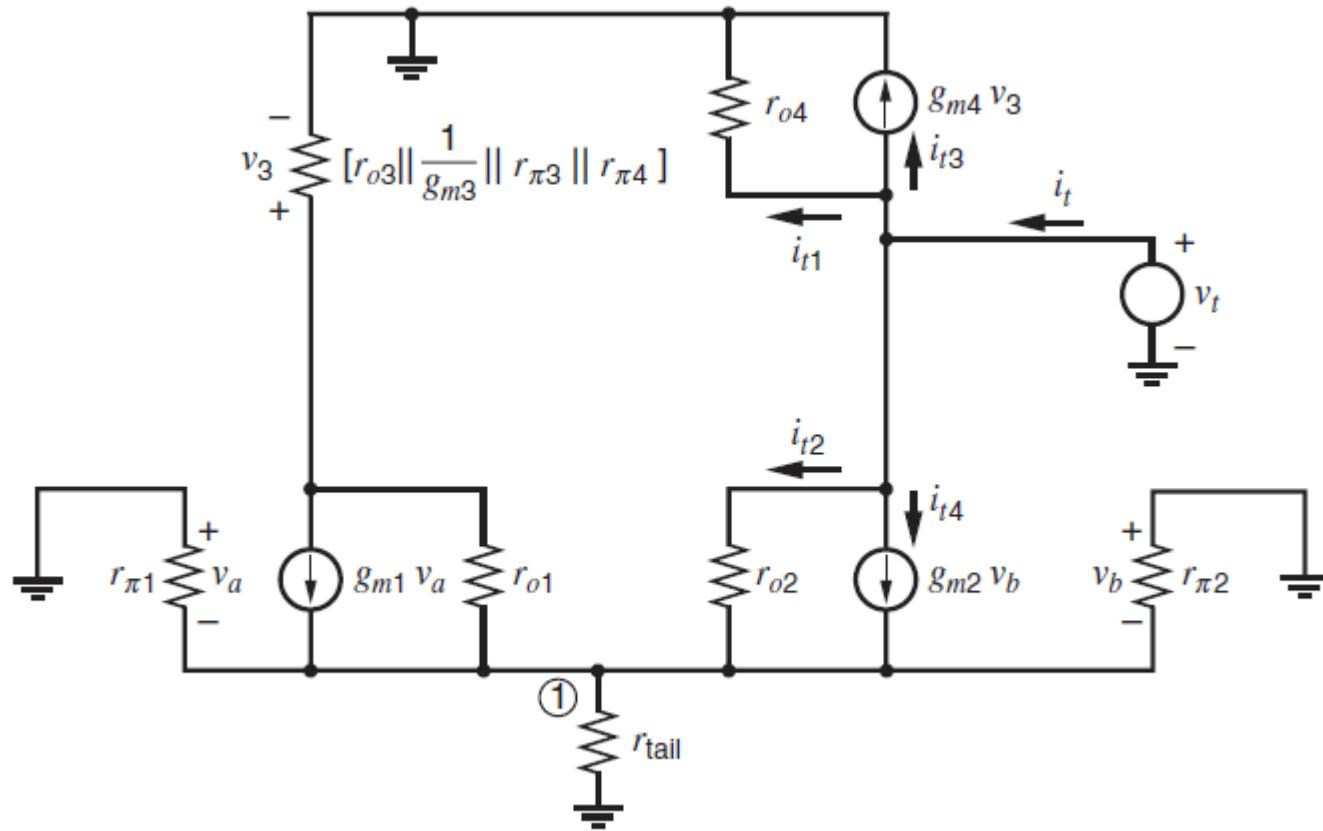Šema za određivanje izlazne otpornosti diferencijalnog para sa aktivnim opterećenjem



Izlazna otpornost diferencijalnog para sa aktivnim opterećenjem i jednostrukim izlazom

$$i_{t1} = \frac{v_t}{r_{o4}}$$

$$R_{o2} \simeq r_{o2} \left(1 + g_{m2} \frac{1}{g_{m1}} \right) = 2r_{o2}$$

$$i_{t2} + i_{t4} \simeq \frac{v_t}{2r_{o2}}$$

$$i_{t3} \simeq i_{t2} + i_{t4} \simeq \frac{v_t}{2r_{o2}}$$

$$i_t = i_{t1} + i_{t2} + i_{t3} + i_{t4} \simeq v_t \left(\frac{1}{r_{o4}} + \frac{1}{r_{o2}} \right)$$

$$R_o = \frac{v_t}{i_t} \Big|_{\substack{v_{i1}=0 \\ v_{i2}=0}} \simeq \frac{1}{\frac{1}{r_{o(dp)}} + \frac{1}{r_{o(mir)}}} = r_{o(dp)} || r_{o(mir)}$$

Efektivna izlazna otpornost T2

$$r_{tail} \gg 1/g_{m1}$$



Strujno ogledalo T3 – T4.

$$r_{o2} = r_{o(dp)}$$



Diferencijalni
pojačavač

Strujno
ogledalo

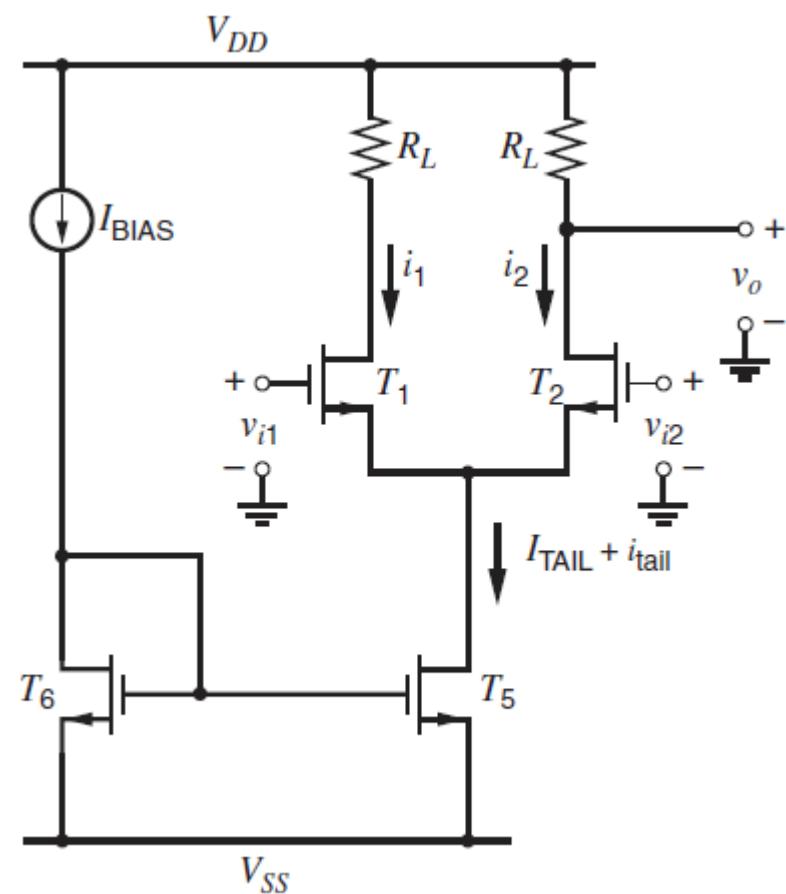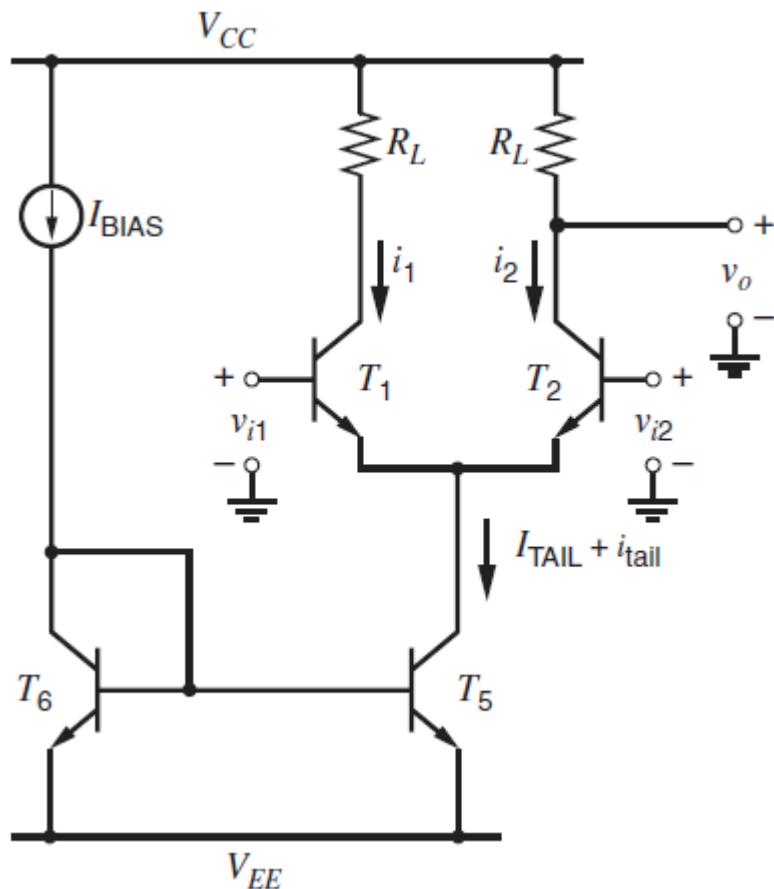Diferencijalni par sa otpornim opterećenjem i jednostrukim izlazom



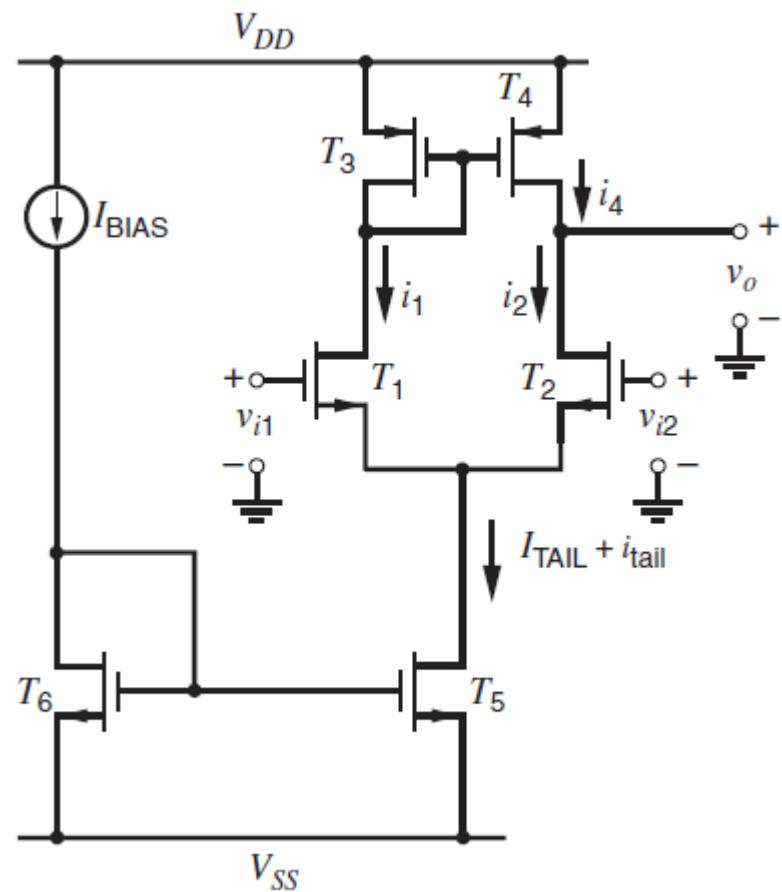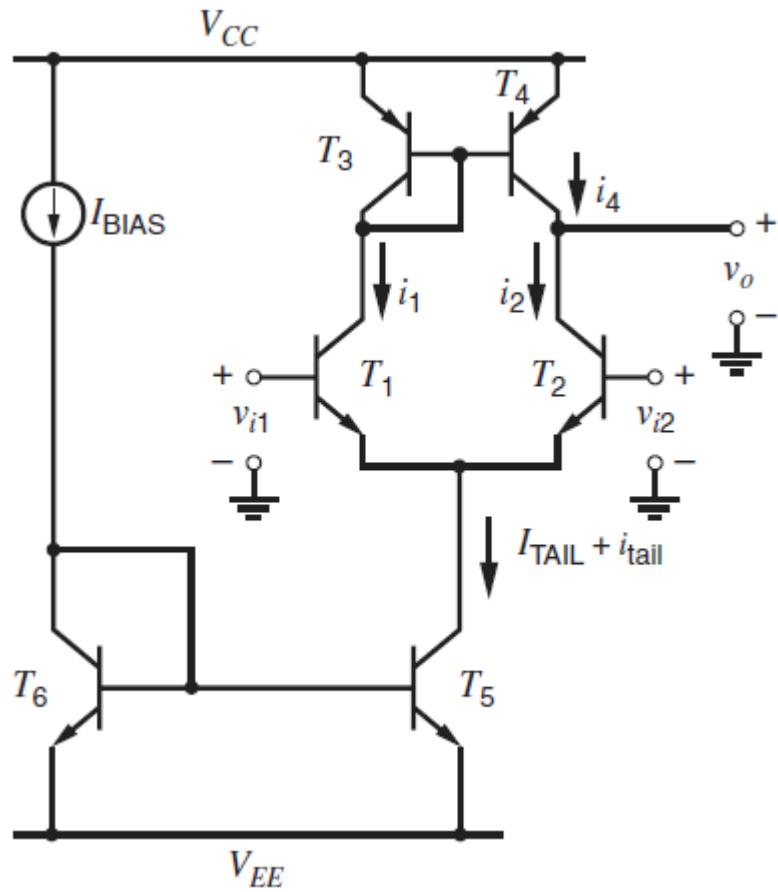Diferencijalni par sa aktivnim opterećenjem za svodenje na jednostruki izlaz



Osnove elektronike

III semestar

AKTIVNO OPTEREĆENJE