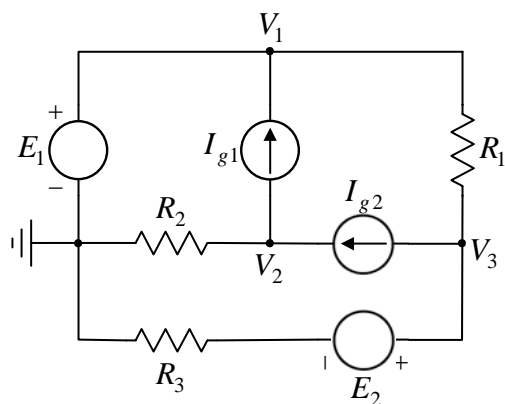


Osnovi elektronike - Odsek za SI

Ispit održan 02.02.2008. – rešenja zadatka

Prvi deo

3.



a) $V_1 = 3 \text{ V}; V_2 = 4 \text{ V}; V_3 = 6 \text{ V}$

b) $P_{R2} = 8 \text{ W}; P_{I_{g2}} = -8 \text{ W}; P_{E2} = 80 \text{ W}$

Drugi deo

3. $v(t) = 2V \cdot \cos(\omega t - 45^\circ) \Rightarrow \underline{V} = \sqrt{2} \cdot e^{-j45^\circ} V = (1 - j)V$


$i(t) = 2\sqrt{2}A \cdot \sin(\omega t) = 2\sqrt{2}A \cdot \cos(\omega t - 90^\circ) \Rightarrow \underline{I} = 2 \cdot e^{-j90^\circ} A = -j2A$

$\underline{Z}_L = j\omega \cdot 40\mu H = j2\Omega$

$\underline{Z}_C = \frac{1}{j\omega \cdot 20\mu F} = -j1\Omega$

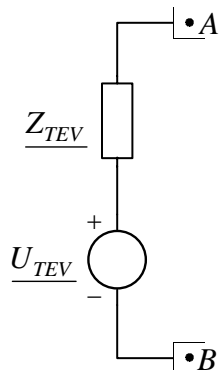a) $\underline{U}_{TEV} = (1 - 2j)V$

$\underline{Z}_{TEV} = \frac{7 + j}{10} \Omega$



$$\text{b) } \underline{S}_P = \frac{25}{14} - j \frac{25}{98}; \quad P_P = \frac{25}{14} \text{ W}; \quad Q_P = -\frac{25}{98} \text{ VAR}; \quad S_P = \frac{125\sqrt{2}}{98} \text{ VA}; \quad \cos \phi = \frac{P_P}{S_P} = \frac{7}{5\sqrt{2}}$$

Treći kolokvijum

$$\text{4. a) } I_D = 1 \text{ mA}; \quad V_G = 4 \text{ V}; \quad V_S = 1 \text{ V}; \quad V_D = 12 \text{ V};$$

$$\text{b) } g_m = \sqrt{2I_D B} = 1 \text{ mS}; \quad a_v = \frac{g_m(R_S \parallel R_P)}{1 + g_m(R_S \parallel R_P)} = 0,4545; \quad R_{ul} = R_1 \parallel R_2 = \frac{20}{3} \text{ k}\Omega;$$

$$R_{izl} = R_S \parallel \frac{1}{g_m} = 500 \Omega$$

$$\text{5. } v_I = v_2 \cdot \left(\frac{R_4}{R_3} + \frac{R_2 R_4}{R_3 R_5} + \frac{R_4}{R_5} + 1 \right) - v_1 \cdot \left(\frac{R_4}{R_3} + \frac{R_2 R_4}{R_3 R_5} + \frac{R_4}{R_5} + \frac{R_2 R_4}{R_1 R_3} \right)$$