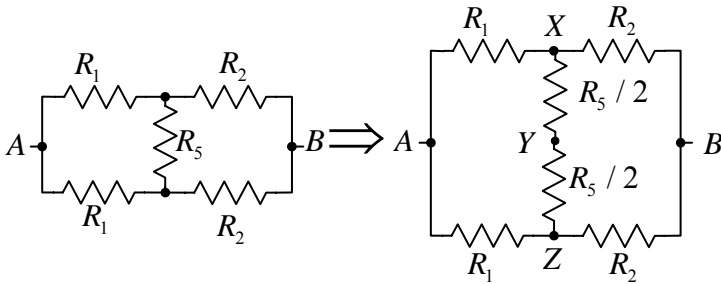


Osnovi elektronike - Odsek za SI

Januar 2009. - rešenja


1. Ako se uzme u obzir ekvivalencija otpornika, kolo se može transformisati prema sledećim slikama




Jednačine po metodi potencijala čvorova za X i Z:

$$\left. \begin{aligned} V_X(1/R_1 + 1/R_2 + 2/R_5) - V_A/R_1 - V_B/R_2 - 2V_Y/R_5 &= 0 \\ V_Z(1/R_1 + 1/R_2 + 2/R_5) - V_A/R_1 - V_B/R_2 - 2V_Y/R_5 &= 0 \end{aligned} \right\} \Rightarrow V_X = V_Z$$

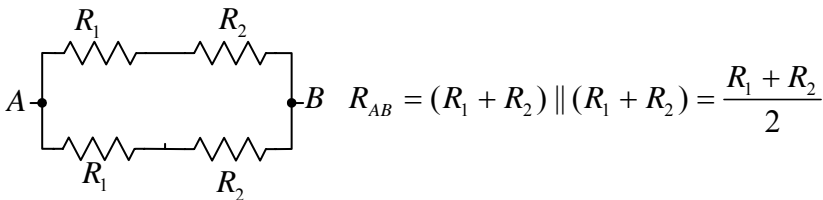Jasno je da su potencijali čvorova X i Z jednaki pa kroz R_5 ne protiče struja. Zbog toga se R_5 može ukloniti iz kola:



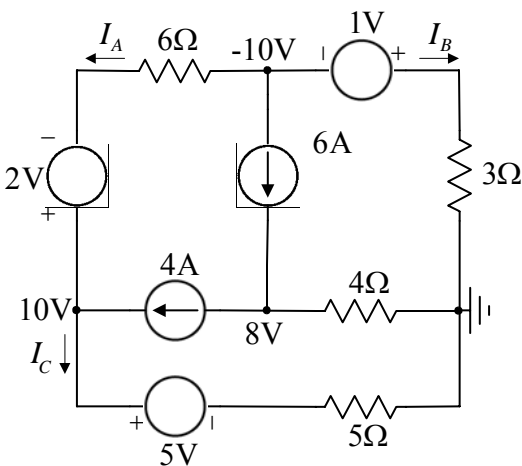2. Potencijali čvorova u kolu su prikazani na sledećoj slici:



Tražene struje su:

$$I_A = -3 \text{ A}, I_B = -3 \text{ A}, I_C = 1 \text{ A},$$

a snage koje predaju strujni generatori:

$$P_{4A} = 8 \text{ W}, P_{6A} = 108 \text{ W}.$$

3. Kako je $\cos \phi = 0.55 \Rightarrow \phi = 56.6^\circ \Rightarrow \tan \phi = 1.52$ dobija se da je bez kompenzacije

$$\tan \phi = Q / P = X / R = \omega L / R = 1.52 \Rightarrow \omega L = 15.2 \Omega$$

Kada se poveže kondenzator u paralelu, dobija se admitansa

$$Y = G + jB = Y_1 + Y_2 = j\omega C + \frac{1}{R + j\omega L} = j\omega C + \frac{R - j\omega L}{R^2 + (\omega L)^2} = 0.03 \Omega + j(\omega C - 0.046 \Omega)$$

a) $\cos \phi = 0.7 \Rightarrow \phi \approx \pm 45^\circ \Rightarrow \tan \phi \approx \pm 1$

$$\tan \phi = Q / P = -B / G = (0.046 - \omega C) / 0.03 = \pm 1 \Rightarrow \omega C = 0.016 \Omega, \text{ ili } 0.076 \Omega$$

b) $\cos \phi = 0.9 \Rightarrow \phi \approx \pm 26^\circ \Rightarrow \tan \phi \approx \pm 0.5$

$$\tan \phi = Q / P = -B / G = (0.046 - \omega C) / 0.03 = \pm 0.5 \Rightarrow \omega C = 0.031 \Omega, \text{ ili } 0.06 \Omega$$

Napomena:

Kompenzacija se može ostvariti i rednim dodavanjem kondenzatora, što se retko primenjuje u praksi.


4. $\underline{V} = (4 + j4)V$

$$\underline{I} = -j2A$$

$$\underline{Z}_L = j\omega \cdot 200 \mu H = j2 \Omega$$

a) $\underline{U}_{TEV} = j12V$


$$\underline{Z}_{TEV} = (5 + j)\Omega$$

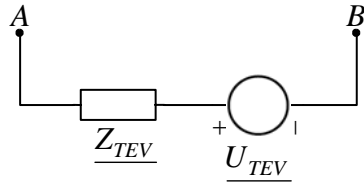

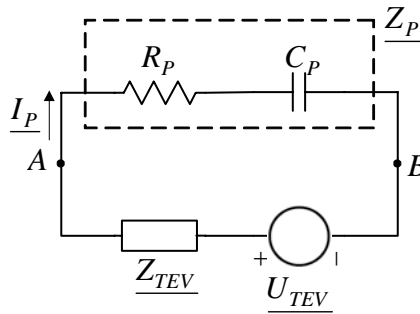b) $\underline{Z}_{C_P} = -\frac{j}{\omega C_P} = -j3 \Omega$

$$\underline{Z}_P = (1 - j3)\Omega$$

$$\underline{I}_P = \frac{\underline{U}_{TEV}}{\underline{Z}_{TEV} + \underline{Z}_P} = \left(-\frac{3}{5} + j\frac{9}{5}\right)A$$



$$\underline{S}_P = \underline{U}_P \cdot \underline{I}_P^* = \underline{Z}_P \cdot \underline{I}_P^2 = \frac{18}{5} - j\frac{54}{5}$$

$$P = \frac{18}{5} W; \quad Q = -\frac{54}{5} VAR; \quad S = \frac{18\sqrt{10}}{5} VA; \quad \cos \phi = \frac{P}{S} = \frac{1}{\sqrt{10}}$$

6. $v_I = -\frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) v_G; \quad R_4 = 10 k\Omega.$

7. Za naizmeničnu komponentu kondenzator predstavlja kratak spoj pa je $a_d = 100$, dok je za jednosmerni signal otvorena veza $A_D = 50$

Pošto je $v_D = V_D + v_d = v_2 - v_1 = 5\text{mV} - 35\text{mV} \cdot \cos(\omega t)$ dobija se da je

$$v_I = V_I + v_i = A_D \cdot 5\text{mV} - a_d \cdot 35\text{mV} \cdot \cos(\omega t) = 250\text{mV} - 3.5\text{V} \cdot \cos(\omega t)$$

8. a) $V_G = 4,8\text{ V}$; $V_S = 2,51\text{ V}$; $V_D = 7\text{ V}$; $I_D = 418\text{ }\mu\text{A}$.

b) $a_v = -\frac{g_m(R_D \parallel R_P)}{1 + g_m R_{S2}} = -4,2$; $R_{ul} = R_1 \parallel R_2 = 600\text{ k}\Omega$; $R_{izl} = R_D = 12\text{ k}\Omega$.