

**REŠENJA**

1. a)

$$\underline{Z} = \underline{V} / \underline{I} = \frac{1-j}{1+j} = \frac{(1-j)^2}{1-j^2} = \frac{1-2j+j^2}{2} = -j$$

$$R=0, X=-1, G=0, B=1, S = VI = \sqrt{2} \cdot \sqrt{2} = 2VA$$

b)

$$P = RI^2 \quad Q = XI^2 \quad S = \sqrt{P^2 + Q^2} \quad V = \frac{S}{I} = ZI$$

c) Ukupna admitansa i susceptansa potrosaca iznose

$$\underline{Y}_p = j\omega C_p - j\omega \frac{L_p}{R_p^2 + \omega^2 L_p^2} + \frac{R_p}{R_p^2 + \omega^2 L_p^2}$$

$$\underline{B}_p = \omega \left( C_p - \frac{L_p}{R_p^2 + \omega^2 L_p^2} \right)$$

Da bi se ostvarila kompenzacija reaktivne snage susceptansa treba da bude jednaka nuli  
Razlikuju se 3 slucaja:

I)  $\underline{B}_p = 0$  nema potrebe za kompenzacijom

II)  $\underline{B}_p < 0, C_p$  je malo, treba da se doda paralelno  $C = - \left( C_p - \frac{L_p}{R_p^2 + \omega^2 L_p^2} \right)$

$\underline{B}_p > 0$   $C_p$  je preveliko, treba da se doda paralelno  $L$  takoda je ispunjeno

III)  $\frac{1}{\omega L} - \omega \left( C_p - \frac{L_p}{R_p^2 + \omega^2 L_p^2} \right) = 0$

2.

$$a) V_I = \frac{(1 + \beta_F)R_E}{R_B + (1 + \beta_F)R_E} (V_{CC} - V_Z - V_{BE}) \approx \frac{6.2V}{2} = 3.1V$$

$$b) V_{CCmin} = V_\gamma + V_Z = 3.8V$$

3.

$$a) a = 5, \rho \rightarrow \infty$$


b)

$$v_I = \left( \frac{5.5R}{6.5R} \right) \left( 1 + \frac{5R}{R} \right) v_2 - \frac{5R}{R} v_1 = 5.08v_2 - 5v_1 = a_1v_1 + a_2v_2$$

$$a_s = 0.08, a_d = 5.04, \rho = 67.5$$


4. a)  $Z_{TEV} = j\Omega$

$$\underline{U}_{TEV} = -2(1+j)V$$

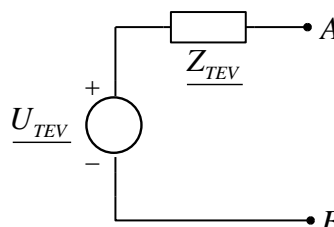

b)  $\underline{S} = 0 + j2$ ;  $P = 0$ ;  $Q = 2\text{VAr}$ .

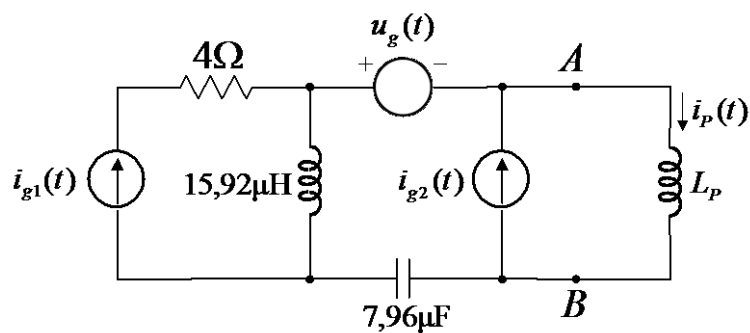c)  $\underline{I}_p = -1 + j$ ;  $i_p(t) = 2\text{A} \cos(2\pi ft + 135^\circ)$



5.  $v_o = \frac{1}{3}v_1 + \frac{1}{2}v_2$