


REŠENJA

$$1. \quad v_I = \frac{2R_2}{3R_1} v_G$$

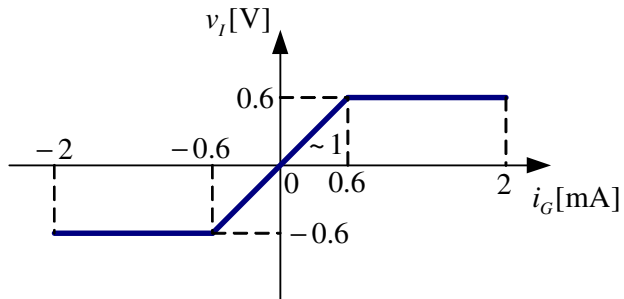3. Za $-2\text{mA} \leq i_G \leq -0.6\text{mA}$: D_1 -ON, D_2 -OFF, $v_I = -0.6\text{V} = \text{const.}$

Za $-0.6\text{mA} \leq i_G \leq 0.6\text{mA}$: D_1 -OFF, D_2 -OFF, $v_I[\text{V}] = 1 \frac{\text{V}}{\text{mA}} \cdot i_G[\text{mA}]$.

Za $0.6\text{mA} \leq i_G \leq 2\text{mA}$: D_1 -OFF, D_2 -ON, $v_I = 0.6\text{V} = \text{const.}$



5. a) $I_D = 2\text{mA}$, $V_D = 6\text{V}$, $V_S = -3\text{V}$.

b) $a_i = i_p / i_u = 0,25$.

c) $R_{ul} = 750\Omega$, $R_{izl} = 2\text{k}\Omega$.

d) $R_R = 8,5\text{k}\Omega$.