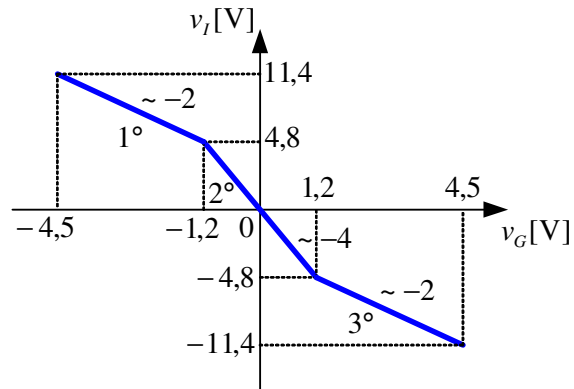


## REŠENJA ZADATAKA

1.

 $v_I[\text{V}] = -2v_G[\text{V}] + 2.4$ , za  $-4.5\text{V} \leq v_G \leq -1.2\text{V}$  (IOP- lin. režim,  $D_1$ -OFF,  $D_2$ -ON);

 $v_I[\text{V}] = -4v_G[\text{V}]$ , za  $-1.2\text{V} \leq v_G \leq 1.2\text{V}$  (IOP-lin. režim,  $D_1$ -OFF,  $D_2$ -OFF);

 $v_I[\text{V}] = -2v_G[\text{V}] - 2.4$ , za  $1.2\text{V} \leq v_G \leq 4.5\text{V}$  (IOP-lin. režim,  $D_1$ -ON,  $D_2$ -OFF);


3. a)  $I_E = 2\text{mA}$ ,  $I_B = 19,8\mu\text{A}$ ,  $I_C = 1,98\text{mA}$ ,  $V_E = -0,6\text{V}$ ,  $V_C = 6,04\text{V}$ .

b)  $a_i = i_p / i_g = 0,2475$ .

c)  $R_{ul} = 262,6\Omega$ ,  $R_{izl} = 2\text{k}\Omega$ .

5. a)  $I_1 = 4\text{mA}$ ;  $I_3 = 8\text{mA}$

b)  $B_1 = 8\text{mA/V}^2$