

REŠENJA

1. a)  $R_X = R \Rightarrow a_r = 3 + 2 \frac{R}{R_X} = 5$

b)

$$\frac{v_X - v_U}{R} = \frac{v_U}{R} \Rightarrow v_X = 2v_U$$

$$\frac{v_X}{R_X} + \frac{v_X - v_I}{R} + \frac{v_U}{R} = 0 \Rightarrow v_I = \left(3 + 2 \frac{R}{R_X}\right)v_U$$

$$a_r = \frac{v_I}{v_U} = 3 + 2 \frac{R}{R_X}$$

c) Kada pojačanje  $a \rightarrow \infty$  tada je  $a_r = 5 = 1/\beta \Rightarrow \beta = 1/5$

Kada je pojačanje  $a = 3$  tada je  $a_r = \frac{a}{1 + \beta a} = \frac{3}{1 + 3/5} = 15/8$

d)  $v_{I\max} = V_{CC} = \left(3 + 2 \frac{R}{R_{X\min}}\right)v_m \Rightarrow R_{X\min} = \frac{2R}{\frac{V_{CC}}{v_m} - 3} = 2k\Omega$

2.  $v_I[\text{V}] = \frac{1}{3}v_G[\text{V}] + 2,27$ , za  $-1,5\text{V} \leq v_G \leq 1,36\text{V}$  (D - ON)

$v_I[\text{V}] = 2v_G[\text{V}]$ , za  $1,36\text{V} \leq v_G \leq 1,5\text{V}$  (D - OFF)

3. a)  $R_2 = 4,4k\Omega$ ;  $R_3 = 1k\Omega$ ;  $R_4 = 5k\Omega$ .

b)  $a_v = 8533,3$

c)  $R_{ul} \rightarrow \infty$ ,  $R_{izl} = 5k\Omega$ .

4. a) Pošto su kolektorske struje u odnosu 1:10:100, bazne struje u DC analizi utiču sa 10% i mogu da se zanemare.  $R_1=7k$ ,  $R_3=1.2k$ ,  $R_2=12.7k$

b)

$$g_{m1} = g_{m2} = I_{C1} / V_T = 100\mu\text{A} / 25\text{mV} = 4\text{ms}$$

$$r_{\pi1} = r_{\pi2} = 25k\Omega$$

$$g_{m3} = I_{C3} / V_T = 1\text{mA} / 25\text{mV} = 40\text{ms}$$

$$r_{\pi3} = 2.5k\Omega$$

$$g_{m4} = I_{C4} / V_T = 10\text{mA} / 25\text{mV} = 400\text{ms}$$

$$r_{\pi4} = 250\Omega$$

$$a = \left(-\frac{g_{m1}}{2}(R_1 \parallel r_{\pi3})\right) \left(-g_{m3} \left(\underbrace{R_2 \parallel (r_{\pi4} + (1 + \beta_0)R_3)}_{\approx R_2}\right)\right) \left(\underbrace{\frac{g_{m4}R_3}}{1 + g_{m4}R_3}}_{\approx 1}\right) \approx 1700$$

c)  $2r_{\pi1}$

d)  $R_3 \parallel \frac{r_{\pi4} + R_2}{1 + \beta_0} \approx 130\Omega$

5.  $M_1$ -triodna oblast;  $M_2$ -zasićenje;  $V_I = 1,025\text{V}$ .