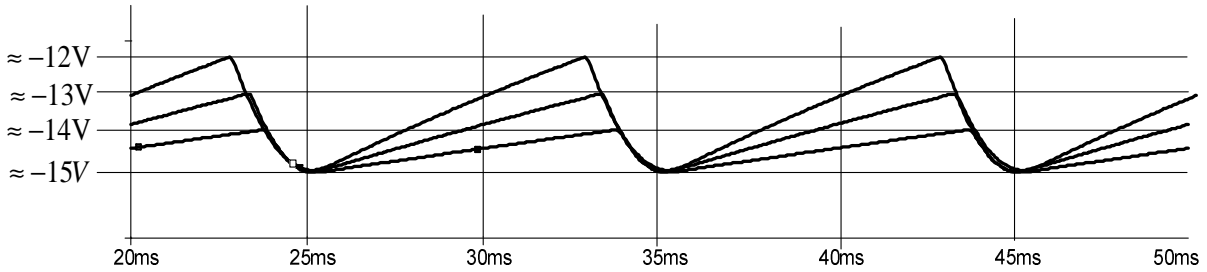



REŠENJA

1. a)  $v_g = 220\sqrt{2} \times \sin \omega t = n v_s = n \cdot 14.82V \cdot \sin \omega t, \Rightarrow n = 21.$


b)




c)

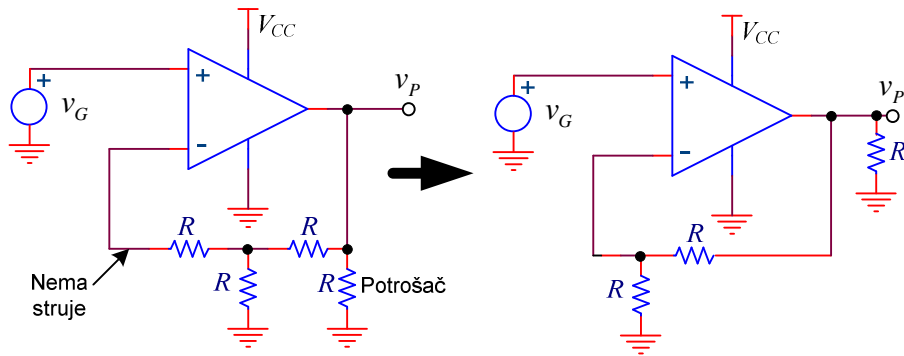

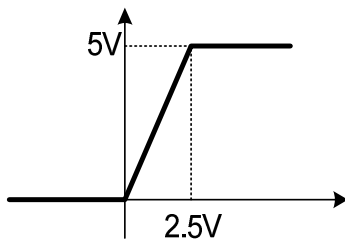Radi se o neinvertujućem pojačavaču sa pojačanjem 2!




2.  
a)

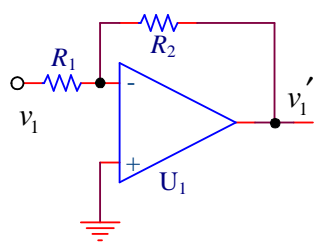

Invertujući pojačavač
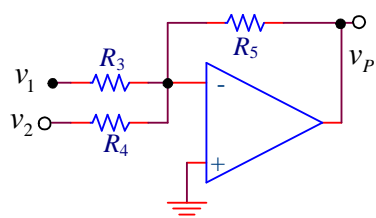
$$v_1' = -(R_2 / R_1) \cdot v_1 \Rightarrow -5V = -(R_2 / 100k\Omega) \cdot 100V \Rightarrow R_2 = 5k\Omega$$



Sabirac

$$v_P = -\frac{R_5}{R_3} v_1 - \frac{R_5}{R_4} v_2 = \frac{R_5}{R_3} \frac{R_2}{R_1} v_1 - \frac{R_5}{R_4} v_2$$

$$a_s = k_1 + k_2 = 0 = \frac{R_5}{R_3} \frac{R_2}{R_1} - \frac{R_5}{R_4}$$

$$\frac{1}{R_3} \frac{R_2}{R_1} - \frac{1}{R_4} = \frac{1}{R_3} \frac{R_2}{1} - \frac{1}{1} = 0 \Rightarrow R_3 = R_2 = 5k\Omega$$

b)


$$v_P = \frac{R_5}{R_3} \frac{R_2}{R_1} v_1 - \frac{R_5}{R_4} v_2$$

$$a_s = k_1 + k_2 = \frac{300}{100} - \frac{300}{101} \approx 0.03$$


$$a_D = \frac{k_1 - k_2}{2} = \frac{150}{100} + \frac{150}{101} \approx 3$$

$\rho \approx 100$


C)

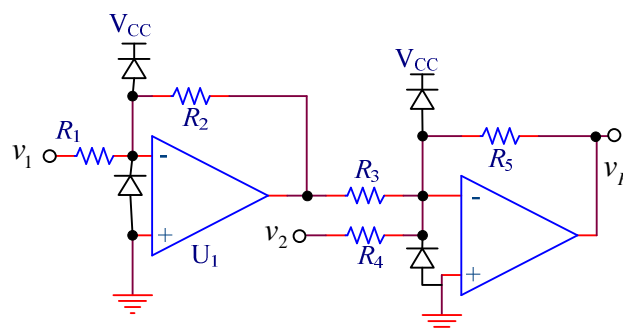

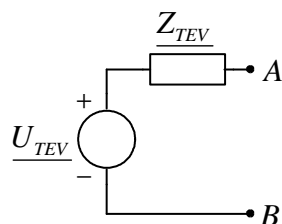3. a)  $\underline{U}_{TEV} = -j3V$ ,  $\underline{Z}_{TEV} = (1 + j)\Omega$



b)  $\underline{Z}_P = (4 - j5)\Omega$

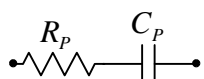

$$R_p = 4\Omega, \quad C_p = 1,06\mu F$$


c)  $i_p(t) = 0,53A \cdot \sin(2\pi ft)$

## 4. a)

Za  $-10\text{V} \leq v_G \leq 0$ :  $D - \text{OFF}$ ,  $DZ - \text{direktno polarisana}$ ,  $v_{I2} = 0 = \text{const.}$

Za  $0 \leq v_G \leq 4\text{V}$ :  $D - \text{ON}$ ,  $DZ - \text{OFF}$ ,  $v_{I2}[\text{V}] = 0,5v_G[\text{V}]$

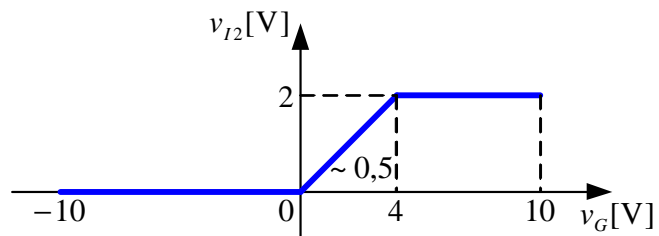Za  $4\text{V} \leq v_G \leq 10\text{V}$ :  $D - \text{ON}$ ,  $DZ - \text{proboj}$ ,  $v_{I2} = 2\text{V} = \text{const.}$



## b)

