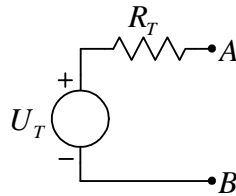


REŠENJA

1. a) $U_{AB} = -2R(I_{G1} + I_{G2})$

b) $U_T = -2R(I_{G1} + I_{G2})$

$R_T = 2R$



c) $P_{G1} = 2R(I_{G1} + I_{G2})I_{G1}$

d) $P_{5\Omega} = 0$


e) $|q| = \frac{4}{3}R(I_{G1} + I_{G2})C$

f) $R_p = R_T = 2R$

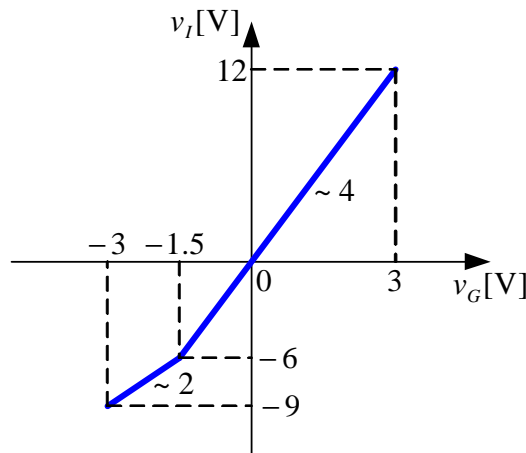2.

$v_I[V] = 2v_G[V] - 3$, za $-3V \leq v_G \leq -1,5V$ (IOP-lin. režim, D-ON);

$v_I[V] = 4v_G[V]$, za $-1,5V \leq v_G \leq 3V$ (IOP-lin. režim, D-OFF).



3. Struje I_R je struja drejnova tranzistora M_1 i M_2 ($I_{D1} = I_{D2} = I_R$), pa oni sigurno rade (provode).

Tranzistor M_2 radi u zasićenju jer su mu drejn i gejt kratkospojeni ($V_{G2} = V_{D2} = V_I$).

Za tranzistor M_1 važi $V_{GS1} = V_{G1} - V_{S1} = V_I - 0 = V_I$, dok je $V_{DS1} = V_I - V_{GS2}$.

Poznavajući struju drejna $I_{D2} = \frac{\beta_2}{2} (V_{GS2} - V_{TN})^2 = I_R$ možemo odrediti napon

$$V_{GS2} = V_{TN} + \sqrt{\frac{2I_D}{\beta_2}} = 1.3V$$

Sada na osnovu napona V_{GS1} i V_{DS1} zaključujemo da važi $V_{DS1} \leq V_{GS1} - V_{TN}$ pa je tranzistor M_1 u triodnoj oblasti.

$I_{D1} = \beta_1((V_{GS1} - V_{TN})V_{DS1} - V_{DS1}^2/2)$, zamenom izraza $V_{GS1} = V_I$ i $V_{DS1} = V_I - V_{GS2}$ u prethodnu jednačinu dobijamo $V_I^2 - 2V_I V_{TN} + 2V_{TN} V_{GS2} - V_{GS2}^2 - \frac{2I_R}{\beta_1} = 0$, tj. $V_I^2 - 2V_I + 0.64 = 0$. Dobijamo dva

rešenja $V_I = 1.6V$ i $V_I = 0.4V$. Pošto je izlazni napon ujedno i napon gejt-sors tranzistora M_1 on mora biti veći od napona praga pa je tačno rešenje $V_I = 1.6V$.

4.

a)

$$V_{GS} - V_T = \sqrt{20} = 4.47 \Rightarrow V_{GS} = 6.47V$$

$$(24V - 6.47V) / R_D = 1mA \Rightarrow R_D = 17.53k\Omega$$

b)

$$I_{B5} \approx 2\% \cdot 0.5mA = 10\mu A$$

$$I_{E5} = 101 \cdot I_{B5} \approx 1mA \Rightarrow V_I \approx 2V$$

c)

$$g_{m1} = g_{m2} = g_m = 20mS$$

$$g_{m5} = 40mS$$

$$a = \beta \cdot g_m \cdot R_E = 20000$$

d)

$$\frac{g_{m5} R_E}{1 + g_{m5} R_E} \approx 1 \Rightarrow a_1 \approx a$$

e) Sinusoida srednje vrednosti 2V amplitude 2V, sa negativnim predznakom

f) Dobija se jedinični pojačavač, AC signal je sinusoida amplitude 1V

5. a) $I_E = I_R = 1.01mA \rightarrow I_B = \frac{I_E}{(\beta_f + 1)} = 0.01mA, I_C = 1mA$

$$V_E = V_{CC} - I_C R_C - V_{CE} = 0 - I_B R_B - V_{BE}, \rightarrow R_C = \frac{V_{CC} - V_{CE} + V_{BE} + I_B R_B}{I_C} = 5k\Omega$$

$$g_m = \frac{I_C}{V_T} = 0.04S, r_{\pi} = \frac{\beta_f}{g_m} = 2.5k\Omega$$

b) $v_{be} = v_g \frac{R_B || r_{\pi}}{R_B || r_{\pi} + R_g}, v_p = -g_m v_{be} R_C || R_P$

$$a_v = \frac{v_p}{v_g} = -\frac{g_m R_C || R_P}{\frac{R_B || r_{\pi} + R_g}{R_B || r_{\pi}}} \approx -\frac{g_m R_C || R_P}{1 + \frac{R_g}{R_B || r_{\pi}}} = -26.7$$

c) $a_i = a_v \frac{R_g + R_B || r_{\pi}}{R_P} = -33.3$

d) $R_u = R_g + R_B || r_{\pi} \approx R_g + r_{\pi} = 12.5k\Omega,$
 $R_i = R_C = 5k\Omega$

