

REŠENJA

4. a) $V_Z/R_8=10\text{mA} \rightarrow V_Z=5\text{V}$.

b) $V_{out}=-105\Omega \cdot 10\text{mA} \cdot 10=-10.5\text{V}$.

c) Kada je temperatura nula na izlazu treba da bude nula, prema tome V_{ref} treba da bude jednako 10V.

d) Minimalni mogući napon na izlazu je -12V .

$-12\text{V} = -100\text{mV} \cdot T_{\max} / ^\circ\text{C} \rightarrow T_{\max} = 12\text{V} \cdot ^\circ\text{C} / 100\text{mV} = 120^\circ\text{C}$

e) $I = 10\text{mA} - \frac{10\text{mA}}{(1+\beta)^2} = 10\text{mA} \left(1 - \frac{1}{(1+\beta)^2} \right)$

5. a)

$B_1 = B_2 = B_3 = B_4 = 2\text{mA}/\text{V}^2$

$I_{D1} = I_{D2} = I_{D3} = I_{D4} = I_R = 1\text{mA}$

$V_{SG4} = |V_{T4}| + \sqrt{\frac{2I_{D4}}{B_4}} = 2\text{V}$

$V_{GS1} = V_{T1} + \sqrt{\frac{2I_{D1}}{B_1}} = 2\text{V}$

$V_{DD} - V_{SG4} - I_R R_R - V_{GS1} - V_{SS} = 0$

$R_R = \frac{V_{DD} - V_{SG4} - V_{GS1} - V_{SS}}{I_R} = 20\text{k}\Omega$

b)

$g_{m3} = \sqrt{2I_{D3}B_3} = 2\text{mS}$

$g_{m6} = \sqrt{2I_{D6}B_6} = 4\text{mS}$

$v_{gs3} = -v_u$

$v_{gs6} = -g_{m3} v_{gs3} R_{D1}$

$v_p = g_{m6} g_{m3} R_{D2} || R_P$

$A_v = -g_{m3} g_{m6} R_{D1} \cdot R_{D2} || R_P = -2\text{mS} \cdot 4\text{mS} \cdot 5\text{k}\Omega \cdot \frac{5\text{k}\Omega \cdot 15\text{k}\Omega}{20\text{k}\Omega} = -150$

c)

$i_u = -g_{m3} v_{gs3} = g_{m3} v_u$

$R_u = \frac{v_u}{i_u} = \frac{1}{g_{m3}} = 500\Omega$

$A'_v = \frac{R_u}{R_u + R_{gen}} A_v = -150 \frac{500\Omega}{500\Omega + 500\Omega} = -75$

d)

$R_i = R_{D2} = 5\text{k}\Omega$

6. a)

$I_C = \frac{V_{CC} - V_C}{R_C} = 1.5\text{mA}$


$I_B = \frac{I_C}{\beta} = 30\mu\text{A}$

$I_E = \frac{\beta + 1}{\beta} I_C = 1.53\text{mA}$

$V_{CC} - R_{B1}(I_B + I_{RB2}) - V_{BE} - R_E(I_E + I_{RB2}) = 0$

$I_{RB2} = \frac{V_{CC} - R_{B1}I_B - V_{BE} - R_E I_E}{R_{B1} + R_E} \approx 0.68\text{mA}$

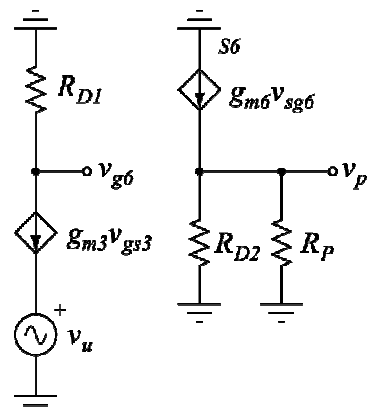$R_{B2} = \frac{V_{BE}}{I_{RB2}} \approx 1.03\text{k}\Omega$



b)


$$v_i = -g_m R_C v_{be} = -g_m R_C v_u$$

$$A_v = -g_m R_C = -\frac{I_C}{V_T} R_C = -120$$

$$i_i = \frac{v_i}{R_C} = -g_m v_u$$

$$i_u = \frac{v_u}{R_{B1} || R_{B2} || r_\pi}$$

$$A_i = \frac{i_i}{i_u} = -g_m R_{B1} || R_{B2} || r_\pi \approx -60 \text{mS} \cdot 440 \Omega \approx -26.4$$

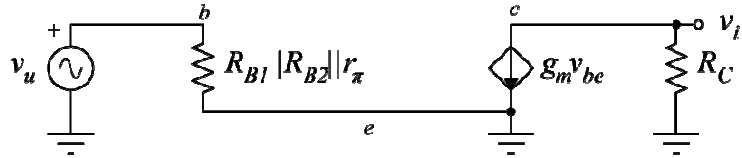

c)

$$i_u = \frac{v_u}{R_{B1} || R_{B2} || r_\pi}$$

$$R_u = \frac{v_u}{i_u} = R_{B1} || R_{B2} || r_\pi \approx 440 \Omega$$

$$A'_v = \frac{R_u}{R_u + R_{gen}} A_v \approx -62.85$$

$$v_u = 1 \text{mV} \cdot \sin \omega t$$

$$v_i = A_v v_u = -120 \text{mV} \cdot \sin \omega t$$

$$v'_i = A'_v v_u = -62.85 \text{mV} \cdot \sin \omega t$$

7. a) Svi tranzistori imajo približno istu jednosmernu struju:

$$g_m = 4 \text{mS}$$

$$r_\pi = \beta / g_m = 25 \text{k}\Omega$$

b) Tačno rešenje se dobija ako se računaju bazne struje

$$I_p = 100 \mu\text{A} \cdot 0.99 \cdot 0.98 - 100 \mu\text{A} \cdot 0.99 \cdot 0.98 \cdot 0.98 = 100 \mu\text{A} \cdot 0.99 \cdot 0.98 \cdot 0.02 = 1.9 \mu\text{A}$$

$$V_p = 19 \mu\text{V}$$

$$c) a = -g_m \cdot R_p = -0.04$$

d)

$$\underline{V}_{g1} = 1 \text{mV} / \sqrt{2}$$

$$\underline{V}_{g2} = (-2 \text{mV} / \sqrt{2}) \left(\cos \frac{\pi}{6} + j \sin \frac{\pi}{6} \right)$$

$$\underline{V}_d = \underline{V}_{g1} - \underline{V}_{g2} = \frac{1 \text{mV}}{\sqrt{2}} (\sqrt{3} + 2j) = V_d e^{j\varphi}$$

$$V_d = 1 \text{mV} \cdot \sqrt{\frac{7}{2}} \approx 1.9 \text{mV}$$

$$V_p = -0.04 V_d \approx -0.08 \text{mV}$$