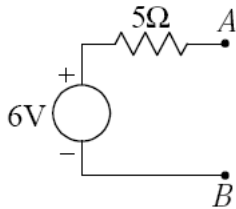



REŠENJA

1.

a) $U_{TEV1} = 6V$, $R_{TEV1} = 5\Omega$.



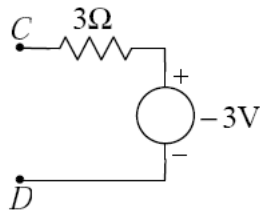b) $U_{TEV2} = -3V$, $R_{TEV2} = 3\Omega$.




c) $I_X = 0,5A$, $P_{4\Omega} = 1W$.

3.

Za $-10V \leq v_G \leq 0,7V$: $D - OFF$, $DZ - OFF$, $v_I = 0 = const.$

Za $0,7V \leq v_G \leq 7,367V$: $D - ON$, $DZ - OFF$, $v_I [V] = 0,75v_G [V] - 0,525$

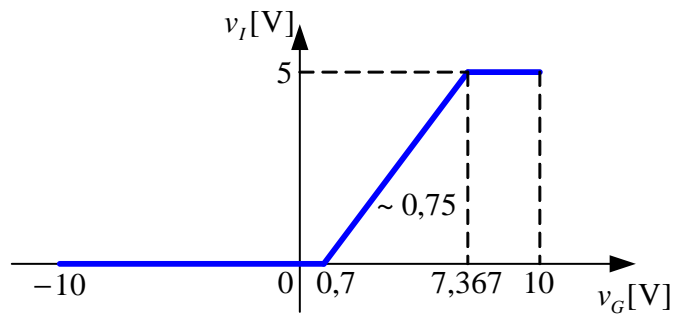Za $7,367V \leq v_G \leq 10V$: $D - ON$, $DZ - proboj$, $v_I = 5V = const.$



6. a)

$$I_D = \frac{k_p}{2} (V_{SG} - |V_P|)^2$$

$$V_{SG} = V_S - V_G$$


$$V_G = V_D = I_D R_D$$

$$V_{SG} = V_{DD} - I_D R_D$$

$$I_D = \frac{k_p}{2} (V_{DD} - I_D R_D - |V_P|)^2$$

$$I_D = 2mA$$

b)

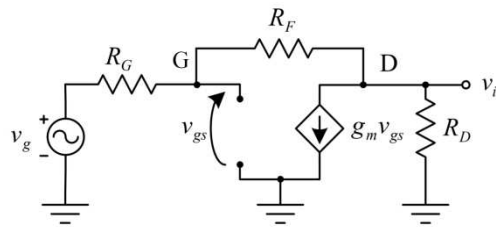


$$A_V = \frac{R_D(1 - g_m R_F)}{R_D + R_F + R_G + g_m R_D R_G} = -3.26$$

c)

$$i_g = \frac{v_g - v_i}{R_G + R_F} = \frac{v_g - A_V v_g}{R_G + R_F}$$
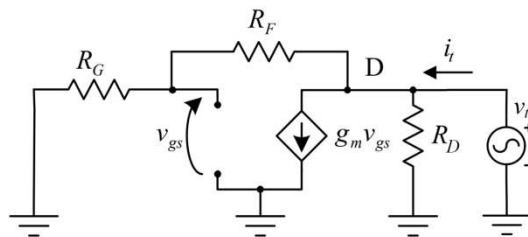
$$R_U = \frac{v_g}{i_g} = \frac{R_G + R_F}{1 - A_V} \approx 14.1 \text{ k}\Omega$$



$$i_t = g_m v_{gs} + \frac{v_t}{R_F + R_G} + \frac{v_t}{R_D}$$

$$v_{gs} = v_t \frac{R_G}{R_G + R_F}$$

$$R_i = \frac{v_t}{i_t} = \frac{1}{\frac{g_m R_G}{R_G + R_F} + \frac{1}{R_F + R_G} + \frac{1}{R_D}} \approx 983 \Omega$$