

REŠENJA

1. a)

$$U_X' = U_X(I_{G1} \neq 0, I_{G2} = 0, U_{G1} = 0, U_{G2} = 0) = 0$$

$$U_X'' = U_X(I_{G1} = 0, I_{G2} \neq 0, U_{G1} = 0, U_{G2} = 0) = -\frac{1}{2}RI_{G2}$$

$$U_X''' = U_X(I_{G1} = 0, I_{G2} = 0, U_{G1} \neq 0, U_{G2} = 0) = 0$$

$$U_X'''' = U_X(I_{G1} = 0, I_{G2} = 0, U_{G1} = 0, U_{G2} \neq 0) = \frac{1}{2}U_{G2}$$

$$U_{OUT} = U_X' + U_X'' + U_X''' + U_X'''' = \frac{1}{2}U_{G2} - \frac{1}{2}RI_{G2}$$

b)

$$P = \frac{(U_X - U_{G2})^2}{R} = \frac{(U_{G2} + RI_{G2})^2}{4R}$$

2.

$$R_{AB} = \frac{R_1 + R_3}{\beta + 1}$$

3.

a) $\underline{U}_1 = (-1 + j)V$

b) $\underline{I}_2 = (j2)A$

c) $u_3(t) = 5\sqrt{2}V \cdot \cos(20000\pi t - 53.13^\circ)$

d) $i_4(t) = \sqrt{10}A \cdot \cos(20000t + 243.43^\circ)$

4.

a)

$$V_1: V_1 = U_{G3}$$

$$V_2: -\frac{1}{R_3}V_1 + \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3}\right)V_2 - \frac{1}{R_1 + R_2}V_3 = \frac{U_{G1}}{R_1 + R_2} + I_{G1}$$

$$V_3: -\frac{1}{R_3}V_1 - \frac{1}{R_3 + R_3}V_2 + \left(\frac{1}{R_1 + R_2} + \frac{1}{R_4}\right)V_3 = \frac{U_{G1}}{R_1 + R_2} + I_{G1} - \frac{U_{G2}}{R_4}$$

$$V_1: V_1 = 2V \qquad V_1 = 2V$$

$$V_2: -\frac{1}{2}V_1 + \left(\frac{1}{4} + \frac{1}{2}\right)V_2 - \frac{1}{4}V_3 = \frac{9}{4} + 1 \qquad V_2 = 6V$$

$$V_3: -\frac{1}{1}V_1 - \frac{1}{4}V_2 + \left(1 + \frac{1}{4}\right)V_3 = \frac{9}{4} + 5 - 5 \qquad V_3 = 1V$$

b)

$$I_4 = I_1 - I_{G2} = -4A; I_2 = I_{G1} + I_{G2} = 6A$$

$$I_1 = \frac{(V_3 + U_{G1}) - V_2}{R_1 + R_2} = 1A; I_3 = \frac{V_2 - V_1}{R_3} = I_{G1} + I_1 = 2A$$

c)

$$P_{I_{G1}} = U_{I_{G1}} I_{G1} = 15W; U_{I_{G1}} = V_2 + I_{G1}(R_5 + R_6) = 15V$$

$$P_{I_{G2}} = U_{I_{G2}} I_{G2} = 80W; U_{I_{G2}} = V_3 - (-I_{G2}R_7) = 16V$$

$$P_{U_{G1}} = U_{G1} I_1 = 9W; P_{U_{G2}} = U_{G2} (-I_4) = 20W; P_{U_{G3}} = U_{G3} (-I_2) = -12W;$$

5.

a)

$$V_1: \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_4 + R_6}\right)V_1 = \frac{U_{G1}}{R_1} + I_{G1} + \frac{U_{G2}}{R_4 + R_6}$$

$$V_1: V_1 = \frac{11}{7}V = U_{AB} = E_T$$

$$\frac{1}{R_T} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} + \frac{1}{R_4 + R_6}\right)$$

$$R_T = \frac{6}{7}\Omega$$

b)

$$I_x = \frac{E_T}{R_T + R_7 + R_8} = \frac{11}{34}A$$