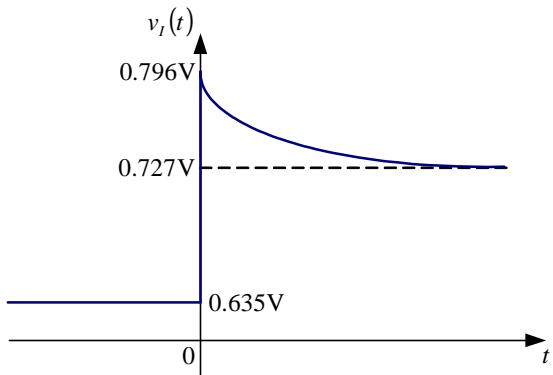


REŠENJA ZADATAKA

1. KOLOKVIJUM

2.

$$v_I(t) = \begin{cases} 0.635V = \text{const}, & \text{za } t < 0 \\ 0.727V + 0.069 \cdot e^{-\frac{t}{118.44\mu s}}, & \text{za } t > 0 \end{cases}$$



2. KOLOKVIJUM





2. $v_B(t) = 3V - 2V \cdot e^{-\frac{t}{100\mu s}}$, za $0 < t < T_1$

$$v_B(t) = 2V \cdot e^{-\frac{t-T_1}{100\mu s}}, \text{ za } T_1 < t < T_2$$

$$T_1 = 69,3\mu s$$

$$T_2 = 138,6\mu s$$

$$f = \frac{1}{T_2} = 7,21\text{kHz}$$

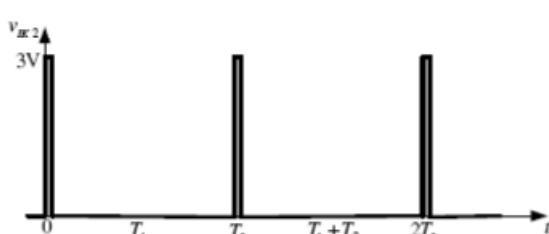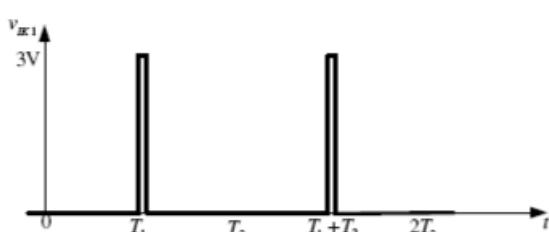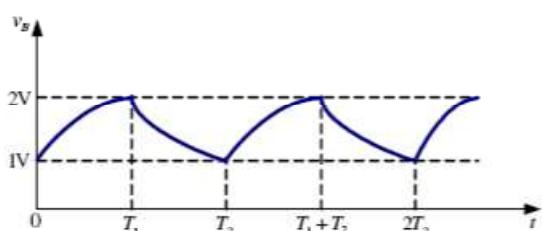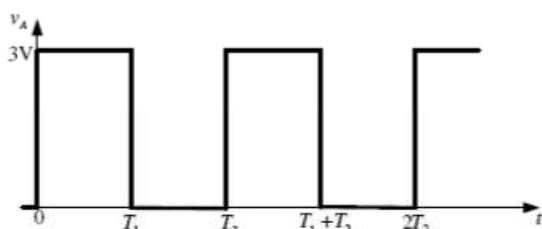

3. KOLOKVIJUM

2. $R_D = 10\text{k}\Omega$, $R_0 = 76\text{k}\Omega$, $R_1 = 33\text{k}\Omega$, $R_2 = 10,5\text{k}\Omega$, $R_3 = 750\Omega$