

REŠENJA ZADATAKA

1. KOLOKVIJUM

$$2. v_X(t) = \begin{cases} 5V, & \text{za } t < 0 \\ 5V \cdot e^{-\frac{t}{C_{UL} \cdot r_{dsNMOS}}} = 5V \cdot e^{-\frac{t}{5 \cdot 10^{-10} s}}, & \text{za } t \geq 0 \end{cases}$$

$$v_X(T_1) = 2,5V \Rightarrow T_1 = 5 \cdot 10^{-10} s \cdot \ln 2 = 347 \text{ps}$$

$$v_Y(t) = \begin{cases} 0, & \text{za } t < T_1 \\ 5V \cdot \left(1 - e^{-\frac{t-T_1}{C_M \cdot r_{dsPMOS}}}\right) = 5V \cdot \left(1 - e^{-\frac{t-T_1}{10^{-9} s}}\right), & \text{za } t \geq T_1 \end{cases}$$

$$v_Y(T_2) = 2,5V \Rightarrow T_2 = T_1 + 10^{-9} s \cdot \ln 2 = 1,04 \text{ns}$$

$$v_Z(t) = \begin{cases} 5V, & \text{za } t < T_2 \\ 5V \cdot e^{-\frac{t-T_2}{C_M \cdot r_{dsNMOS}}} = 5V \cdot e^{-\frac{t-T_2}{2 \cdot 10^{-9} s}}, & \text{za } t \geq T_2 \end{cases}$$

$$v_Z(T_3) = 2,5V \Rightarrow T_3 = T_2 + 2 \cdot 10^{-9} s \cdot \ln 2 = 2,426 \text{ns}$$

$$T_d = T_3 = 2,426 \text{ns}$$

