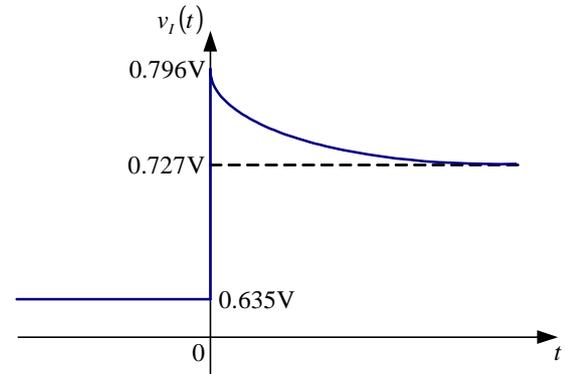


REŠENJA ZADATAKA

1. KOLOKVIJUM

2.

$$v_I(t) = \begin{cases} 0.635\text{V} = \text{const}, & \text{za } t < 0 \\ 0.727\text{V} + 0.069 \cdot e^{-\frac{t}{118.44\mu\text{s}}}, & \text{za } t > 0 \end{cases}$$



2. KOLOKVIJUM

2. za $0 < t < T_1$:


$$v_B(t) = 7,5\text{V} \cdot e^{-2000t}$$

za $T_1 < t < T_1 + T_2$:

$$v_B(t) = 5\text{V} - 7,5\text{V} \cdot e^{-2000(t-T_1)}$$

$$T_1 = 549,3\mu\text{s}$$

$$T_2 = 549,3\mu\text{s}$$

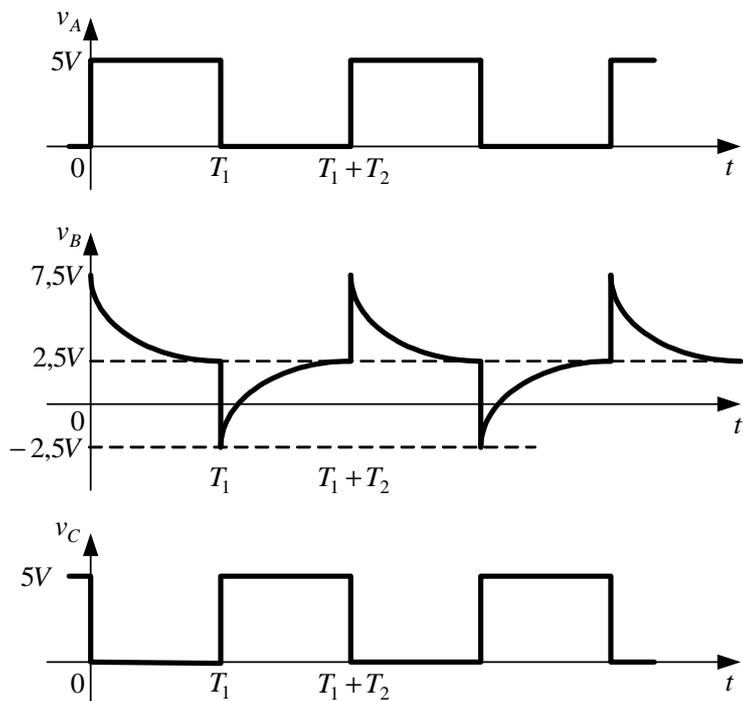

3. KOLOKVIJUM

2. a) $v_I = -\frac{3}{5} \cdot (8\overline{Q_3} + 4\overline{Q_2} + 2\overline{Q_1} + \overline{Q_0})$.

b) Analogni izlazni napon D/A konvertora je minimalan za $Q_3Q_2Q_1Q_0 = 0000$ i iznosi $v_{I\text{min}} = -9\text{V}$.

c) Analogni izlazni napon D/A konvertora je maksimalan za $Q_3Q_2Q_1Q_0 = 1111$ i iznosi $v_{I\text{max}} = 0$.