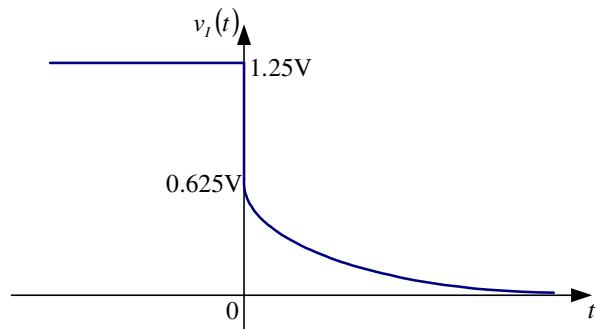


REŠENJA ZADATAKA

2.


$$v_I(t) = \begin{cases} 1.25V = \text{const}, & \text{za } t < 0 \\ 0.625V \cdot e^{-\frac{t}{100\mu s}}, & \text{za } t > 0 \end{cases}$$



4. $v_C(t) = 5V \cdot e^{-100t}$, za $0 < t < T_1$,

$$v_C(t) = 5V - 2,5V \cdot e^{-100(t-T_1)}, \text{ za } t > T_1.$$

$$T_1 = 0,01 \ln 2 = 6,93 \text{ ms}.$$

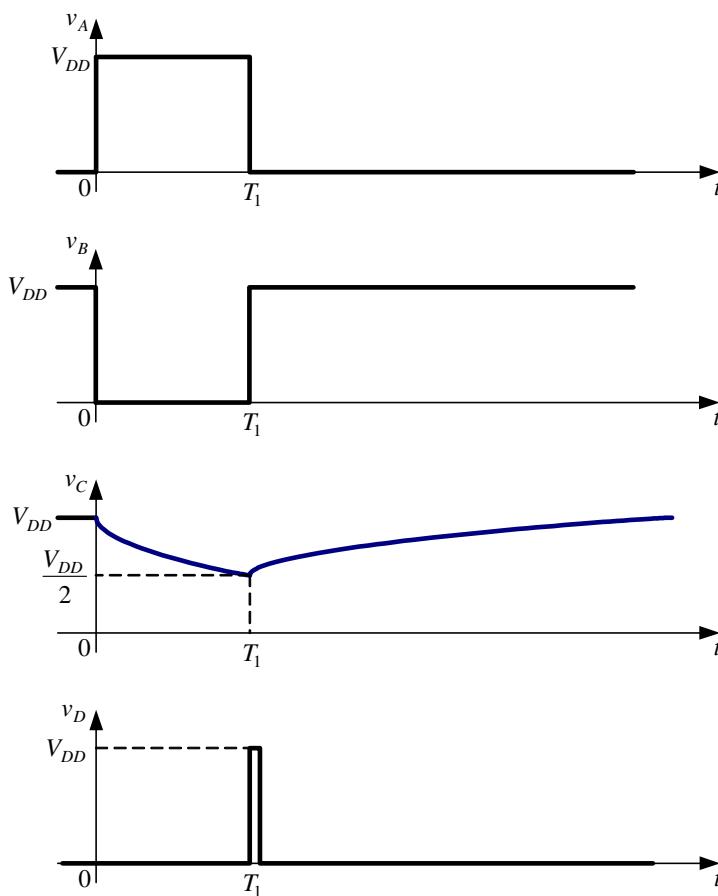

6. $R_D = 10\text{k}\Omega$, $R_0 = 76\text{k}\Omega$, $R_1 = 33\text{k}\Omega$, $R_2 = 10.5\text{k}\Omega$, $R_3 = 750\Omega$.