

REŠENJA ZADATAKA


2. a)

$$v_A(t) = \begin{cases} 3,66\text{V} \cdot e^{-2 \cdot 10^8 \cdot t}, & 0 \leq t \leq 5\text{ns} \\ 5\text{V} - 3,66\text{V} \cdot e^{-2 \cdot 10^8 \cdot (t-5\text{ns})}, & 5\text{ns} \leq t \leq 10\text{ns} \end{cases}, \text{ signal se dalje periodično ponša.}$$

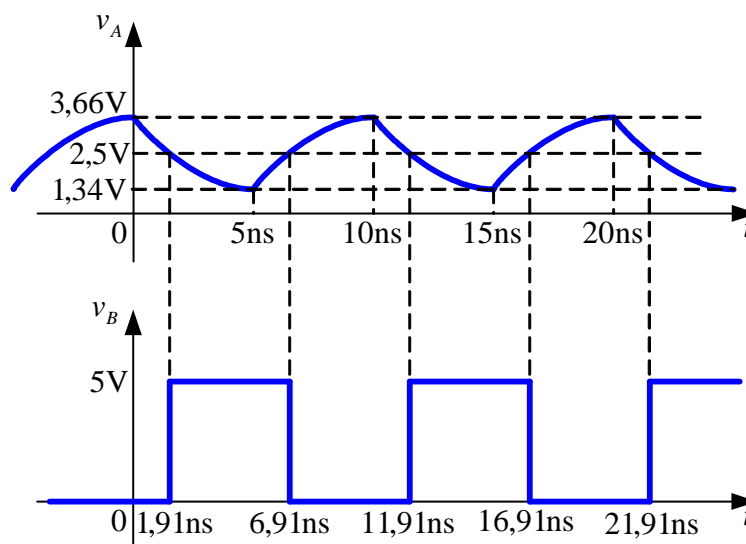b) $v_A(t_1) = 2,5\text{V}$ (za $0 < t < 5\text{ns}$) $\Rightarrow t_1 = 1,91\text{ns}$

$v_A(t_2) = 2,5\text{V}$ (za $5\text{ns} < t < 10\text{ns}$) $\Rightarrow t_2 = 6,91\text{ns}$

$$v_B(t) = \begin{cases} 5\text{V}, & 1,91\text{ns} \leq t \leq 6,91\text{ns} \\ 0, & 6,91\text{ns} \leq t \leq 11,91\text{ns} \end{cases}, \text{ signal se dalje periodično ponša.}$$



4. Za $t < 0$ je: $v_X = V_{DD}$, $v_Y = V_{DD}$, $v_Z = 0$.

Ako se zanemari Δt , za $0 < t < T_p$ je:

$$v_X = 0$$

$$v_Y(t) = V_{DD} - [V_{DD} - 0] \cdot e^{-\frac{t}{RC}} = 5V \cdot (1 - e^{-1000t})$$

$$v_Z = V_{DD}$$

Ako se zanemari Δt , za $T_p < t < 2T_p$ je:

$$v_X = 0$$

$$v_Y(t) = V_{DD} - [V_{DD} - 0] \cdot e^{-\frac{t-T_p}{RC}} = 5V \cdot (1 - e^{-1000(t-T_p)})$$

$$v_Z = V_{DD}$$

Ako se zanemari Δt , za $2T_p < t < 3T_p$ je:

$$v_X = 0$$

$$v_Y(t) = V_{DD} - [V_{DD} - 0] \cdot e^{-\frac{t-2T_p}{RC}} = 5V \cdot (1 - e^{-1000(t-2T_p)})$$

$$v_Z = V_{DD}$$

Ako se zanemari Δt , za $3T_p < t < T_1$ je:

$$v_X = 0$$

$$v_Y(t) = V_{DD} - [V_{DD} - 0] \cdot e^{-\frac{t-3T_p}{RC}} = 5V \cdot (1 - e^{-1000(t-3T_p)})$$

$$v_Z = V_{DD}$$





Ako se zanemari Δt , za $t > T_1$ je:

$$v_X = V_{DD}$$

$$v_Y(t) = V_{DD} - [V_{DD} - \frac{3V_{DD}}{2}] \cdot e^{-\frac{t-T_1}{RC}} = 5V + 2,5V \cdot e^{-1000(t-T_1)}$$

$$v_Z = 0$$

$$T_1 = 3T_p + 0,001 \ln 2 = 2,193ms$$

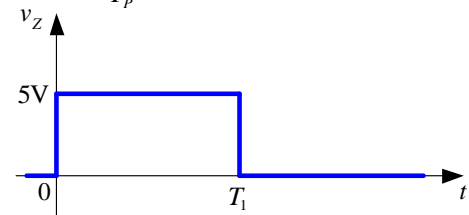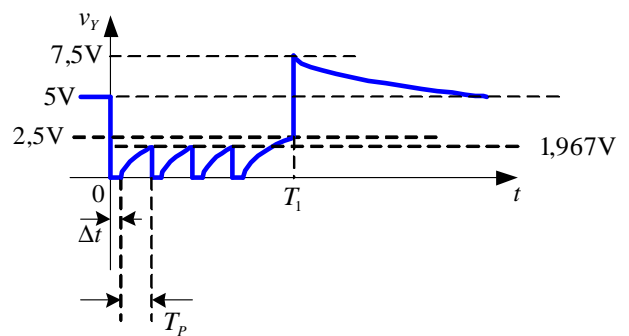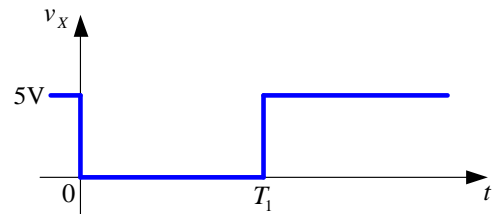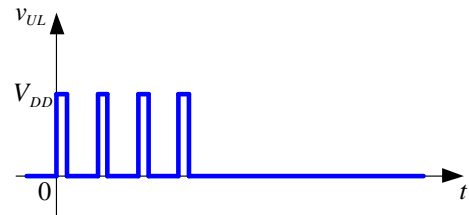

6. a) $v_{IZ} = -\frac{V_{REF}}{48R} R_f (8Q_3 + 4Q_2 + 2Q_1 + Q_0)$.

b) $R_f = 2,4k\Omega$.

S obzirom da je D/A konvertor unipolaran i da je $v_{IZ} \geq 0$, na osnovu rezultata iz tačke a) sledi da mora biti $V_{REF} < 0$.