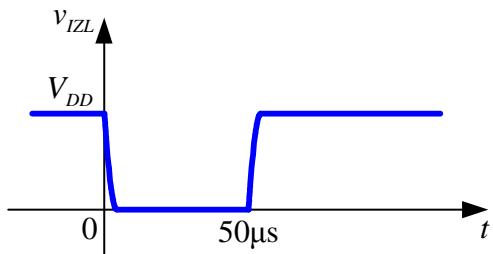


REŠENJA ZADATAKA

2.

$$v_{IZL}(t) = \begin{cases} 5V, & t < 0 \\ 5V \cdot e^{-8,333 \cdot 10^8 \cdot t}, & 0 \leq t < 50\mu s \\ 5V \cdot (1 - e^{-8,333 \cdot 10^8 \cdot (t - 50\mu s)}) & t > 50\mu s \end{cases}$$




4. a)

$$v_Y(t) = 5V - 7,5V \cdot e^{-2000t}, \text{ za } 0 < t < T_1$$

$$v_Y(t) = 7,5V \cdot e^{-2000(t-T_1)}, \text{ za } T_1 < t < T_1 + T_2$$
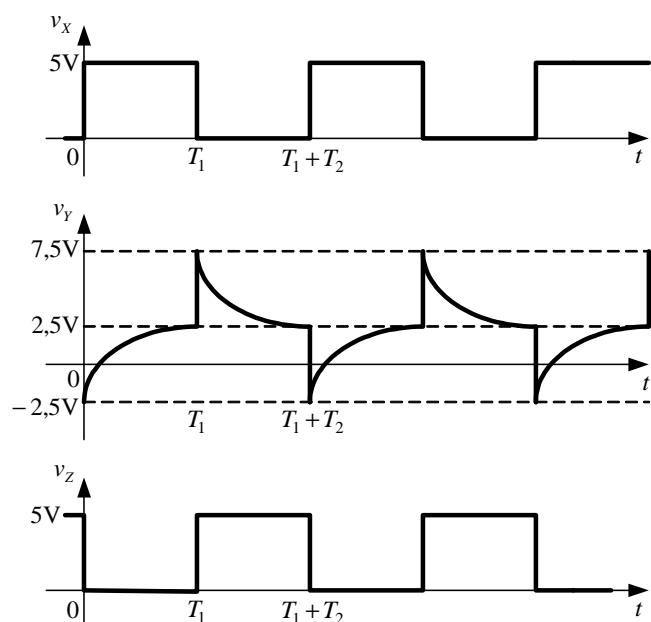
$$f = \frac{1}{T_1 + T_2} = 910,25\text{Hz}$$




b)

$$v_Y(t) = 5V - 5V \cdot e^{-2000t}, \text{ za } 0 < t < T_1$$

$$v_Y(t) = 5V \cdot e^{-2000(t-T_1)}, \text{ za } T_1 < t < T_1 + T_2$$
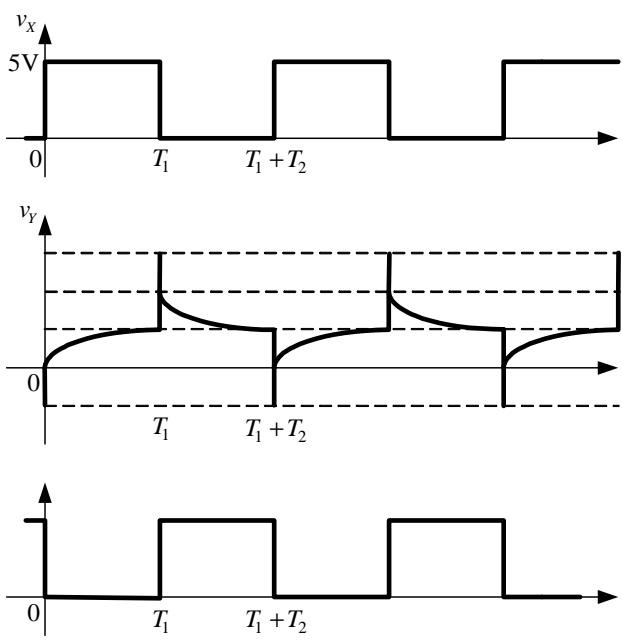
$$f = \frac{1}{T_1 + T_2} = 1443\text{Hz}$$



6. a) Prekidač je zatvoren za $Q_i = 0$, a otvoren za $Q_i = 1$.

b) $R_D = 10\text{k}\Omega$ $R_0 = 90\text{k}\Omega$ $R_1 = 40\text{k}\Omega$ $R_2 = 15\text{k}\Omega$ $R_3 = 2,5\text{k}\Omega$

c) $R_{bo} = 12,5\text{k}\Omega$ $V_{MAX} = 3,5\text{V}$ $V_{MIN} = -4\text{V}$

5.

$$A = a_2 a_1 a_0$$

$$B = b_2 b_1 b_0$$

$$\text{"1"} = V_{DD} = 5V$$

$$\text{"0"} = 0V$$

