

REŠENJA ZADATAKA

1. KOLOKVIJUM

$$2. v_X(t) = \begin{cases} 5V, & za \quad t < 0 \\ 5V \cdot e^{\frac{t}{C_{UL} \cdot r_{dsNMOS}}} = 5V \cdot e^{-\frac{t}{5 \cdot 10^{-10}s}}, & za \quad t \geq 0 \end{cases}$$

$$v_X(T_1) = 2,5V \Rightarrow T_1 = 5 \cdot 10^{-10}s \cdot \ln 2 = 347ps$$


$$v_Y(t) = \begin{cases} 0, & za \quad t < T_1 \\ 5V \cdot \left(1 - e^{\frac{t-T_1}{C_{UL} \cdot r_{dsPMOS}}}\right) = 5V \cdot \left(1 - e^{-\frac{t-T_1}{10^{-9}s}}\right), & za \quad t \geq T_1 \end{cases}$$

$$v_Y(T_2) = 2,5V \Rightarrow T_2 = T_1 + 10^{-9}s \cdot \ln 2 = 1,04ns$$

$$v_Z(t) = \begin{cases} 5V, & za \quad t < T_2 \\ 5V \cdot e^{\frac{t-T_2}{C_M \cdot r_{dsNMOS}}} = 5V \cdot e^{-\frac{t-T_2}{2 \cdot 10^{-9}s}}, & za \quad t \geq T_2 \end{cases}$$

$$v_Z(T_3) = 2,5V \Rightarrow T_3 = T_2 + 2 \cdot 10^{-9}s \cdot \ln 2 = 2,426ns$$

$$T_d = T_3 = 2,426ns$$

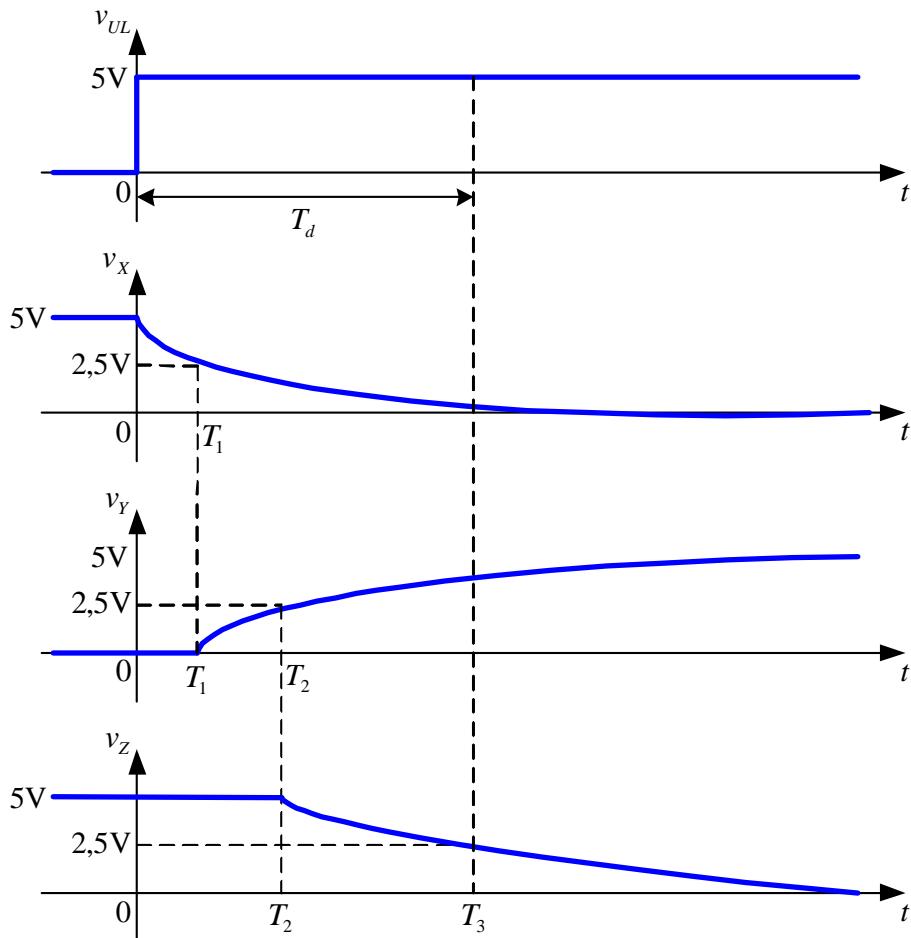



2. KOLOKVIJUM

2.

$$v_{I1} = \begin{cases} -2,4 \cdot 10^5 \cdot \left(t - \frac{T}{4} \right), & za \quad 0 \leq t \leq \frac{T}{2} \\ 2,4 \cdot 10^5 \cdot \left(t - \frac{3T}{4} \right), & za \quad \frac{T}{2} \leq t \leq T \end{cases}, \text{ signal se dalje periodično ponaša.}$$

$$T = 83,33\mu s,$$

$$f = 12\text{kHz}.$$

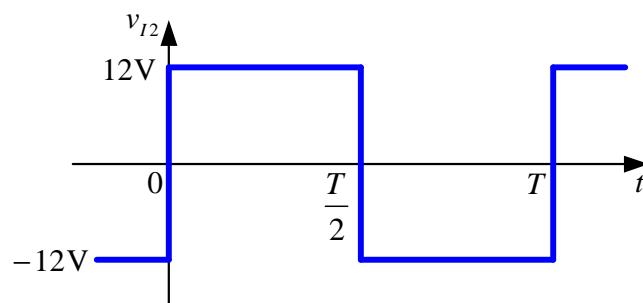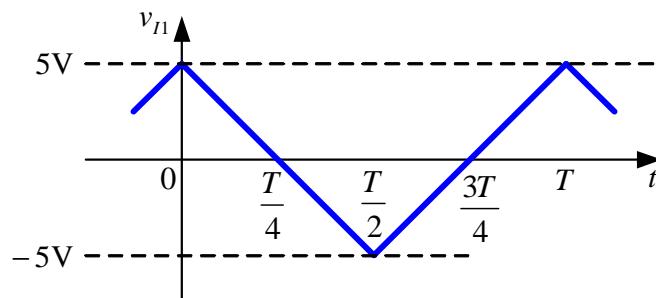

3. KOLOKVIJUM

2. a) Prekidač je zatvoren za $Q_i = 0$, a otvoren za $Q_i = 1$.

b) $R_s = 0,95\text{k}\Omega \quad R_0 = 56\text{k}\Omega \quad R_1 = 26\text{k}\Omega \quad R_2 = 11\text{k}\Omega \quad R_3 = 3,5\text{k}\Omega$

c) $R_{bo} = 1,28\text{k}\Omega \quad V_{MAX} = 5,6\text{V} \quad V_{MIN} = -6,4\text{V}$