

REŠENJA ZADATAKA


2. a)

$$v_A(t) = \begin{cases} 3,66V \cdot e^{-2 \cdot 10^8 \cdot t}, & 0 \leq t \leq 5\text{ns} \\ 5V - 3,66V \cdot e^{-2 \cdot 10^8 \cdot (t-5\text{ns})}, & 5\text{ns} \leq t \leq 10\text{ns} \end{cases}, \text{ signal se dalje periodično ponaša.}$$

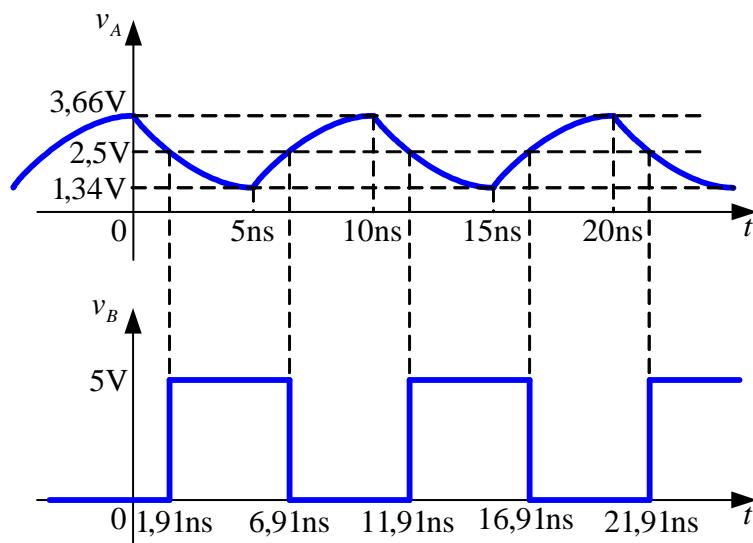b) $v_A(t_1) = 2,5\text{V}$ (za $0 < t < 5\text{ns}$) $\Rightarrow t_1 = 1,91\text{ns}$

$v_A(t_2) = 2,5\text{V}$ (za $5\text{ns} < t < 10\text{ns}$) $\Rightarrow t_2 = 6,91\text{ns}$

$$v_B(t) = \begin{cases} 5\text{V}, & 1,91\text{ns} \leq t \leq 6,91\text{ns} \\ 0, & 6,91\text{ns} \leq t \leq 11,91\text{ns} \end{cases}, \text{ signal se dalje periodično ponaša.}$$



4.





$$v_B(t) = 3\text{V} - 2\text{V} \cdot e^{-\frac{t}{100\mu\text{s}}}, \text{ za } 0 < t < T_1$$

$$v_B(t) = 2\text{V} \cdot e^{-\frac{t-T_1}{100\mu\text{s}}}, \text{ za } T_1 < t < T_2$$

$$T_1 = 69,3\mu\text{s}$$

$$T_2 = 138,6\mu\text{s}$$

$$f = \frac{1}{T_2} = 7,21\text{kHz}$$

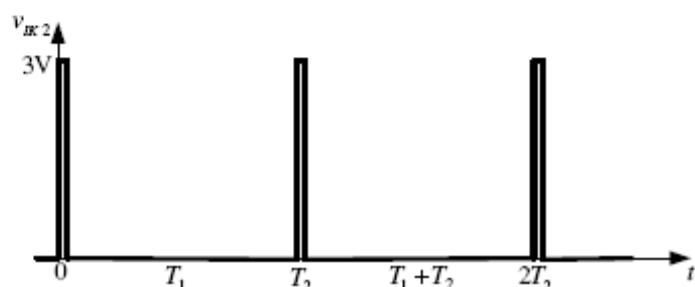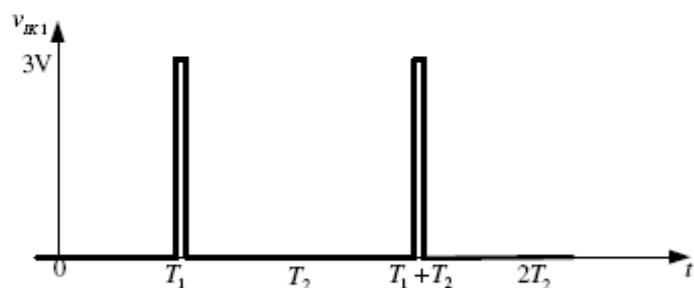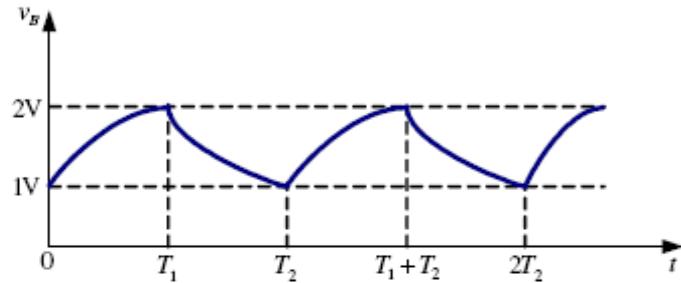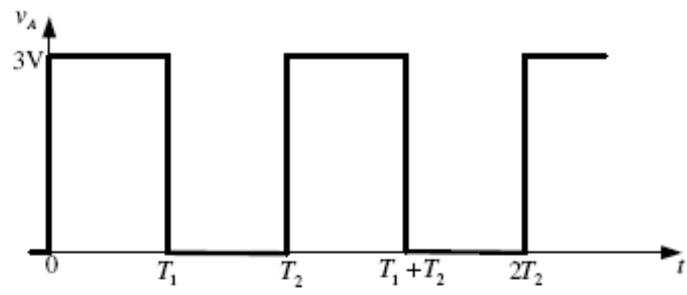

6. $R_D = 10\text{k}\Omega$, $R_0 = 76\text{k}\Omega$, $R_l = 33\text{k}\Omega$, $R_2 = 10,5\text{k}\Omega$, $R_3 = 750\Omega$