



Federal University of Santa Catarina
Center for Technology
Computer Science & Electronics Engineering

Integrated Circuits & Systems

INE 5442


Lecture 18

CMOS Sequential Circuits - 1

Prof. José Luís Güntzel
guntzel@inf.ufsc.br

CMOS Sequential Circuits

Sequential Logic

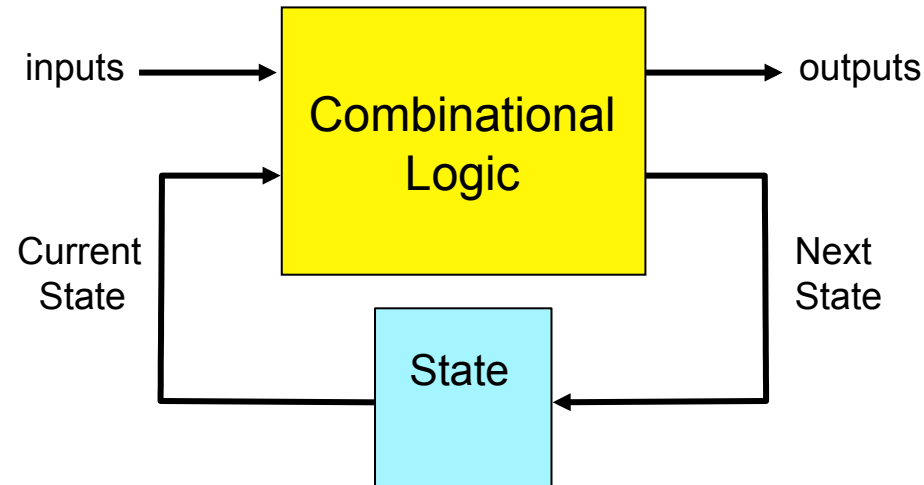


2 Storage Mechanisms:

- Positive feedback
- Charge-Based

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Sequential Logic

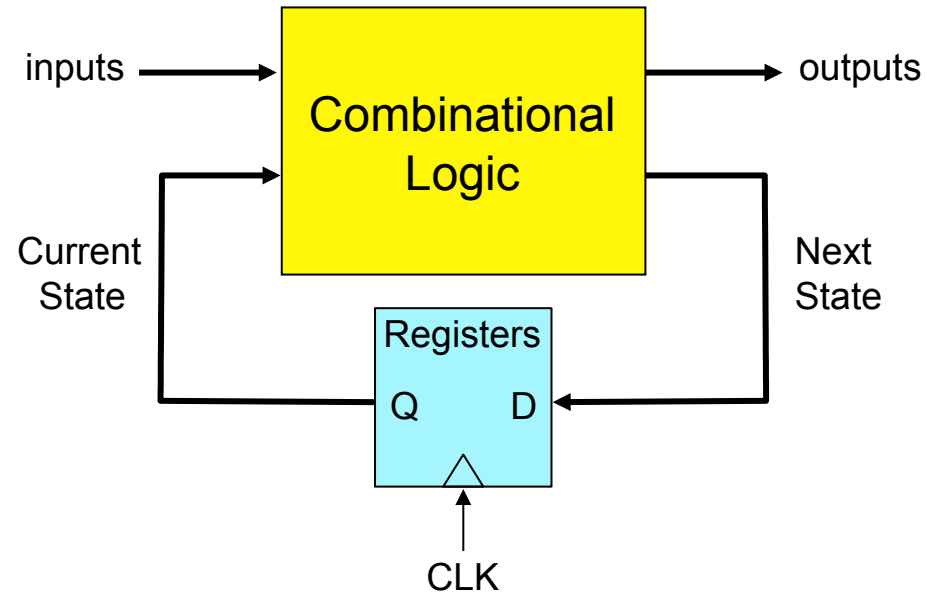

Positive Feedback: uses latches or registers

CMOS Sequential Circuits

Naming Conventions

- ❑ **In Rabaey's IC book:**
 - A latch is **level sensitive**
 - A register is **edge-triggered**
- ❑ **Many other books:**
 - Flip-flop is an edge-triggered



Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Latch Versus Register



□ Latch

stores data when clock is low

  

□ Register

stores data when clock rises

  


Source: Rabaey; Chandrakasan; Nikolic, 2003


CMOS Sequential Circuits

Characterizing Timing

Register


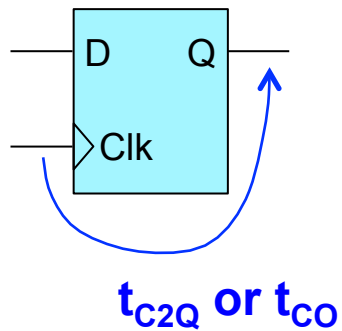


Latch

 

CMOS Sequential Circuits

Timing Definitions

 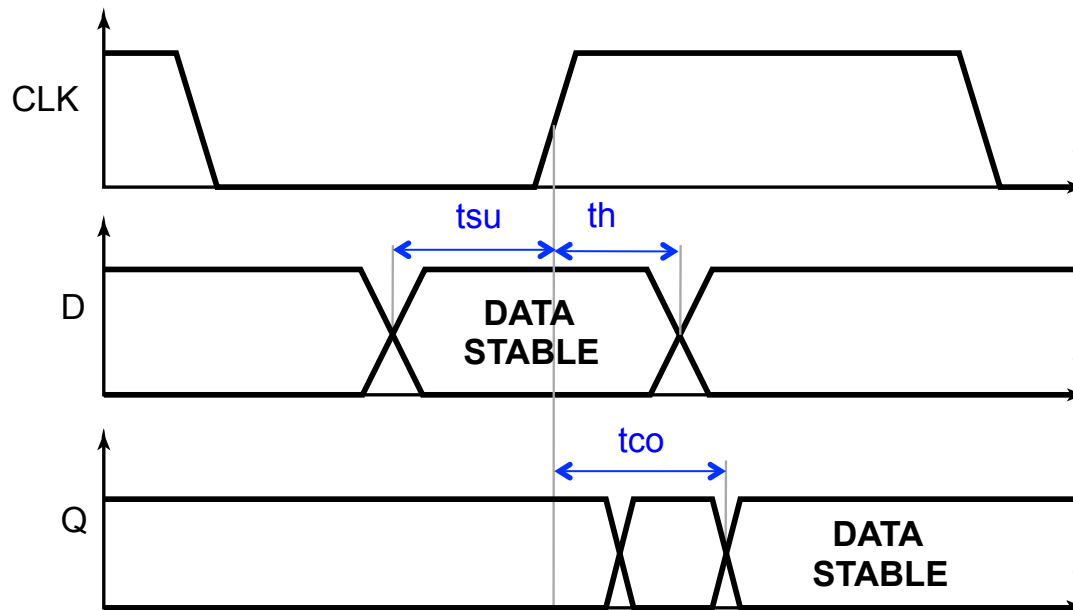

t_{su} = setup time

t_h = hold time

t_{co} = t_{c2q} = maximum propagation delay (or time from clock to output Q)

t_{cd} = minimum propagation delay (or *contamination delay*)



Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Maximum Clock Frequency

t_{d_Logic} = maximum propagation delay

 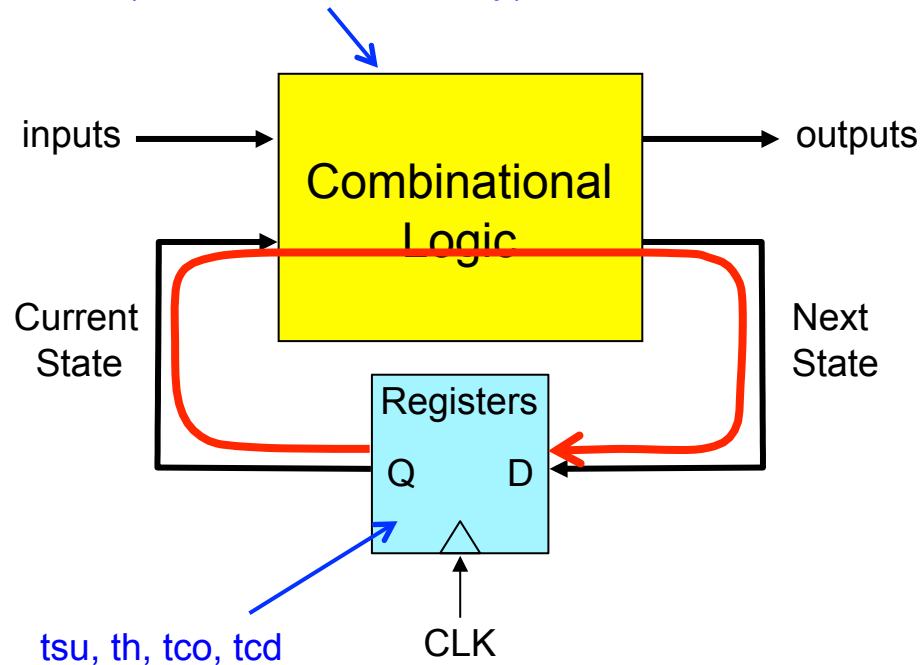t_{c_Logic} = minimum propagation delay
(or *contamination delay*)



$$T \geq t_{co} + t_{d_Logic} + t_{su}$$



$$f = 1/T$$

CMOS Sequential Circuits

Avoiding Race Condition



td_{Logic} = maximum propagation delay

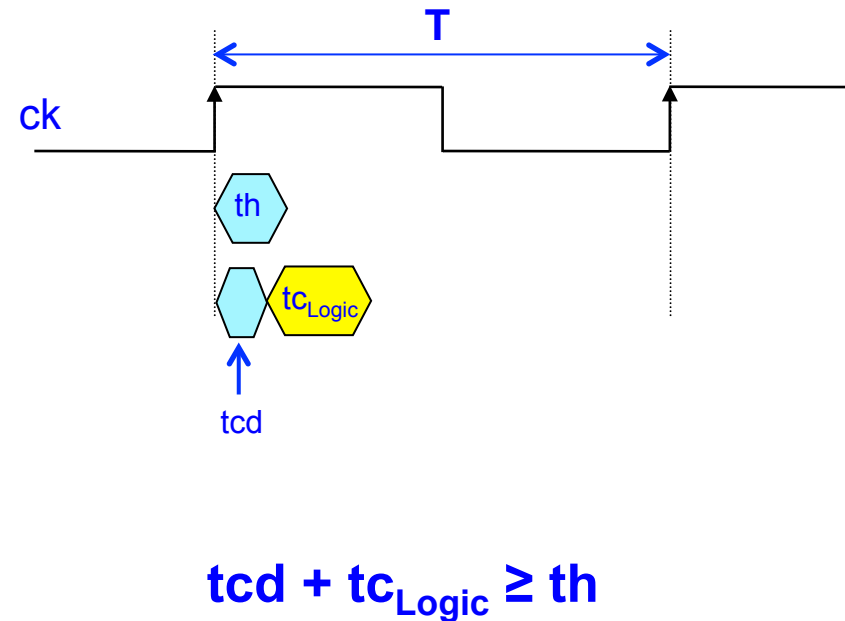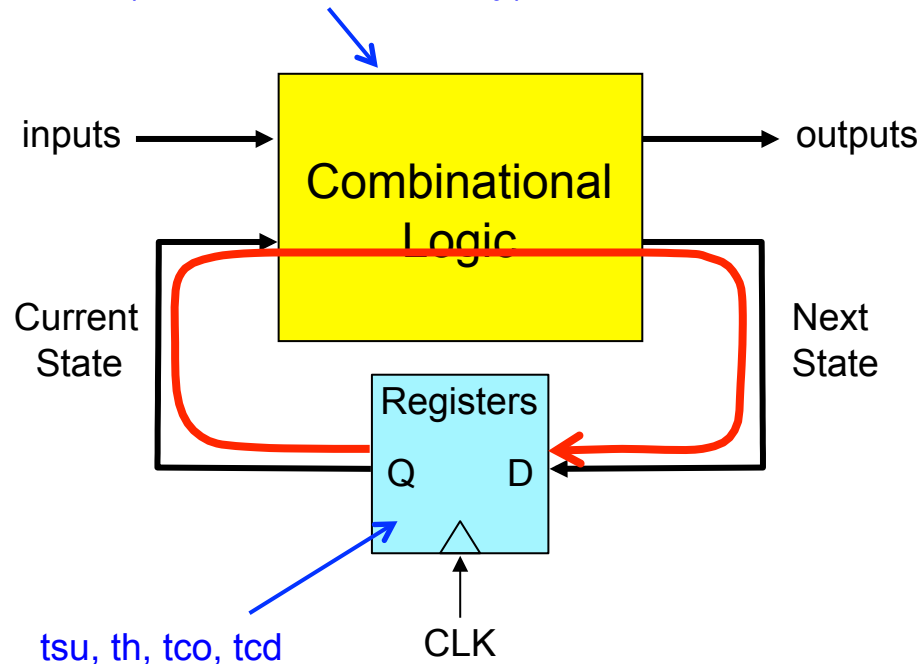tc_{Logic} = minimum propagation delay
(or *contamination delay*)



CMOS Sequential Circuits

Maximum Clock Frequency

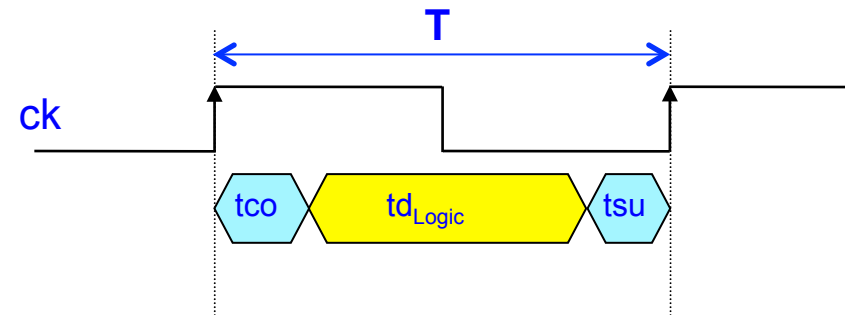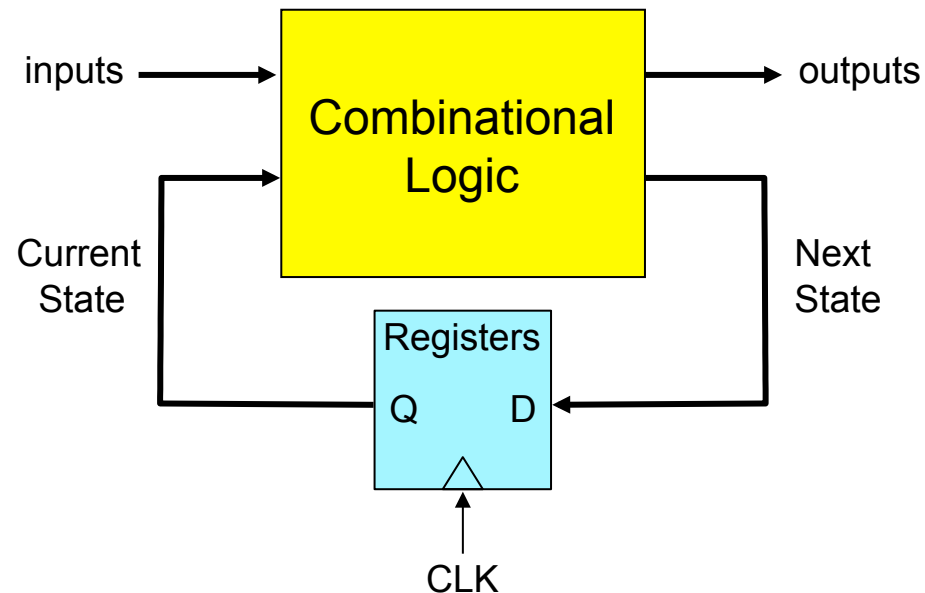


In contemporary designs:

- ❑ The maximum logic depth is around 12 gates
- ❑ Approx. 15% of the clock period is due to register overheads
- ❑ $t_{cd} + t_{c_{Logic}} \geq t_h$ is quite easy to meet if clock slew can be disregarded

CMOS Sequential Circuits


Positive Feedback: Bi-Stability

 

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits



Positive Feedback: Bi-Stability

 

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Meta-Stability

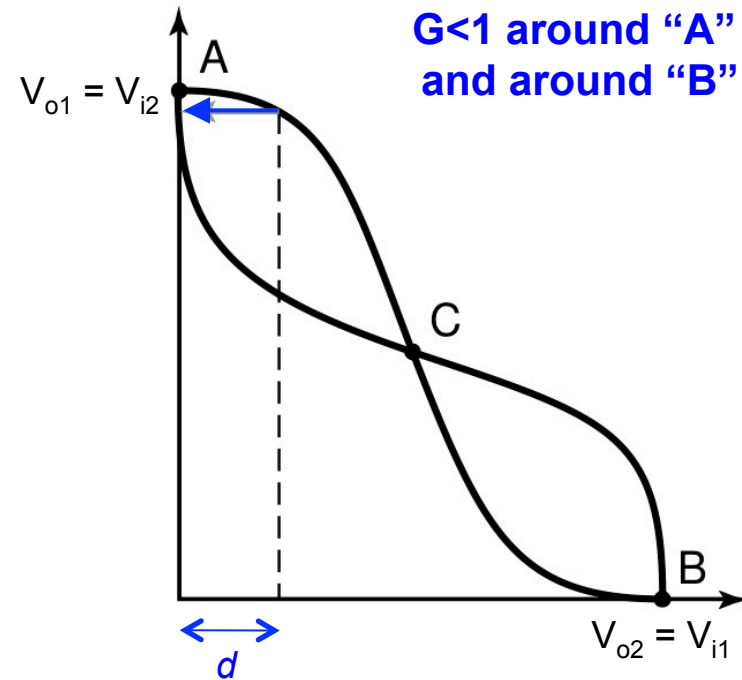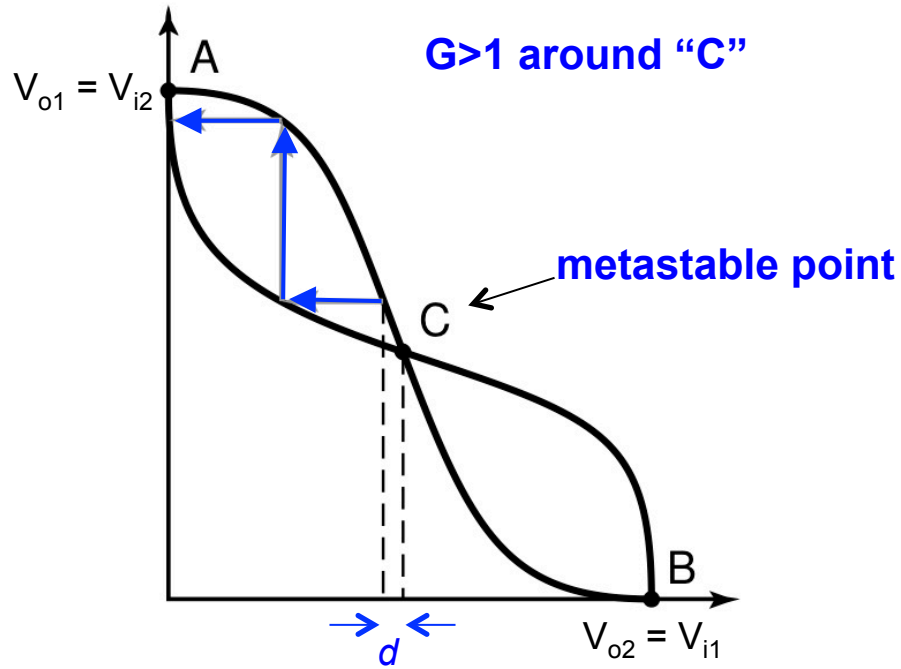

G is the loop gain

Source: Rabaey; Chandrakasan; Nikolic, 2003

INE/CTC/UFSC
Integrated Circuits and Systems

Slide 18.14


Lecture 18 – 2012/2
Prof. José Luís Güntzel

CMOS Sequential Circuits

Changing the State of a Bistable

❑ Cutting the feedback loop:

 
- Multiplexer-based structure
- Once the loop is open, a new value can be easily written in
- This is the most popular approach in today's latches



$$Q = Clk \cdot Q + \overline{Clk} \cdot D$$

❑ Overpowering the feedback loop:


 
- By applying a trigger signal at the input of the bistable a new value is forced into the cell
- Careful sizing of the transistors in the feedback loop and trigger circuitry
- Currently, is used to built static background memories



CMOS Sequential Circuits

Writing into a Static Latch

  Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states





Converting into a MUX

CMOS Sequential Circuits

Writing into a Static Latch

 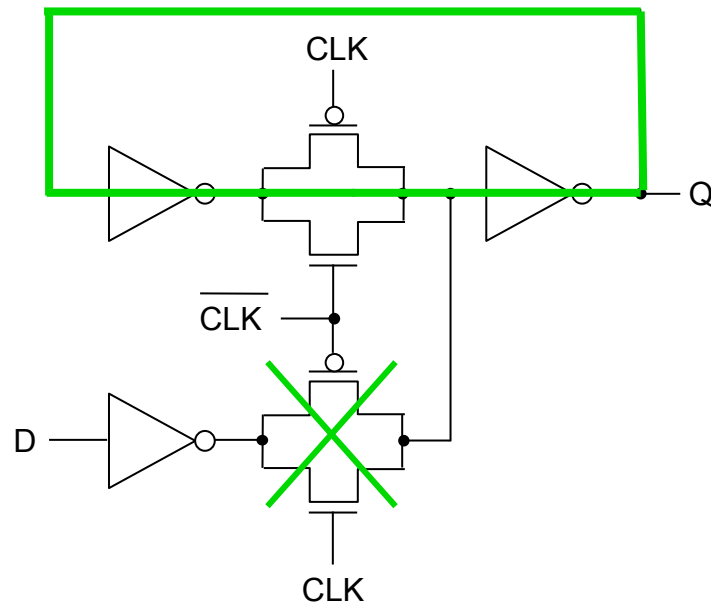Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states





Converting into a MUX

CMOS Sequential Circuits

Writing into a Static Latch

  Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states





Forcing the state

If the transmission gate has minimum sized transistors, the lower inverter must be even weaker!

CMOS Sequential Circuits

Writing into a Static Latch

  
Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states




Forcing the state

CMOS Sequential Circuits

Writing into a Static Latch

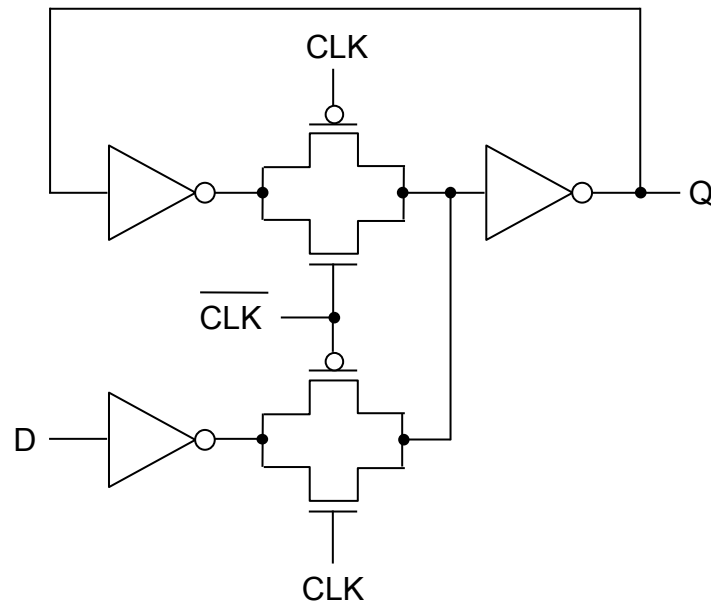

Converting into a MUX

 


Forcing the state

CMOS Sequential Circuits


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 

$$Q = Clk \cdot Q + \overline{Clk} \cdot D$$

Positive latch
(transparent when CLK= 1)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot D$$

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Mux-Based Latch

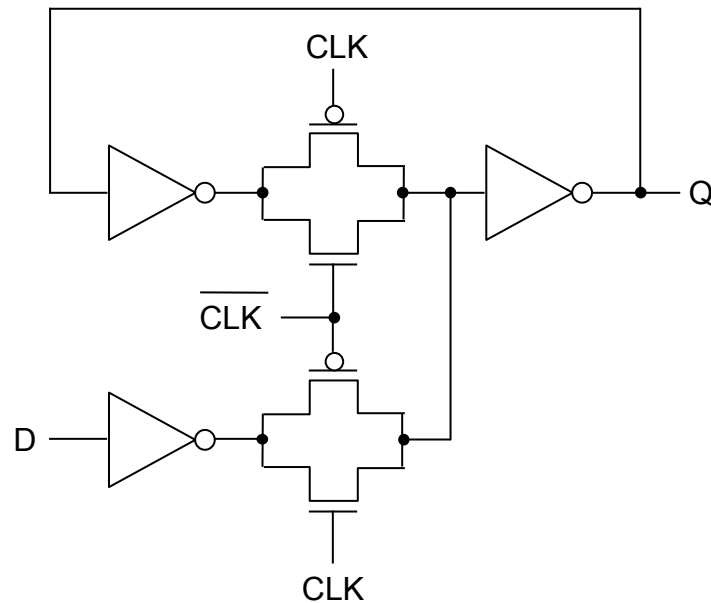

$$P = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{DD}^2 \cdot f$$


$$\text{CLK: } \alpha_{0 \rightarrow 1} = 1$$

How many transistor loads seen by CLK per bit?

CMOS Sequential Circuits


Mux-Based Latch

$$V_{OH} = V_{DD} - V_{Tn}$$

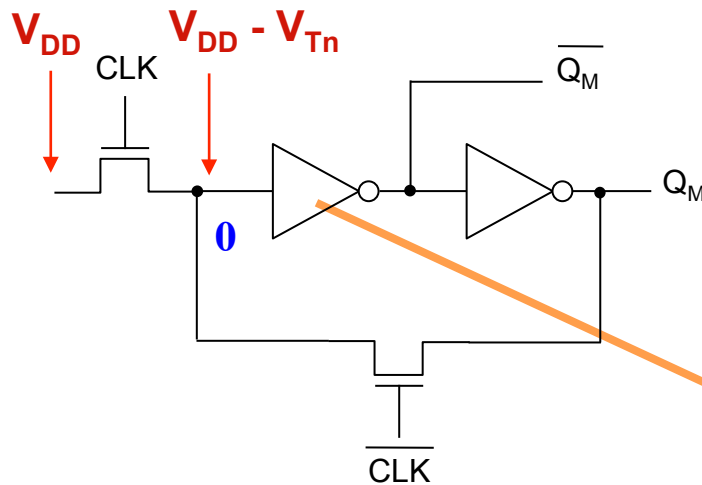


NMOS only

Noise margin degradation

 

CMOS Sequential Circuits

Mux-Based Latch

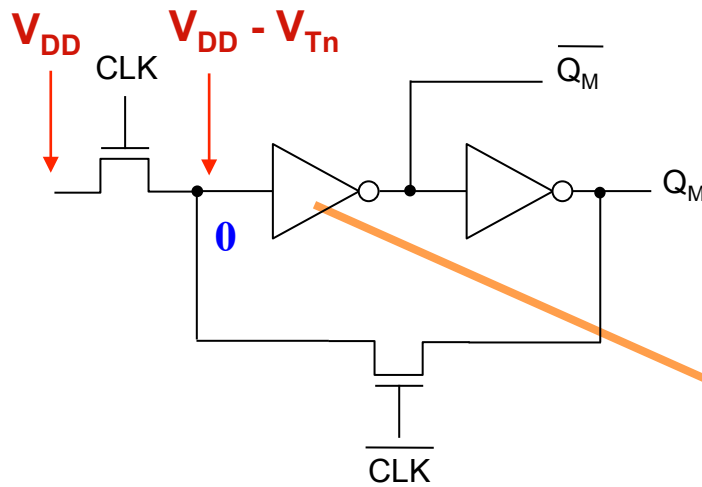

NMOS only


Switching performance degradation

$$t_{pHL} \approx 0.69 R_{eq-NMOS} C_L$$

$$R_{eq} \approx (R_{on}(t_1) + R_{on}(t_2))/2$$


$$R_{on}(t) \approx V_{DS}(t)/I_D(t)$$
 
$$I_D \approx \frac{k'_n W}{2 L} (V_{GS} - V_T)^2$$




CMOS Sequential Circuits

Mux-Based Latch

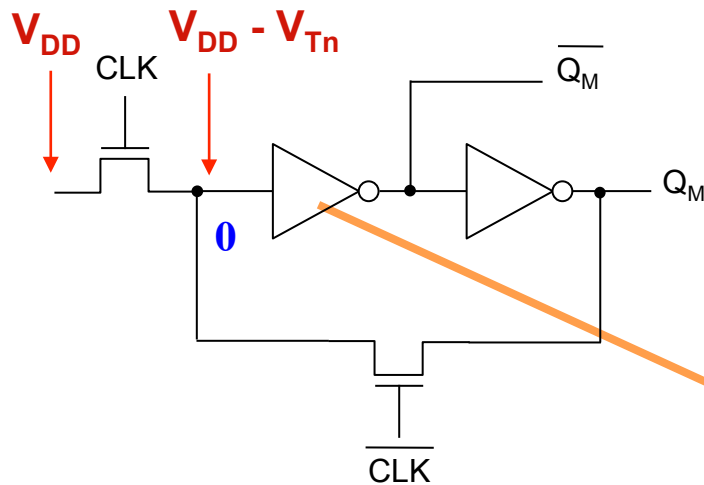

NMOS only


Not completely OFF

 

Short-circuit power increases

CMOS Sequential Circuits

Master-Slave (Edge-Triggered) Register

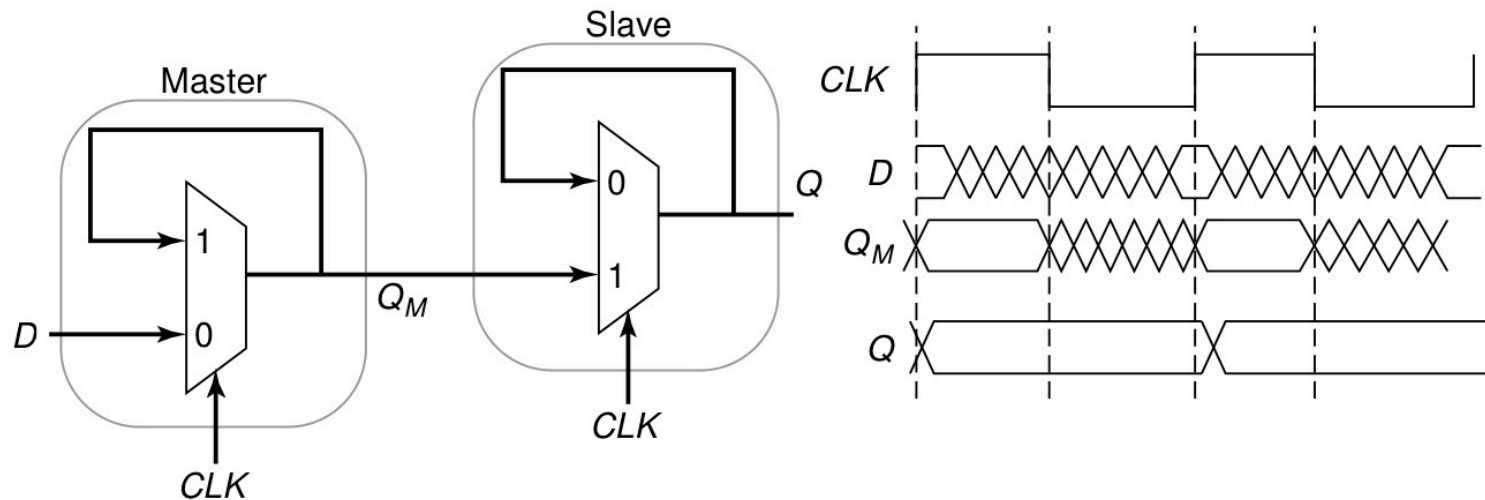


Two opposite latches trigger on edge
Also called master-slave latch pair

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Master-Slave Register



Multiplexer-based latch pair

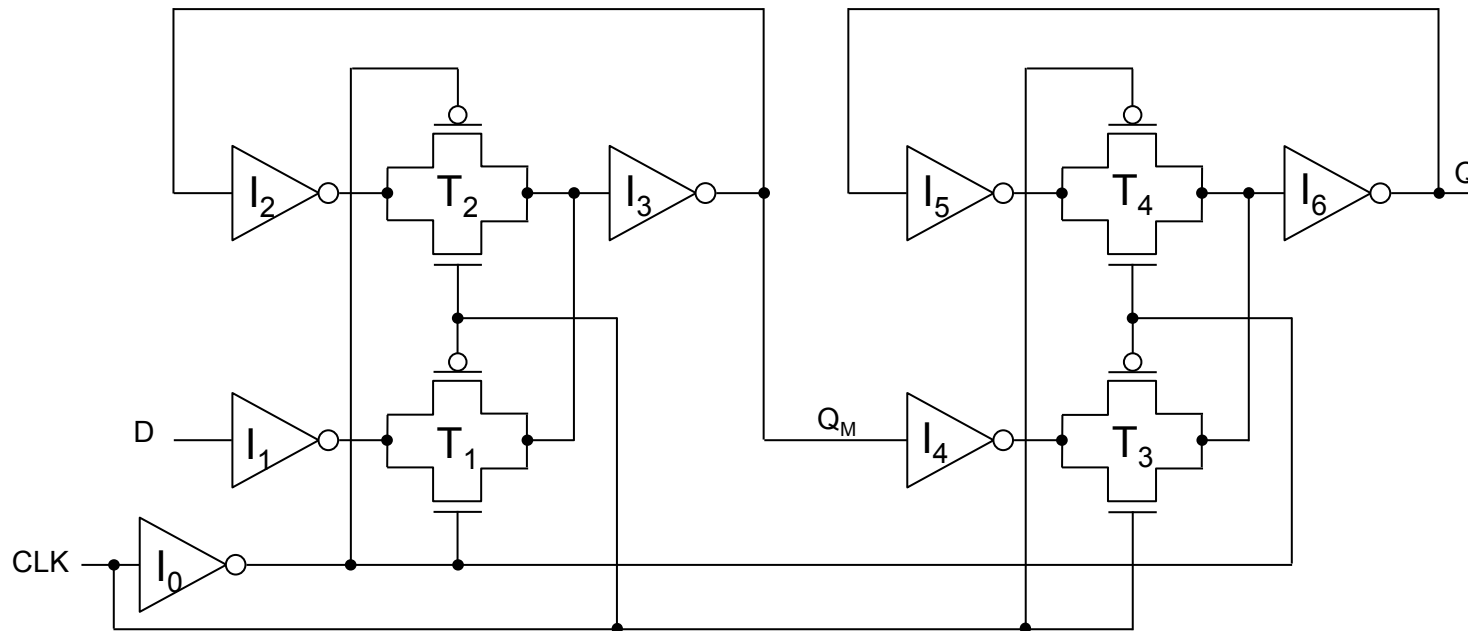

CMOS Sequential Circuits



Master-Slave Register

Multiplexer-based latch pair

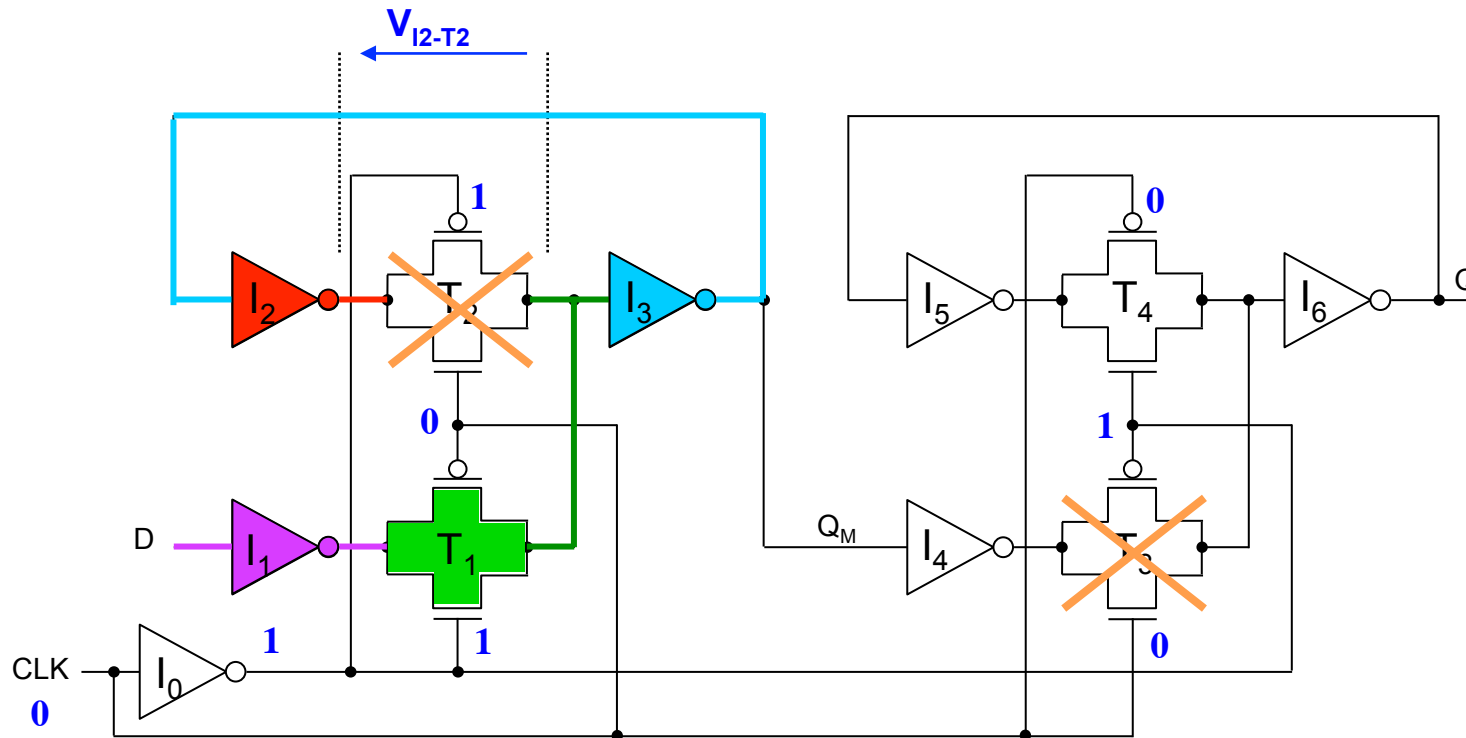 

CMOS Sequential Circuits

Setup Time

 
 


Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Master-Slave Register



Multiplexer-based latch pair

 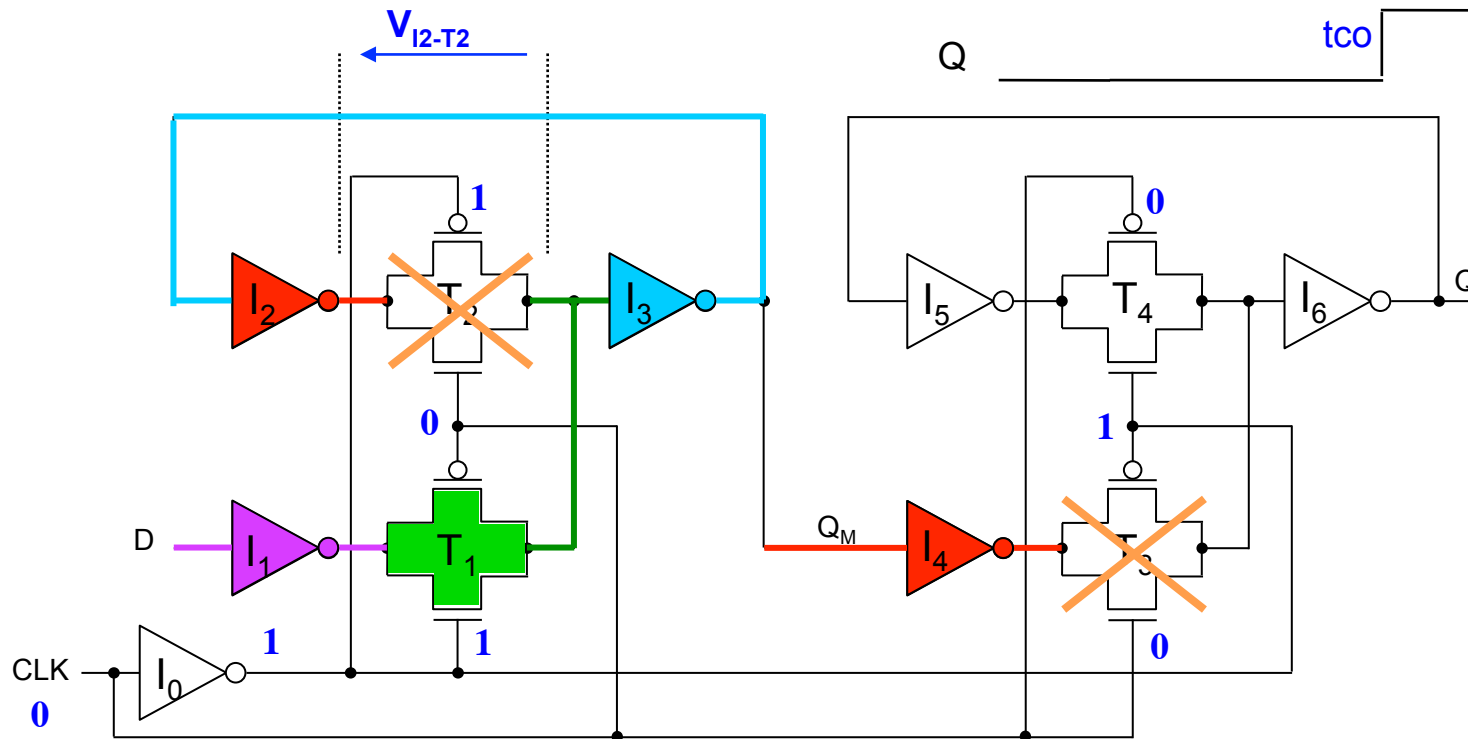

CMOS Sequential Circuits


Master-Slave Register

Multiplexer-based latch pair

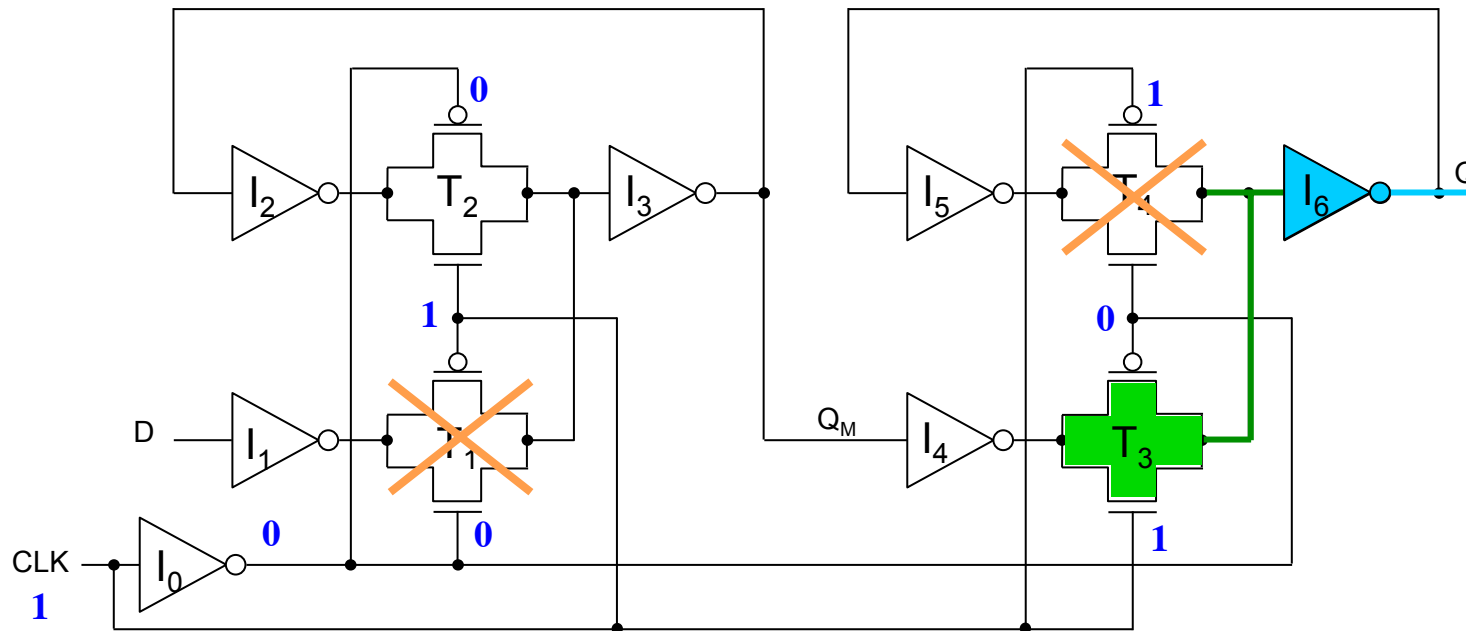 

CMOS Sequential Circuits


Clk to Output (Q) Delay

 

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits



Reduced Clock Load Master-Slave Register

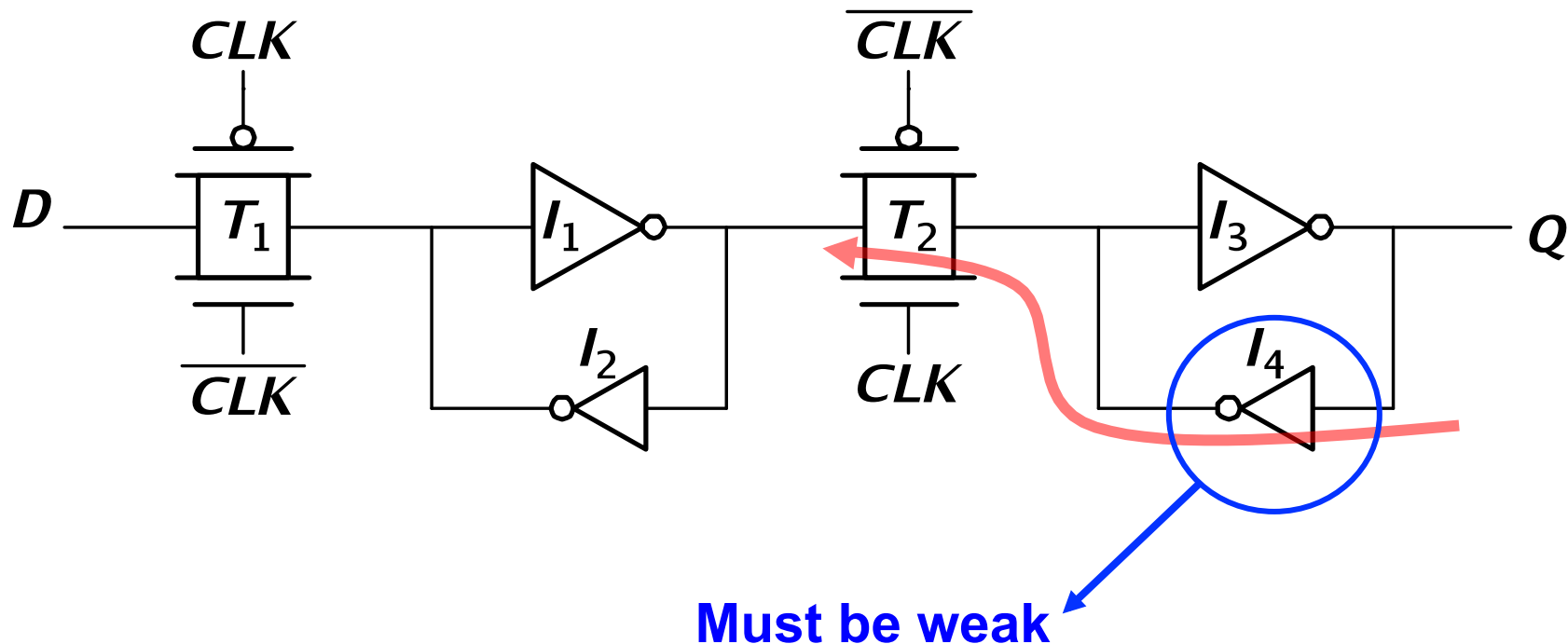

Source: Rabaey; Chandrakasan; Nikolic, 2003

CMOS Sequential Circuits

Avoiding Clock Overlap

 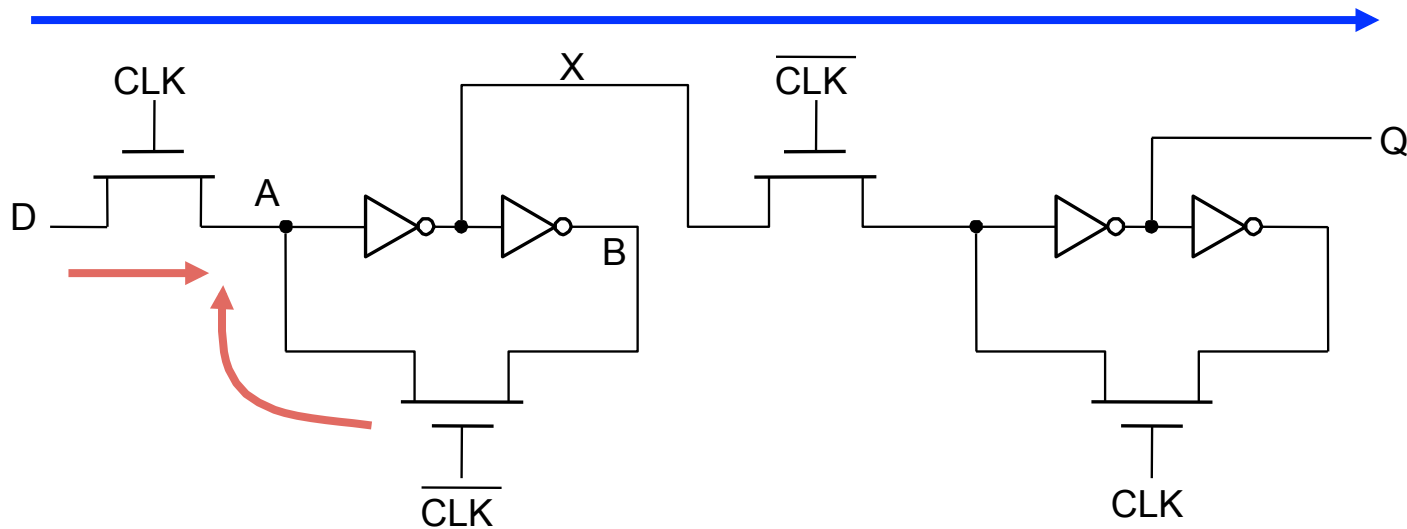


Q may change on the rising edge!

Node A driven by D and B: undefined state!

Source: Rabaey; Chandrakasan; Nikolic, 2003


CMOS Sequential Circuits

Avoiding Clock Overlap

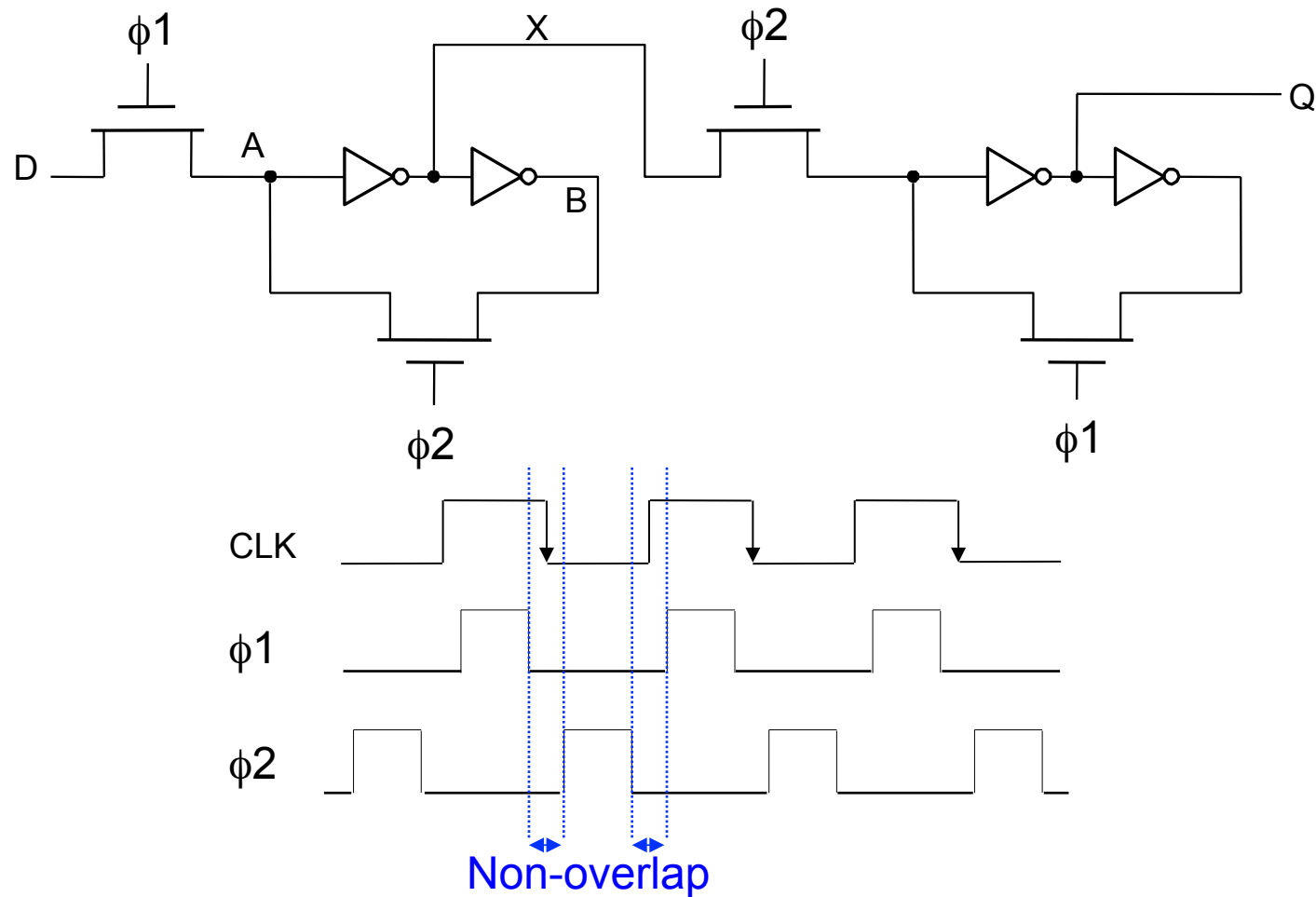


CMOS Sequential Circuits

Avoiding Clock Overlap

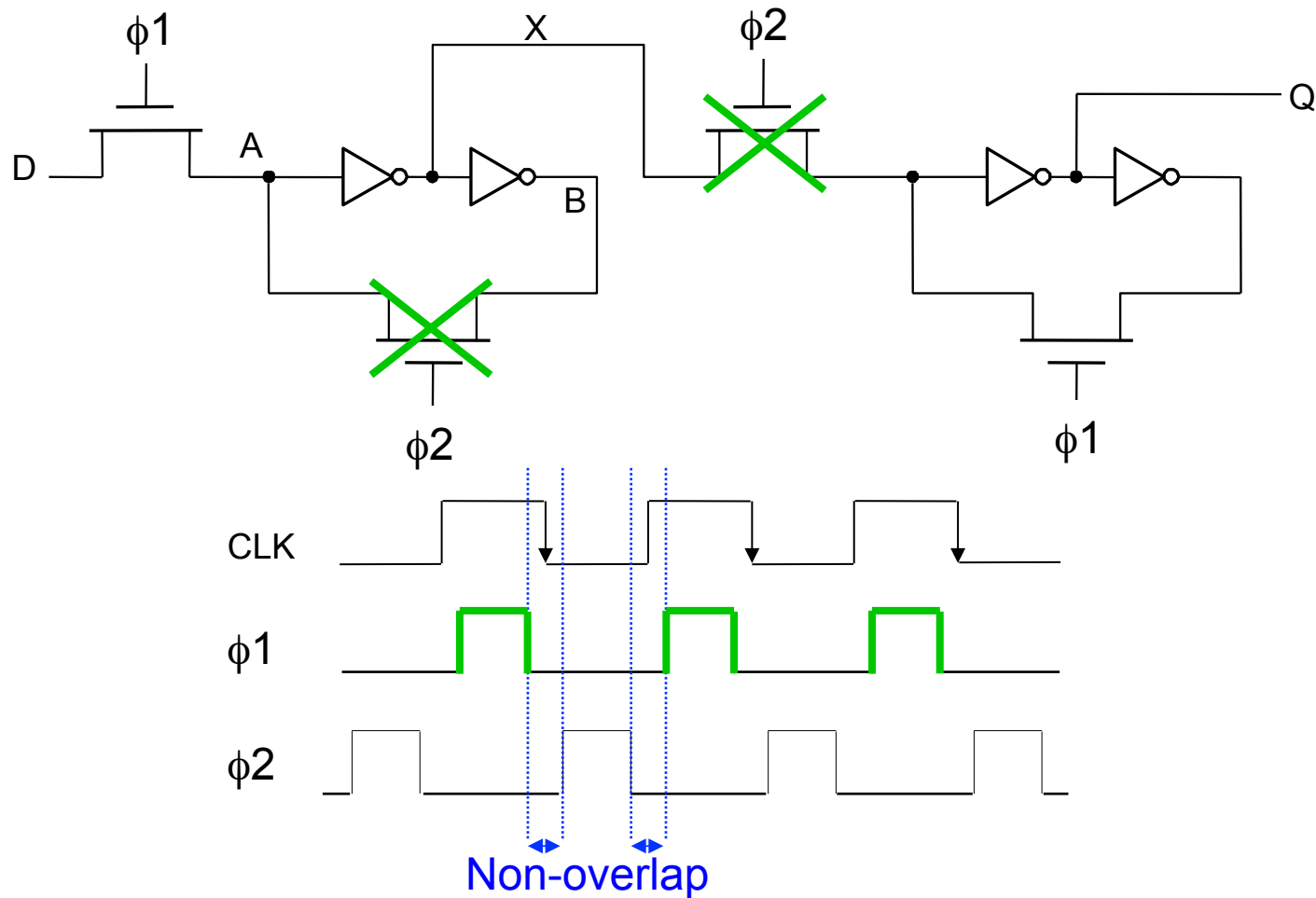


CMOS Sequential Circuits

Avoiding Clock Overlap

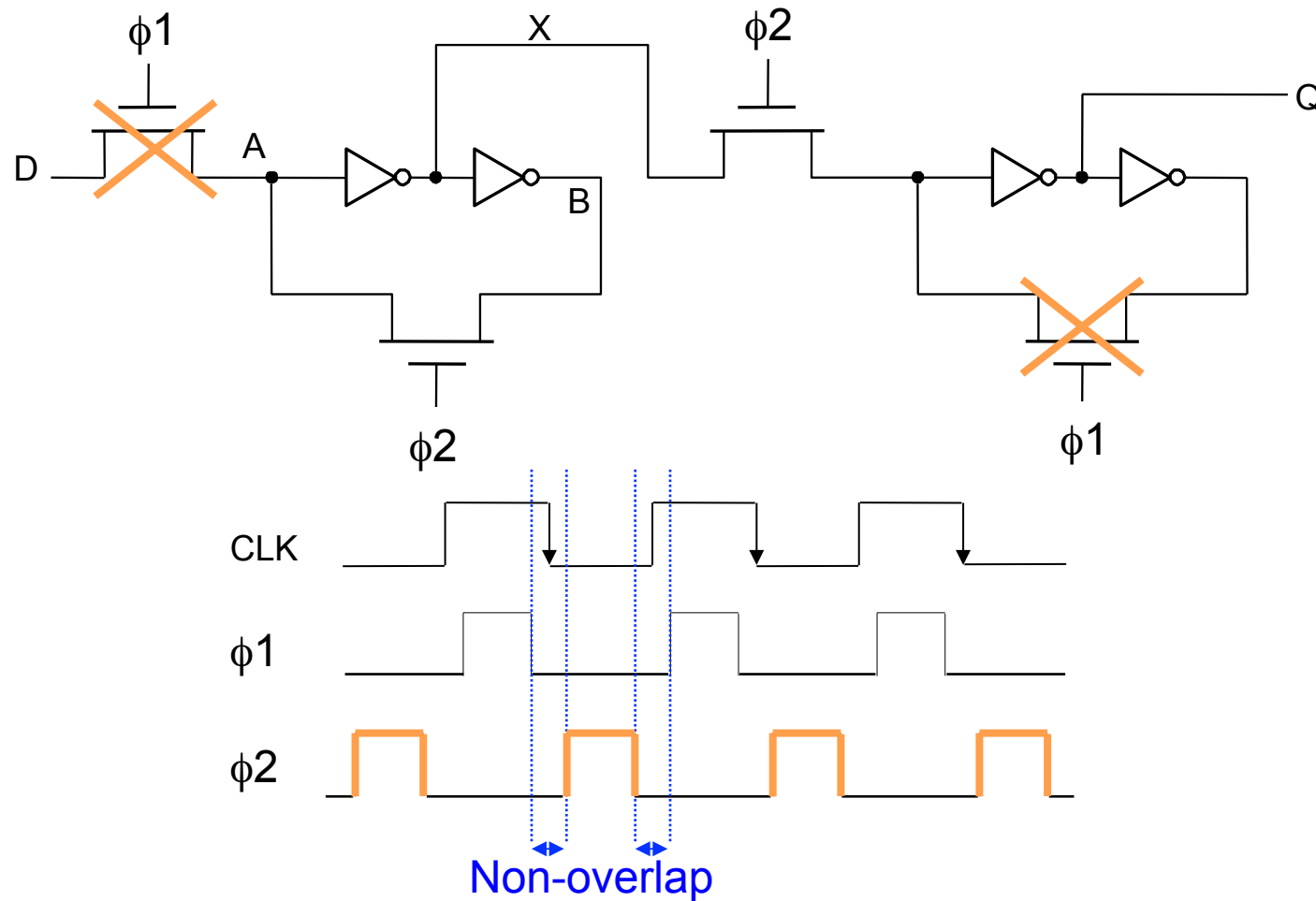

CMOS Sequential Circuits



Avoiding Clock Overlap

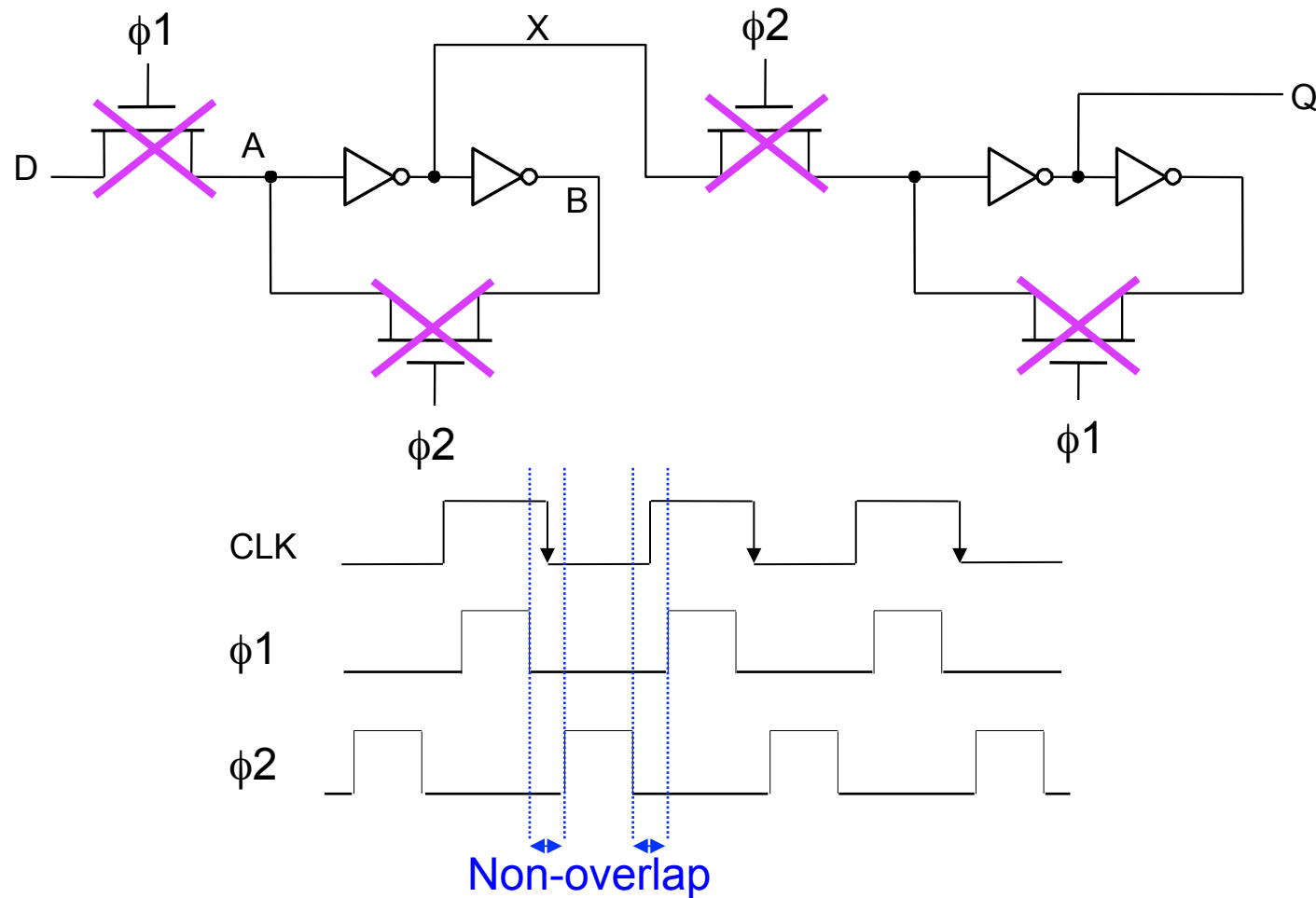

CMOS Sequential Circuits

Overpowering the Feedback Loop – Cross-Coupled Pairs

NOR-based set-reset

  

S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

Source: Rabaey; Chandrakasan; Nikolic, 2003


Asynchronous doesn't fit in dominant methodology!
(99% of the ICs are synchronous)

How to turn it into a synchronous circuit?

CMOS Sequential Circuits

Ratioed CMOS SR Latch

 This is not used in datapaths any more, but is a basic building memory cell



$$(W/L)_{M2} = 3 (W/L)_{M1}$$

$$(W/L)_{M4} = 3 (W/L)_{M3}$$


CMOS Sequential Circuits

Ratioed CMOS SR Latch

$Q = 1: R = 1 @ CLK = 1 \rightarrow Q = 0$

$$3(W/L)_{M7-M8} \approx (W/L)_{M4}$$

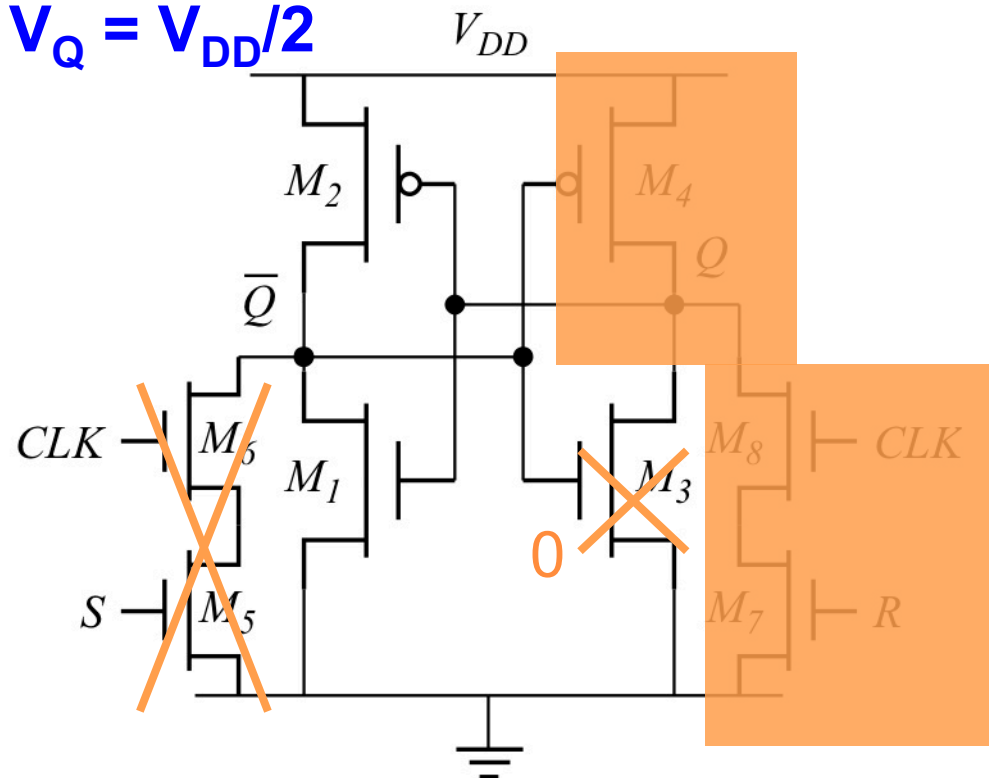$V_Q = V_{DD} \rightarrow V_Q = V_{DD}/2$



$$(W/L)_{M2} = 3 (W/L)_{M1}$$

$$(W/L)_{M4} = 3 (W/L)_{M3}$$


CMOS Sequential Circuits

Ratioed CMOS SR Latch

$Q = 0: S = 1 @ CLK = 1 \rightarrow Q = 1$

$$3(W/L)_{M5-M6} \approx (W/L)_{M2}$$

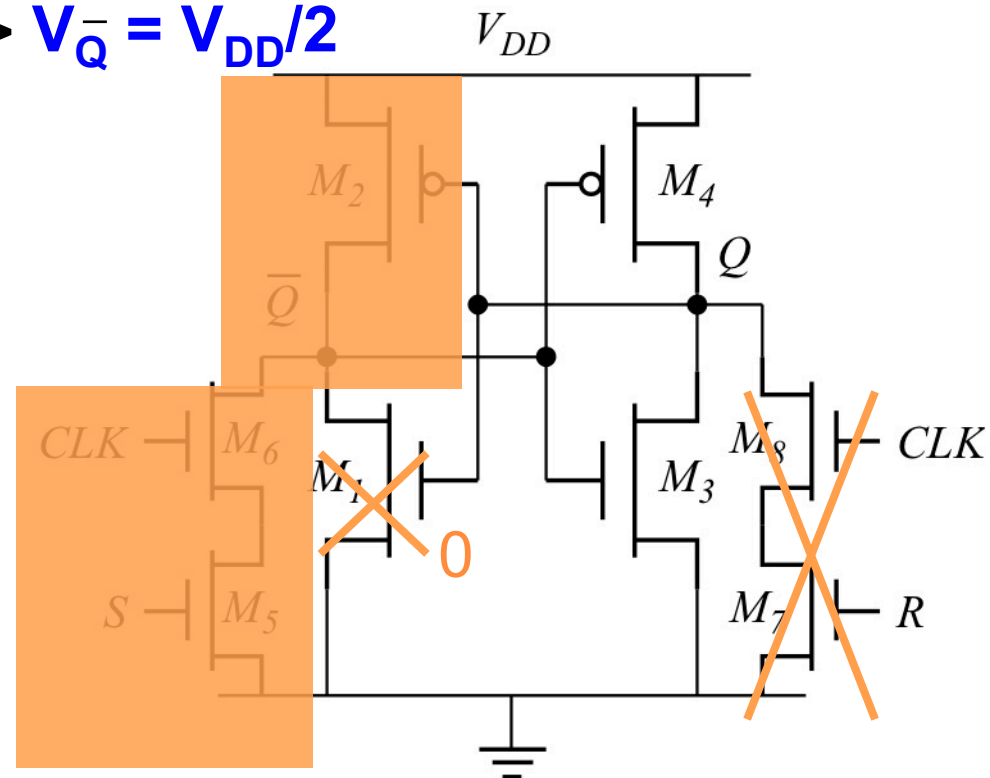$V_{\bar{Q}} = V_{DD} \rightarrow V_{\bar{Q}} = V_{DD}/2$



$$(W/L)_{M2} = 3 (W/L)_{M1}$$

$$(W/L)_{M4} = 3 (W/L)_{M3}$$


CMOS Sequential Circuits

Ratioed CMOS SR Latch

$$3(W/L)_{M5-M6} \approx (W/L)_{M2} = (W_{M2}/L_{min}) = (3W_{M1}/L_{min})$$

$$(W/L)_{M5-M6} = W/(2 L_{min})$$

$$W = W_{M5} = W_{M6}$$

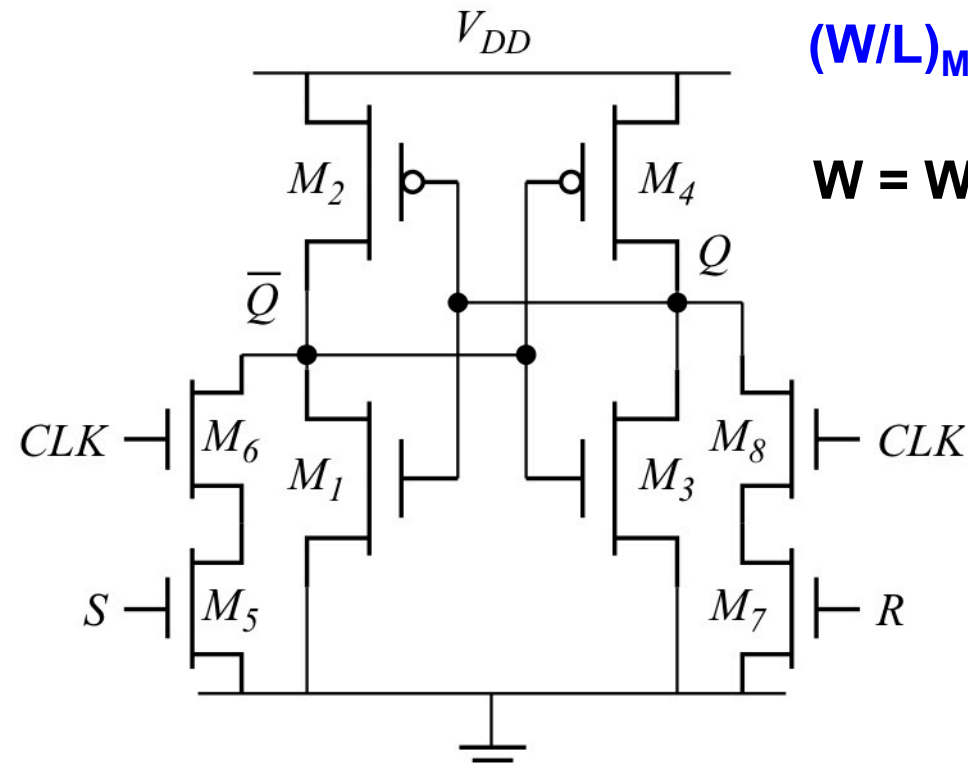


$$(W_{M2}/L_{min}) = 3 (W_{M1}/L_{min})$$

CMOS Sequential Circuits

Ratioed CMOS SR Latch
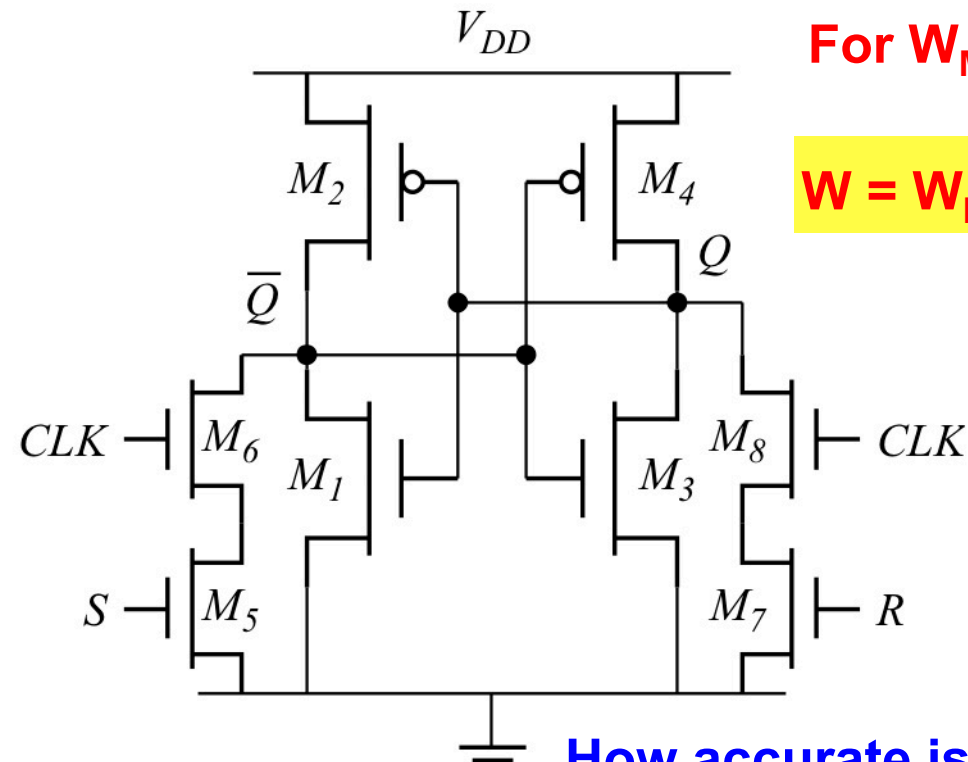
$$3(W/L)_{M5-M6} \approx 3 W/(2 L_{\min}) = 3 W_{M1}/L_{\min}$$



For $W_{M1} = 2 L_{\min}$:

$$W = W_{M5} = W_{M6} \approx 4 L_{\min}$$


$$(W_{M2}/L_{\min}) = 3 (W_{M1}/L_{\min})$$

How accurate is the value of W for $L_{\min} = 0.25 \mu$ and $W_{M1} = 0.5 \mu$?

CMOS Sequential Circuits

Ratioed CMOS SR Latch Sizing Issues


$W \approx 3 L_{\min}$ is enough!

 

Transient response

CMOS Sequential Circuits


Synchronized Cross-Coupled NAND

 

Requires proper transistor sizing: ratioed design.

CMOS Sequential Circuits

Cross-Coupled NAND

 


What is the corresponding truth table?

For a given t_p , which requires more area
synchronized cross-coupled NOR or NAND?

CMOS Sequential Circuits

 
Generating Two-Phase Non-Overlapping Clock



Initial Values

CMOS Sequential Circuits

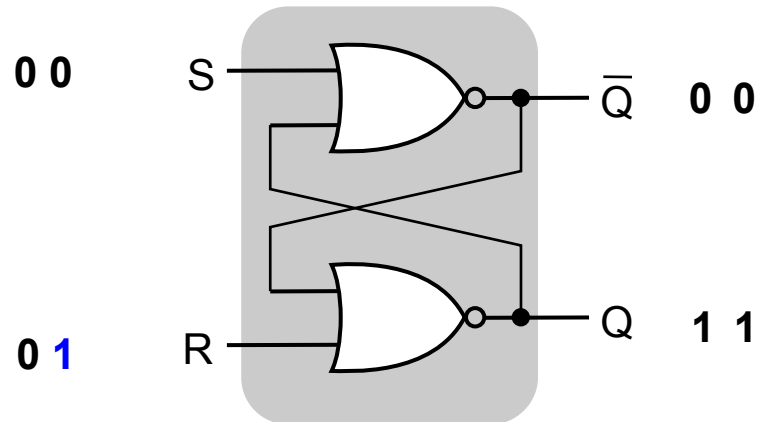
Generating Two-Phase Non-Overlapping Clock



Time = t_0

CMOS Sequential Circuits

 
Generating Two-Phase Non-Overlapping Clock



$$\text{Time} = t_0 + d$$

CMOS Sequential Circuits


 
Generating Two-Phase Non-Overlapping Clock



$$\text{Time} = t_0 + 2d$$

CMOS Sequential Circuits

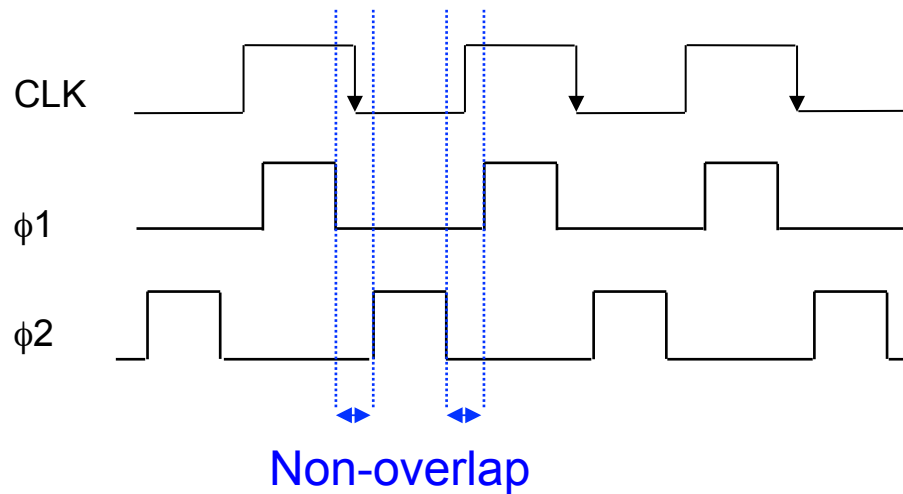 Generating Two-Phase Non-Overlapping Clock



References

1. RABAEY, J; CHANDRAKASAN, A.; NIKOLIC, B. **Digital Integrated Circuits: a design perspective.** 2nd Edition. Prentice Hall, 2003. ISBN: 0-13-090996-3.
2. WESTE, Neil; HARRIS, David. **CMOS VLSI Design: a circuits and systems perspective.** Addison-Wesley, 4th Edition, 2010. ISBN 978-0321547743.

