
 


Bistabilna kola
Leč kolo
Flip-Flop


Standard sequential circuits – SR latch

 


Standard sequential circuits – SR latch



Standard sequential circuits – SR latch

 


Standard sequential circuits – SR latch


 


R	S	$Q[n+1]$
0	0	$Q[n]$
0	1	1
1	0	0
1	1	?


Standard sequential circuits – D latch

 

Standard sequential circuits – D latch


 
 


Standard sequential circuits – D FF


 


D	C_p	$Q[n+1]$
x	0	$Q[n]$
0	$0 \rightarrow 1$	0
1	$0 \rightarrow 1$	1
x	1	$Q[n]$


D FF master-slave operation

   

D FF with /preset and /clear

  


D FF with /preset=1 and /clear

 


74HC73

 JK flip-flop with reset; negative-edge trigger




74HC73

 JK flip-flop with reset; negative-edge trigger




001aab982

Dual J-K Flip-Flop with Set and Reset

 


Registers

 - n -bit register is a set of n D flip-flops, one per bit
 - Data inputs are D_0, D_1, \dots, D_{n-1}
 - Data outputs are Q_0, Q_1, \dots, Q_{n-1}
 - Common Clock for all flip-flops
 - Optional preset or clear







n bit latch

 - n -bit latch is a set of n single bit latches, one per bit
- Data inputs are D_0, D_1, \dots, D_{n-1}
- Data outputs are Q_0, Q_1, \dots, Q_{n-1}
- Common LE for all latches
- Optional preset or clear




ROM $4 \times 6\text{bit}$

 

   


Memory Cell: Static RAM (8 transistors)

 - 8-transistor cell
 - Bit_i is the data bus
 - S_j is the word line
- Bus drivers
 - Sense Amplifier (inverter with high gain) used for fast switching
 - Make sure inverters in cell are weaker than the combination of “write buffer” and pass transistor




Memory Cell: Static RAM (6 transistors)

 - 6-transistor cell
 - Must adjust inverters for input coming through n-type pass gate
- Bus drivers
 - Must adjust senseAmp for input coming through n-type pass gate
 - Harder to drive 1 than 0 through write buffer (high resistance via n-transistor)
 - One side is sending 0 anyway (bit or bit') → written correctly




6-Transistor Memory Array

 - 8 words deep RAM,
2 bits wide words
- To write to word j :
 - Set $S_j=1$, all other S lines to 0
 - Send data on the global bit_0 , bit_0' , bit_1 , bit_1'
- To read word k :
 - Set $S_k=1$, all other S lines to 0
 - Sense data on bit_0 and bit_1 .




Dynamic RAM 4-Transistor Cell

 - 4-transistor cell
- Dynamic charge storage must be refreshed
- Dedicated busses for reading and writing



Dynamic RAM 3-Transistor Cell

 - 3-transistor cell
 - No p-type transistors yield a very compact layout for cell
 - No Vdd connection
 - Sense Amplifier must be able to quickly detect dropping voltage



Dynamic RAM 1-Transistor Cell

- 1-transistor cell
 - Storage capacitor is source of cell transistor
 - Special processing steps to make the storage capacitor large
 - Charge sharing with bus capacitance ($C_{cell} \ll C_{bus}$)
 - Extra demand on sense amplifier to detect small changes
 - Destructive read (must write immediately)

